

MOS Translinear Principle for All Inversion Levels

Bradley A. Minch

Mixed Analog-Digital VLSI Circuits and Systems Lab
Franklin W. Olin College of Engineering
Needham, MA 02492-1200

bradley.minch@olin.edu

March 17, 2008




Translinear Principles for Alternating MOS Translinear Loops

Translinear Principle:

$$\prod_{j \in \text{CW}} \frac{I_j}{S_j} = \prod_{j \in \text{CCW}} \frac{I_j}{S_j}$$

Voltage-Translinear Principle:

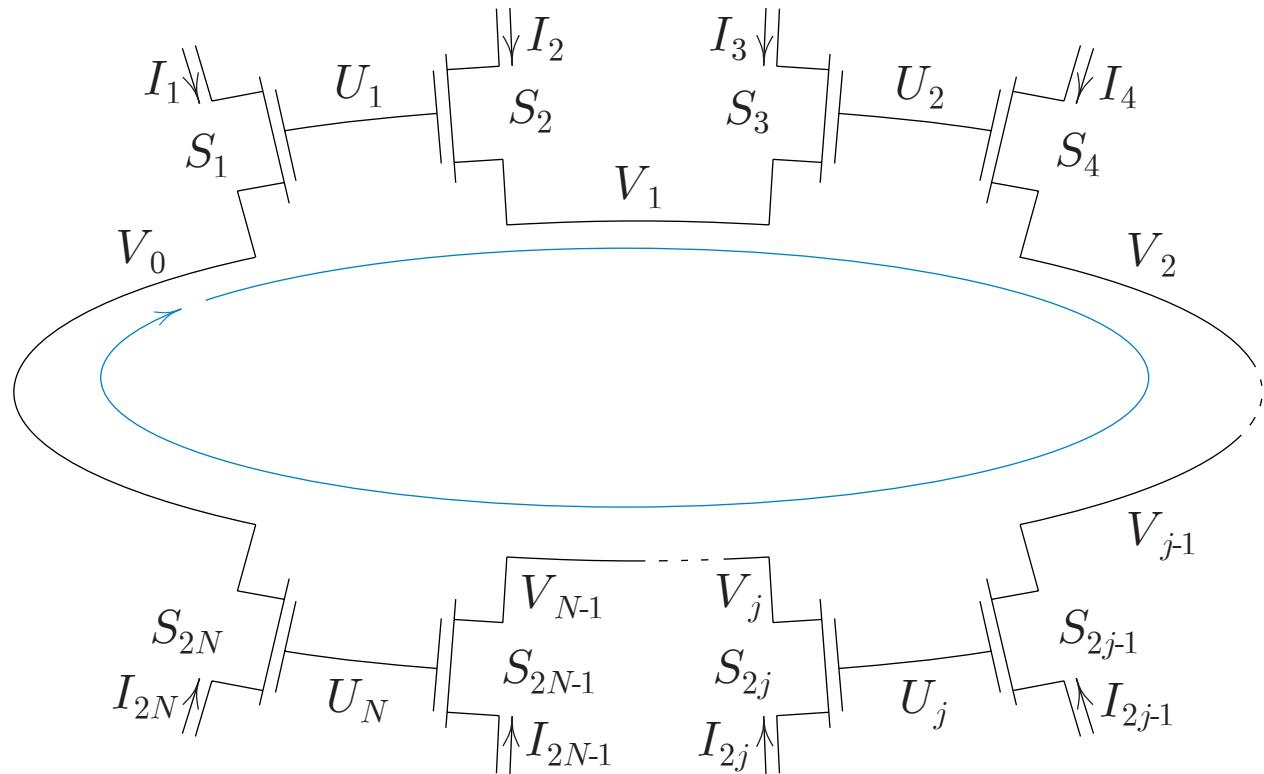
$$\sum_{j \in \text{CW}} \sqrt{\frac{I_j}{S_j}} = \sum_{j \in \text{CCW}} \sqrt{\frac{I_j}{S_j}}$$



Simple EKV MOS Transistor Model

We model the channel current of an n MOS transistor as the difference between a **forward current** and a **reverse current**,

$$I = I_F - I_R,$$

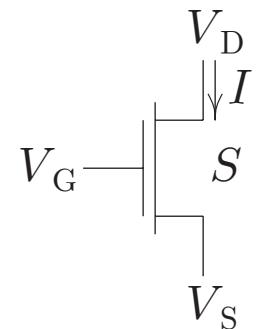

whose values are given by

$$I_{F(R)} = SI_s \log^2 \left(1 + e^{(\kappa(V_G - V_{T0}) - V_{S(D)})/2U_T} \right),$$

where


$$U_T = \frac{kT}{q}, \quad S = \frac{W}{L}, \quad I_s = \frac{2\mu C_{\text{ox}} U_T^2}{\kappa}, \quad \text{and} \quad \kappa = \frac{C_{\text{ox}}}{C_{\text{ox}} + C_{\text{dep}}}.$$

Note that SI_s is approximately twice the saturation current at threshold. This simple model covers all regions of normal MOS transistor operation.

Simple EKV MOS Transistor Model

The expressions for I_F and I_R reduce asymptotically to an exponential form in weak inversion and a quadratic form in strong inversion, given by
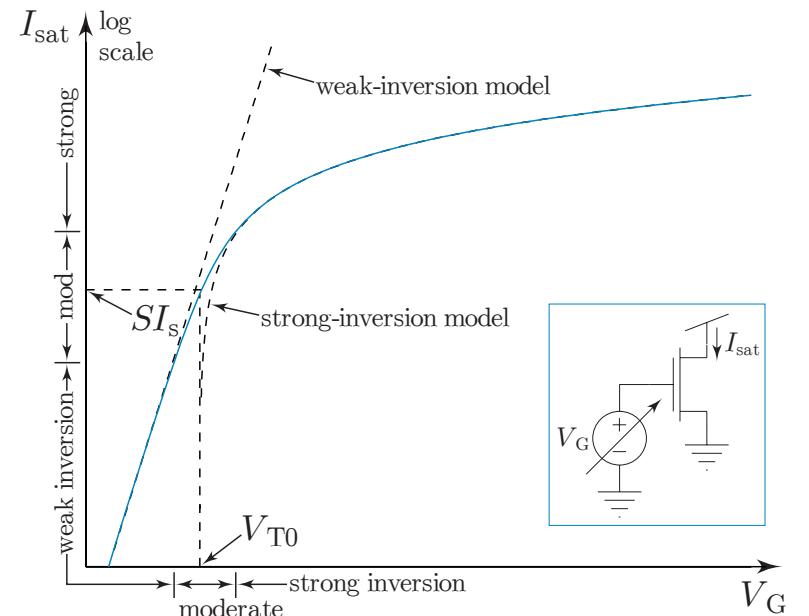
$$I_{F(R)} \approx \begin{cases} SI_s e^{(\kappa(V_G - V_{T0}) - V_{S(D)})/U_T}, & V_G < V_{T0} + \frac{V_{S(D)}}{\kappa} \\ \frac{SI_s}{4U_T^2} (\kappa(V_G - V_{T0}) - V_{S(D)})^2, & V_G > V_{T0} + \frac{V_{S(D)}}{\kappa}. \end{cases}$$



Simple EKV MOS Transistor Model

The expressions for I_F and I_R are also explicitly invertible; the inverses are given by


$$\begin{aligned} \kappa(V_G - V_{T0}) - V_{S(D)} &= 2U_T \log \left(e^{\sqrt{I_{F(R)}/SI_s}} - 1 \right) \\ &\approx \begin{cases} U_T \log \frac{I_{F(R)}}{SI_s}, & I_{F(R)} \ll SI_s \\ 2U_T \sqrt{\frac{I_{F(R)}}{SI_s}}, & I_{F(R)} \gg SI_s. \end{cases} \end{aligned}$$

Simple EKV Model: The Onset of Saturation

Note that I_F depends only on V_G and V_S and that I_R depends only on V_G and V_D . If $I_F \gg I_R$, then $I \approx I_F$ and is nearly independent of V_D , which corresponds qualitatively to the **saturation** region of operation, so $I_{\text{sat}} \approx I_F$. We can define the onset of saturation operationally in terms of an arbitrary parameter, $A \gg 1$: We say that an MOS transistor is saturated if $I_F/I_R \geq A$. Using this notion, we can find an expression for V_{DSSat} , given by

$$V_{DSSat} = 2U_T \log \frac{e^{\sqrt{I_{\text{sat}}/SI_s}} - 1}{e^{\sqrt{I_{\text{sat}}/ASI_s}} - 1}$$

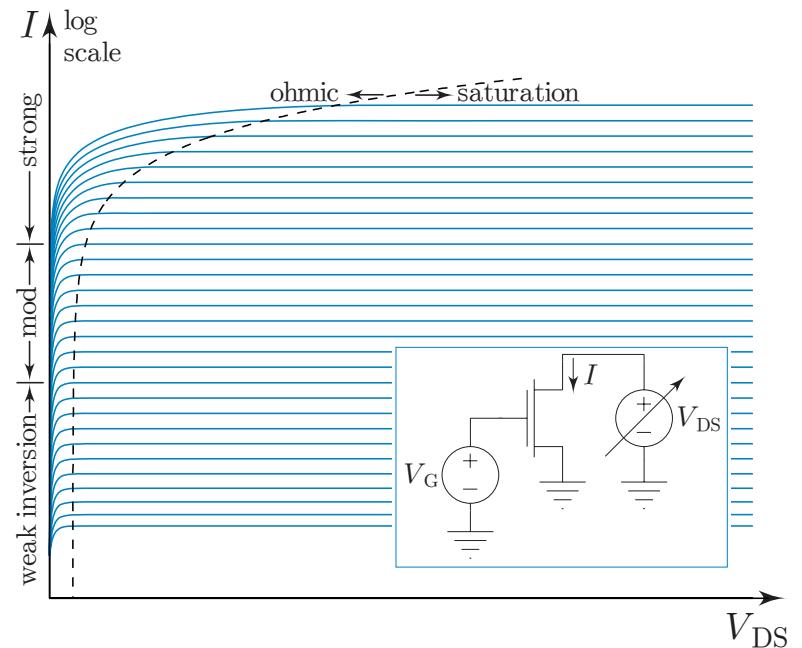
$$\approx \begin{cases} U_T \log A, & I_{\text{sat}} \ll SI_s \\ 2U_T \left(1 - \frac{1}{\sqrt{A}}\right) \sqrt{\frac{I_{\text{sat}}}{SI_s}}, & I_{\text{sat}} \gg SI_s \end{cases}$$



Counterclockwise/Clockwise Pairs

For the counterclockwise transistor, indexed by $2j - 1$, we have that
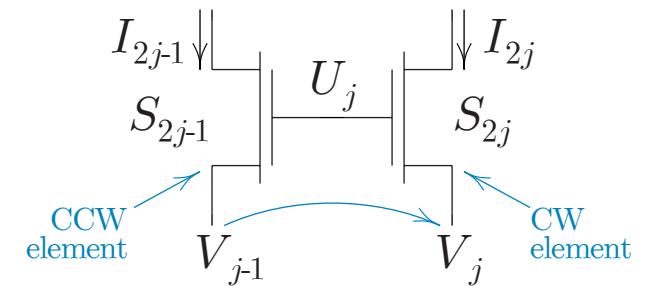
$$\kappa(U_j - V_{T0}) - V_{j-1} = 2U_T \log \left(e^{\sqrt{I_{2j-1}/S_{2j-1}I_s}} - 1 \right),$$




and for the clockwise transistor, indexed by $2j$, we have that

$$\kappa(U_j - V_{T0}) - V_j = 2U_T \log \left(e^{\sqrt{I_{2j}/S_{2j}I_s}} - 1 \right).$$

By subtracting these equations, we obtain

$$V_{j-1} - V_j = 2U_T \log \frac{e^{\sqrt{I_{2j}/S_{2j}I_s}} - 1}{e^{\sqrt{I_{2j-1}/S_{2j-1}I_s}} - 1}.$$

Alternating MOS Translinear Loop

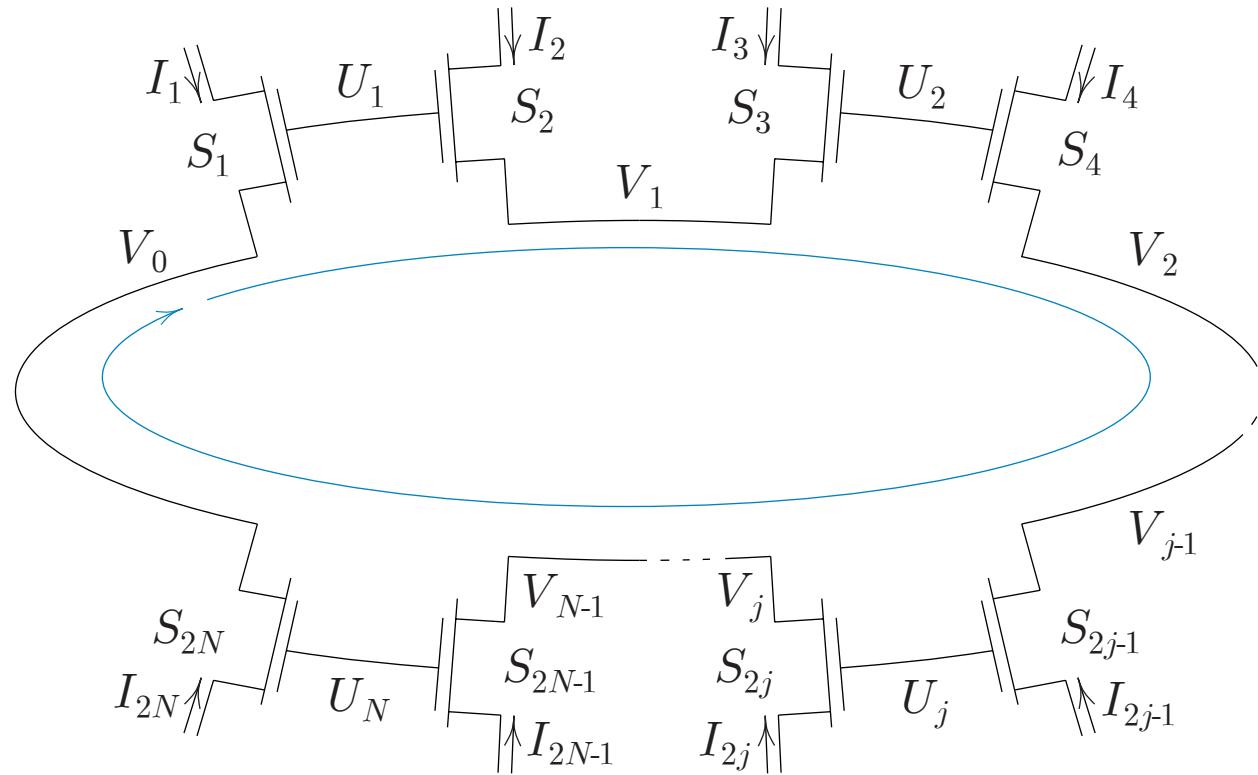

Generalized MOS Translinear Principle

Kirchhoff's voltage law (KVL) around the loop implies that

$$\begin{aligned}
 (V_0 - V_1) + \cdots + (V_{j-1} - V_j) + \\
 \cdots + (V_{N-1} - V_0) &= 0 \\
 \sum_{j=1}^N 2U_T \log \frac{e^{\sqrt{I_{2j}/S_{2j}I_s}} - 1}{e^{\sqrt{I_{2j-1}/S_{2j-1}I_s}} - 1} &= 0 \\
 2U_T \log \prod_{j=1}^N \frac{e^{\sqrt{I_{2j}/S_{2j}I_s}} - 1}{e^{\sqrt{I_{2j-1}/S_{2j-1}I_s}} - 1} &= 0 \\
 \log \prod_{j=1}^N \frac{e^{\sqrt{I_{2j}/S_{2j}I_s}} - 1}{e^{\sqrt{I_{2j-1}/S_{2j-1}I_s}} - 1} &= 0.
 \end{aligned}$$

Generalized MOS Translinear Principle

By exponentiating both sides of this equation, we have that

$$\prod_{j=1}^N \frac{e^{\sqrt{I_{2j}/S_{2j}I_s}} - 1}{e^{\sqrt{I_{2j-1}/S_{2j-1}I_s}} - 1} = 1$$

$$\prod_{j=1}^N \left(e^{\sqrt{I_{2j}/S_{2j}I_s}} - 1 \right) = \prod_{j=1}^N \left(e^{\sqrt{I_{2j-1}/S_{2j-1}I_s}} - 1 \right)$$

$$\prod_{j \in \text{CW}} \left(e^{\sqrt{I_j/S_jI_s}} - 1 \right) = \prod_{j \in \text{CCW}} \left(e^{\sqrt{I_j/S_jI_s}} - 1 \right),$$

which is a generalized TLP for alternating loops of saturated MOS transistors.

Generalized MOS TLP: Weak Inversion Limit

If $I_j \ll S_j I_s$ (i.e., weak inversion operation) for all j ,

$$\prod_{j \in \text{CW}} \left(e^{\sqrt{I_j/S_j I_s}} - 1 \right) = \prod_{j \in \text{CCW}} \left(e^{\sqrt{I_j/S_j I_s}} - 1 \right)$$

$$\prod_{j \in \text{CW}} \left(1 + \sqrt{\frac{I_j}{S_j I_s}} - 1 \right) = \prod_{j \in \text{CCW}} \left(1 + \sqrt{\frac{I_j}{S_j I_s}} - 1 \right)$$

$$\prod_{j \in \text{CW}} \sqrt{\frac{I_j}{S_j I_s}} = \prod_{j \in \text{CCW}} \sqrt{\frac{I_j}{S_j I_s}}$$

$$\prod_{j \in \text{CW}} \sqrt{\frac{I_j}{S_j}} = \prod_{j \in \text{CCW}} \sqrt{\frac{I_j}{S_j}}$$

$$\prod_{j \in \text{CW}} \frac{I_j}{S_j} = \prod_{j \in \text{CCW}} \frac{I_j}{S_j}$$

Generalized MOS TLP: Strong Inversion Limit

If $I_j \gg S_j I_s$ (i.e., strong inversion operation) for all j ,

$$\prod_{j \in \text{CW}} \left(e^{\sqrt{I_j/S_j I_s}} - 1 \right) = \prod_{j \in \text{CCW}} \left(e^{\sqrt{I_j/S_j I_s}} - 1 \right)$$


$$\prod_{j \in \text{CW}} e^{\sqrt{I_j/S_j I_s}} = \prod_{j \in \text{CCW}} e^{\sqrt{I_j/S_j I_s}}$$

$$\exp \left(\sum_{j \in \text{CW}} \sqrt{\frac{I_j}{S_j I_s}} \right) = \exp \left(\sum_{j \in \text{CCW}} \sqrt{\frac{I_j}{S_j I_s}} \right)$$

$$\sum_{j \in \text{CW}} \sqrt{\frac{I_j}{S_j I_s}} = \sum_{j \in \text{CCW}} \sqrt{\frac{I_j}{S_j I_s}}$$

$$\sum_{j \in \text{CW}} \sqrt{\frac{I_j}{S_j}} = \sum_{j \in \text{CCW}} \sqrt{\frac{I_j}{S_j}}$$

Simple MOS Translinear Circuit

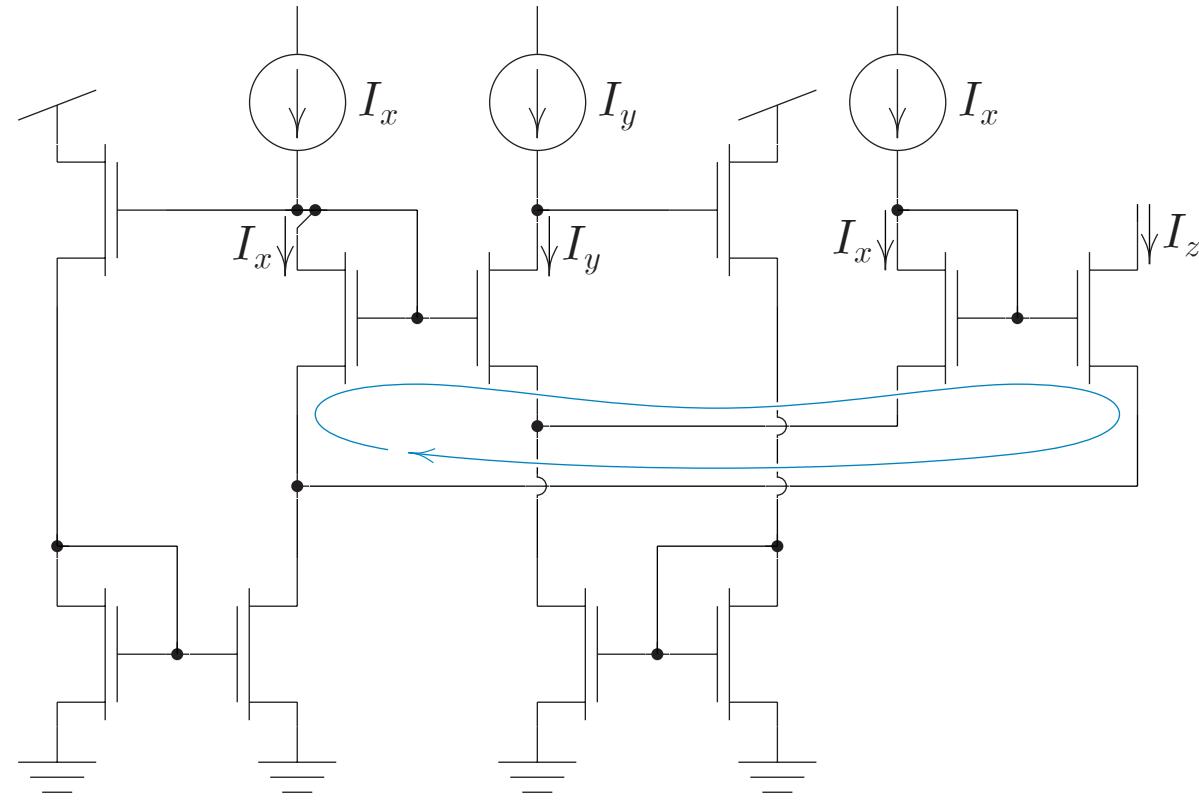

Simple MOS Translinear Circuit


By applying the generalized TLP around the loop indicated, we have that

$$\left(e^{\sqrt{I_y/SI_s}} - 1\right) \left(e^{\sqrt{I_z/SI_s}} - 1\right) = \left(e^{\sqrt{I_x/SI_s}} - 1\right)^2,$$

which we can solve for I_z , thereby obtaining

$$\begin{aligned} I_z &= SI_s \log^2 \left(1 + \frac{\left(e^{\sqrt{I_x/SI_s}} - 1\right)^2}{e^{\sqrt{I_y/SI_s}} - 1} \right) \\ &\approx \begin{cases} \frac{I_x^2}{I_y}, & I_x, I_y, I_z \ll SI_s \\ 4I_x + I_y - 4\sqrt{I_x I_y}, & I_x, I_y, I_z \gg SI_s. \end{cases} \end{aligned}$$

Simple MOS Translinear Circuit

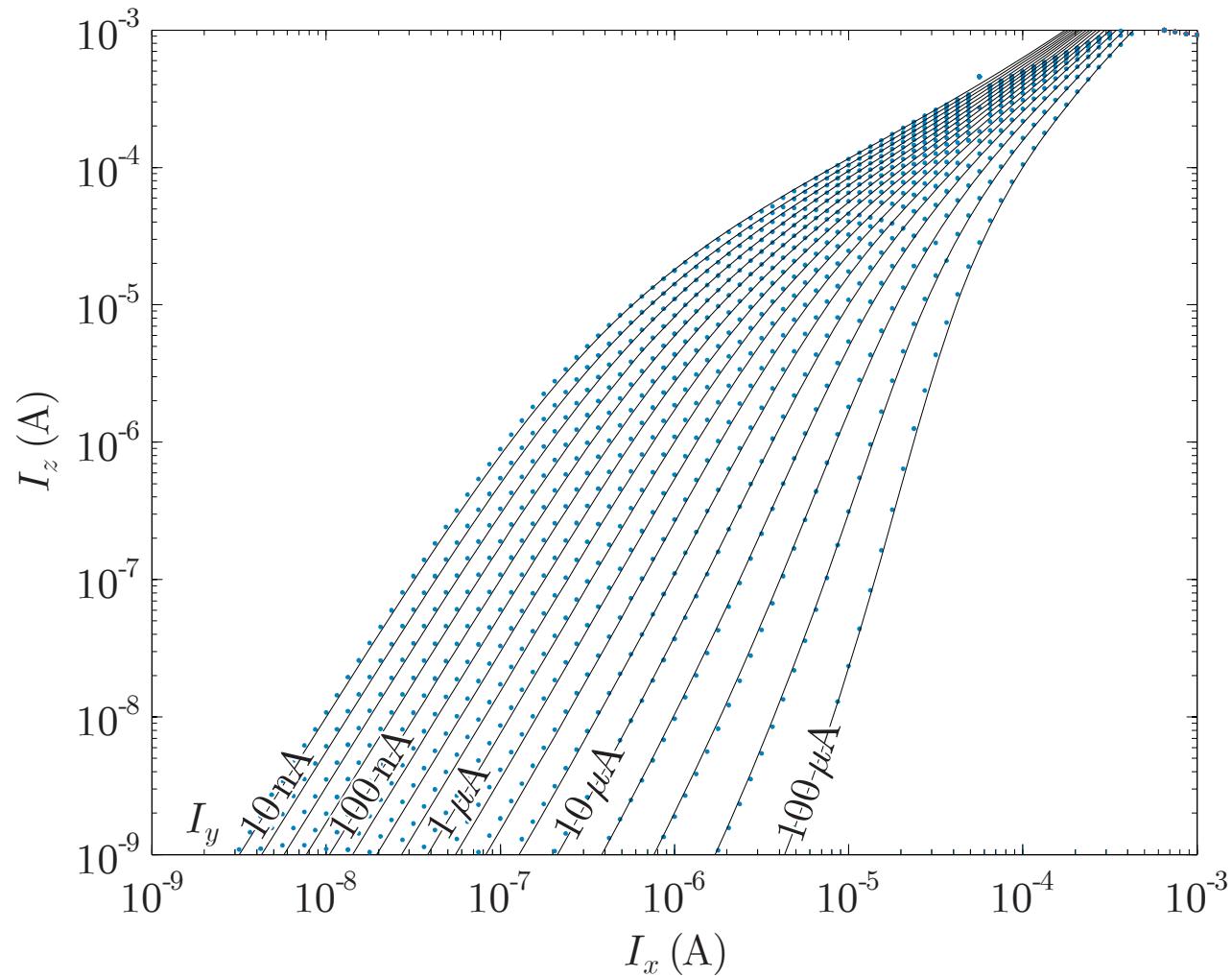

Simple MOS Translinear Circuit

