

A Simple Class-AB Transconductor in CMOS

Bradley A. Minch

Mixed Analog-Digital VLSI Circuits and Systems Lab
Franklin W. Olin College of Engineering
Needham, MA 02492-1200

bradley.minch@olin.edu

May 19, 2008



Simple EKV MOS Transistor Model

We model the channel current of an n MOS transistor as the difference between a forward current and a reverse current,

$$I = I_F - I_R,$$


whose values are given by

$$I_{F(R)} = SI_s \log^2 \left(1 + e^{(\kappa(V_G - V_{T0}) - V_{S(D)})/2U_T} \right),$$

where

$$U_T = \frac{kT}{q}, \quad S = \frac{W}{L}, \quad I_s = \frac{2\mu C_{ox} U_T^2}{\kappa}, \quad \text{and} \quad \kappa = \frac{C_{ox}}{C_{ox} + C_{dep}}.$$

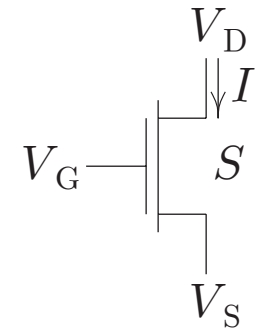
Note that SI_s is approximately twice the saturation current at threshold. This simple model covers all regions of normal MOS transistor operation.



Simple EKV MOS Transistor Model

The expressions for I_F and I_R reduce asymptotically to an exponential form in weak inversion and a quadratic form in strong inversion, given by
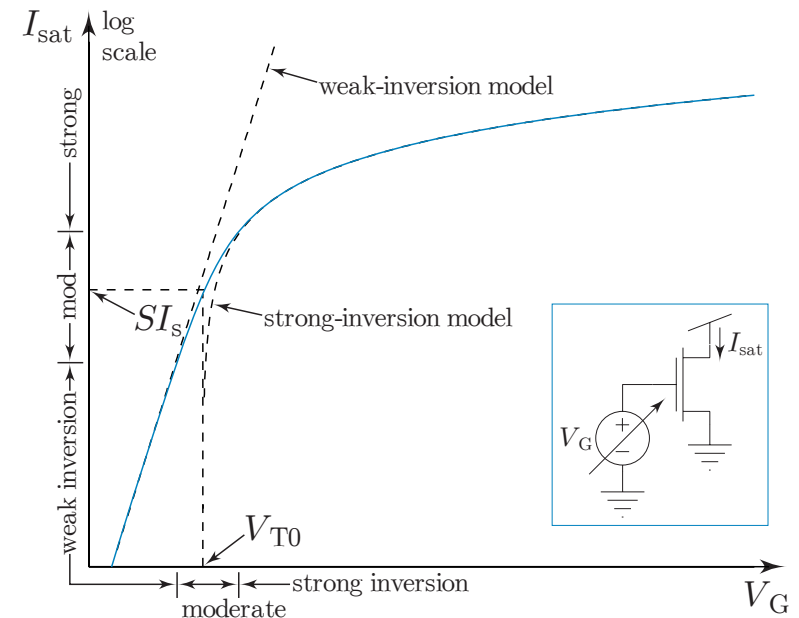
$$I_{F(R)} \approx \begin{cases} SI_s e^{(\kappa(V_G - V_{T0}) - V_{S(D)})/U_T}, & V_G < V_{T0} + \frac{V_{S(D)}}{\kappa} \\ \frac{SI_s}{4U_T^2} (\kappa(V_G - V_{T0}) - V_{S(D)})^2, & V_G > V_{T0} + \frac{V_{S(D)}}{\kappa} \end{cases}$$



Simple EKV MOS Transistor Model

The expressions for I_F and I_R are also explicitly invertible; the inverses are given by


$$\begin{aligned} \kappa (V_G - V_{T0}) - V_{S(D)} &= 2U_T \log \left(e^{\sqrt{I_{F(R)}/SI_s}} - 1 \right) \\ &\approx \begin{cases} U_T \log \frac{I_{F(R)}}{SI_s}, & I_{F(R)} \ll SI_s \\ 2U_T \sqrt{\frac{I_{F(R)}}{SI_s}}, & I_{F(R)} \gg SI_s. \end{cases} \end{aligned}$$

Delbrück's Bump/Antibump Circuit

If the bias current, I_b , is in weak inversion, then the **bump current**, I_3 , is an even-symmetric, bell-shaped function of the differential-mode input voltage, $V_{dm} = V_1 - V_2$, given by

$$I_3 = \frac{I_b}{2} \operatorname{sech}^2 \left(\frac{\kappa V_{dm}}{2U_T} \right).$$

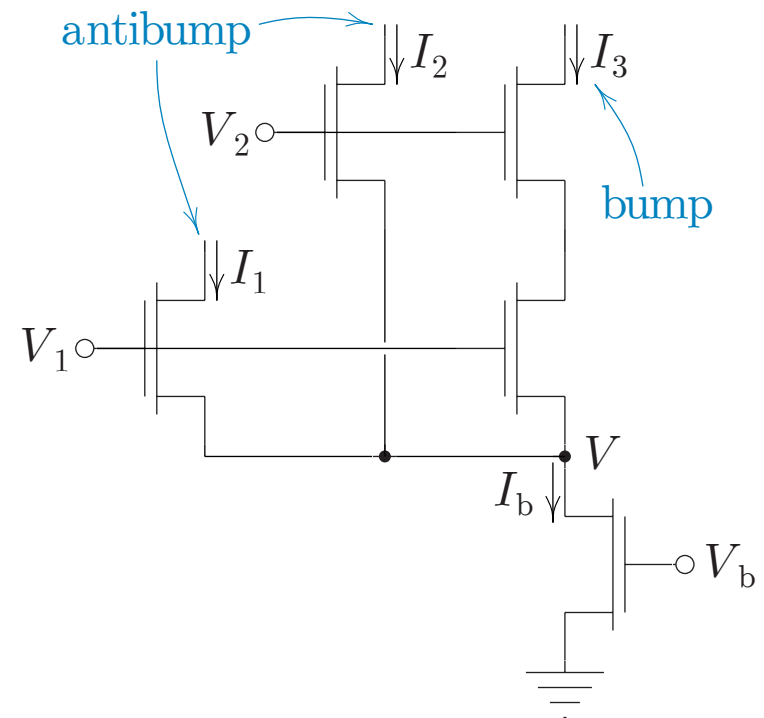Note that the three output currents sum to a constant, I_b , so the sum $I_1 + I_2$ is just I_b less the bump current, which is the **antibump current**.



A Variation of the Bump/Antibump Circuit


Now, suppose that we fix the bump current to be a constant, I_b . If I_1 , I_2 , and I_b are in weak inversion, we have that

$$I_1 = SI_s e^{(\kappa(V_1 - V_{T0}) - V)/U_T},$$

$$I_2 = SI_s e^{(\kappa(V_2 - V_{T0}) - V)/U_T},$$

and
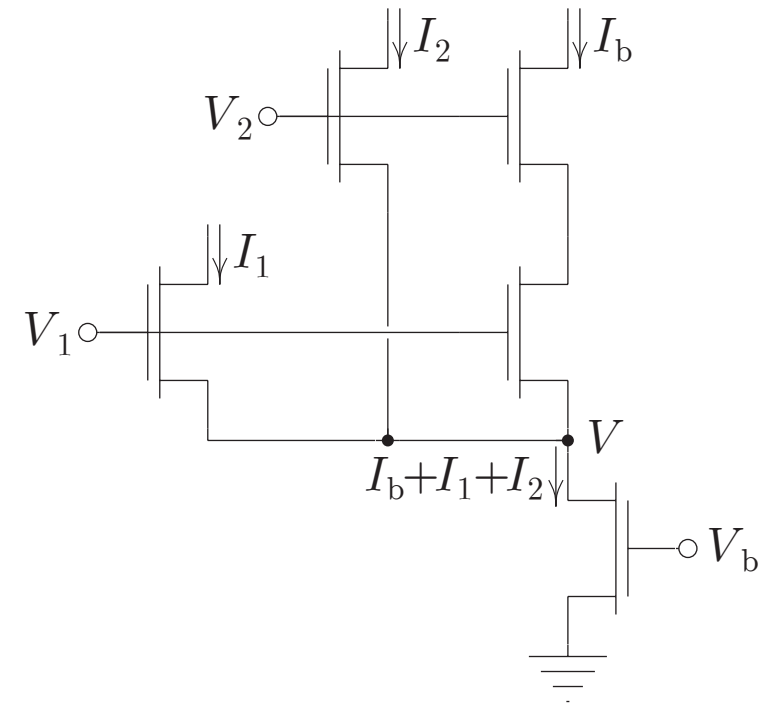
$$I_b = \frac{I_1 I_2}{I_1 + I_2} = I_1 \parallel I_2.$$



A Variation of the Bump/Antibump Circuit

Now, consider the quantity

$$\begin{aligned} I_b &= I_1 \parallel I_2 \\ &= S I_s e^{(\kappa(V_1 - V_{T0}) - V)/U_T} \parallel S I_s e^{(\kappa(V_2 - V_{T0}) - V)/U_T} \\ &= S I_s e^{-\kappa V_{T0}/U_T} e^{-V/U_T} \left(e^{\kappa V_1/U_T} \parallel e^{\kappa V_2/U_T} \right), \end{aligned}$$

which implies that

$$S I_s e^{-\kappa V_{T0}/U_T} e^{-V/U_T} = \frac{I_b}{e^{\kappa V_1/U_T} \parallel e^{\kappa V_2/U_T}}.$$

A Variation of the Bump/Antibump Circuit

By substituting this result back into the equations for I_1 and I_2 , we find that

$$I_1 = \frac{I_b e^{\kappa V_1 / U_T}}{e^{\kappa V_1 / U_T} \parallel e^{\kappa V_2 / U_T}} = I_b \left(1 + e^{\kappa(V_1 - V_2) / U_T} \right) = I_b \left(1 + e^{\kappa V_{dm} / U_T} \right),$$



that

$$I_2 = \frac{I_b e^{\kappa V_2 / U_T}}{e^{\kappa V_1 / U_T} \parallel e^{\kappa V_2 / U_T}} = I_b \left(1 + e^{-\kappa(V_1 - V_2) / U_T} \right) = I_b \left(1 + e^{-\kappa V_{dm} / U_T} \right),$$


and that

$$I_1 - I_2 = I_b \left(e^{\kappa V_{dm} / U_T} - e^{-\kappa V_{dm} / U_T} \right) = 2I_b \sinh \left(\frac{\kappa V_{dm}}{U_T} \right).$$

Fixing the Bump Current at I_b

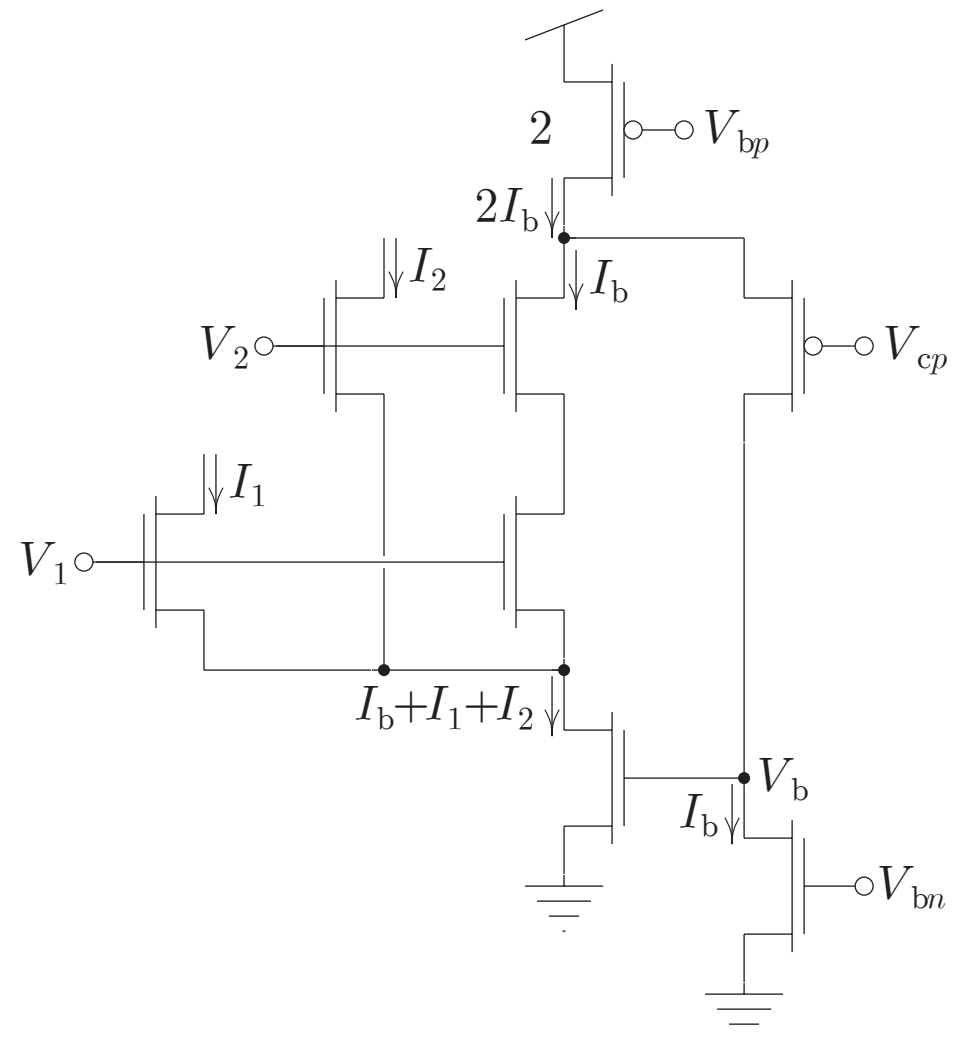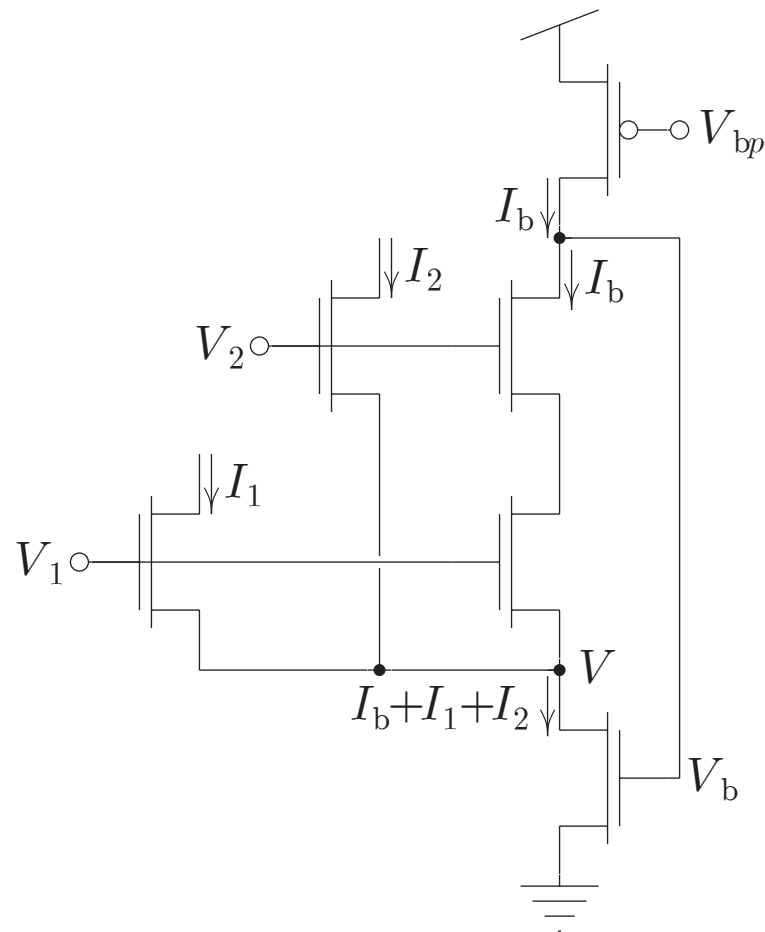

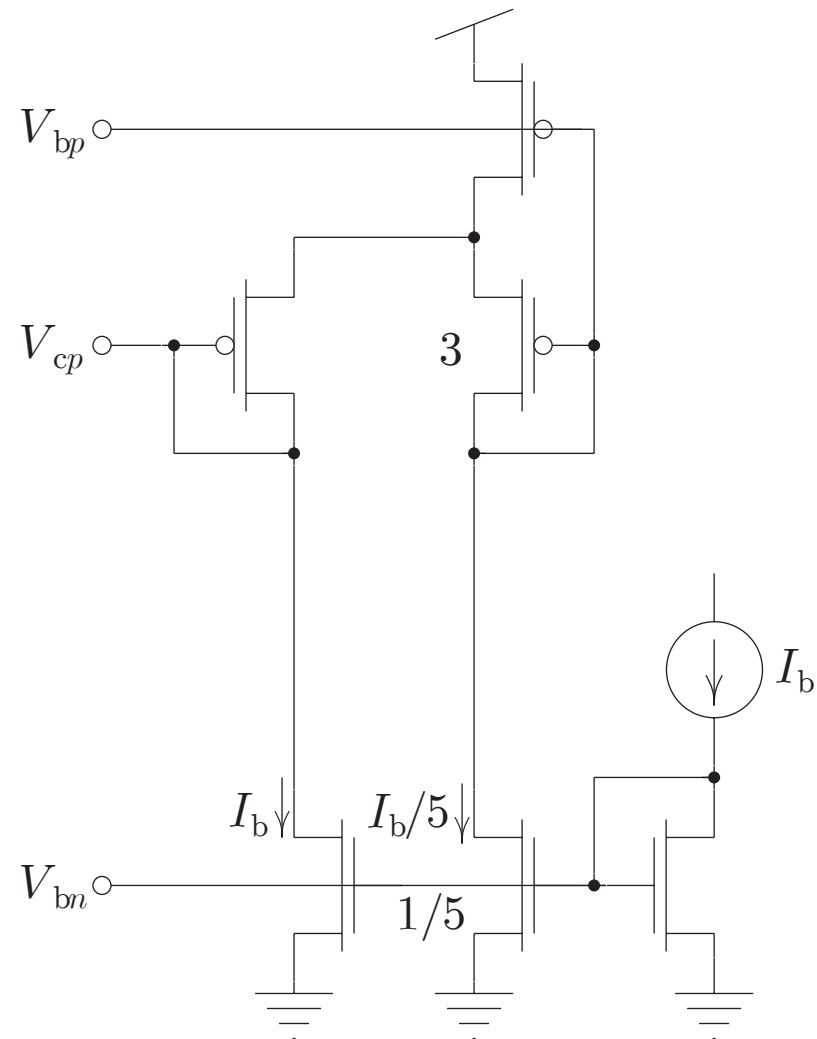Bias Circuit for Folded-Cascode/Flipped-Follower



Analytical Model of Output Current versus V_{dm}

By using the simplified EKV model of the MOS transistor, we can show that

$$I_1 = I_b + SI_s \log^2 \left(1 + e^{\kappa V_{dm}/2U_T} \left(e^{\sqrt{I_b/SI_s}} - 1 \right) \right)$$


and that

$$I_2 = SI_s \log^2 \left(1 + e^{-\kappa V_{dm}/2U_T} \left(e^{\sqrt{I_1/SI_s}} - 1 \right) \right),$$


where all the symbols have their previously defined meanings.

Note that the model equation for I_2 is expressed in terms of I_1 , which, in turn, is an explicit function of V_{dm} . So, we can obtain explicit expressions for I_2 and $I_1 - I_2$ in terms of V_{dm} , but it is unclear that doing so is of much value, because doing so leads to *very* cumbersome expressions.


Output Currents versus V_{dm}

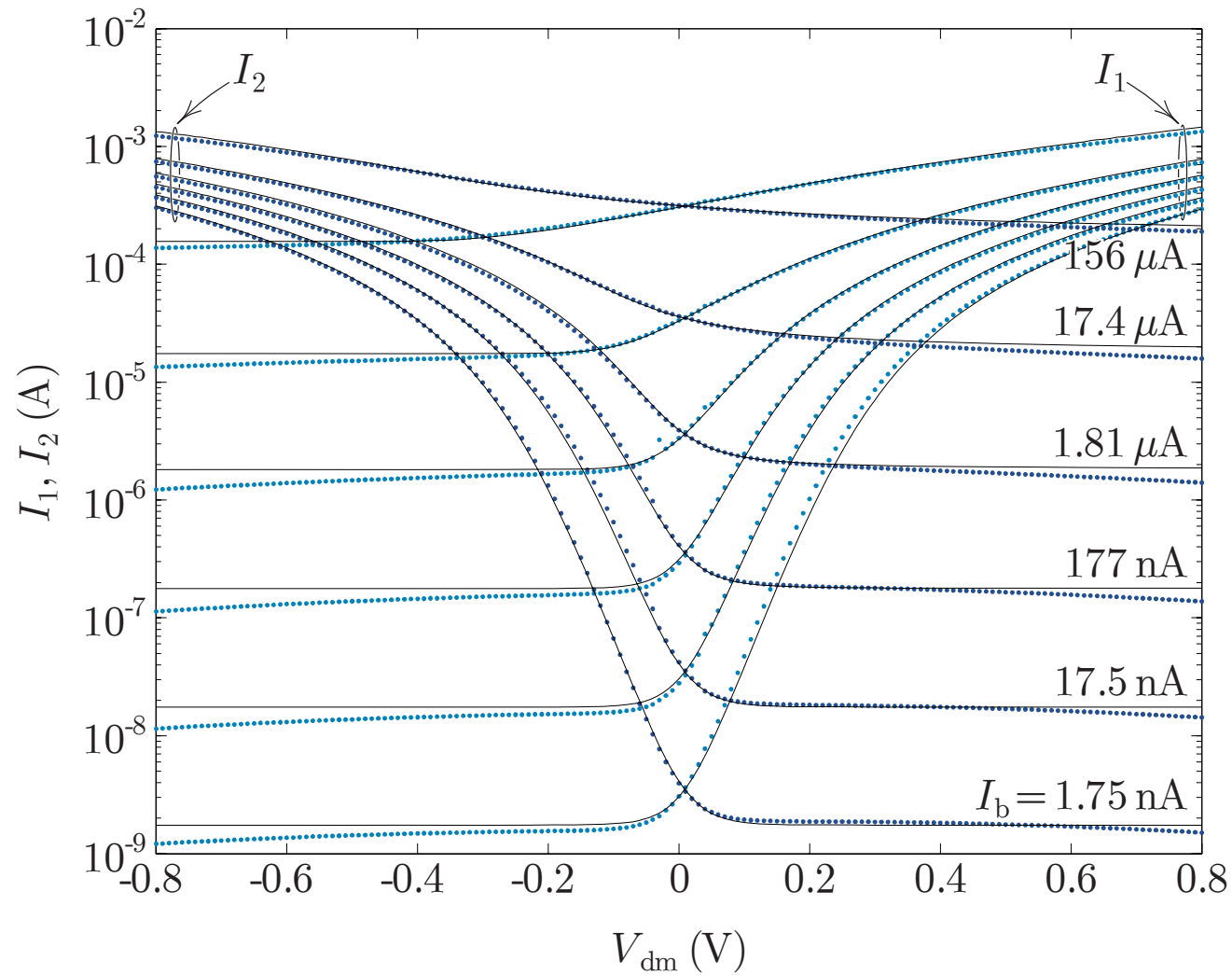

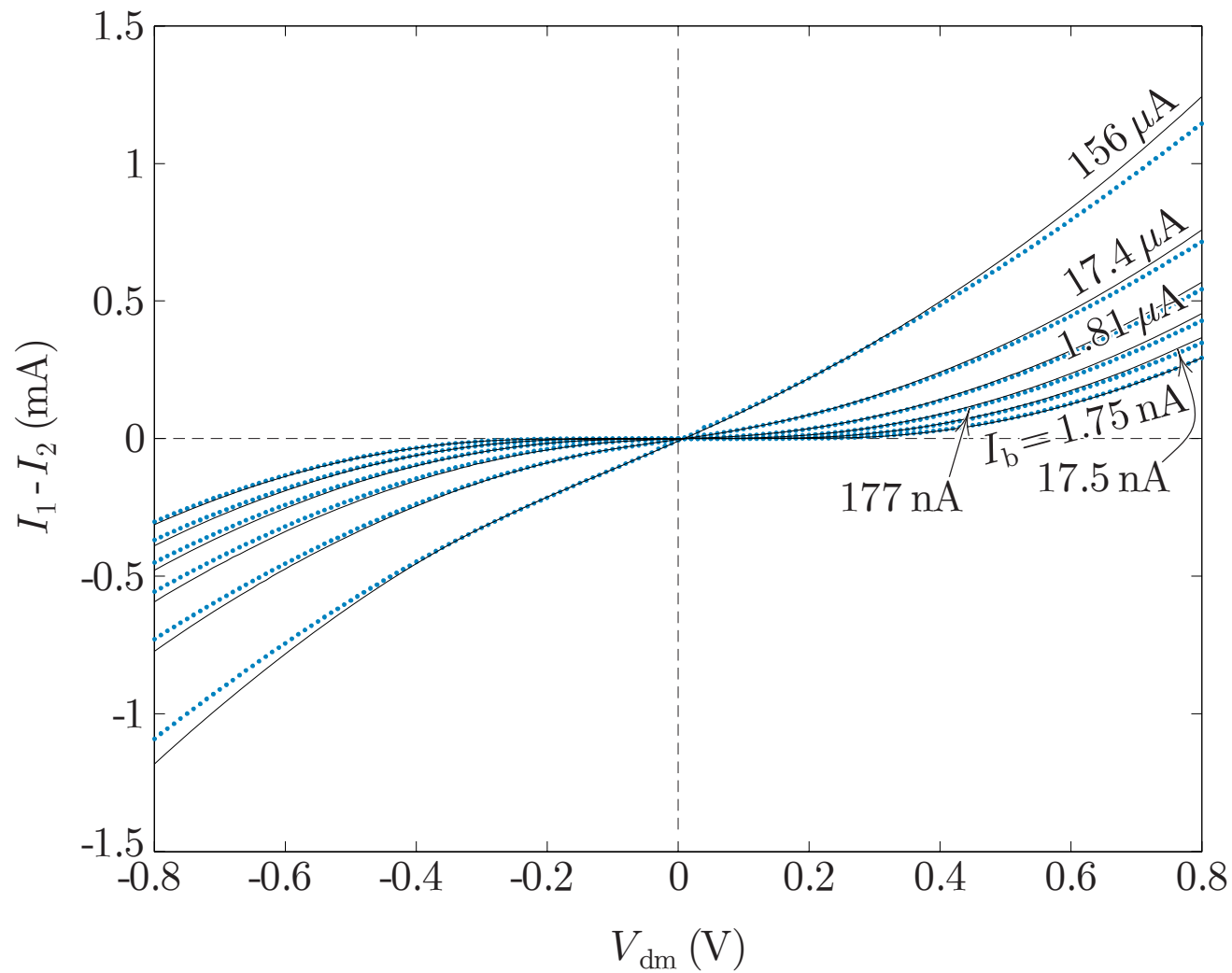
Differential Output Current versus V_{dm}



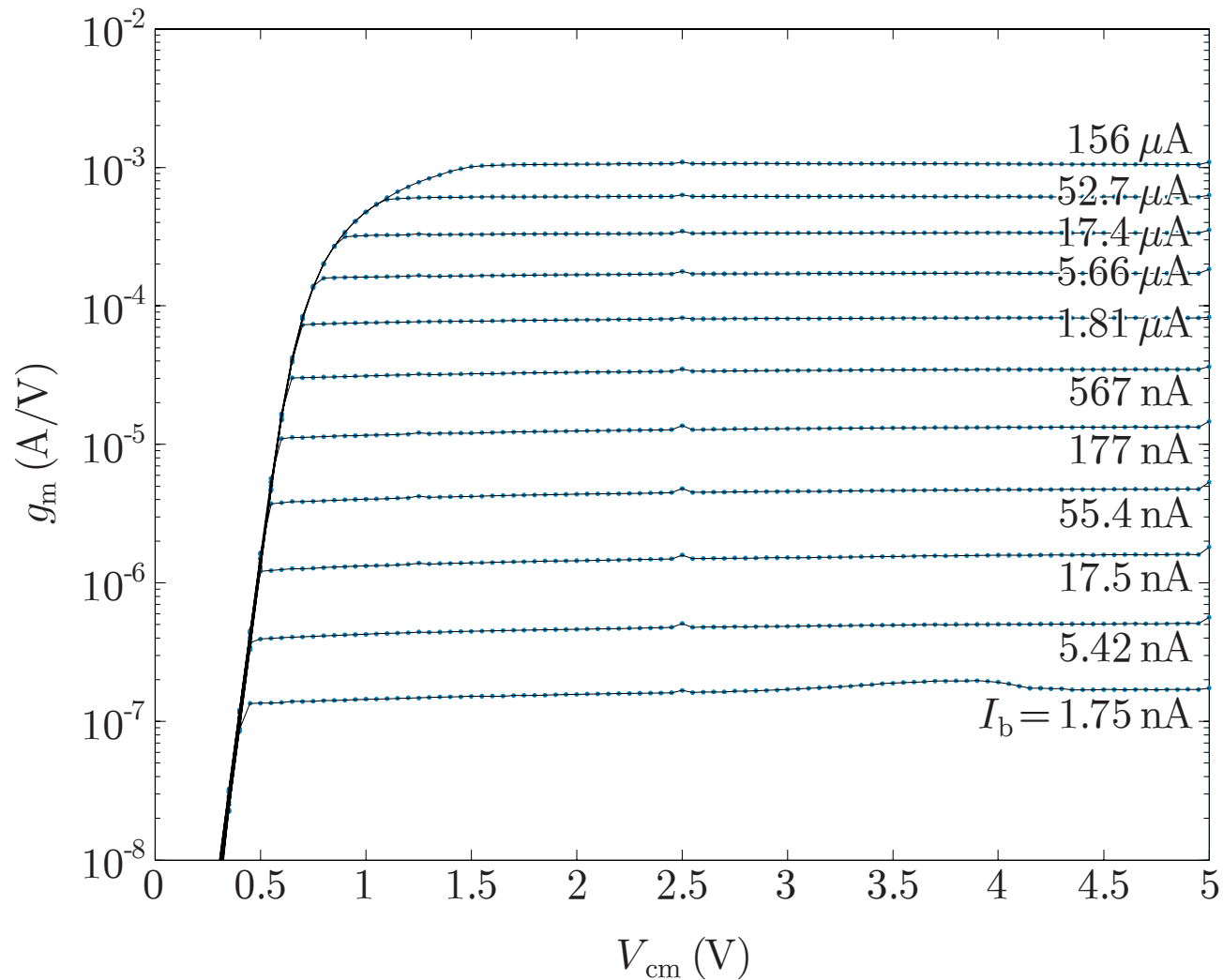Differential-Mode Transconductance versus V_{cm}



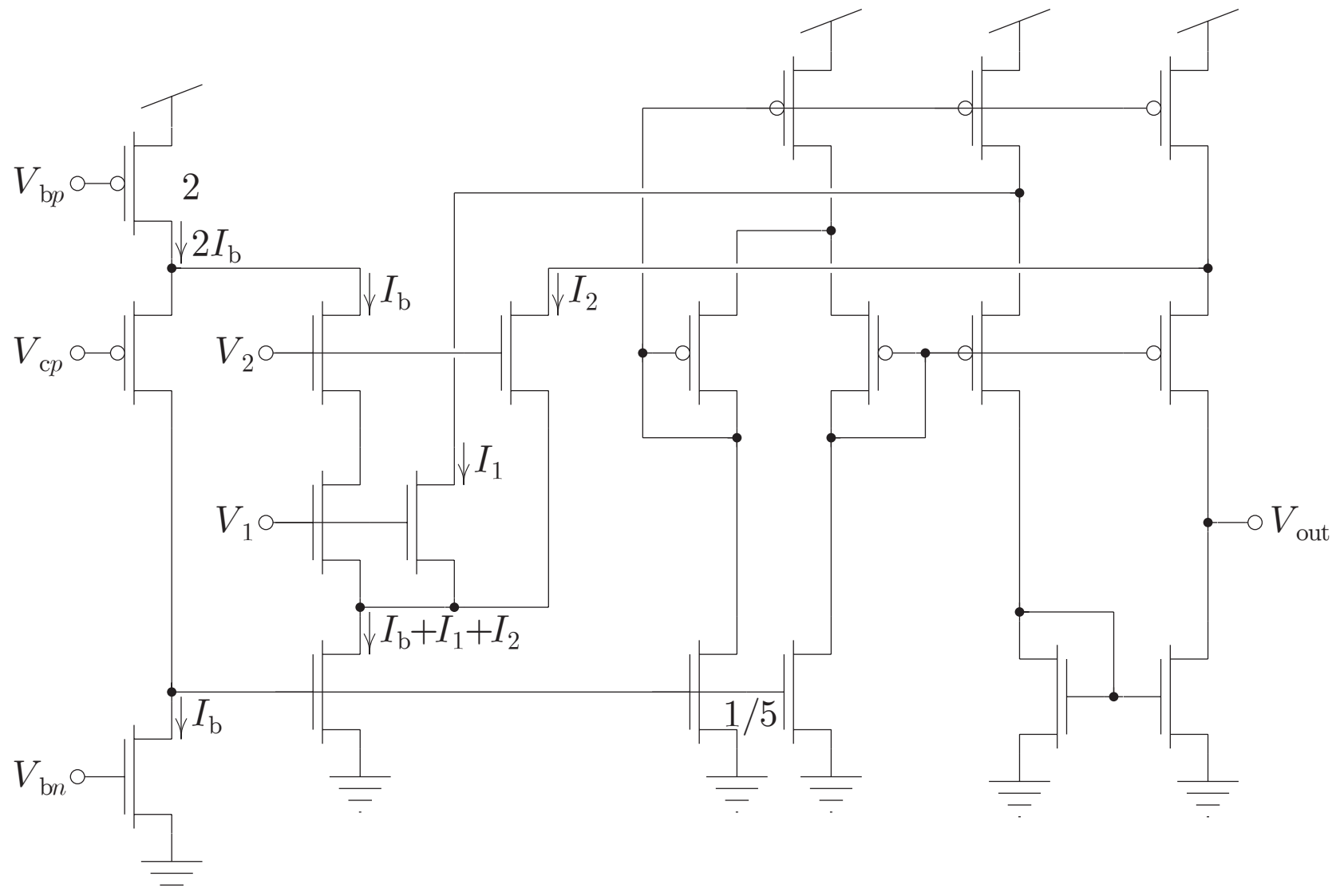Enhanced-Slew-Rate Folded-Cascode Amplifier



Enhanced-Slew-Rate Folded-Cascode Amplifier Step Response

