

# Static and Dynamic Translinear Circuits

Bradley A. Minch

Mixed Analog-Digital VLSI Circuits and Systems Lab  
Franklin W. Olin College of Engineering  
Needham, MA 02492-1200

[bradley.minch@olin.edu](mailto:bradley.minch@olin.edu)

May 20, 2010



---

## Translinear Circuits: What's in a Name?

In 1975, Barrie Gilbert coined the term *translinear* to describe a class of circuits whose large-signal behavior hinges both on the precise exponential  $I/V$  relationship of the bipolar transistor and on the intimate thermal contact and close matching of monolithically integrated devices.

## Translinear Circuits: What's in a Name?

In 1975, Barrie Gilbert coined the term *translinear* to describe a class of circuits whose large-signal behavior hinges both on the precise exponential  $I/V$  relationship of the bipolar transistor and on the intimate thermal contact and close matching of monolithically integrated devices.

The word *translinear* refers to the exponential  $I/V$  characteristic of the bipolar transistor—its *transconductance* is *linear* in its collector current:

$$I_C = I_s e^{V_{BE}/U_T} \implies g_m = \frac{\partial I_C}{\partial V_B} = \underbrace{I_s e^{V_{BE}/U_T}}_{I_C} \cdot \frac{1}{U_T} = \frac{I_C}{U_T}.$$

## Translinear Circuits: What's in a Name?



In 1975, Barrie Gilbert coined the term *translinear* to describe a class of circuits whose large-signal behavior hinges both on the precise exponential  $I/V$  relationship of the bipolar transistor and on the intimate thermal contact and close matching of monolithically integrated devices.

The word *translinear* refers to the exponential  $I/V$  characteristic of the bipolar transistor—its *transconductance* is *linear* in its collector current:



$$I_C = I_s e^{V_{BE}/U_T} \implies g_m = \frac{\partial I_C}{\partial V_B} = \underbrace{I_s e^{V_{BE}/U_T}}_{I_C} \cdot \frac{1}{U_T} = \frac{I_C}{U_T}.$$

Gilbert also meant the word *translinear* to refer to circuit analysis and design principles that bridge the gap between the familiar territory of linear circuits and the uncharted domain of nonlinear circuits.
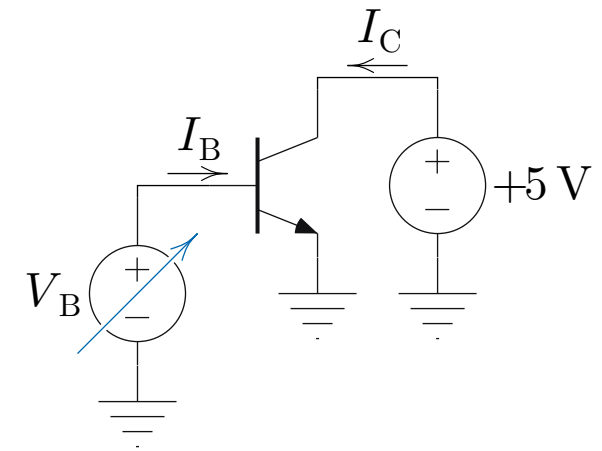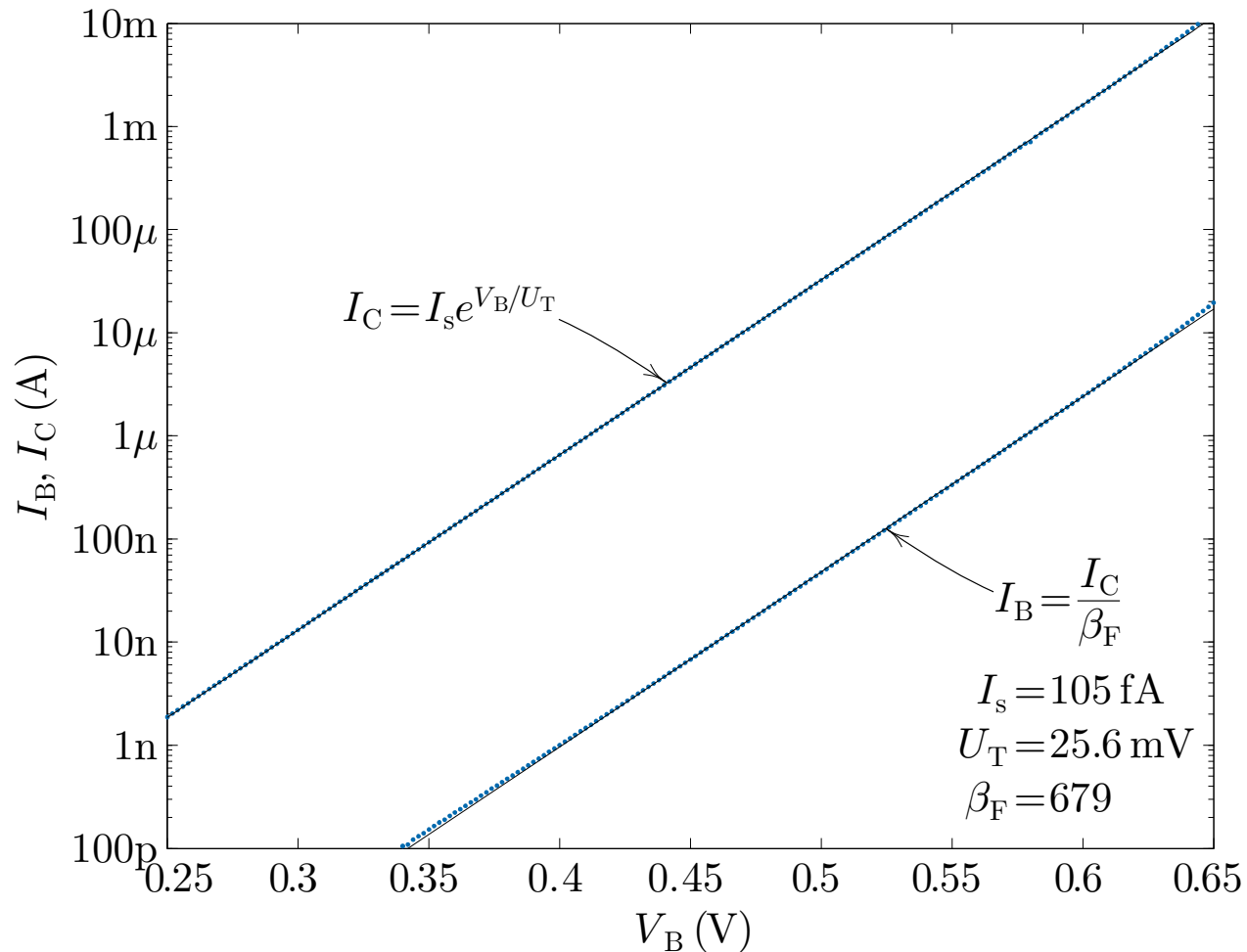
# Gummel Plot of a Forward-Active Bipolar Transistor


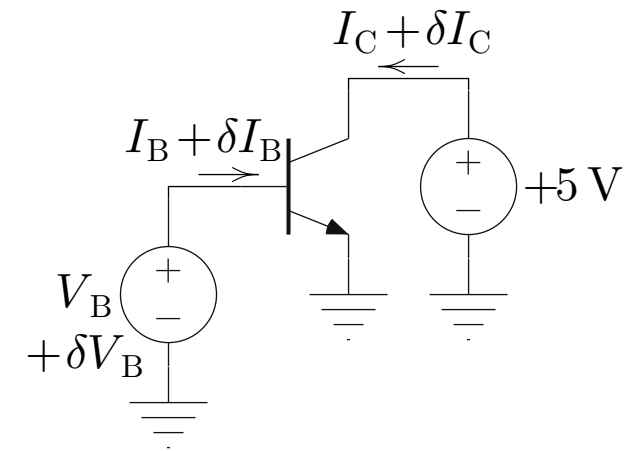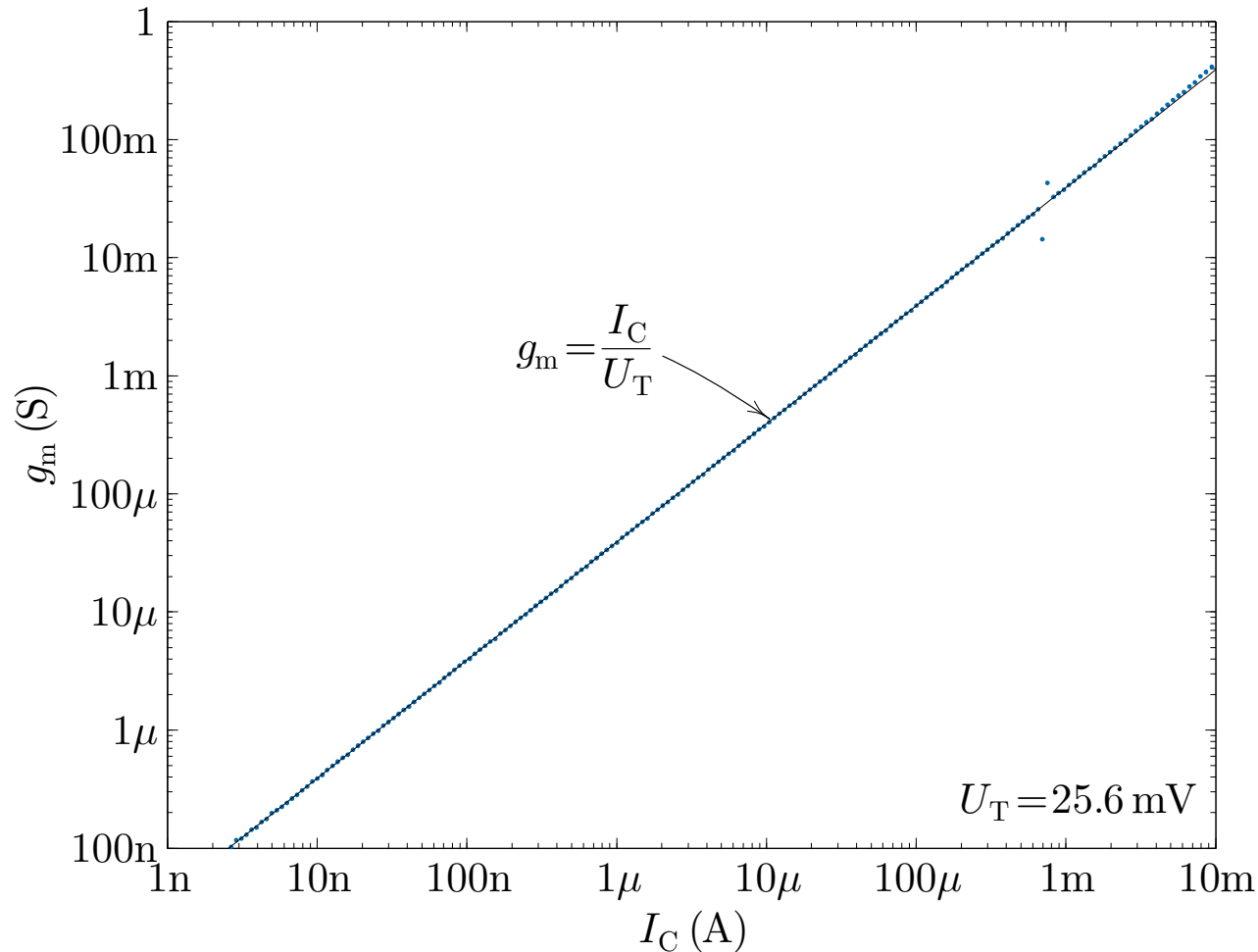
# Translinearity of the Forward-Active Bipolar Transistor




$$g_m = \frac{\partial I_C}{\partial V_B} = \frac{I_C}{U_T}$$

$$\delta I_C \approx g_m \delta V_B$$
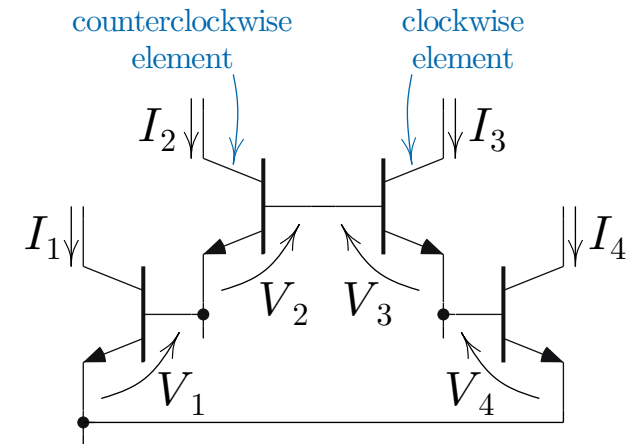
## The Translinear Principle

Consider a closed loop of base-emitter junctions of four closely matched *npn* bipolar transistors biased in the forward-active region and operating at the same temperature. Kirchhoff's voltage law (KVL) implies that

$$\begin{aligned}
 V_1 + V_2 &= V_3 + V_4 \\
 U_T \log \frac{I_1}{I_s} + U_T \log \frac{I_2}{I_s} &= U_T \log \frac{I_3}{I_s} + U_T \log \frac{I_4}{I_s} \\
 \log \frac{I_1 I_2}{I_s^2} &= \log \frac{I_3 I_4}{I_s^2} \\
 \underbrace{I_1 I_2}_{\text{CCW}} &= \underbrace{I_3 I_4}_{\text{CW}}
 \end{aligned}$$



This result is a particular case of Gilbert's *translinear principle* (TLP): The product of the clockwise currents is equal to the product of the counterclockwise currents.

---

# Why Translinear Circuits?



---

## Why Translinear Circuits?

- Translinear circuits are *universal*. *Conjecture*: In principle, we can realize any system whose description we can write down as a nonlinear ODE with time as its independent variable as a dynamic translinear circuit.

---

## Why Translinear Circuits?

- Translinear circuits are *universal*. *Conjecture*: In principle, we can realize any system whose description we can write down as a nonlinear ODE with time as its independent variable as a dynamic translinear circuit.
- Translinear circuits are *synthesizable* via highly structured methods. They should be very amenable to the development both of CAD tools and of reconfigurable FPAA architectures for rapid prototyping and deployment of translinear analog signal processing systems.

## Why Translinear Circuits?

- Translinear circuits are *universal*. *Conjecture*: In principle, we can realize any system whose description we can write down as a nonlinear ODE with time as its independent variable as a dynamic translinear circuit.
- Translinear circuits are *synthesizable* via highly structured methods. They should be very amenable to the development both of CAD tools and of reconfigurable FPAA architectures for rapid prototyping and deployment of translinear analog signal processing systems.
- Translinear circuits are fundamentally *large-signal* circuits. Linear dynamic translinear circuits are linear *because of* device nonlinearities rather than *in spite of* them.

## Why Translinear Circuits?

- Translinear circuits are *universal*. *Conjecture*: In principle, we can realize any system whose description we can write down as a nonlinear ODE with time as its independent variable as a dynamic translinear circuit.
- Translinear circuits are *synthesizable* via highly structured methods. They should be very amenable to the development both of CAD tools and of reconfigurable FPAA architectures for rapid prototyping and deployment of translinear analog signal processing systems.
- Translinear circuits are fundamentally *large-signal* circuits. Linear dynamic translinear circuits are linear *because of* device nonlinearities rather than *in spite of* them.
- Translinear circuits are *tunable* electronically over a wide dynamic range of parameters (e.g., gains, corner frequencies, quality factors).

## Why Translinear Circuits?

- Translinear circuits are *universal*. *Conjecture*: In principle, we can realize any system whose description we can write down as a nonlinear ODE with time as its independent variable as a dynamic translinear circuit.
- Translinear circuits are *synthesizable* via highly structured methods. They should be very amenable to the development both of CAD tools and of reconfigurable FPAA architectures for rapid prototyping and deployment of translinear analog signal processing systems.
- Translinear circuits are fundamentally *large-signal* circuits. Linear dynamic translinear circuits are linear *because of* device nonlinearities rather than *in spite of* them.
- Translinear circuits are *tunable* electronically over a wide dynamic range of parameters (e.g., gains, corner frequencies, quality factors).
- Translinear circuits are *robust*. Carefully designed translinear circuits are temperature insensitive and do not depend on device or technology parameters.

## Simple EKV Model of the Saturated $n$ MOS Transistor

We model the saturation current of an  $n$ MOS transistor by

$$I_{\text{sat}} = SI_s \log^2 \left( 1 + e^{(\kappa(V_G - V_{T0}) - V_S)/2U_T} \right)$$



$$\approx \begin{cases} SI_s e^{(\kappa(V_G - V_{T0}) - V_S)/U_T}, & \kappa(V_G - V_{T0}) - V_S < 0 \\ \frac{SI_s}{4U_T^2} (\kappa(V_G - V_{T0}) - V_S)^2, & \kappa(V_G - V_{T0}) - V_S > 0, \end{cases}$$

where



$$U_T = \frac{kT}{q}, \quad S = \frac{W}{L}, \quad I_s = \frac{2\mu C_{\text{ox}} U_T^2}{\kappa}, \quad \text{and} \quad \kappa = \frac{C_{\text{ox}}}{C_{\text{ox}} + C_{\text{dep}}}.$$

**Weak inversion** operation corresponds to  $I_{\text{sat}} \ll SI_s$ , **moderate inversion** operation corresponds to  $I_{\text{sat}} \approx SI_s$ , and **strong inversion** operation to  $I_{\text{sat}} \gg SI_s$ . Note that  $SI_s$  is approximately twice the saturation current at threshold.
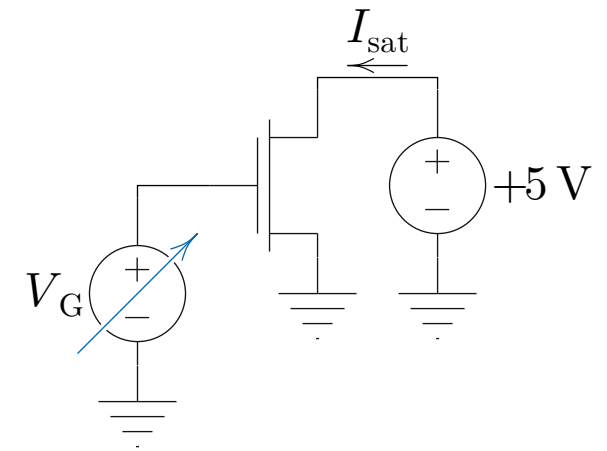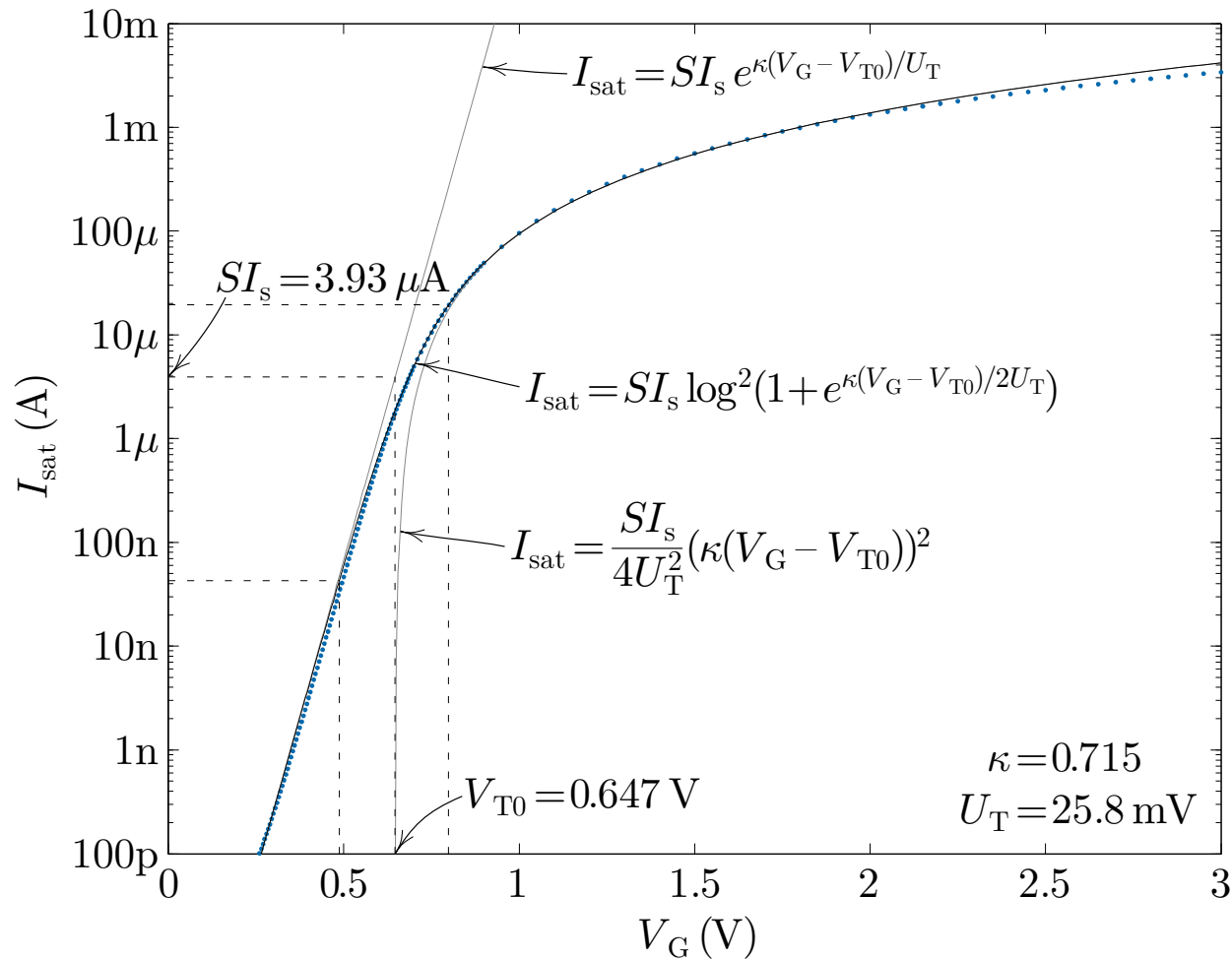
# Saturation Current of an nMOS Transistor


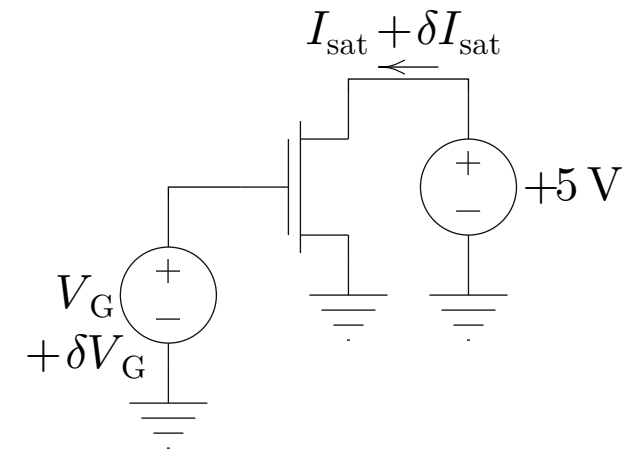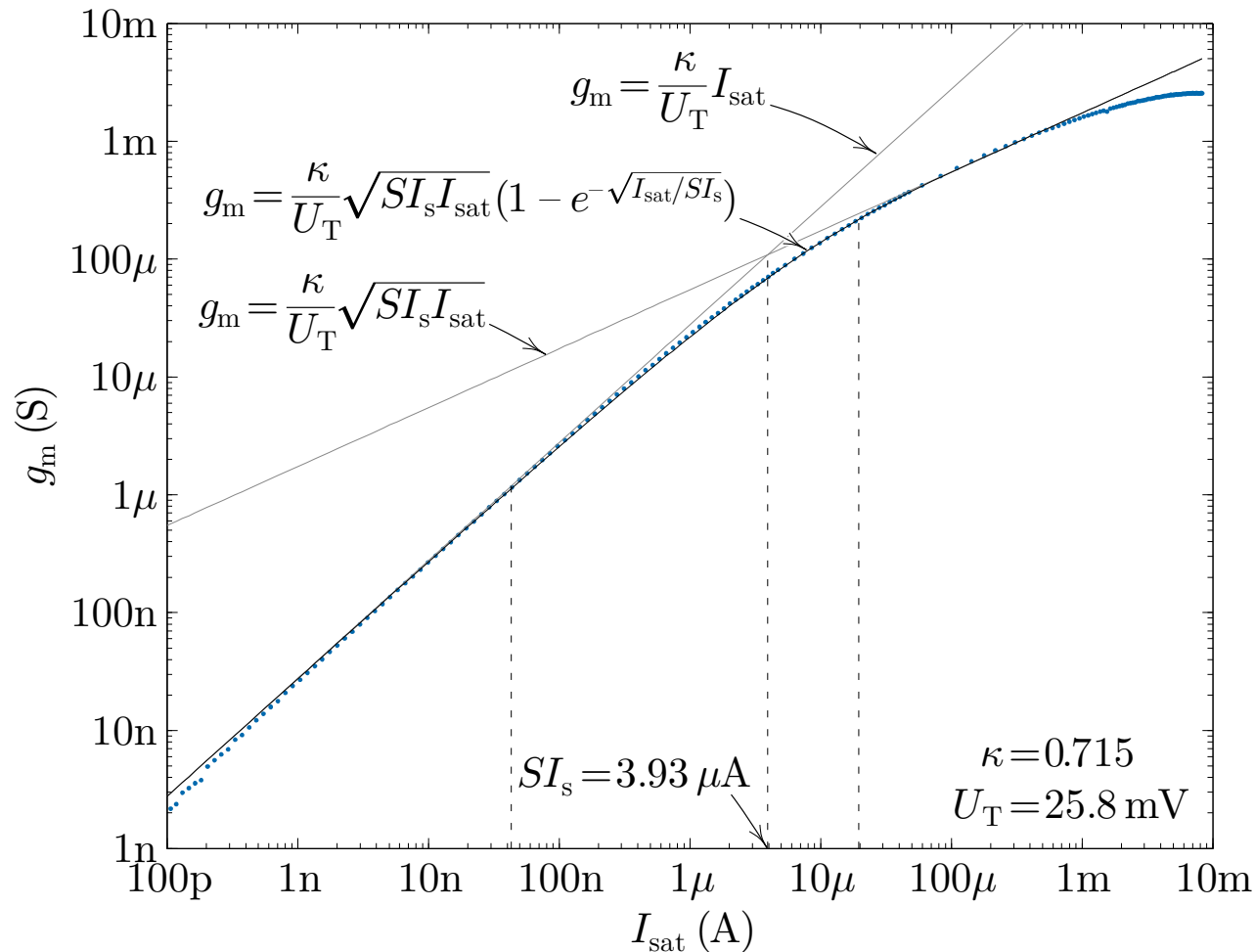
# Translinearity of the Saturated $n$ MOS Transistor




$$g_m = \frac{\partial I_{\text{sat}}}{\partial V_G} = \frac{\kappa I_{\text{sat}}}{U_T}, I_{\text{sat}} \ll S I_s$$

$$\delta I_{\text{sat}} \approx g_m \delta V_G$$



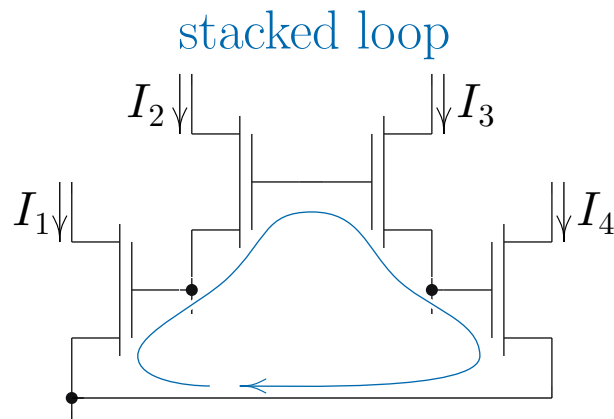
## Weak-Inversion MOS Translinear Principle

When designing weak-inversion MOS translinear circuits, if we restrict ourselves to using translinear loops that **alternate** between clockwise and counterclockwise elements, we obtain Gilbert's original TLP, with no dependence on the body effect (i.e.,  $\kappa$ ).


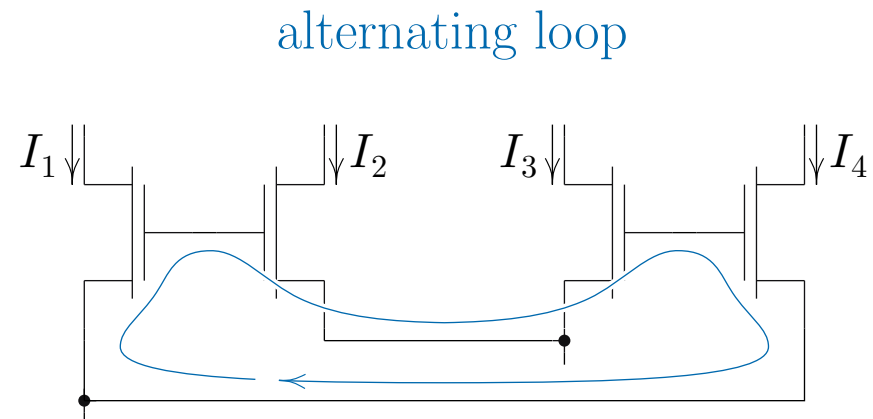
$$\text{TLP: } I_1 I_2^\kappa = I_3^\kappa I_4$$




$$\text{TLP: } I_1 I_3 = I_2 I_4$$



This restriction does not limit the class of systems that we can implement. However, designs based on alternating loops generally consume more current but operate on a lower power supply voltage than do designs based on stacked loops.
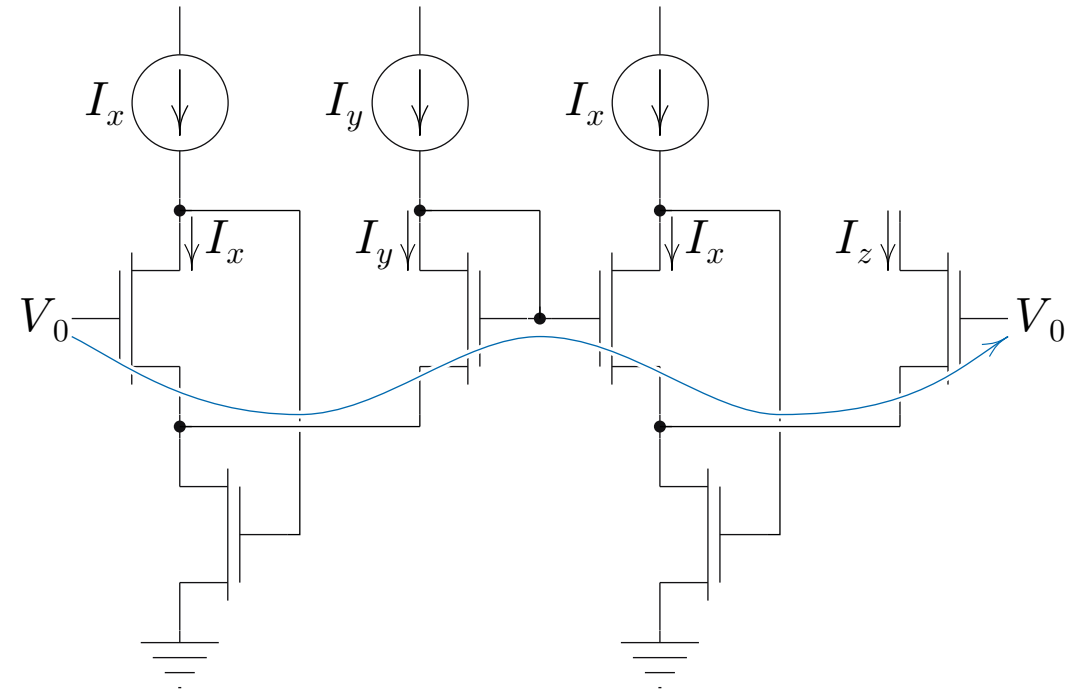
# Static Translinear Circuits: Squaring/Reciprocal

$$\text{TLP} \implies I_x^2 = I_y I_z \implies I_z = \frac{I_x^2}{I_y}$$




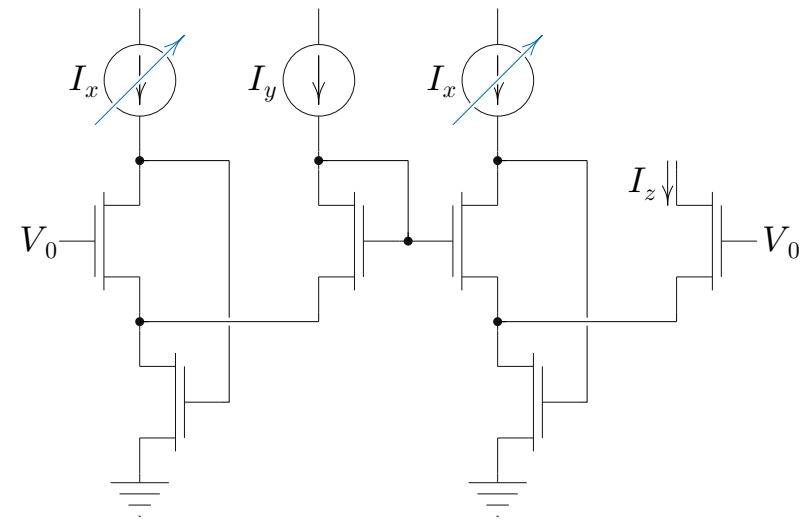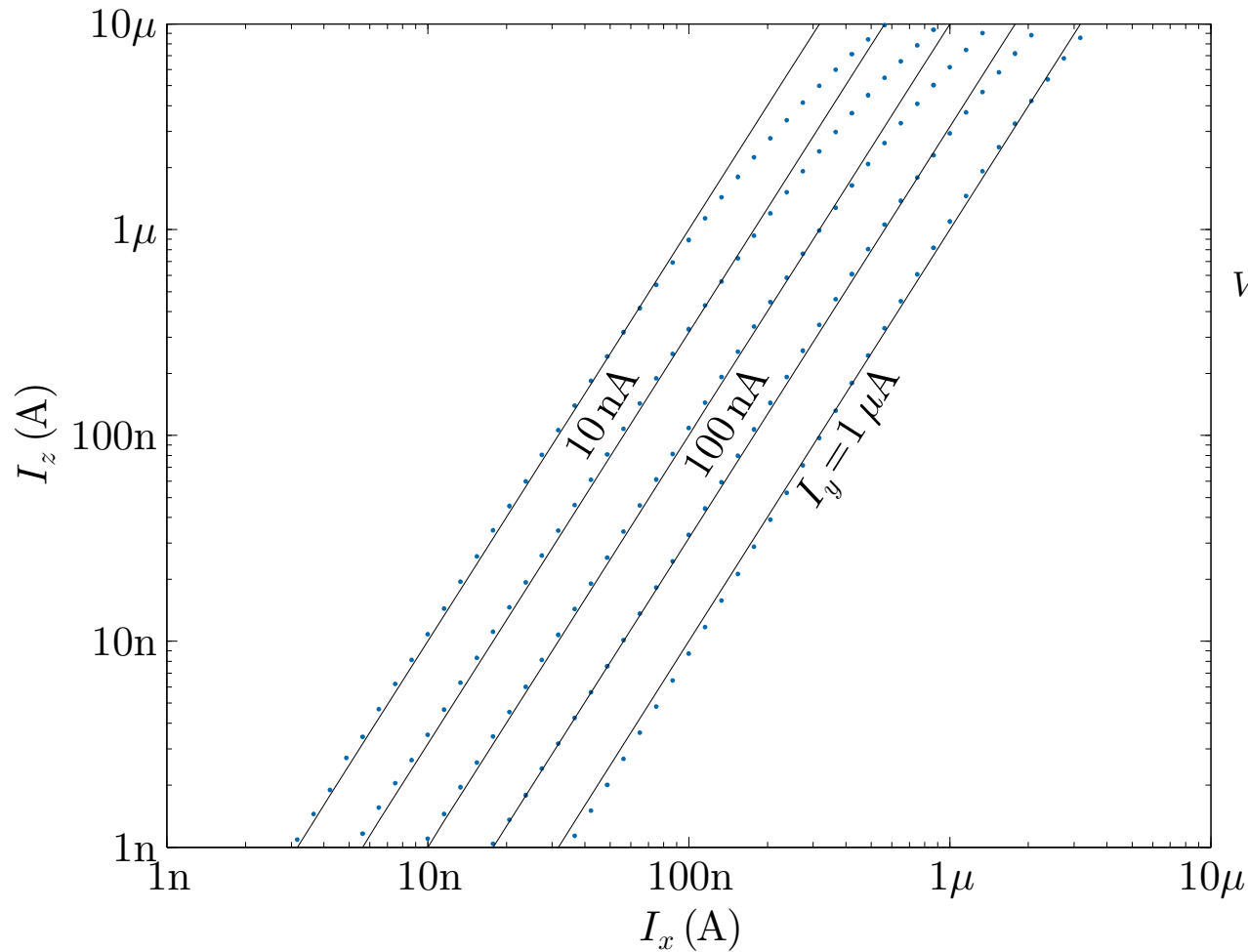
# Static Translinear Circuits: Squaring/Reciprocal



$$I_z = \frac{I_x^2}{I_y}$$
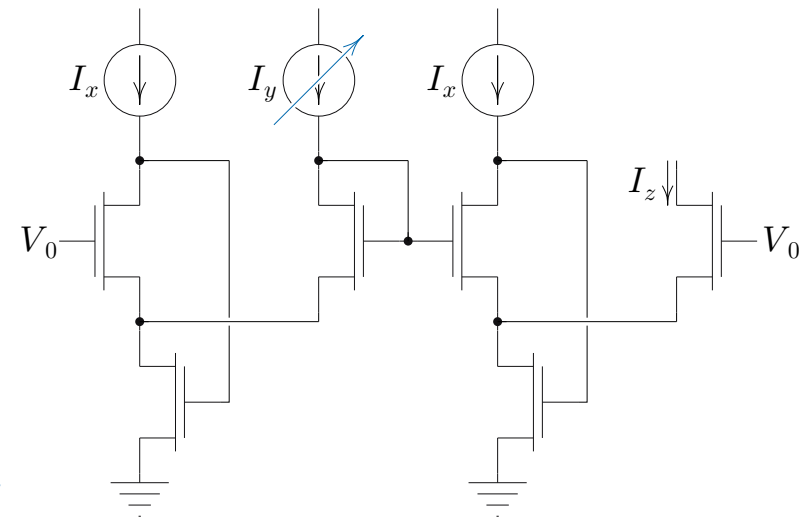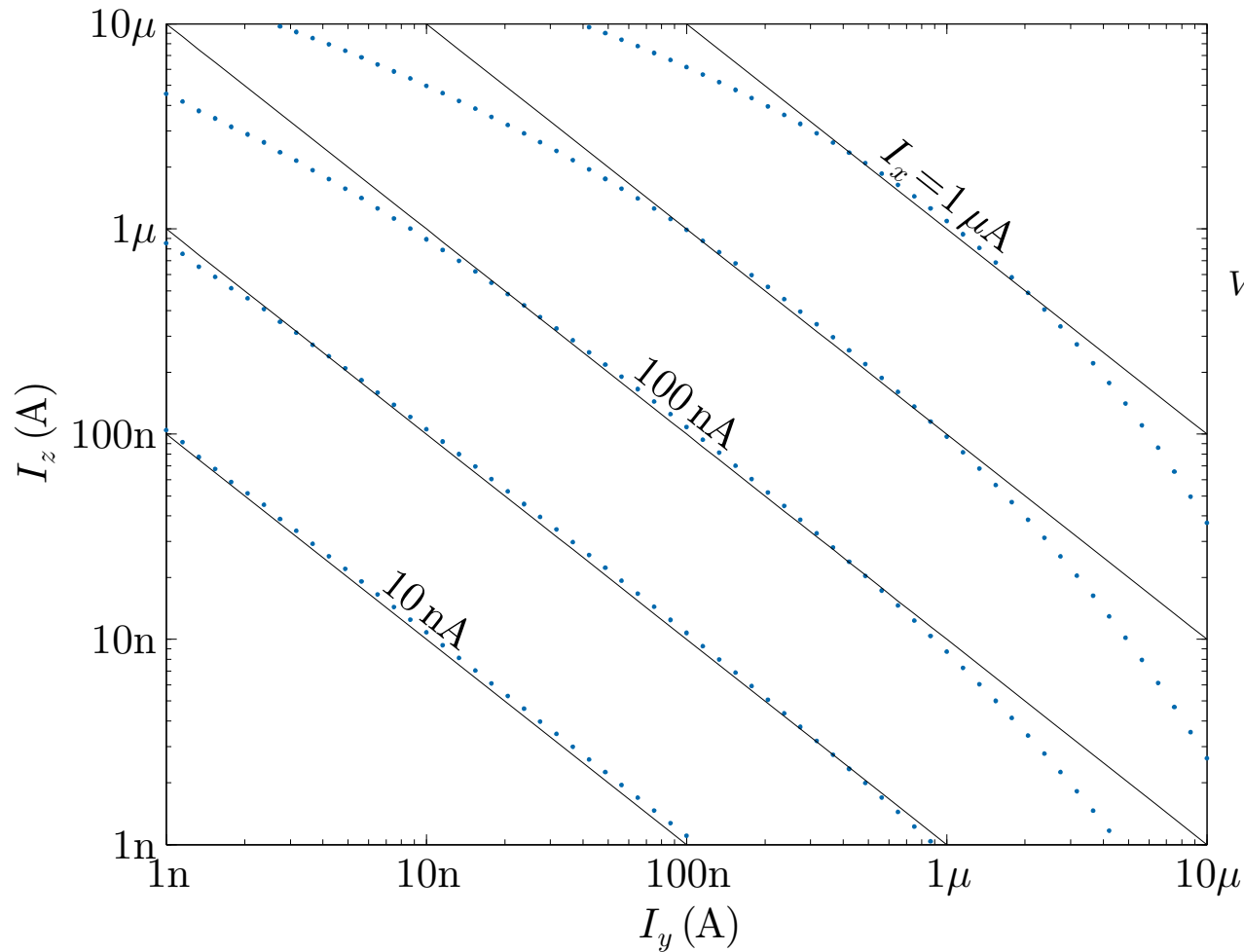
# Static Translinear Circuits: Squaring/Reciprocal



$$I_z = \frac{I_x^2}{I_y}$$

---

## Static Translinear Circuit Synthesis: Pythagorator

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

## Static Translinear Circuit Synthesis: Pythagorator

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

## Static Translinear Circuit Synthesis: Pythagorator

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

We substitute these into the original equation and rearrange to obtain

$$\frac{I_r}{I_1} = \sqrt{\left(\frac{I_x}{I_1}\right)^2 + \left(\frac{I_y}{I_1}\right)^2}$$

## Static Translinear Circuit Synthesis: Pythagorator

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

We substitute these into the original equation and rearrange to obtain

$$\frac{I_r}{I_1} = \sqrt{\left(\frac{I_x}{I_1}\right)^2 + \left(\frac{I_y}{I_1}\right)^2} \quad \Rightarrow \quad I_r^2 = I_x^2 + I_y^2$$



## Static Translinear Circuit Synthesis: Pythagorator

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

We substitute these into the original equation and rearrange to obtain

$$\frac{I_r}{I_1} = \sqrt{\left(\frac{I_x}{I_1}\right)^2 + \left(\frac{I_y}{I_1}\right)^2} \quad \Rightarrow \quad I_r^2 = I_x^2 + I_y^2 \quad \Rightarrow \quad I_r = \frac{I_x^2}{I_r} + \frac{I_y^2}{I_r}$$

## Static Translinear Circuit Synthesis: Pythagorator

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

We substitute these into the original equation and rearrange to obtain

$$\frac{I_r}{I_1} = \sqrt{\left(\frac{I_x}{I_1}\right)^2 + \left(\frac{I_y}{I_1}\right)^2} \quad \Rightarrow \quad I_r^2 = I_x^2 + I_y^2 \quad \Rightarrow \quad I_r = \underbrace{\frac{I_x^2}{I_r}}_{I_{r1}} + \underbrace{\frac{I_y^2}{I_r}}_{I_{r2}}$$

## Static Translinear Circuit Synthesis: Pythagorator


$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$

$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

# Static Translinear Circuit Synthesis: Pythagorator

$$\begin{aligned} \text{TLP: } I_{r1} I_r &= I_x^2 \\ I_{r2} I_r &= I_y^2 \end{aligned}$$



$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

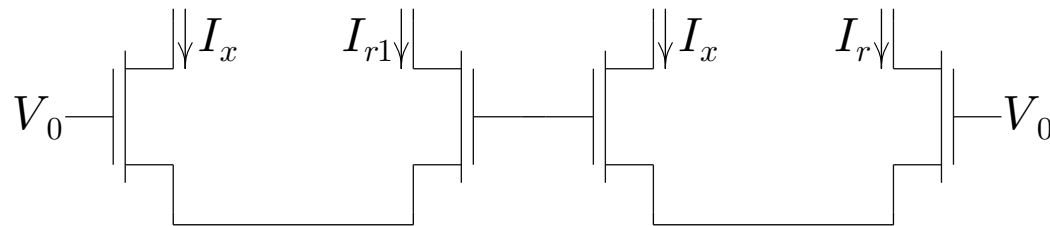

# Static Translinear Circuit Synthesis: Pythagorator

$$\begin{aligned} \text{TLP: } I_{r1} I_r &= I_x^2 \\ I_{r2} I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

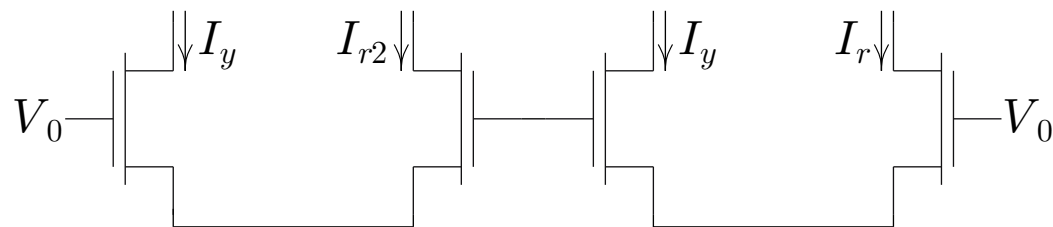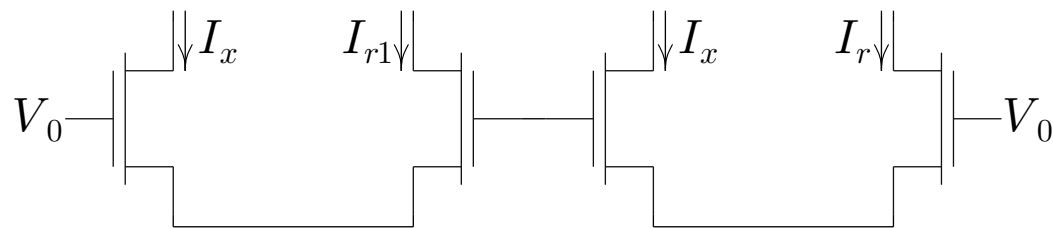

# Static Translinear Circuit Synthesis: Pythagorator

$$\begin{aligned} \text{TLP: } I_{r1} I_r &= I_x^2 \\ I_{r2} I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

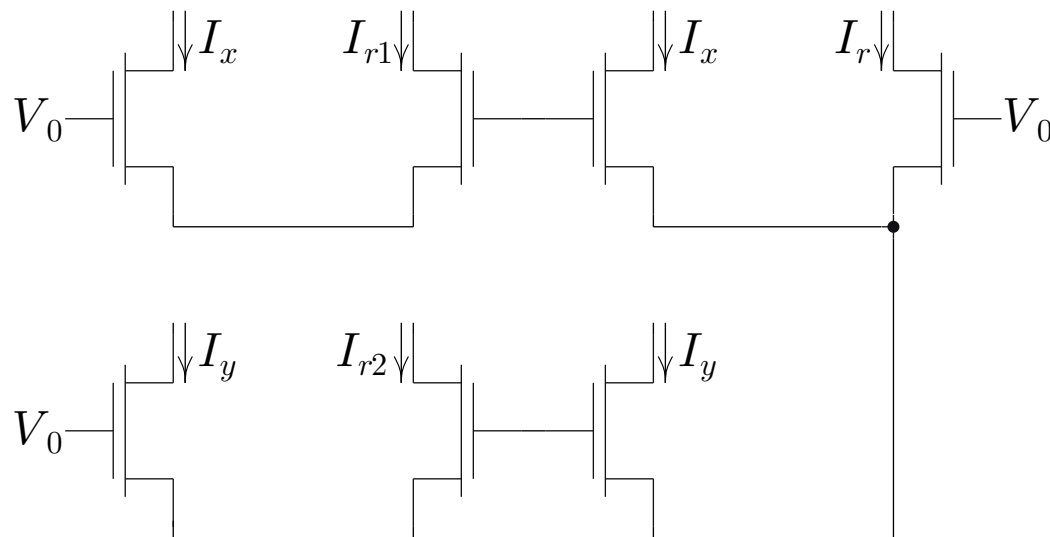

# Static Translinear Circuit Synthesis: Pythagorator

$$\begin{aligned} \text{TLP: } I_{r1} I_r &= I_x^2 \\ I_{r2} I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

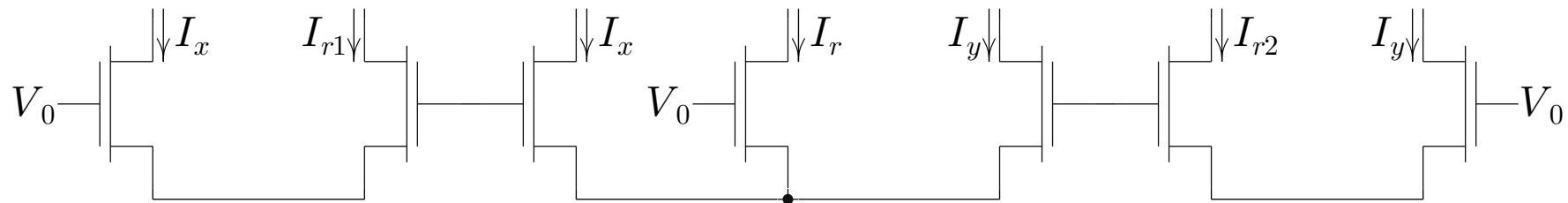

# Static Translinear Circuit Synthesis: Pythagorator

$$\begin{aligned} \text{TLP: } I_{r1} I_r &= I_x^2 \\ I_{r2} I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

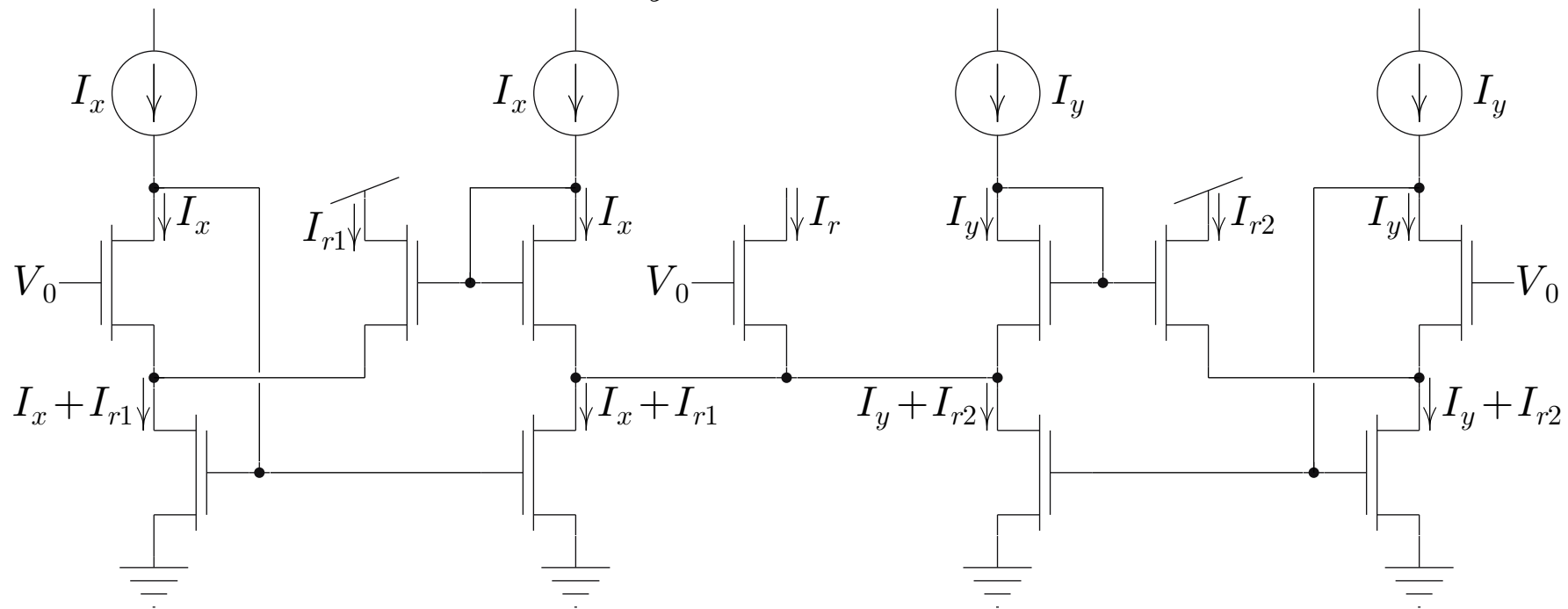



# Dynamic Translinear Circuit Synthesis: Output Structures


noninverting

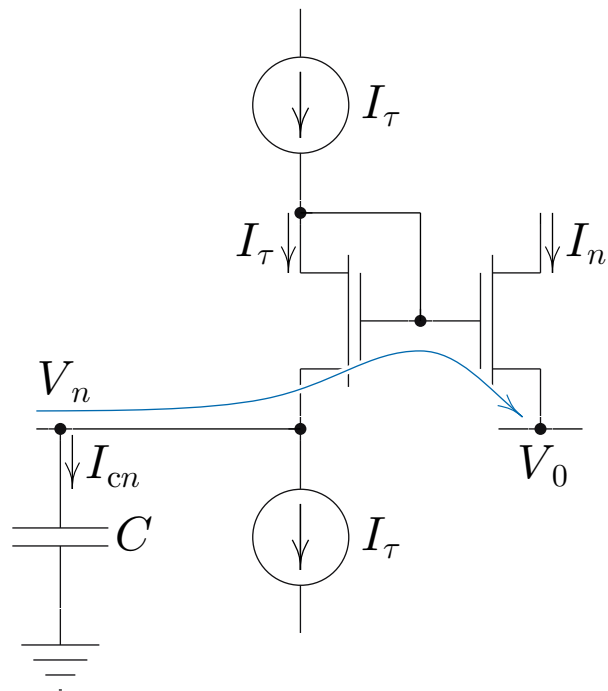

$$I_n = I_\tau e^{(V_n - V_0)/U_T}$$

$$\frac{\partial I_n}{\partial V_n} = \frac{I_n}{U_T}$$

inverting

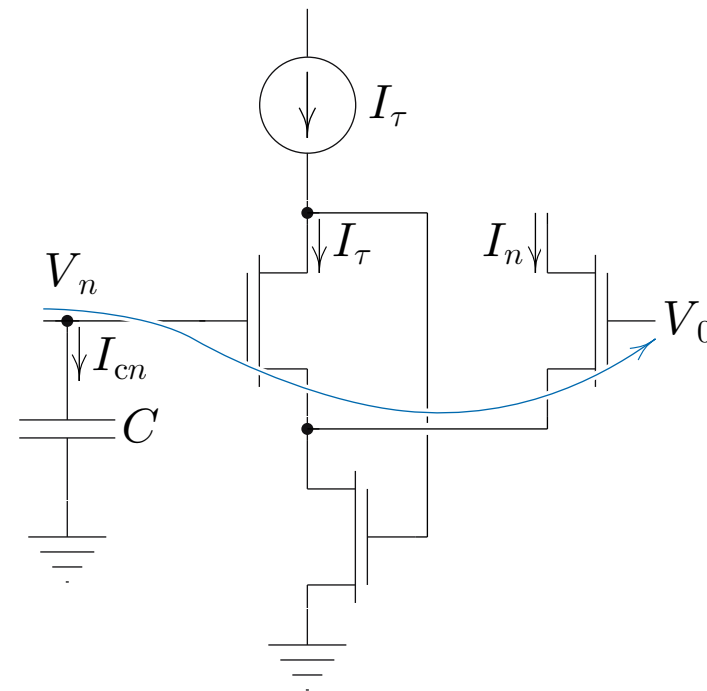

$$I_n = I_\tau e^{\kappa(V_0 - V_n)/U_T}$$

$$\frac{\partial I_n}{\partial V_n} = -\frac{\kappa I_n}{U_T}$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

Synthesize a first-order low-pass filter described by

$$\tau \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

Synthesize a first-order low-pass filter described by

$$\tau \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad y \equiv \frac{I_y}{I_1}.$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

Synthesize a first-order low-pass filter described by

$$\tau \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad y \equiv \frac{I_y}{I_1}.$$

Substituting these into the ODE, we obtain

$$\tau \frac{d}{dt} \left( \frac{I_y}{I_1} \right) + \frac{I_y}{I_1} = \frac{I_x}{I_1}$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

Synthesize a first-order low-pass filter described by

$$\tau \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad y \equiv \frac{I_y}{I_1}.$$

Substituting these into the ODE, we obtain

$$\tau \frac{d}{dt} \left( \frac{I_y}{I_1} \right) + \frac{I_y}{I_1} = \frac{I_x}{I_1} \quad \Longrightarrow \quad \tau \frac{dI_y}{dt} + I_y = I_x.$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_y$ . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_y$ . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Longrightarrow \quad \tau \left( -\frac{\kappa}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_y$ . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Longrightarrow \quad \tau \left( -\frac{\kappa}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

$$\Longrightarrow -\frac{\kappa\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y}$$



## Dynamic Translinear Circuit Synthesis: First-Order LPF

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_y$ . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Longrightarrow \quad \tau \left( -\frac{\kappa}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

$$\Longrightarrow -\frac{\kappa\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} \quad \Longrightarrow \quad -\frac{\kappa\tau}{CU_T} \cdot C \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y}$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_y$ . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Longrightarrow \quad \tau \left( -\frac{\kappa}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

$$\Longrightarrow -\frac{\kappa\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} \quad \Longrightarrow \quad -\underbrace{\frac{\kappa\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C \frac{dV_y}{dt}}_{I_c} + 1 = \frac{I_x}{I_y}$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_y$ . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Longrightarrow \quad \tau \left( -\frac{\kappa}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

$$\Longrightarrow -\frac{\kappa\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} \quad \Longrightarrow \quad -\underbrace{\frac{\kappa\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C \frac{dV_y}{dt}}_{I_c} + 1 = \frac{I_x}{I_y}$$

$$\Longrightarrow -\frac{I_c}{I_\tau} + 1 = \frac{I_x}{I_y}$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_y$ . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Longrightarrow \quad \tau \left( -\frac{\kappa}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

$$\Longrightarrow -\frac{\kappa\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} \quad \Longrightarrow \quad -\underbrace{\frac{\kappa\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C \frac{dV_y}{dt}}_{I_c} + 1 = \frac{I_x}{I_y}$$

$$\Longrightarrow -\frac{I_c}{I_\tau} + 1 = \frac{I_x}{I_y} \quad \Longrightarrow \quad I_\tau - I_c = \frac{I_\tau I_x}{I_y}$$

## Dynamic Translinear Circuit Synthesis: First-Order LPF

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_y$ . Using the chain rule, we can express the preceding equation as

$$\begin{aligned} \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x &\implies \tau \left( -\frac{\kappa}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x \\ \implies -\frac{\kappa\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} &\implies -\underbrace{\frac{\kappa\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C \frac{dV_y}{dt}}_{I_c} + 1 = \frac{I_x}{I_y} \\ \implies -\frac{I_c}{I_\tau} + 1 = \frac{I_x}{I_y} &\implies I_\tau - I_c = \underbrace{\frac{I_\tau I_x}{I_y}}_{I_p} \end{aligned}$$

---

## Dynamic Translinear Circuit Synthesis: First-Order LPF

$$\text{TLP: } I_p I_y = I_x I_\tau \qquad \text{KCL: } I_c + I_p = I_\tau$$

# Dynamic Translinear Circuit Synthesis: First-Order LPF


$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_c + I_p = I_\tau$$



# Dynamic Translinear Circuit Synthesis: First-Order LPF

$$\text{TLP: } I_p I_y = I_x I_\tau$$

$$\text{KCL: } I_c + I_p = I_\tau$$

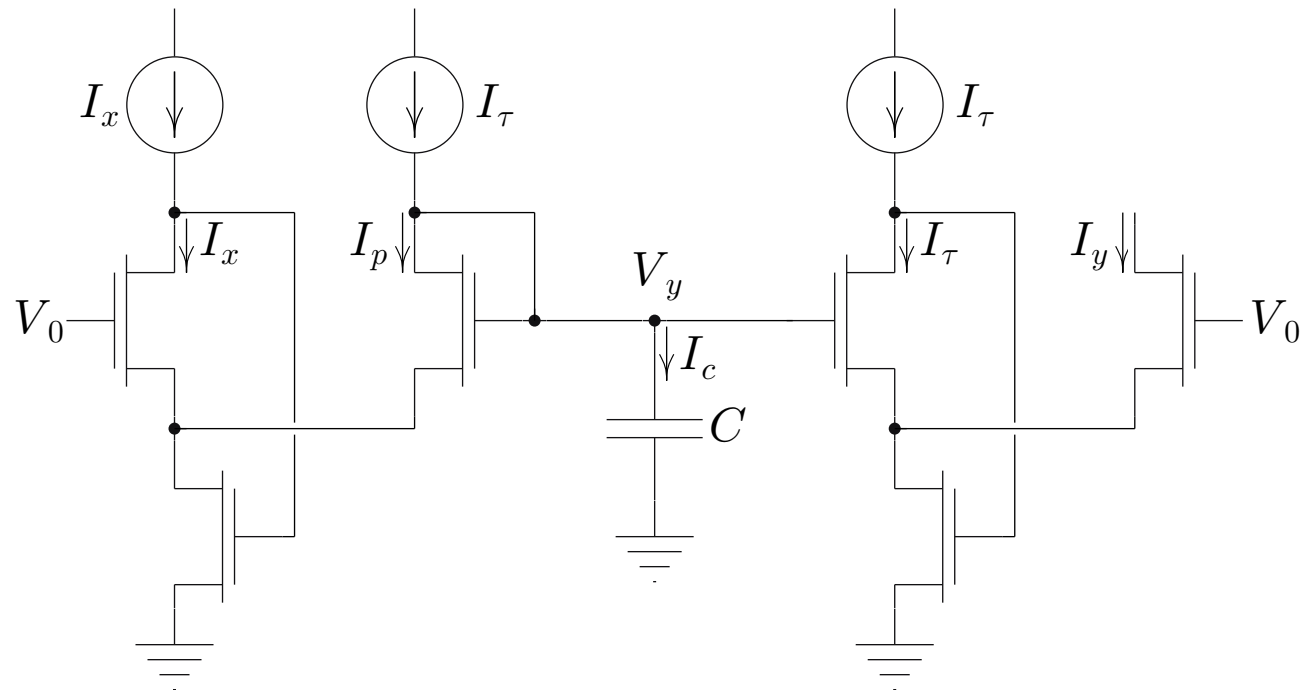



## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

Synthesize an RMS-to-DC converter described by

$$x = w^2, \quad \tau \frac{dy}{dt} + y = x, \quad \text{and} \quad z = \sqrt{y}.$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

Synthesize an RMS-to-DC converter described by

$$x = w^2, \quad \tau \frac{dy}{dt} + y = x, \quad \text{and} \quad z = \sqrt{y}.$$

We can eliminate  $x$  and  $y$  from the system description by substituting

$$x = w^2, \quad y = z^2, \quad \text{and} \quad \frac{dy}{dt} = 2z \frac{dz}{dt}$$

into the linear ODE describing the low-pass filter, obtaining a first-order nonlinear ODE describing the system given by

$$2\tau z \frac{dz}{dt} + z^2 = w^2.$$

# Dynamic Translinear Circuit Synthesis: RMS-DC Converter

$$w_+ \equiv \frac{I_{w+}}{I_1} = \frac{1}{2} (1 + e^{\kappa(V_w - V_0)/U_T})$$

$$w_- \equiv \frac{I_{w-}}{I_1} = \frac{1}{2} (1 + e^{-\kappa(V_w - V_0)/U_T})$$


$$w \equiv \frac{I_w}{I_1} = w_+ - w_-$$

$$= \sinh \frac{\kappa (V_w - V_0)}{U_T}$$

$$w' \equiv \frac{I_{w'}}{I_1} = w_+ + w_- - 1$$

$$= \cosh \frac{\kappa (V_w - V_0)}{U_T}$$

$$w^2 = (w')^2 - 1$$

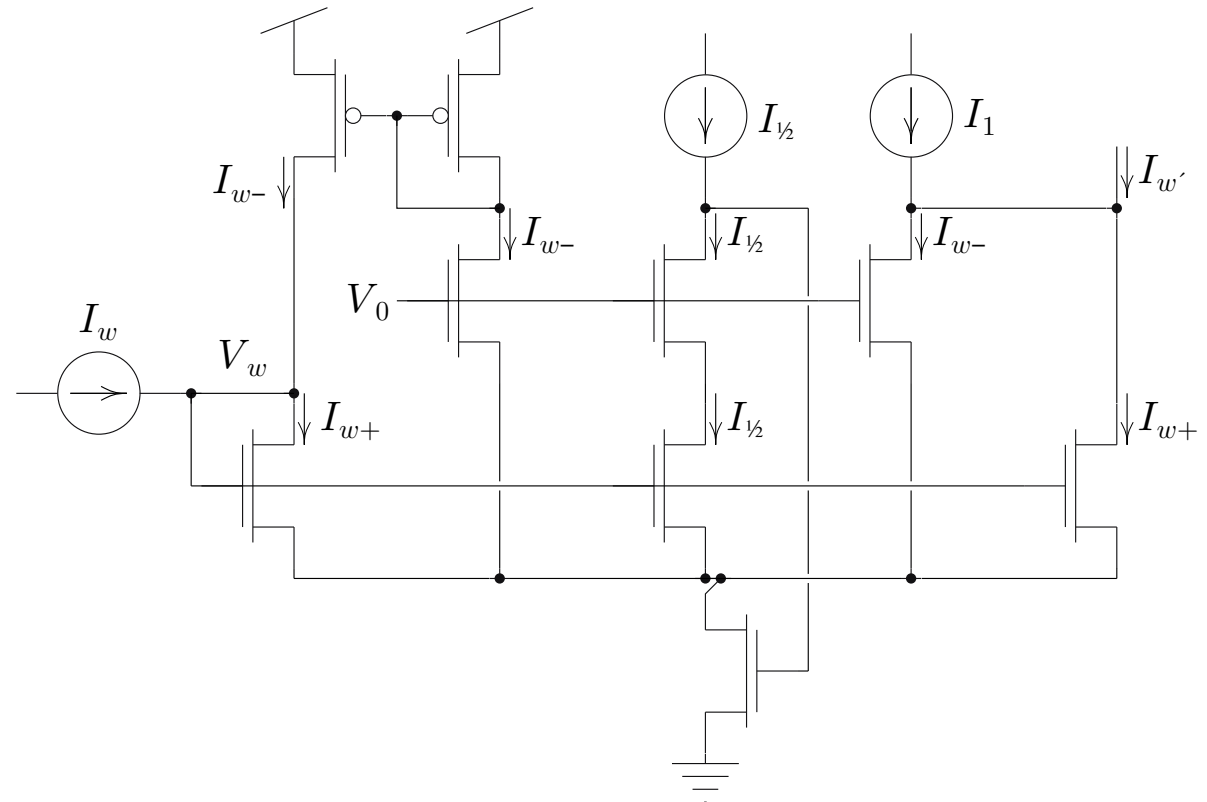

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

The input signal,  $w$ , can be positive or negative. To remedy this situation, we adopt a sinh representation for  $w$  and define an associated signal,  $w'$ , as just described. Substituting  $w^2 = (w')^2 - 1$  into the nonlinear ODE, we obtain

$$2\tau z \frac{dz}{dt} + z^2 = (w')^2 - 1.$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

The input signal,  $w$ , can be positive or negative. To remedy this situation, we adopt a sinh representation for  $w$  and define an associated signal,  $w'$ , as just described. Substituting  $w^2 = (w')^2 - 1$  into the nonlinear ODE, we obtain

$$2\tau z \frac{dz}{dt} + z^2 = (w')^2 - 1.$$

We represent each signal as a ratio of a signal current to the unit current:

$$w' \equiv \frac{I_{w'}}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

The input signal,  $w$ , can be positive or negative. To remedy this situation, we adopt a sinh representation for  $w$  and define an associated signal,  $w'$ , as just described. Substituting  $w^2 = (w')^2 - 1$  into the nonlinear ODE, we obtain

$$2\tau z \frac{dz}{dt} + z^2 = (w')^2 - 1.$$

We represent each signal as a ratio of a signal current to the unit current:

$$w' \equiv \frac{I_{w'}}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the nonlinear ODE, we obtain

$$2\tau \frac{I_z}{I_1} \cdot \frac{d}{dt} \left( \frac{I_z}{I_1} \right) + \left( \frac{I_z}{I_1} \right)^2 = \left( \frac{I_{w'}}{I_1} \right)^2 - 1$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

The input signal,  $w$ , can be positive or negative. To remedy this situation, we adopt a sinh representation for  $w$  and define an associated signal,  $w'$ , as just described. Substituting  $w^2 = (w')^2 - 1$  into the nonlinear ODE, we obtain

$$2\tau z \frac{dz}{dt} + z^2 = (w')^2 - 1.$$

We represent each signal as a ratio of a signal current to the unit current:

$$w' \equiv \frac{I_{w'}}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the nonlinear ODE, we obtain

$$2\tau \frac{I_z}{I_1} \cdot \frac{d}{dt} \left( \frac{I_z}{I_1} \right) + \left( \frac{I_z}{I_1} \right)^2 = \left( \frac{I_{w'}}{I_1} \right)^2 - 1 \implies 2\tau I_z \frac{dI_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2.$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_z$ . Using the chain rule, we can express the preceding equation as

$$2\tau I_z \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2$$



## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_z$ . Using the chain rule, we can express the preceding equation as

$$2\tau I_z \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2 \quad \implies \quad 2\tau I_z \left( -\frac{\kappa}{U_T} I_z \right) \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_z$ . Using the chain rule, we can express the preceding equation as

$$2\tau I_z \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2 \quad \Longrightarrow \quad 2\tau I_z \left( -\frac{\kappa}{U_T} I_z \right) \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2$$

$$\Longrightarrow -\frac{2w\kappa}{U_T} \cdot \frac{dV_z}{dt} + 1 = \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2}$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_z$ . Using the chain rule, we can express the preceding equation as

$$2\tau I_z \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2 \quad \Rightarrow \quad 2\tau I_z \left( -\frac{\kappa}{U_T} I_z \right) \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2$$

$$\Rightarrow -\frac{2w\kappa}{U_T} \cdot \frac{dV_z}{dt} + 1 = \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \quad \Rightarrow \quad -\frac{2\kappa\tau}{CU_T} \cdot C \frac{dV_z}{dt} + 1 = \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2}$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_z$ . Using the chain rule, we can express the preceding equation as

$$2\tau I_z \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2 \quad \Rightarrow \quad 2\tau I_z \left( -\frac{\kappa}{U_T} I_z \right) \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2$$

$$\Rightarrow -\frac{2w\kappa}{U_T} \cdot \frac{dV_z}{dt} + 1 = \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \quad \Rightarrow \quad -\underbrace{\frac{2\kappa\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C}_{I_c} \frac{dV_z}{dt} + 1 = \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2}$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_z$ . Using the chain rule, we can express the preceding equation as

$$\begin{aligned}
 2\tau I_z \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} + I_z^2 &= I_{w'}^2 - I_1^2 \quad \implies \quad 2\tau I_z \left( -\frac{\kappa}{U_T} I_z \right) \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2 \\
 \implies -\frac{2w\kappa}{U_T} \cdot \frac{dV_z}{dt} + 1 &= \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \quad \implies \quad -\underbrace{\frac{2\kappa\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C}_{I_c} \frac{dV_z}{dt} + 1 = \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \\
 \implies -\frac{I_c}{I_\tau} + 1 &= \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2}
 \end{aligned}$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_z$ . Using the chain rule, we can express the preceding equation as

$$\begin{aligned}
 2\tau I_z \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} + I_z^2 &= I_{w'}^2 - I_1^2 \quad \implies \quad 2\tau I_z \left( -\frac{\kappa}{U_T} I_z \right) \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2 \\
 \implies -\frac{2w\kappa}{U_T} \cdot \frac{dV_z}{dt} + 1 &= \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \quad \implies \quad -\underbrace{\frac{2\kappa\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C}_{I_c} \frac{dV_z}{dt} + 1 = \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \\
 \implies -\frac{I_c}{I_\tau} + 1 &= \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \quad \implies \quad I_\tau - I_c = \frac{I_\tau I_{w'}^2}{I_z^2} - \frac{I_\tau I_1^2}{I_z^2}.
 \end{aligned}$$

## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

To implement the time derivative, we introduce a log-compressed voltage state variable,  $V_z$ . Using the chain rule, we can express the preceding equation as

$$\begin{aligned}
 2\tau I_z \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} + I_z^2 &= I_{w'}^2 - I_1^2 \quad \Longrightarrow \quad 2\tau I_z \left( -\frac{\kappa}{U_T} I_z \right) \frac{dV_z}{dt} + I_z^2 = I_{w'}^2 - I_1^2 \\
 \Longrightarrow -\frac{2w\kappa}{U_T} \cdot \frac{dV_z}{dt} + 1 &= \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \quad \Longrightarrow \quad -\frac{2\kappa\tau}{\underbrace{CU_T}_{1/I_\tau}} \cdot \underbrace{C}_{I_c} \frac{dV_z}{dt} + 1 = \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \\
 \Longrightarrow -\frac{I_c}{I_\tau} + 1 &= \frac{I_{w'}^2}{I_z^2} - \frac{I_1^2}{I_z^2} \quad \Longrightarrow \quad I_\tau - I_c = \underbrace{\frac{I_\tau I_{w'}^2}{I_z^2}}_{I_p} - \underbrace{\frac{I_\tau I_1^2}{I_z^2}}_{I_q}.
 \end{aligned}$$


## Dynamic Translinear Circuit Synthesis: RMS-DC Converter

$$\begin{aligned} \text{TLP: } I_p I_z^2 &= I_\tau I_{w'}^2 \\ I_q I_z^2 &= I_\tau I_1^2 \end{aligned} \quad \text{KCL: } I_c + I_p = I_\tau + I_q$$




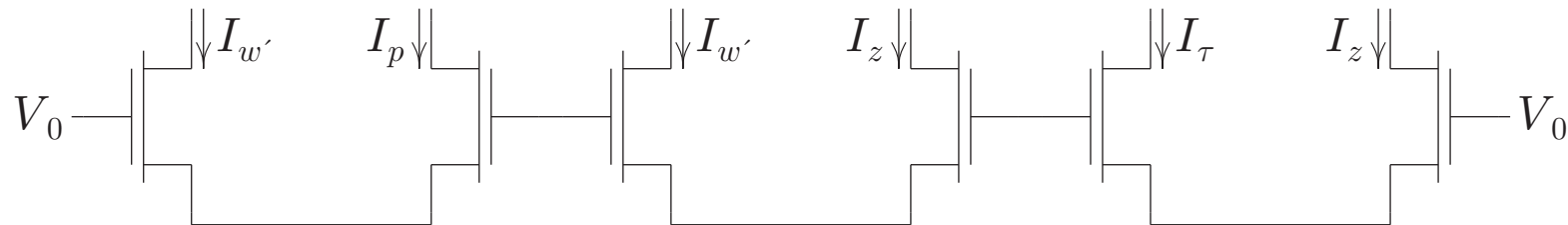
# Dynamic Translinear Circuit Synthesis: RMS-DC Converter

$$\begin{aligned} \text{TLP: } I_p I_z^2 &= I_\tau I_{w'}^2 \\ I_q I_z^2 &= I_\tau I_1^2 \end{aligned} \quad \text{KCL: } I_c + I_p = I_\tau + I_q$$



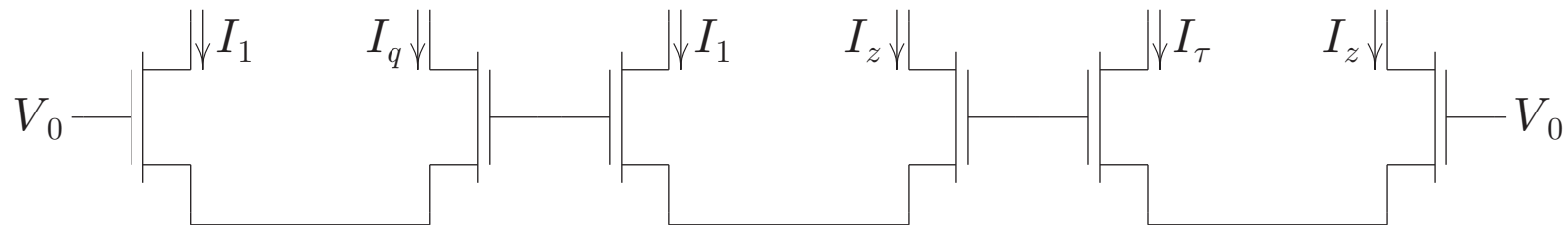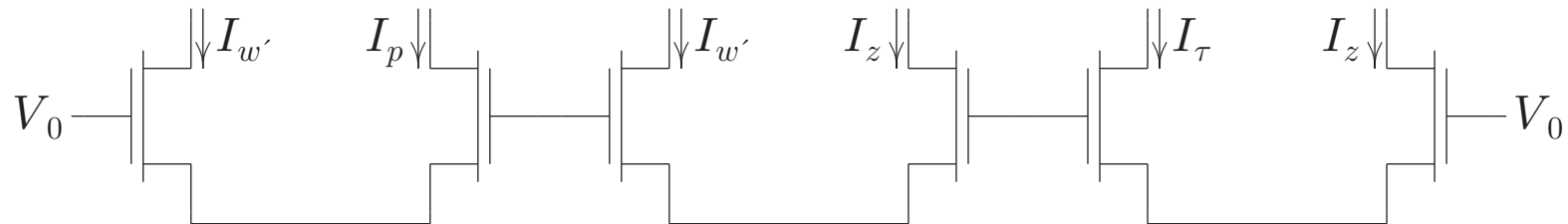
# Dynamic Translinear Circuit Synthesis: RMS-DC Converter

$$\begin{aligned} \text{TLP: } I_p I_z^2 &= I_\tau I_{w'}^2 \\ I_q I_z^2 &= I_\tau I_1^2 \end{aligned} \quad \text{KCL: } I_c + I_p = I_\tau + I_q$$



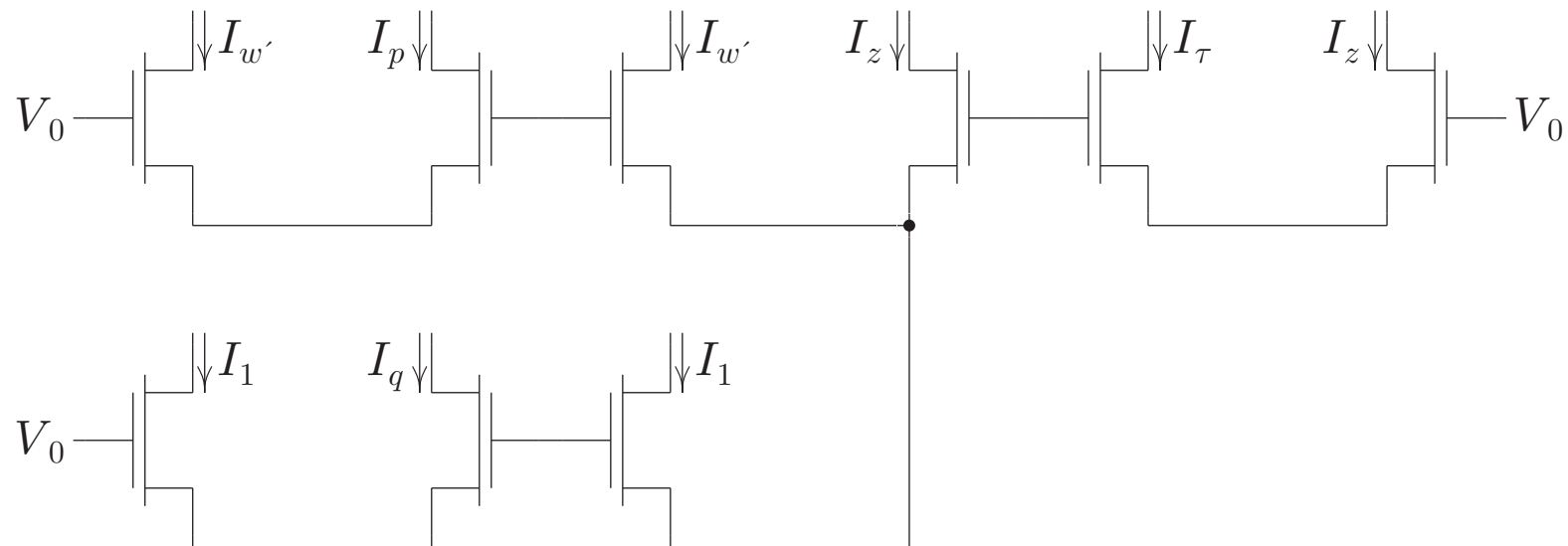
# Dynamic Translinear Circuit Synthesis: RMS-DC Converter

$$\begin{aligned} \text{TLP: } I_p I_z^2 &= I_\tau I_{w'}^2 \\ I_q I_z^2 &= I_\tau I_1^2 \end{aligned} \quad \text{KCL: } I_c + I_p = I_\tau + I_q$$


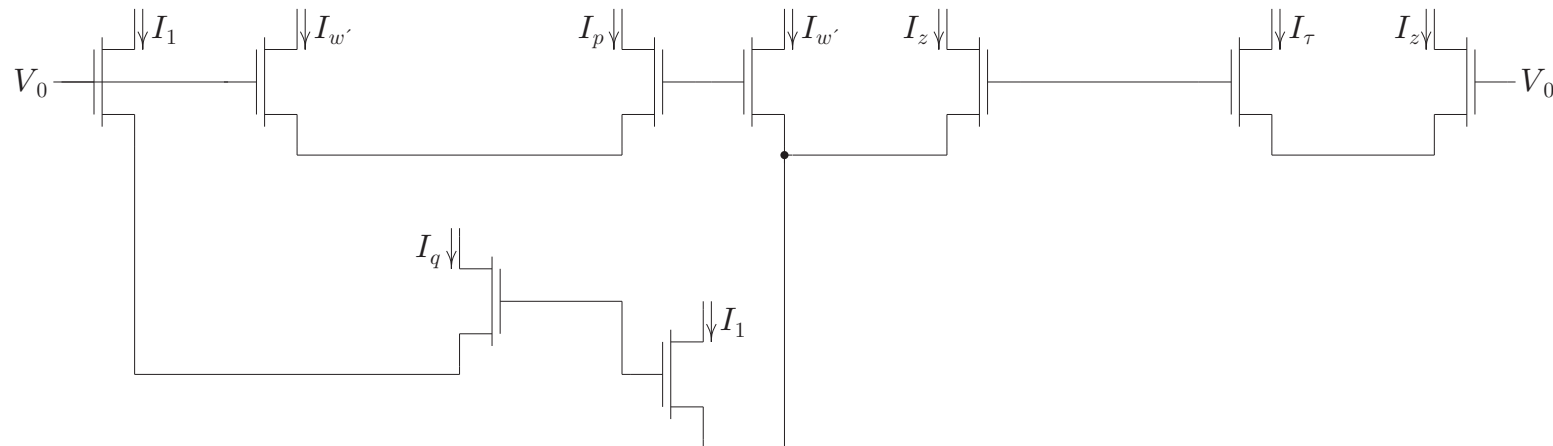
# Dynamic Translinear Circuit Synthesis: RMS-DC Converter


$$\begin{aligned} \text{TLP: } I_p I_z^2 &= I_\tau I_{w'}^2 \\ I_q I_z^2 &= I_\tau I_1^2 \end{aligned} \quad \text{KCL: } I_c + I_p = I_\tau + I_q$$


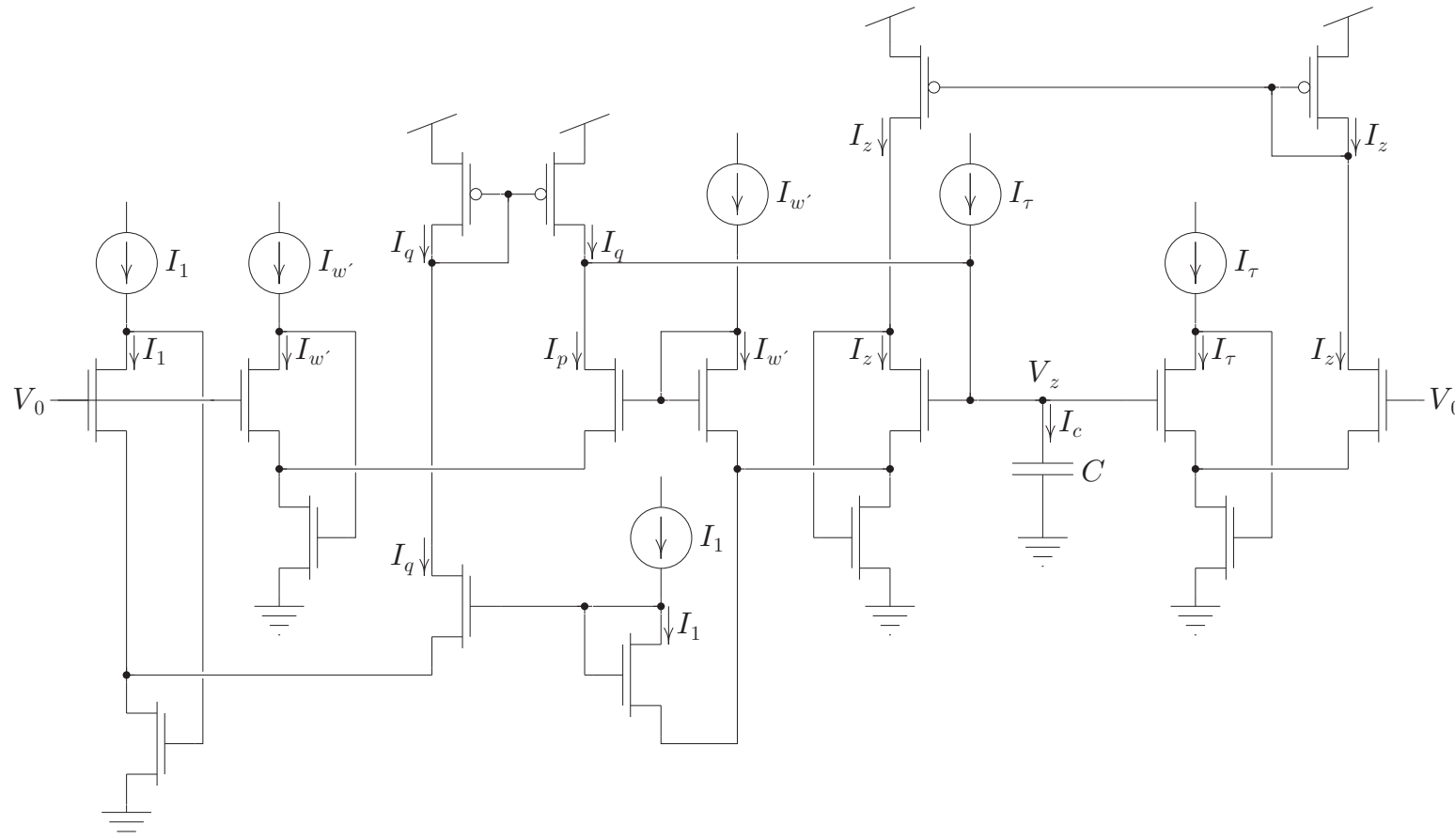
# Dynamic Translinear Circuit Synthesis: RMS-DC Converter

$$\begin{aligned} \text{TLP: } I_p I_z^2 &= I_\tau I_{w'}^2 \\ I_q I_z^2 &= I_\tau I_1^2 \end{aligned}$$

$$\text{KCL: } I_c + I_p = I_\tau + I_q$$



# Dynamic Translinear Circuit Synthesis: RMS-DC Converter

$$\begin{aligned} \text{TLP: } I_p I_z^2 &= I_\tau I_{w'}^2 \\ I_q I_z^2 &= I_\tau I_1^2 \end{aligned}$$

$$\text{KCL: } I_c + I_p = I_\tau + I_q$$

