
TRANSLINEAR ANALOG SIGNAL PROCESSING: A MODULAR APPROACH TO LOW-VOLTAGE ANALOG COMPUTATION WITH LOGARITHMS

Bradley A. Minch

Laboratory of Analogical Information Processing
School of Electrical Engineering
Cornell University
Ithaca, NY 14853-5401

minch@ee.cornell.edu
<http://www.ee.cornell.edu/~minch>

CORNELL
UNIVERSITY

Translinear Circuits: What's in a Name?



- ▶ Circuits made of devices whose *trans*conductances are *linear* in the currents flowing in them:

$$g_m \equiv \frac{\partial I}{\partial V} \propto I$$

$$\Rightarrow \int \frac{\partial I}{I} \propto \int \partial V$$

$$\Rightarrow \log I \propto V$$

$$\Rightarrow I \propto e^V$$

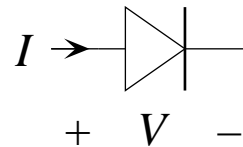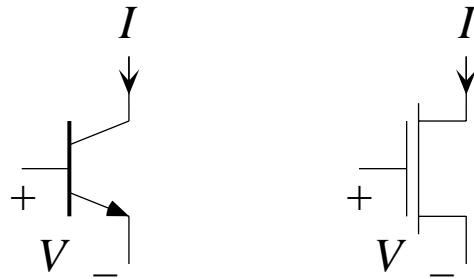


- ▶ Circuits whose behavior is conveniently expressed as a *translation* of *linear* relationships among voltages into product-of-power-law relationships among currents:

$$V_3 = w_1 V_1 + w_2 V_2 \xleftrightarrow{I \propto e^V} I_3 = I_1^{w_1} \times I_2^{w_2}$$

The Multiple-Input Translinear Element

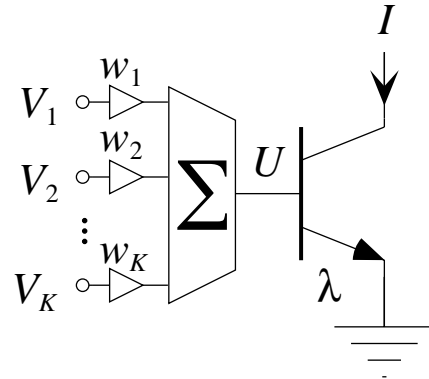
$$I = \lambda I_s \exp \left[\sum_{k=1}^K \frac{w_k V_k}{U_T} \right]$$




- ▶ The MITE has K *trans*conductances, each of which is *linear* in the output current, I :

$$\begin{aligned} g_k &= \frac{\partial I}{\partial V_k} \\ &= \frac{w_k}{U_T} \lambda I_s \exp \left[\sum_{k=1}^K \frac{w_k V_k}{U_T} \right] \\ &= \frac{w_k}{U_T} I \end{aligned}$$

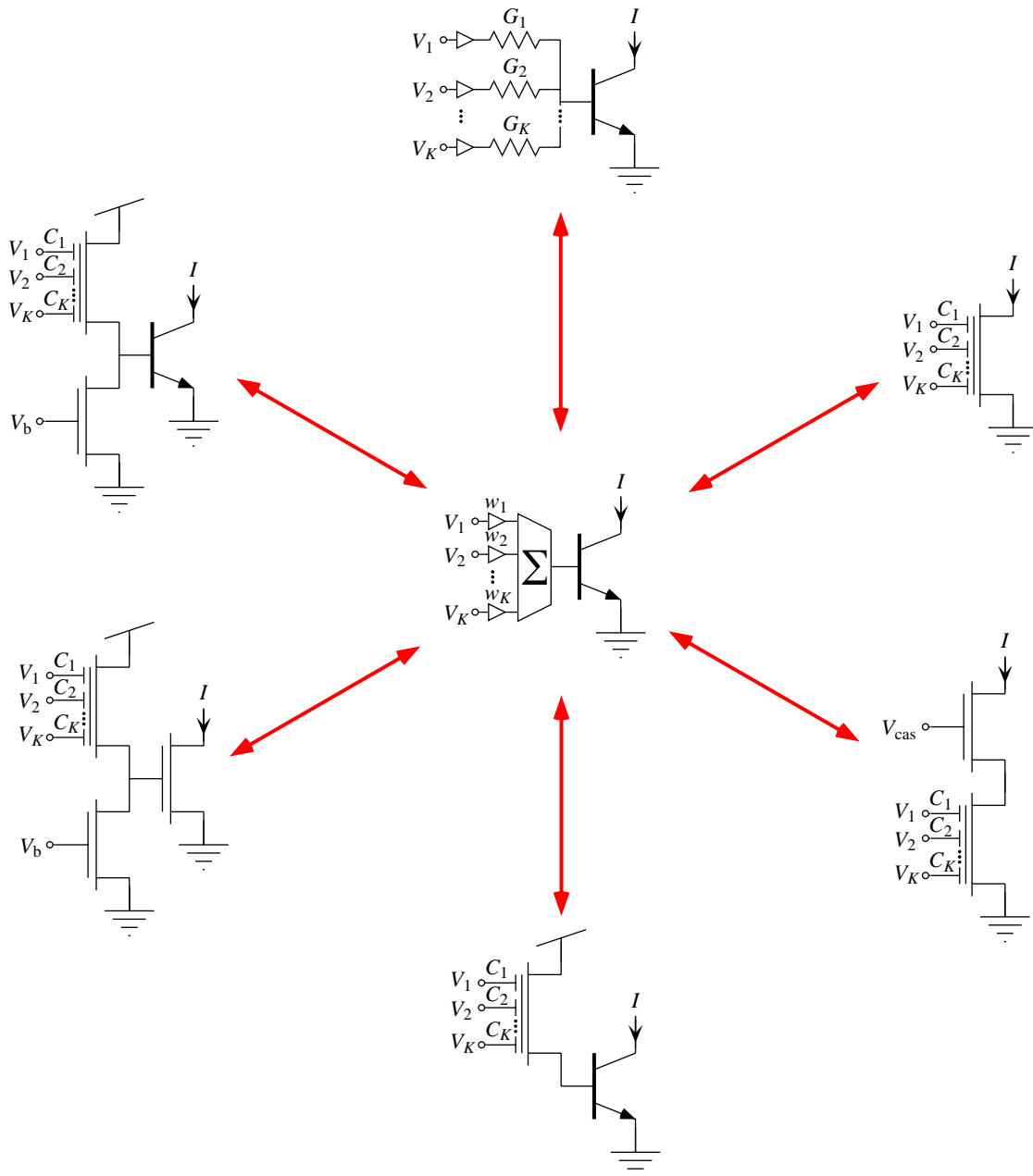Multiple-Input Translinear Element Implementations



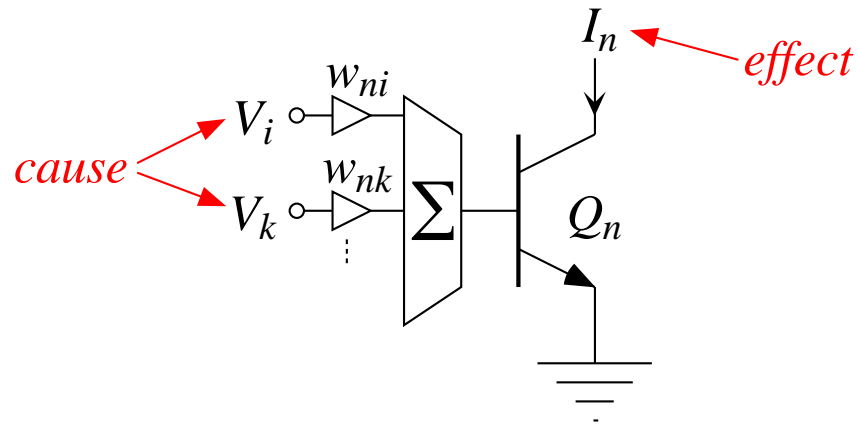
Basic MITE Configurations: Voltage-In, Current-Out



$$I_n \propto \exp \left[\frac{w_{ni} V_i + w_{nk} V_k + \dots}{U_T} \right]$$

$$\Rightarrow I_n \propto \exp \left[\frac{w_{ni} V_i}{U_T} \right] \exp \left[\frac{w_{nk} V_k}{U_T} \right]$$

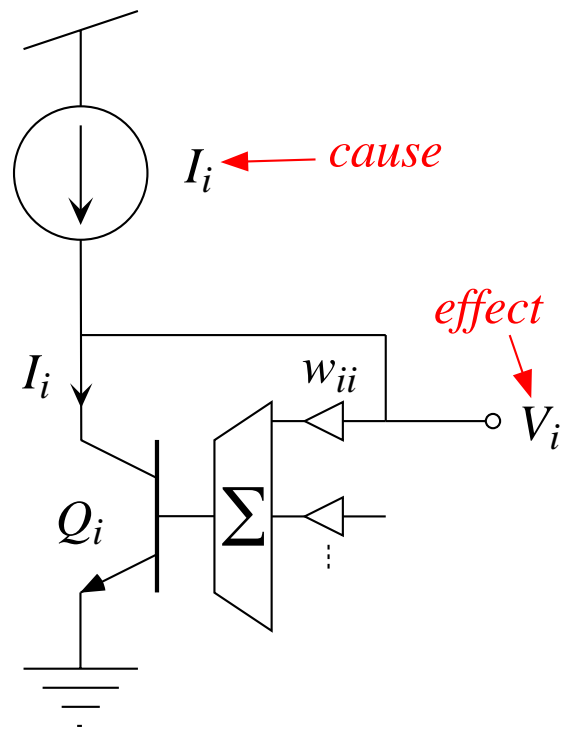
Basic MITE Configurations: Current-In, Voltage-Out



$$I_i \propto \exp \left[\frac{w_{ii} V_i + \dots}{U_T} \right]$$

$$\Rightarrow V_i = \frac{U_T}{w_{ii}} \log I_i - \dots$$

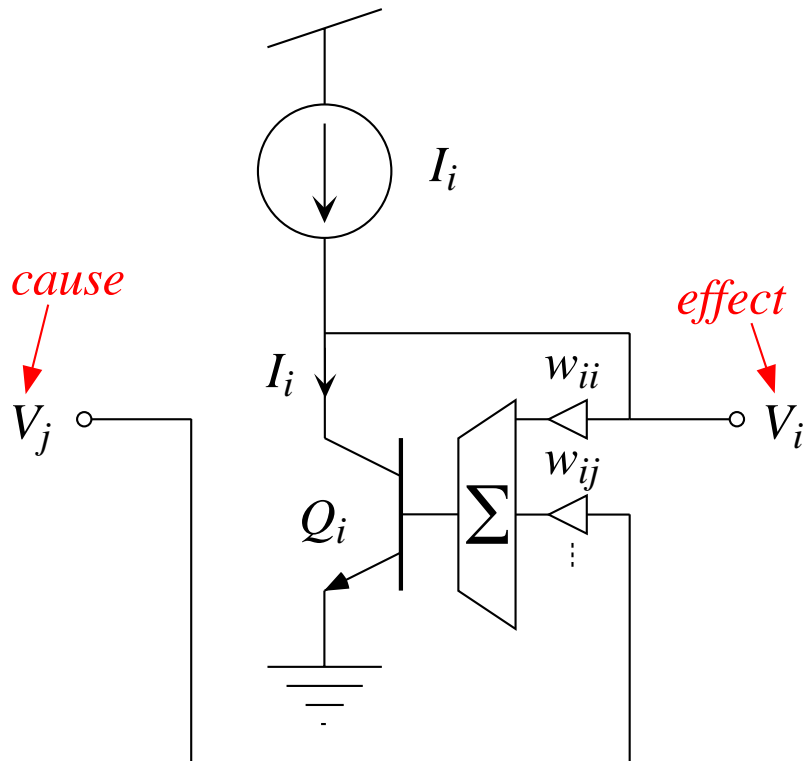
Basic MITE Configurations: Voltage-In, Voltage-Out



$$I_i \propto \exp \left[\frac{w_{ii} V_i + w_{ij} V_j + \dots}{U_T} \right]$$

$$\Rightarrow V_i = \frac{U_T}{w_{ii}} \log I_i - \frac{w_{ij}}{w_{ii}} V_j - \dots$$

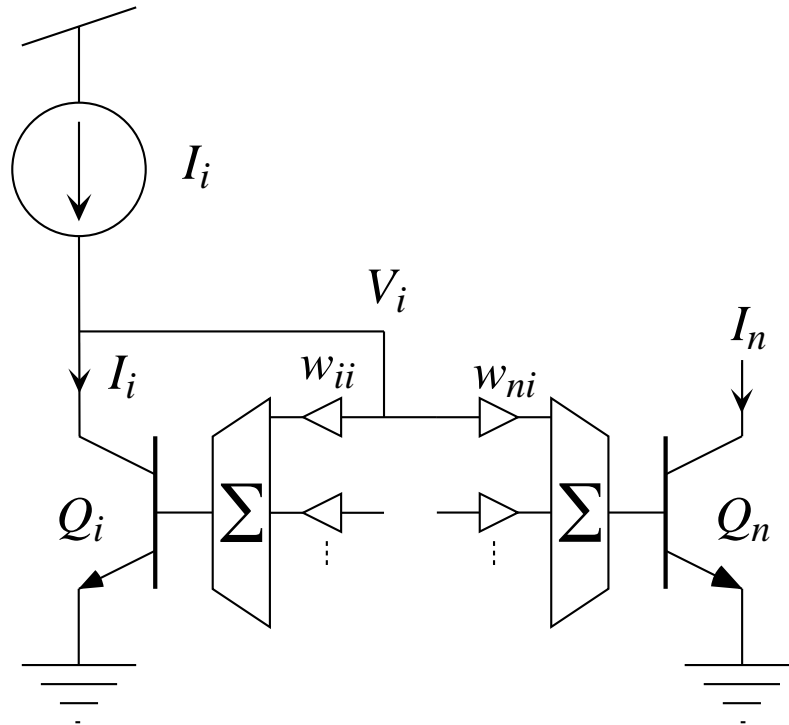MITE Networks: Current-In, Current-Out Power-Law Circuits




$$I_n \propto \exp\left[\frac{w_{ni} V_i + \dots}{U_T}\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{w_{ni}}{U_T} \left(\frac{U_T}{w_{ii}} \log I_i - \dots\right)\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{\cancel{U_T} w_{ni}}{\cancel{U_T} w_{ii}} \log I_i\right]$$

$$\Rightarrow I_n \propto I_i^{\frac{w_{ni}}{w_{ii}}}$$

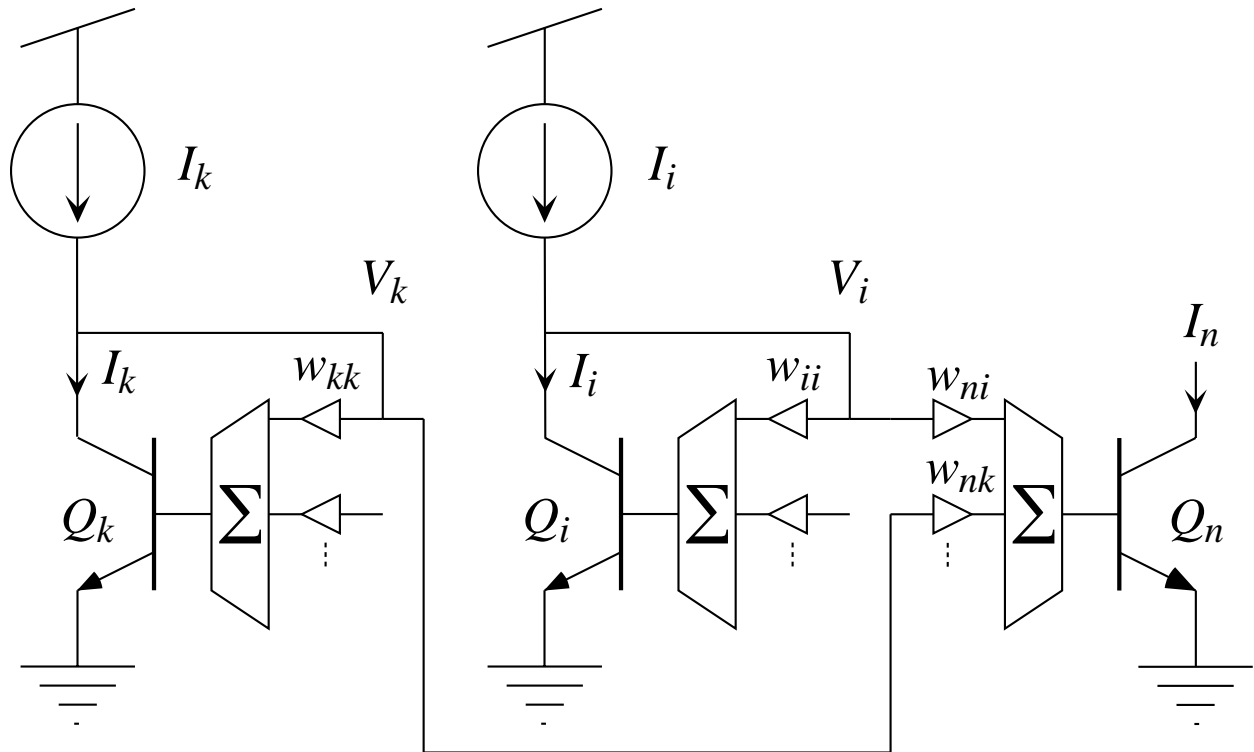MITE Networks: Current-In, Current-Out Product-of-Power-Law Circuits




$$I_n \propto \exp\left[\frac{w_{ni} V_i}{U_T}\right] \exp\left[\frac{w_{nk} V_k}{U_T}\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{w_{ni}}{U_T} \left(\frac{U_T}{w_{ii}} \log I_i - \dots\right)\right] \exp\left[\frac{w_{nk}}{U_T} \left(\frac{U_T}{w_{kk}} \log I_k - \dots\right)\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{\cancel{U_T} w_{ni}}{\cancel{U_T} w_{ii}} \log I_i\right] \exp\left[\frac{\cancel{U_T} w_{nk}}{\cancel{U_T} w_{kk}} \log I_k\right]$$

$$\Rightarrow I_n \propto I_i^{\frac{w_{ni}}{w_{ii}}} \times I_k^{\frac{w_{nk}}{w_{kk}}}$$

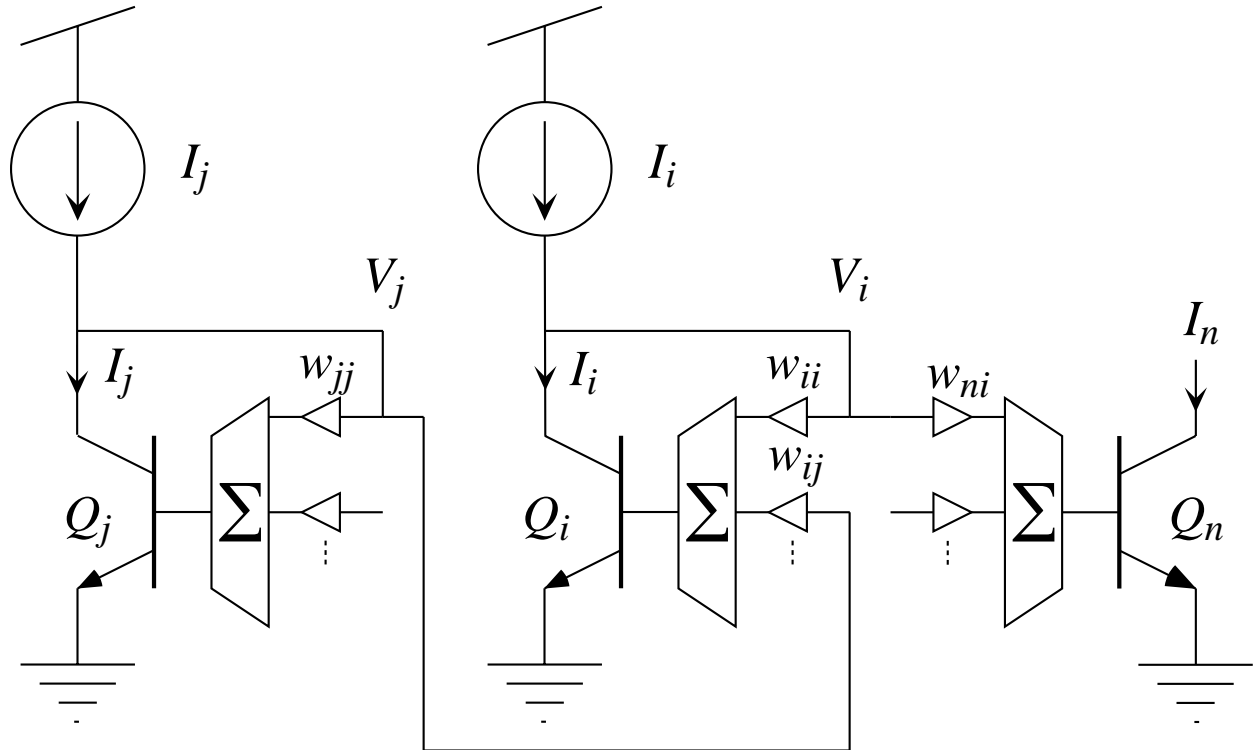MITE Networks: Current-In, Current-Out Quotient-of-Power-Law Circuits




$$I_n \propto \exp\left[\frac{w_{ni} V_i + \dots}{U_T}\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{w_{ni}}{U_T} \left(\frac{U_T}{w_{ii}} \log I_i - \frac{w_{ij}}{w_{ii}} \left(\frac{U_T}{w_{jj}} \log I_j - \dots \right) \dots \right)\right]$$



$$\Rightarrow I_n \propto \exp\left[\frac{\cancel{U_T} w_{ni}}{\cancel{U_T} w_{ii}} \log I_i\right] \exp\left[-\frac{\cancel{U_T} w_{ni} w_{ij}}{\cancel{U_T} w_{ii} w_{jj}} \log I_j\right]$$

$$\Rightarrow I_n \propto I_i^{\frac{w_{ni}}{w_{ii}}} \times I_j^{-\frac{w_{ni} w_{ij}}{w_{ii} w_{jj}}} \Rightarrow I_n \propto I_i^{\frac{w_{ni}}{w_{ii}}} \div I_j^{\frac{w_{ni} w_{ij}}{w_{ii} w_{jj}}}$$


MITE Networks: Square/Reciprocal

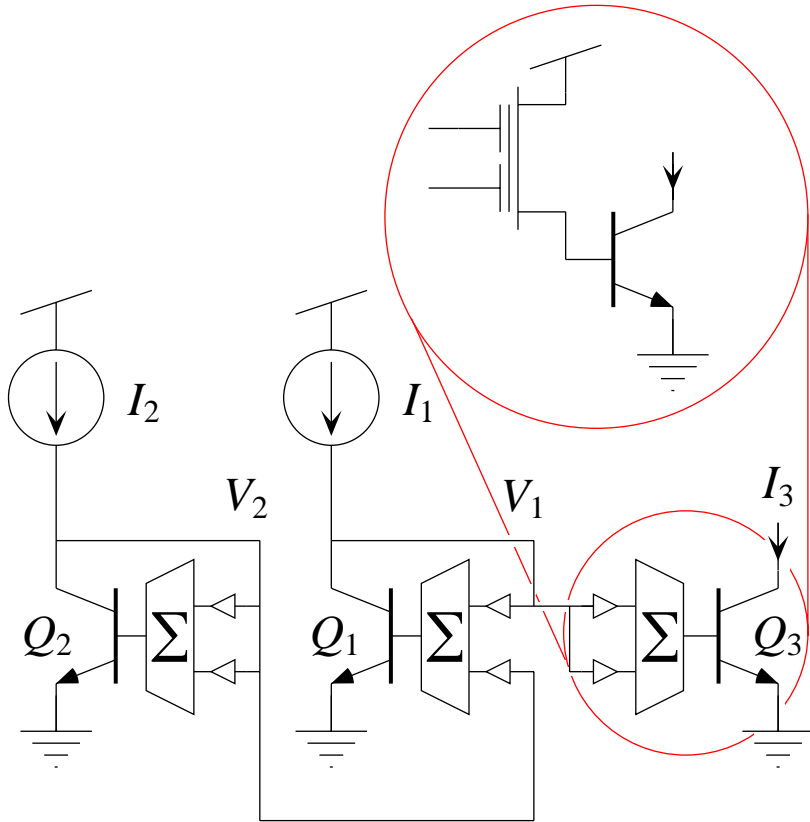



$$I_3 = \frac{I_1^2}{I_2}$$

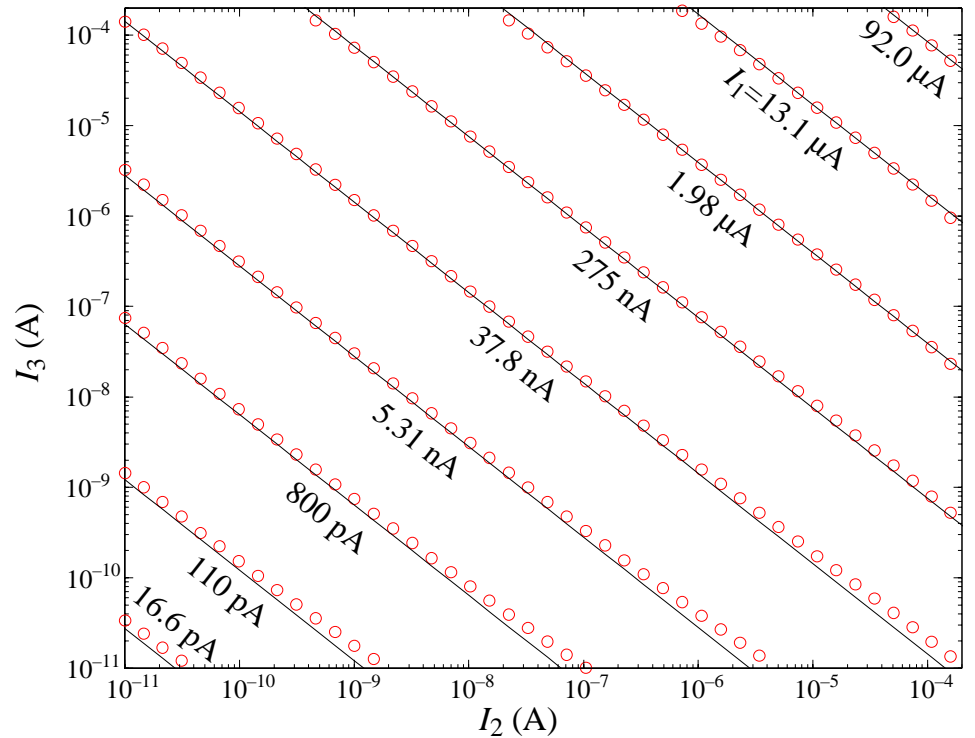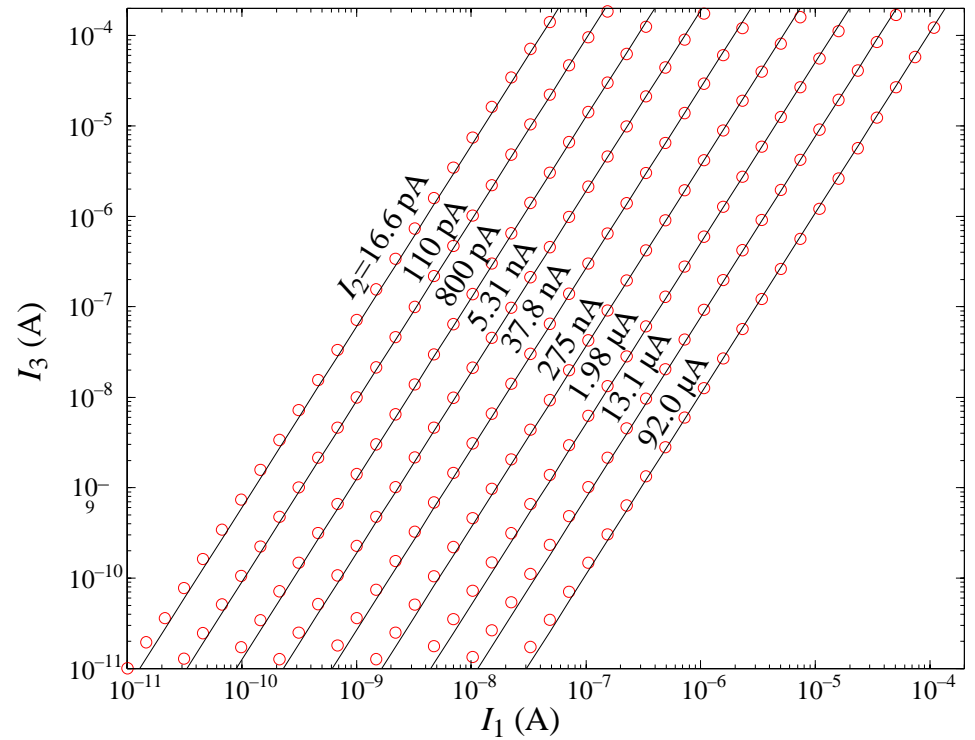


MITE Networks: Multiply/Reciprocal

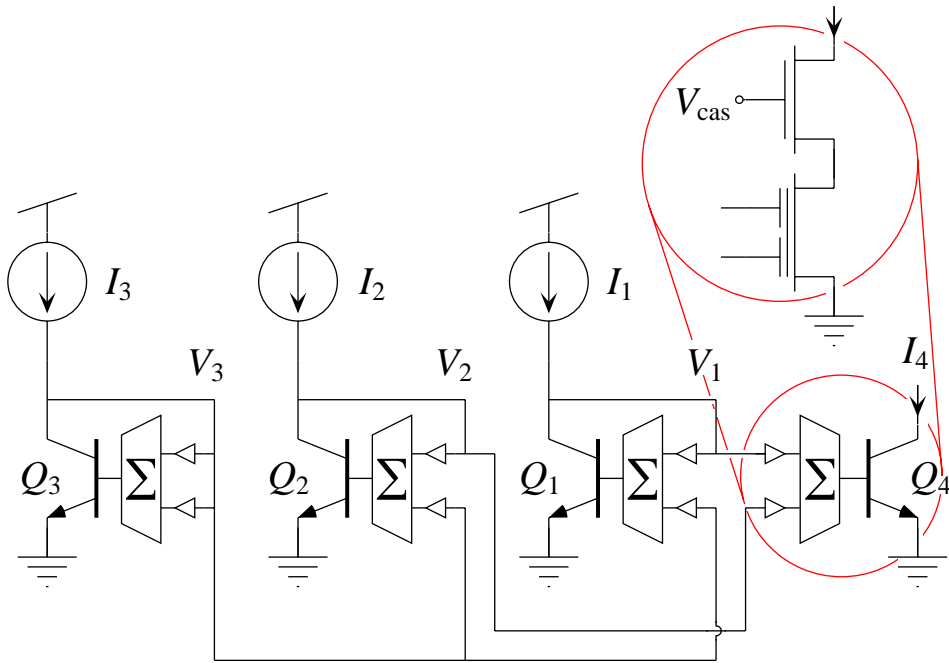

$$I_4 = \frac{I_1 I_2}{I_3}$$

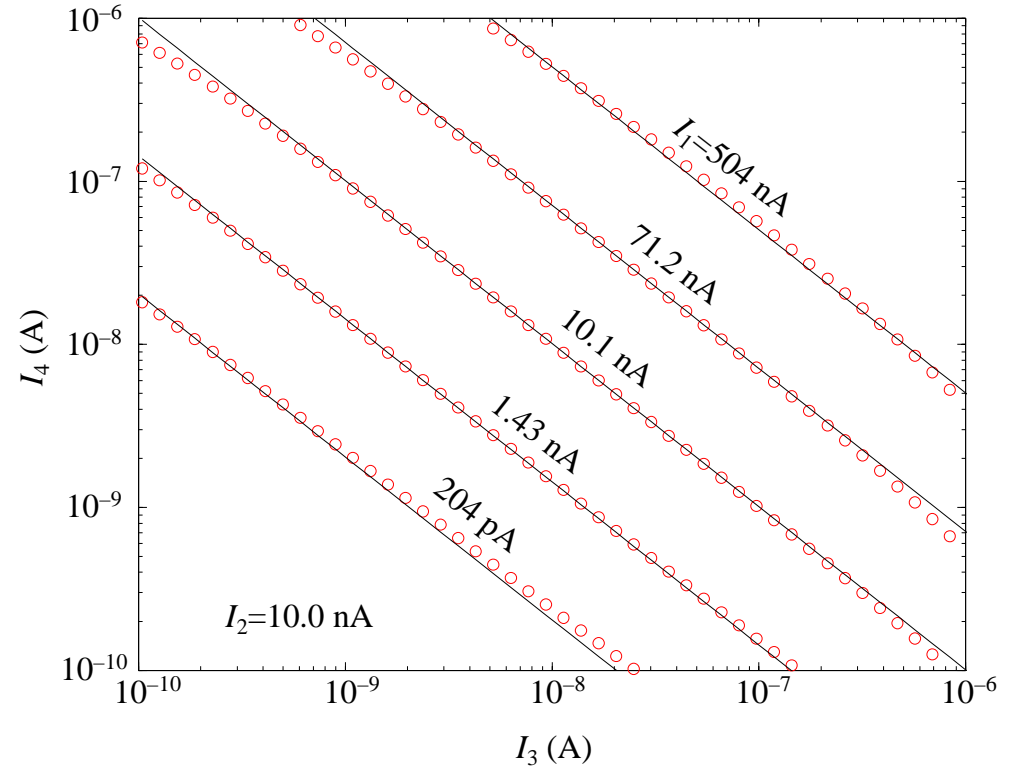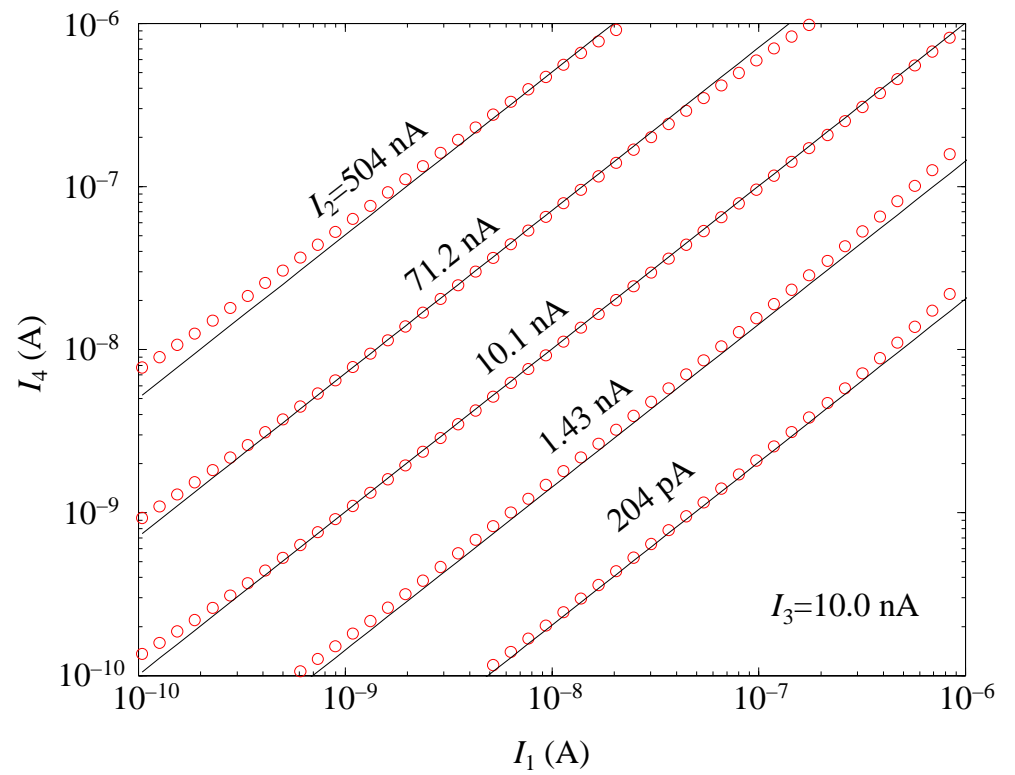

MITE Log-Domain Filter Building Block

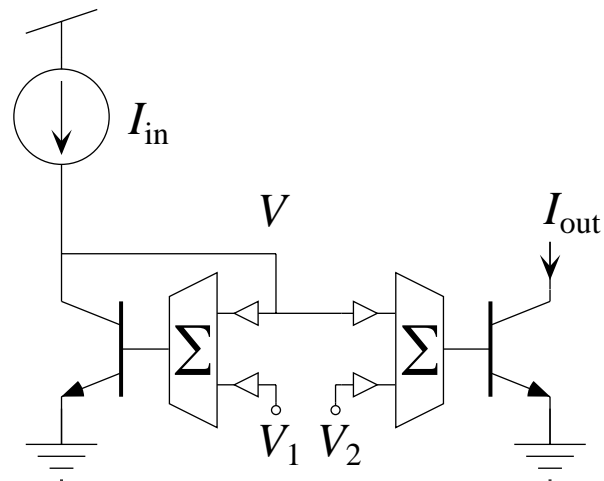


$$I_{\text{in}} = I_s e^{w(V+V_1)/U_T}$$

$$I_{\text{out}} = I_s e^{w(V+V_2)/U_T}$$

$$\Rightarrow \frac{I_{\text{out}}}{I_{\text{in}}} = \frac{\cancel{I_s} e^{wV/U_T} e^{wV_2/U_T}}{\cancel{I_s} e^{wV/U_T} e^{wV_1/U_T}}$$

$$\Rightarrow \boxed{I_{\text{out}} = I_{\text{in}} e^{w(V_2 - V_1)/U_T}}$$

MITE Log-Domain Filters

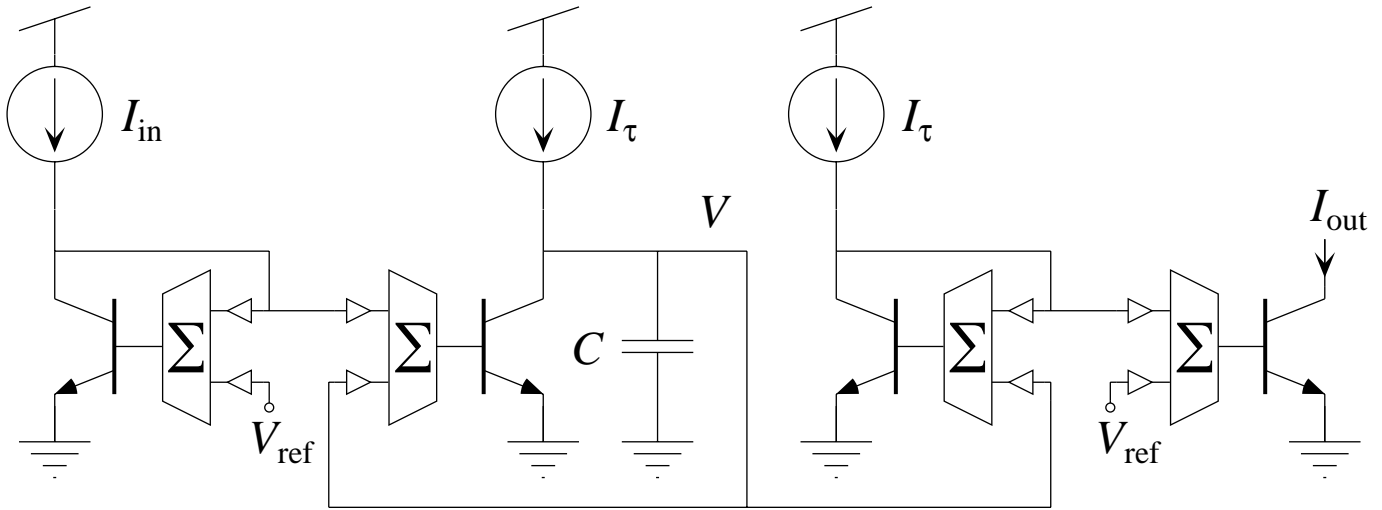

$$I_{out} = I_\tau e^{w(V_{ref} - V)/U_T}$$



$$\Rightarrow \frac{dV}{dt} = -\frac{U_T}{w} \frac{1}{I_{out}} \frac{dI_{out}}{dt} \quad \text{and} \quad e^{w(V - V_{ref})/U_T} = \frac{I_\tau}{I_{out}}$$

$$\text{KCL} \Rightarrow C \frac{dV}{dt} = I_\tau - I_{in} e^{w(V - V_{ref})/U_T}$$


$$\Rightarrow -\frac{CU_T}{w} \frac{1}{I_{out}} \frac{dI_{out}}{dt} = I_\tau - I_{in} \frac{I_\tau}{I_{out}}$$

$$\tau \equiv \frac{CU_T}{wI_\tau} \Rightarrow \tau \frac{dI_{out}}{dt} + I_{out} = I_{in}$$

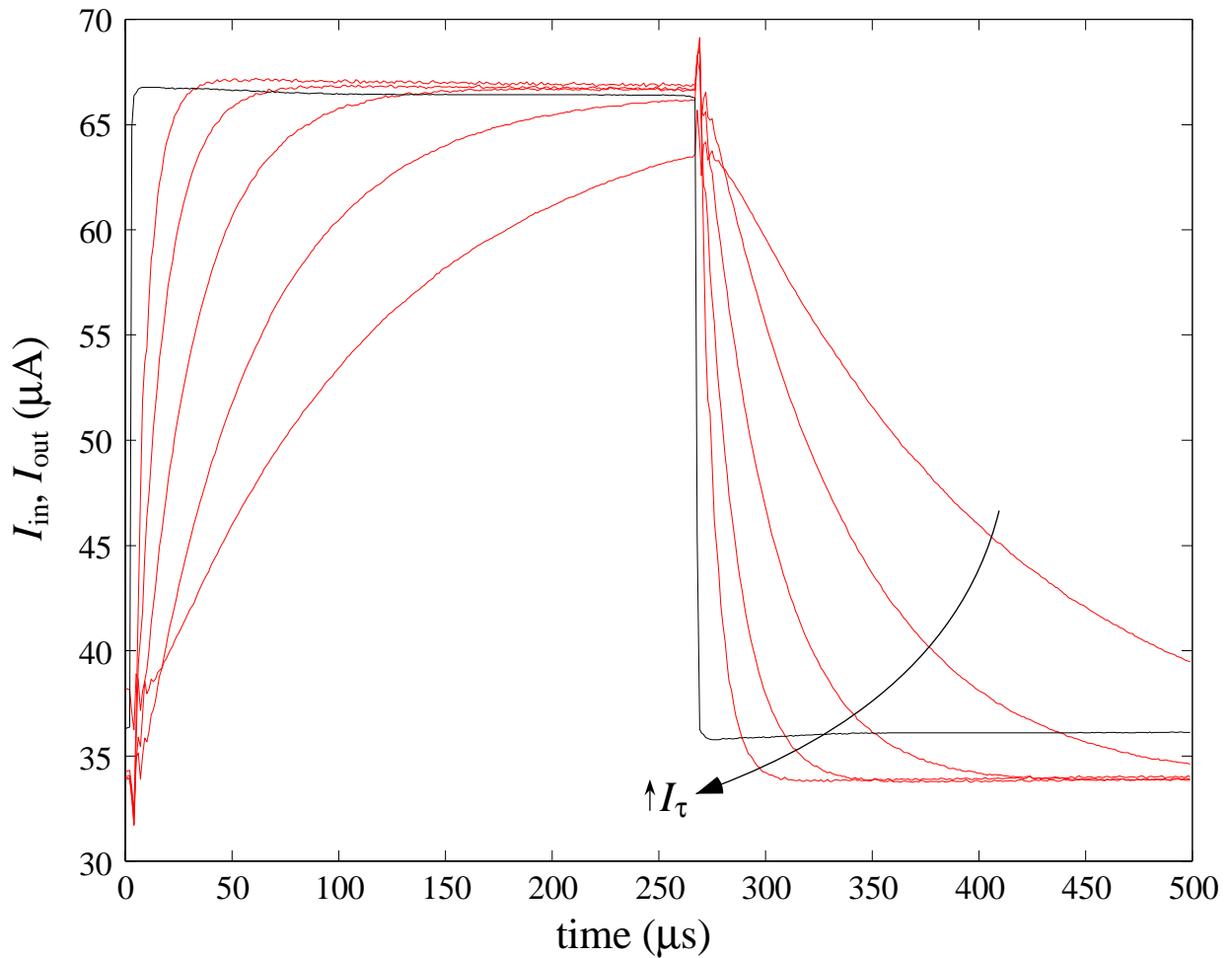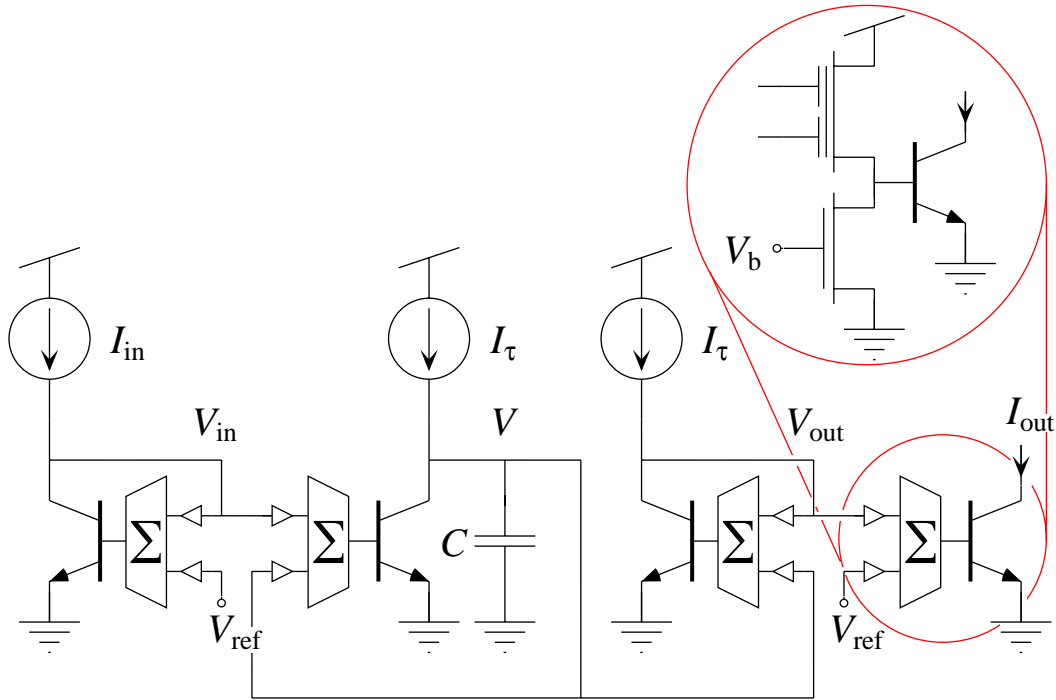MITE Log-Domain First-Order Lowpass Filter




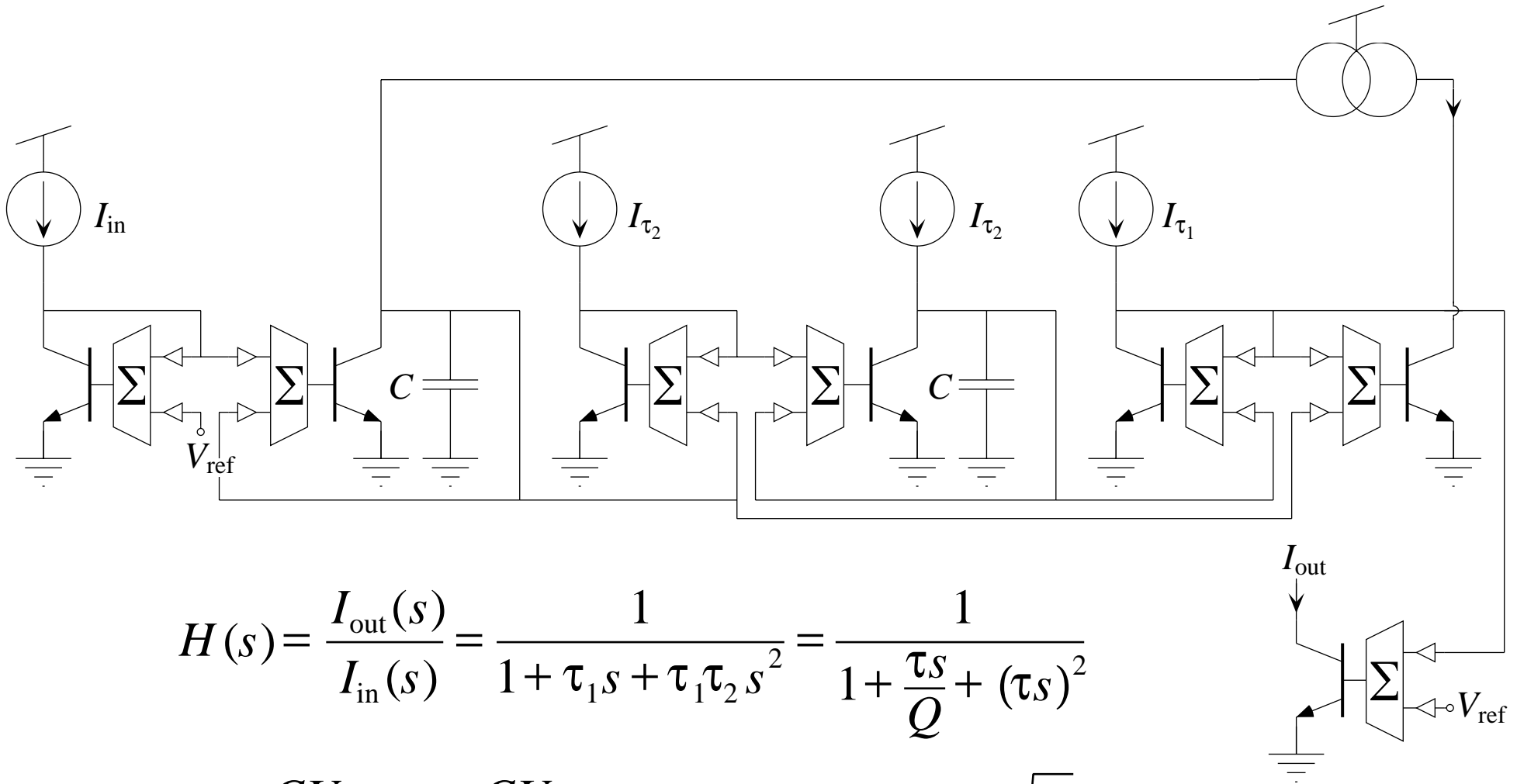
MITE Log-Domain Second-Order Lowpass Filter





$$H(s) = \frac{I_{out}(s)}{I_{in}(s)} = \frac{1}{1 + \tau_1 s + \tau_1 \tau_2 s^2} = \frac{1}{1 + \frac{\tau s}{Q} + (\tau s)^2}$$

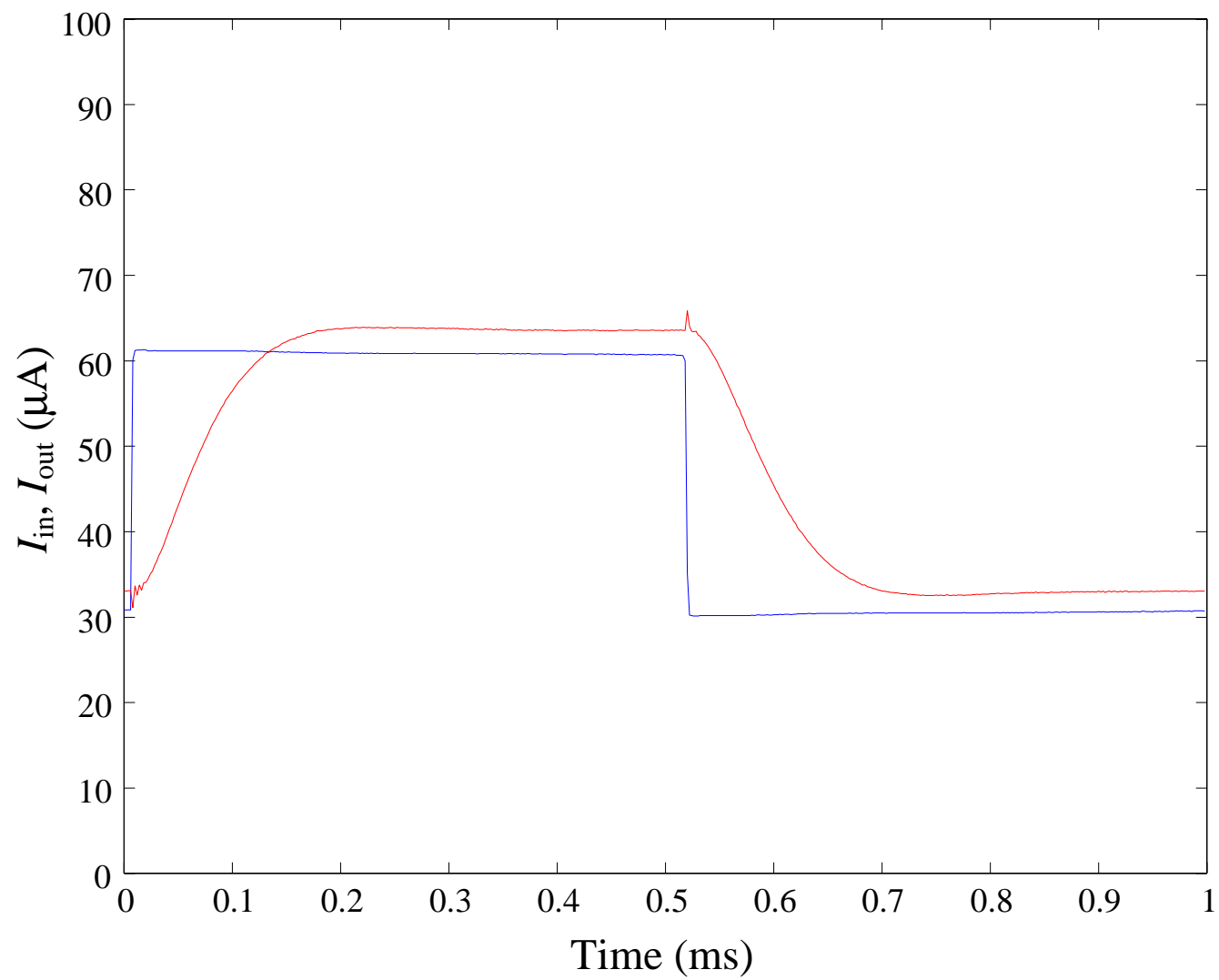
$$\tau_1 = \frac{C U_T}{w I_{\tau_1}} \quad \tau_2 = \frac{C U_T}{w I_{\tau_2}} \quad \tau \equiv \sqrt{\tau_1 \tau_2} \quad Q \equiv \sqrt{\frac{\tau_2}{\tau_1}}$$




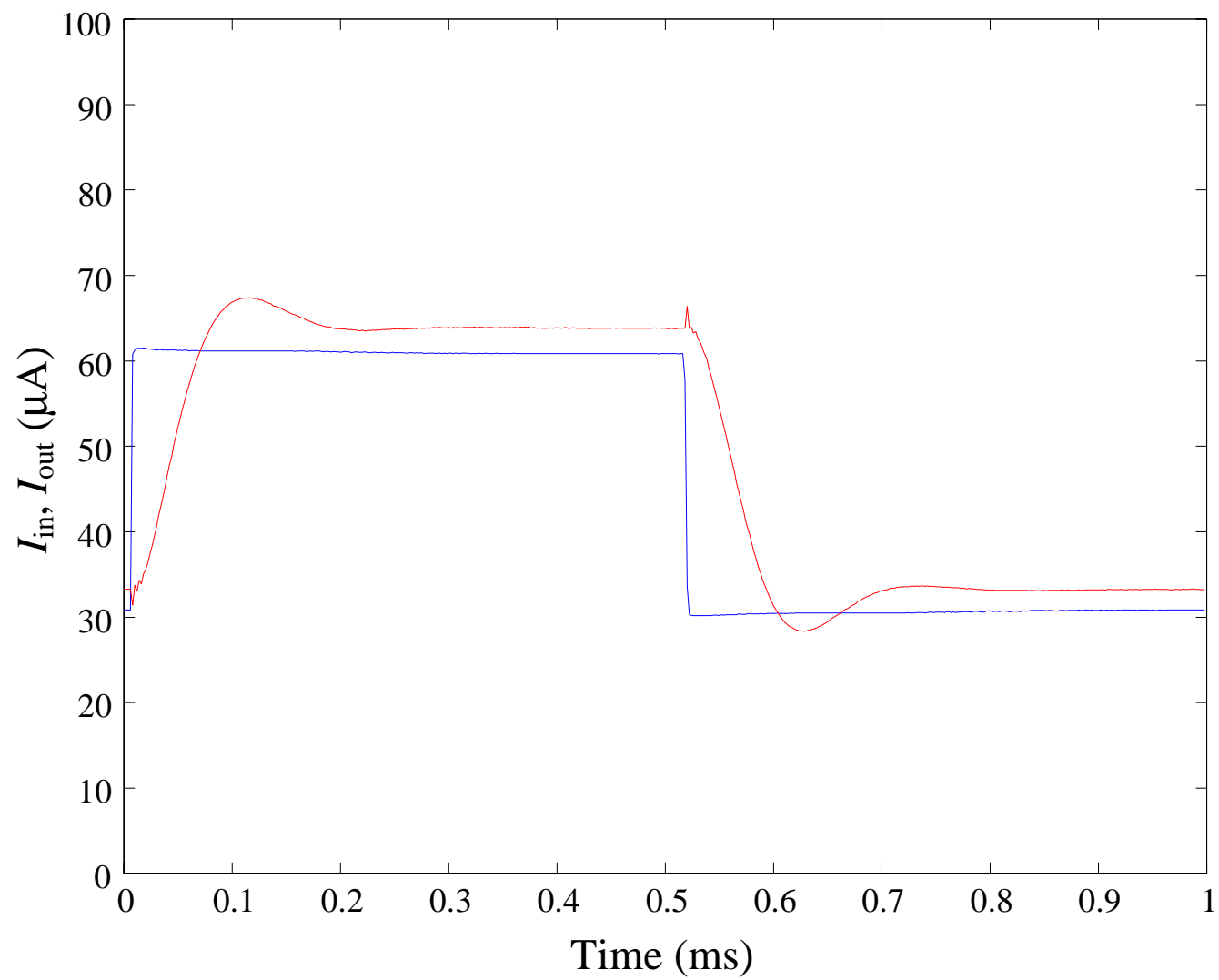

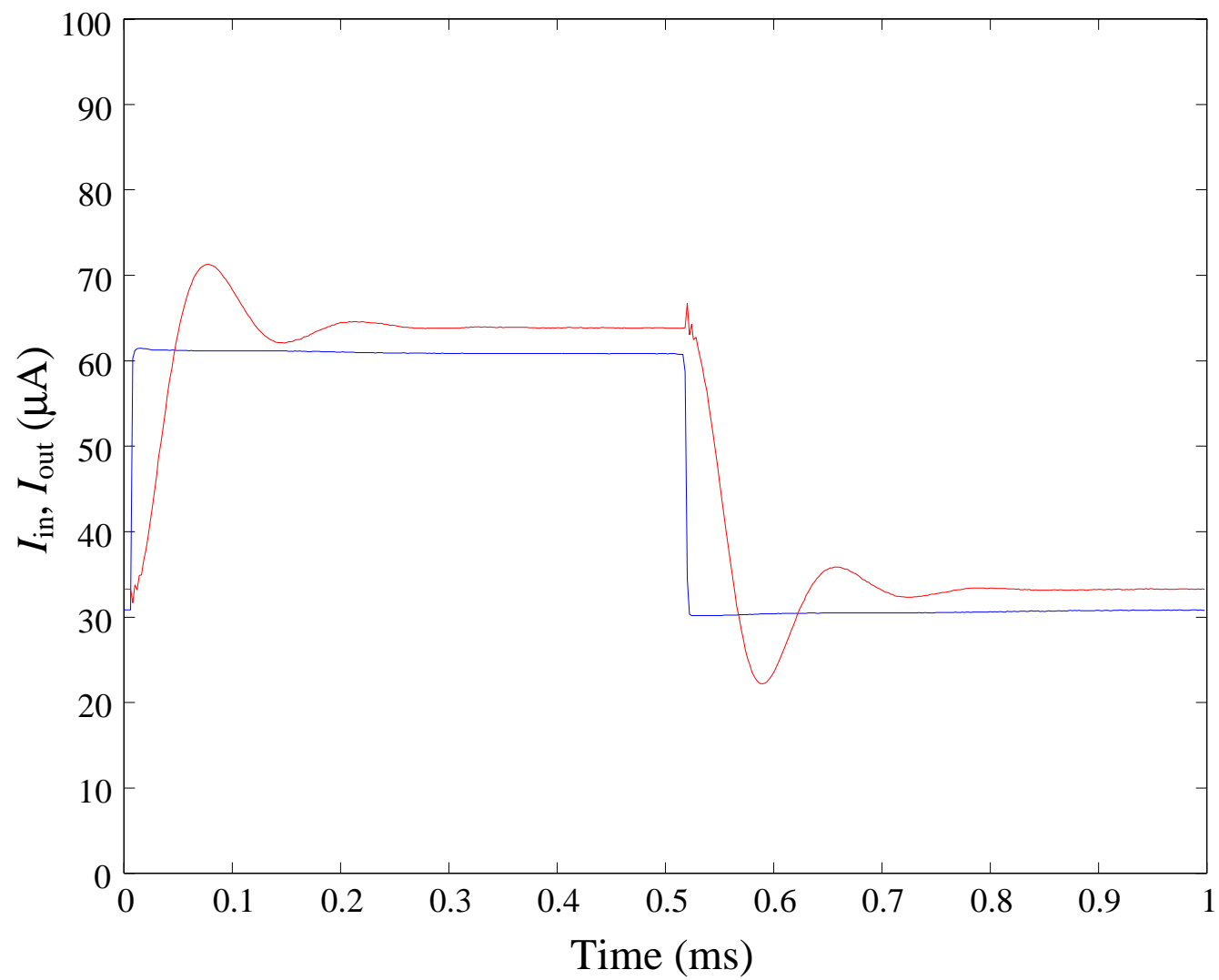


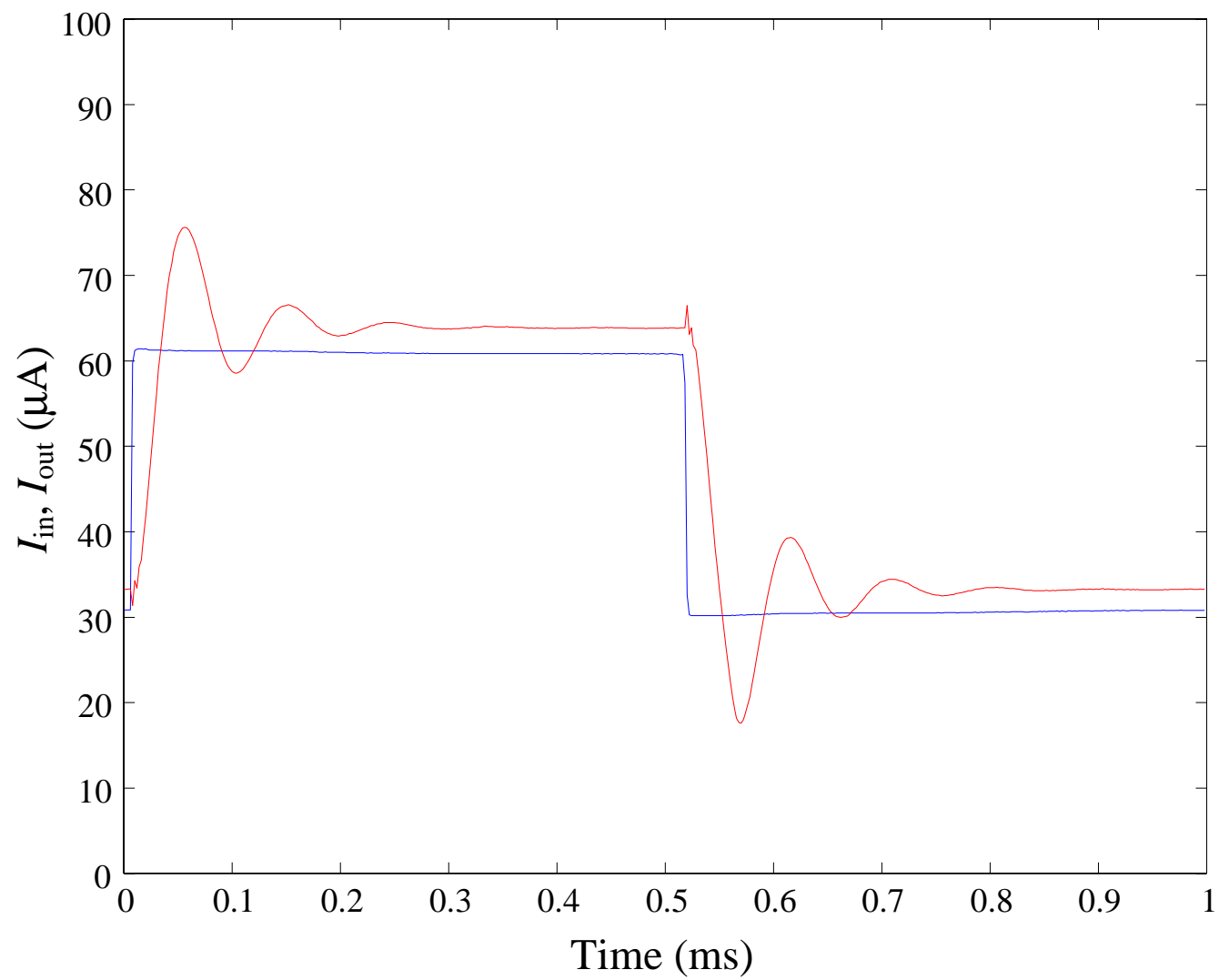

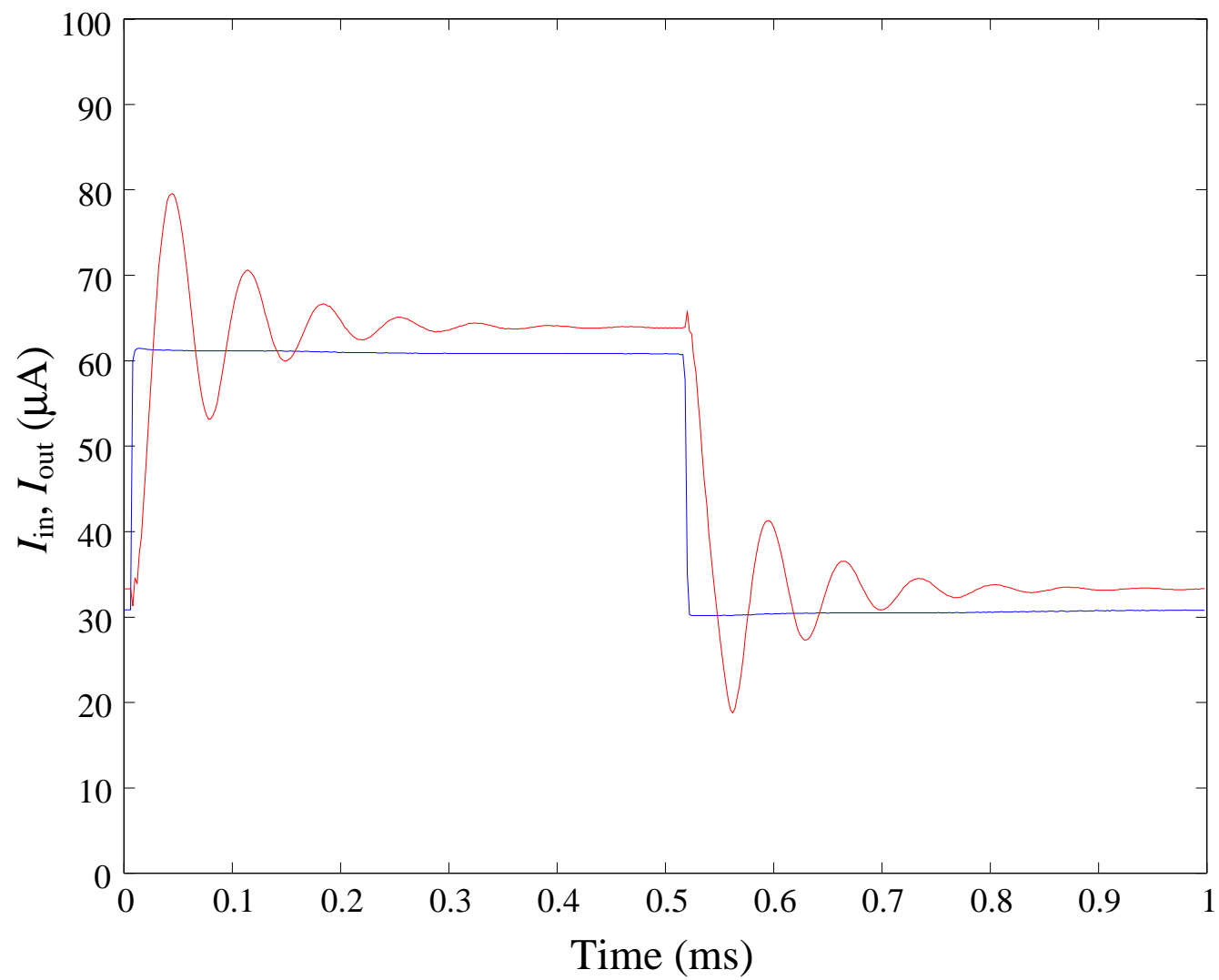

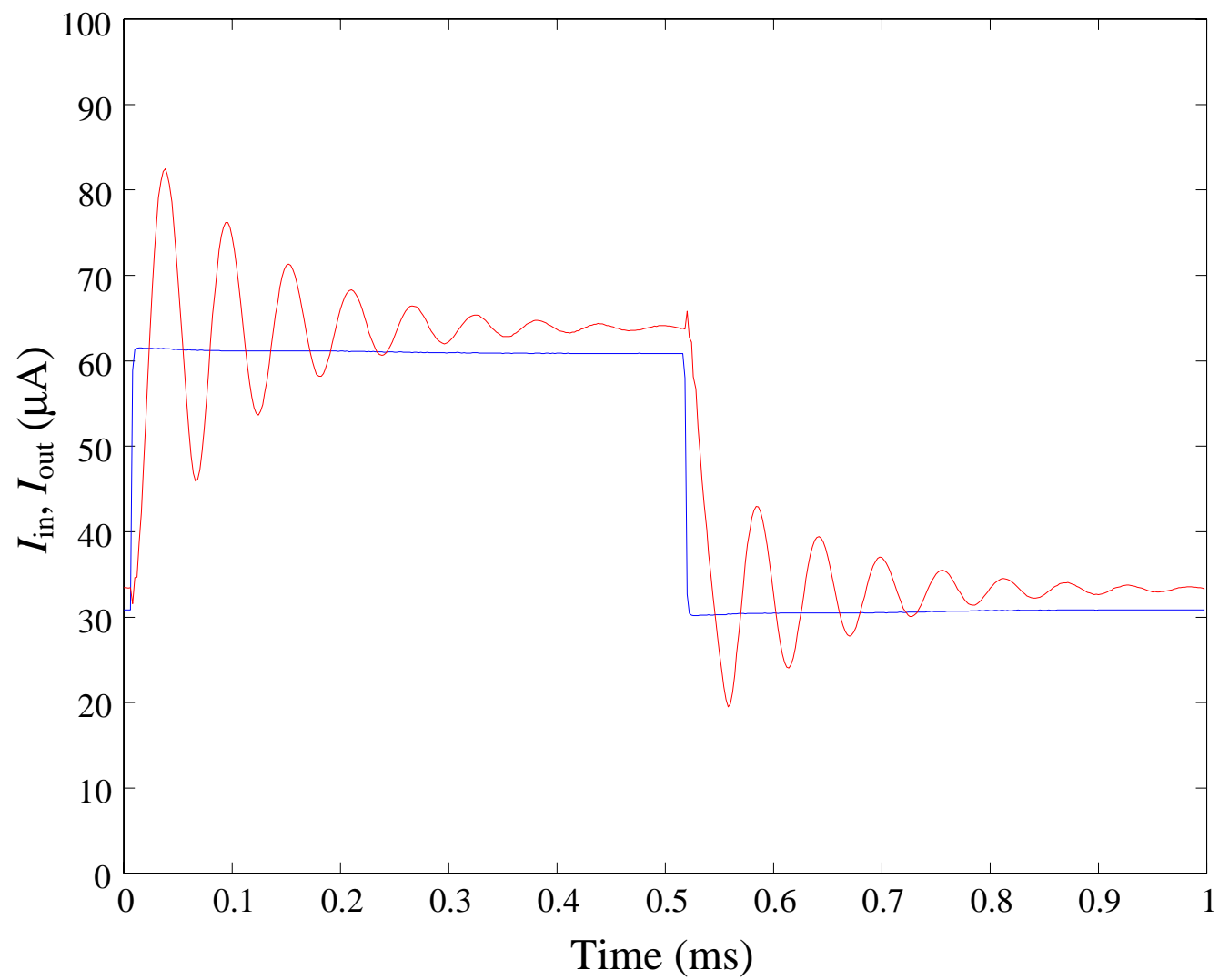

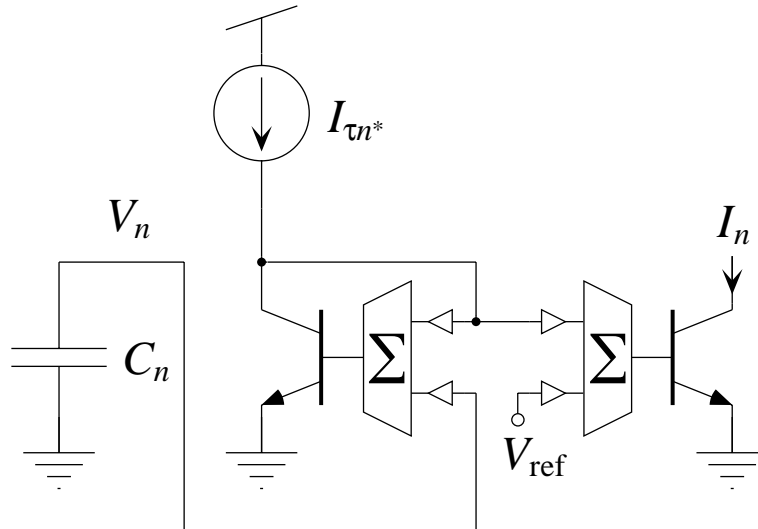MITE Log-Domain Filters: Output Structure



$$\tau_n \frac{dI_n}{dt} = \dots$$


Note: n^* is the index of the state that is excited by the external input.

$$\tau_n = \frac{C_n U_T}{w I_{\tau n}}$$


$$I_n = I_{\tau n^*} e^{w(V_{\text{ref}} - V_n)/U_T}$$

$$\frac{dV_n}{dt} = -\frac{U_T}{w} \frac{1}{I_n} \frac{dI_n}{dt}$$

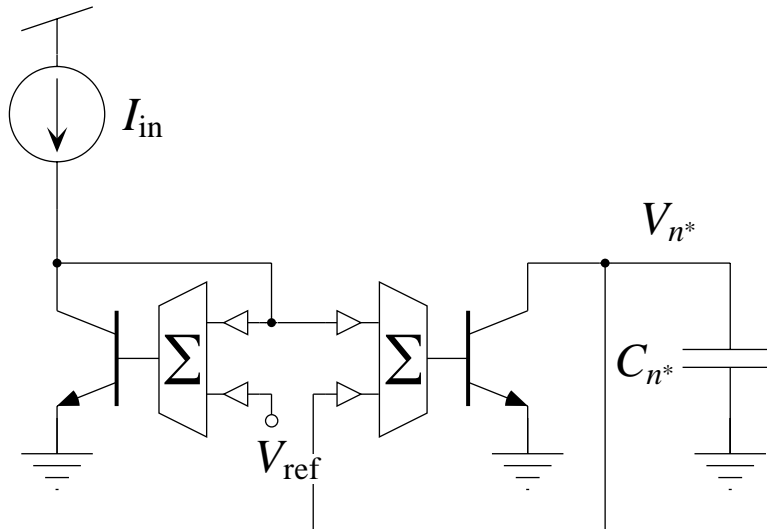MITE Log-Domain Filters: Input Structures



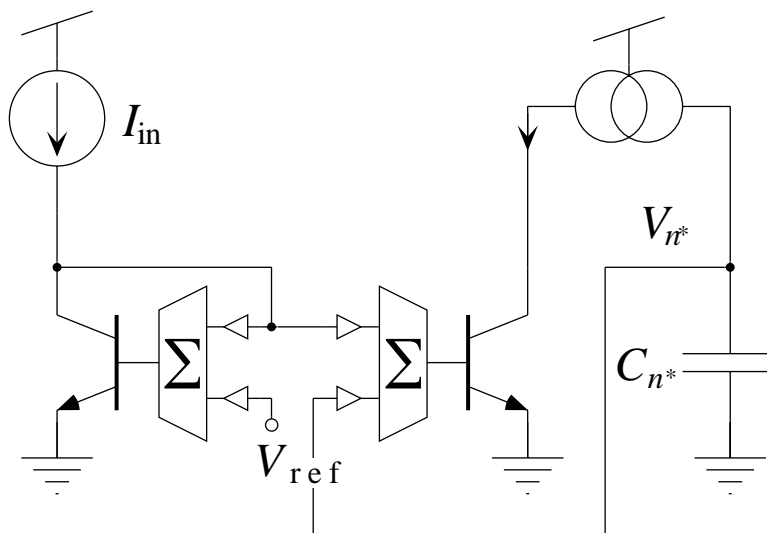
$$\tau_{n^*} \frac{dI_{n^*}}{dt} = \dots + I_{in} - \dots$$




$$\tau_{n^*} \frac{dI_{n^*}}{dt} = \dots - I_{in} - \dots$$

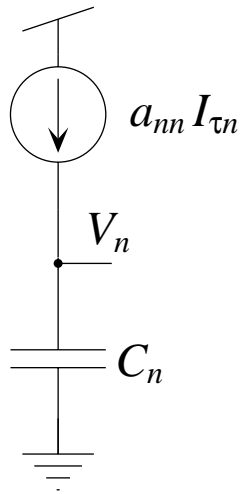MITE Log-Domain Filters: Diagonal Coupling Terms



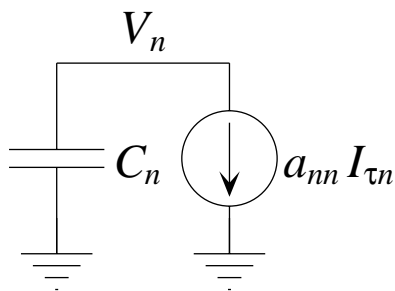
$$\tau_n \frac{dI_n}{dt} = \dots - a_{nn} I_n - \dots$$




$$\tau_n \frac{dI_n}{dt} = \dots + a_{nn} I_n - \dots$$

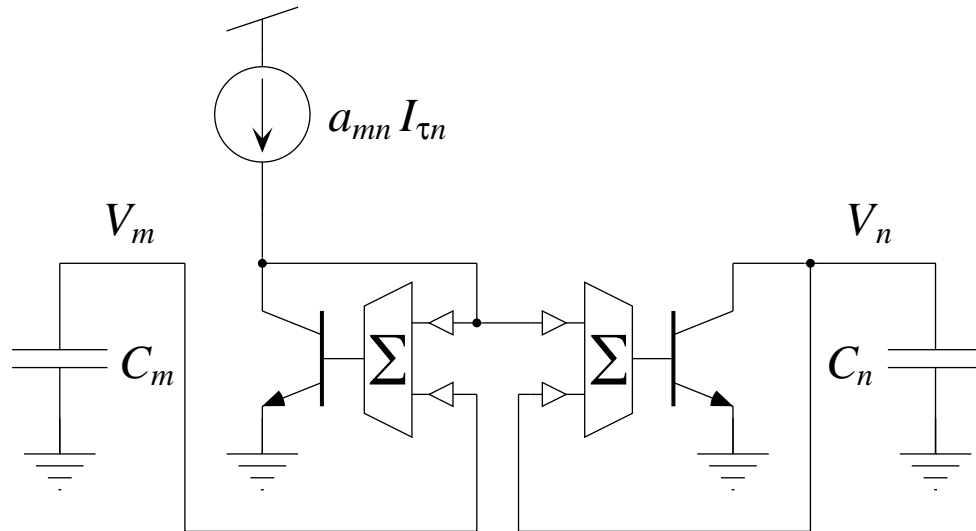MITE Log-Domain Filters: Off-Diagonal Coupling Terms



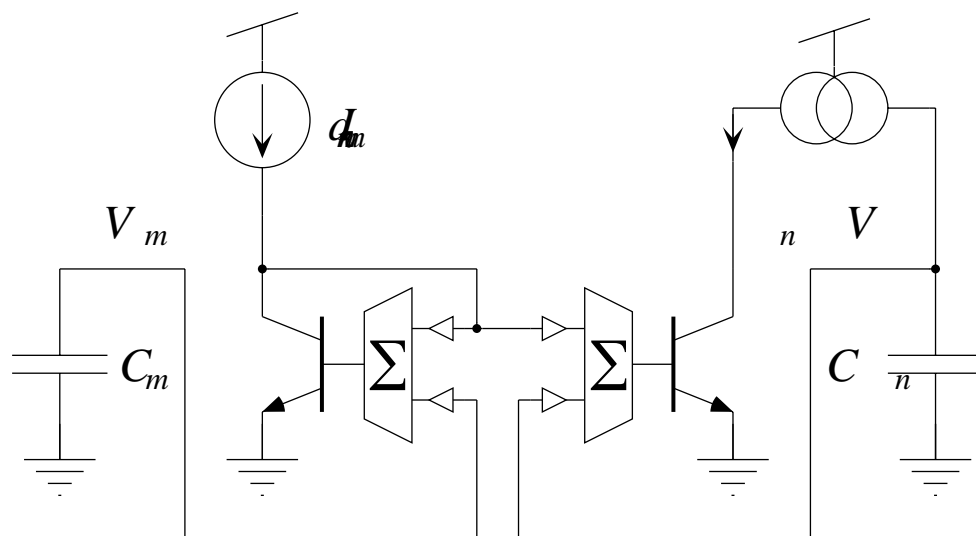
$$\tau_n \frac{dI_n}{dt} = \dots + a_{nm} I_m - \dots$$



$$\tau_n \frac{dI_n}{dt} = \dots - a_{nm} I_m - \dots$$

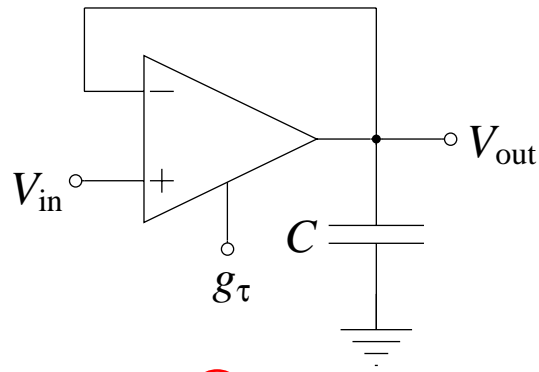MITE Log-Domain Filters: Synthesis of a First-Order Low-Pass




①


$$\textcircled{2} \quad C \frac{dV_{\text{out}}}{dt} = g_{\tau} (V_{\text{in}} - V_{\text{out}})$$

$$\textcircled{3} \quad \tau \frac{dV_{\text{out}}}{dt} = V_{\text{in}} - V_{\text{out}}$$
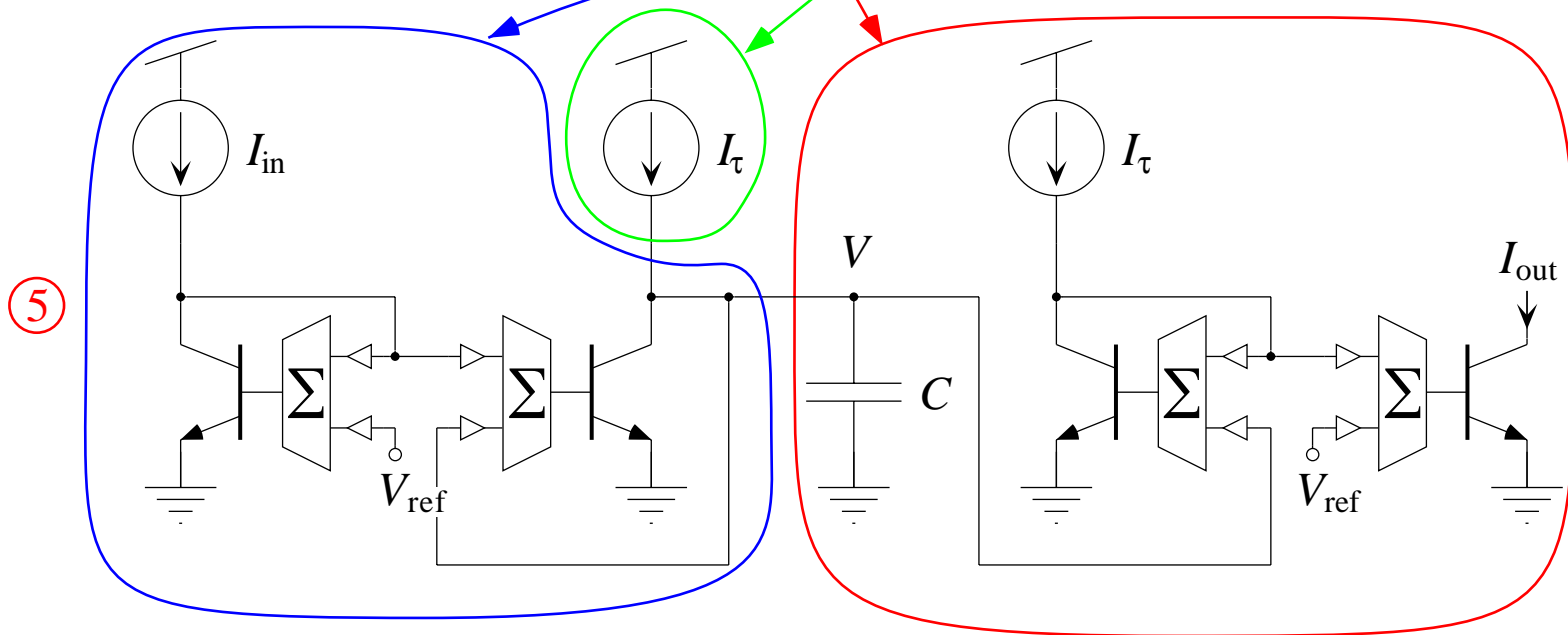
$$\textcircled{4} \quad \tau \frac{dI_{\text{out}}}{dt} = I_{\text{in}} - I_{\text{out}}$$




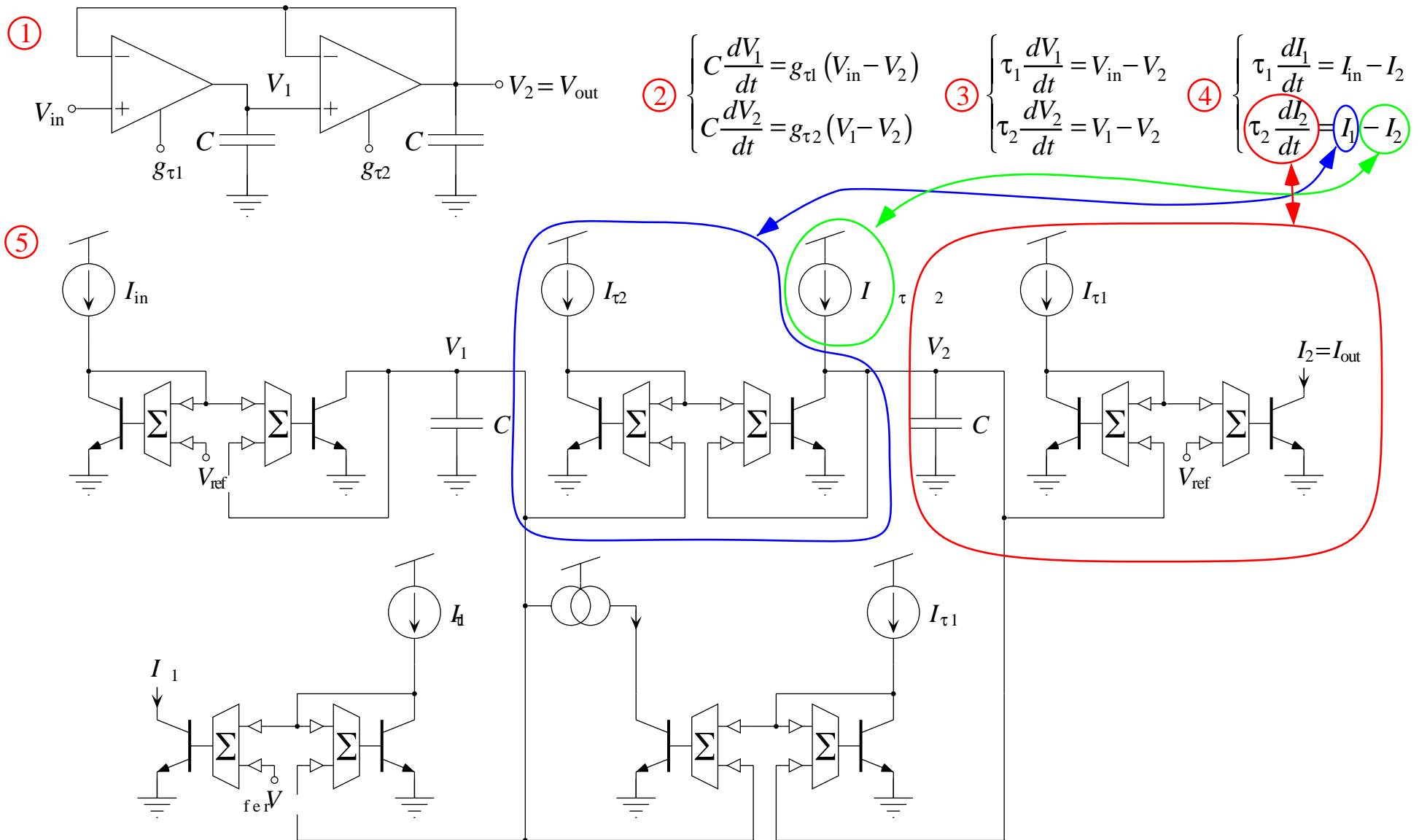MITE Log-Domain Filters: Synthesis of a Second-Order Low-Pass




MITE Log-Domain Filters: Synthesis of a Second-Order Low-Pass

⑤

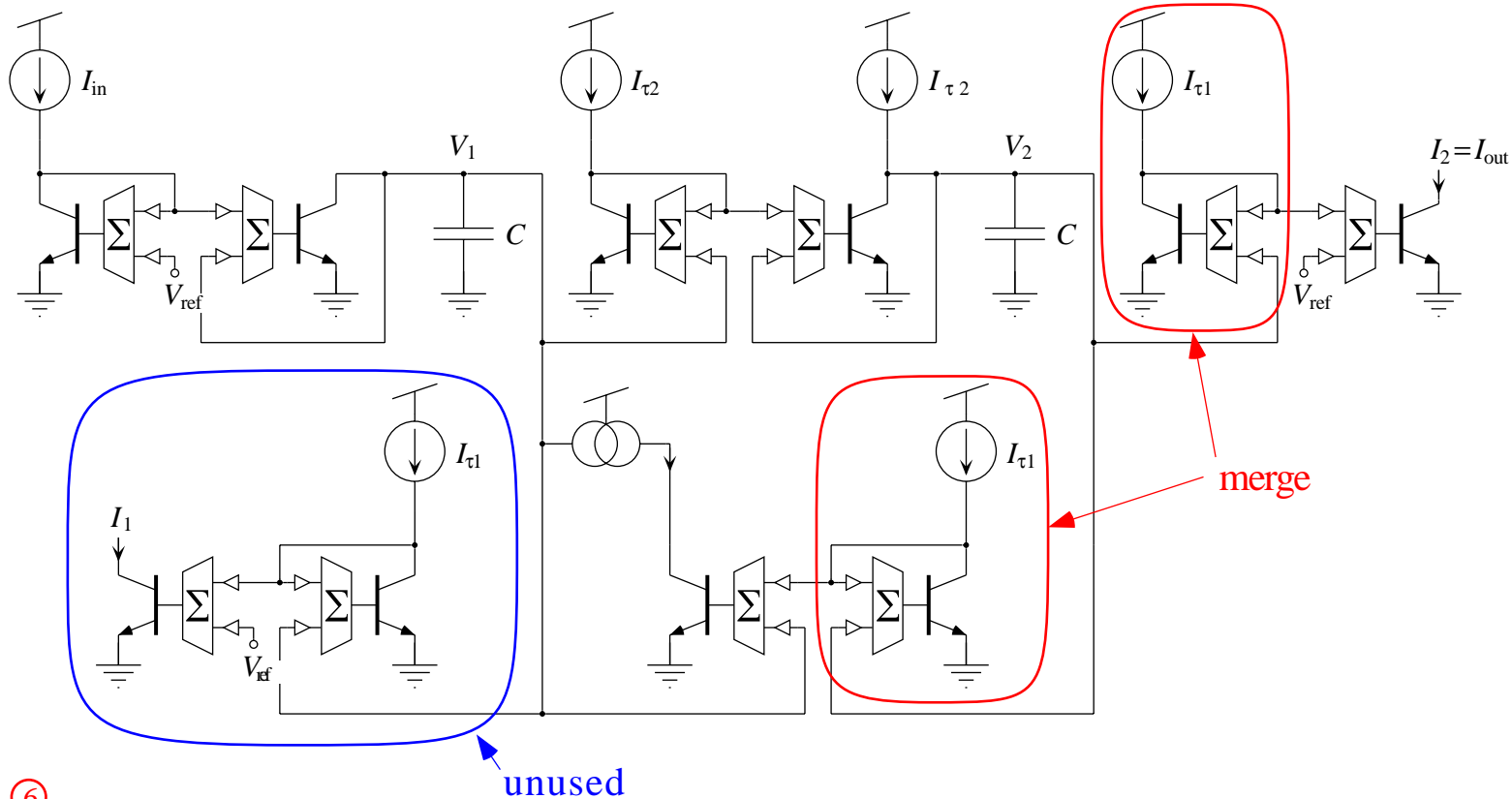

⑥

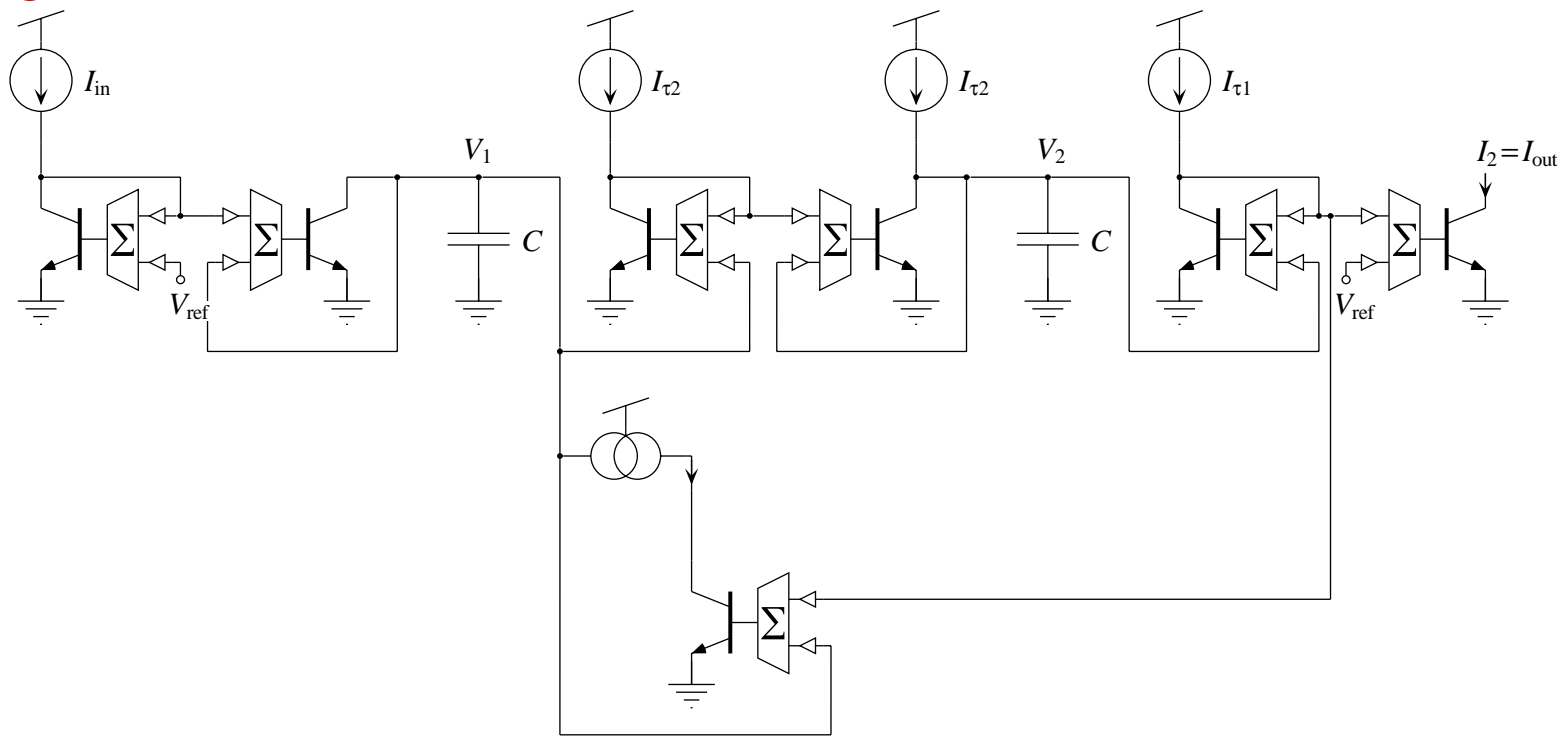

Translinear Analog Signal Processing

