

Static and Dynamic Translinear Circuits

Bradley A. Minch

Mixed Analog-Digital VLSI Circuits and Systems Lab

Cornell University

Ithaca, NY 14853-5401

minch@ece.cornell.edu

March 15, 2004


The logo consists of a solid red square with the word "CORNELL" written in white, serif, uppercase letters across the center.

CORNELL

Translinear Devices and Circuits: What's In A Name?

A **translinear** element is one whose incremental **trans**conductance gain is **linear** in its output current
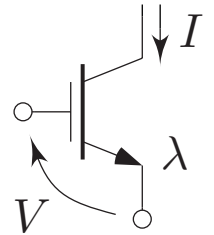
$$I = \lambda I_s e^{V/U_T} \implies g_m = \frac{\partial I}{\partial V} = \underbrace{\lambda I_s e^{V/U_T}}_I \cdot \frac{1}{U_T} = \frac{I}{U_T}$$




The word **translinear** is also meant to convey the notion of bridging the gap between the familiar world of linear circuit design and the largely uncharted territory of nonlinear circuit design.

The Translinear Principle

In a closed loop of junctions comprising an equal number of clockwise and counterclockwise elements, the product of the current densities flowing through the counterclockwise elements is equal to the product of the current densities flowing through the clockwise elements.
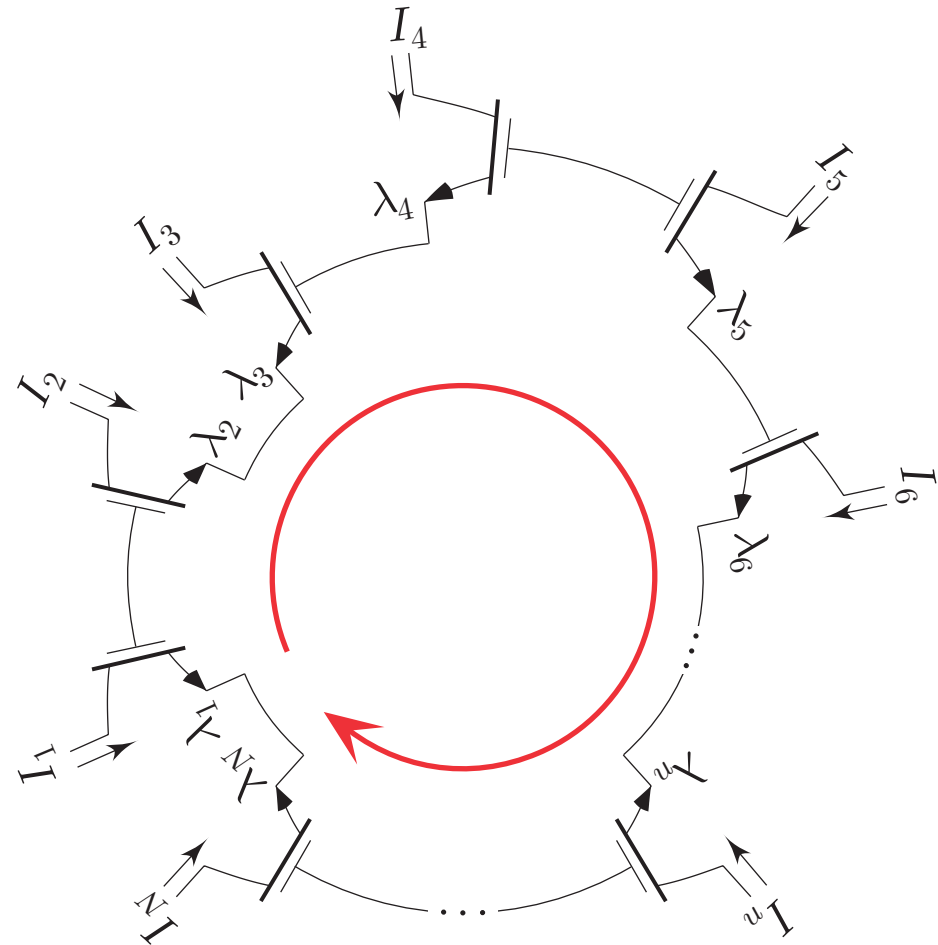
$$\prod_{n \in \text{CW}} \frac{I_n}{\lambda_n} = \prod_{n \in \text{CCW}} \frac{I_n}{\lambda_n}$$




The Ideal **M**ultiple-Input **T**ranslinear **E**lement

The ideal multiple-input translinear element (MITE) produces an output current given by


$$I = \lambda I_s e^{(w_1 V_1 + \dots + w_K V_K) / U_T}$$

where

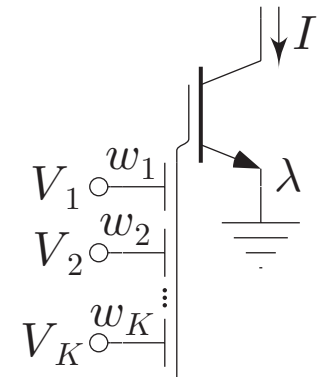
- I_s pre-exponential scaling current
- λ dimensionless constant scaling I_s proportionally
- V_k k th control-gate voltage
- w_k dimensionless positive weight scaling V_k
- U_T thermal voltage, kT/q .



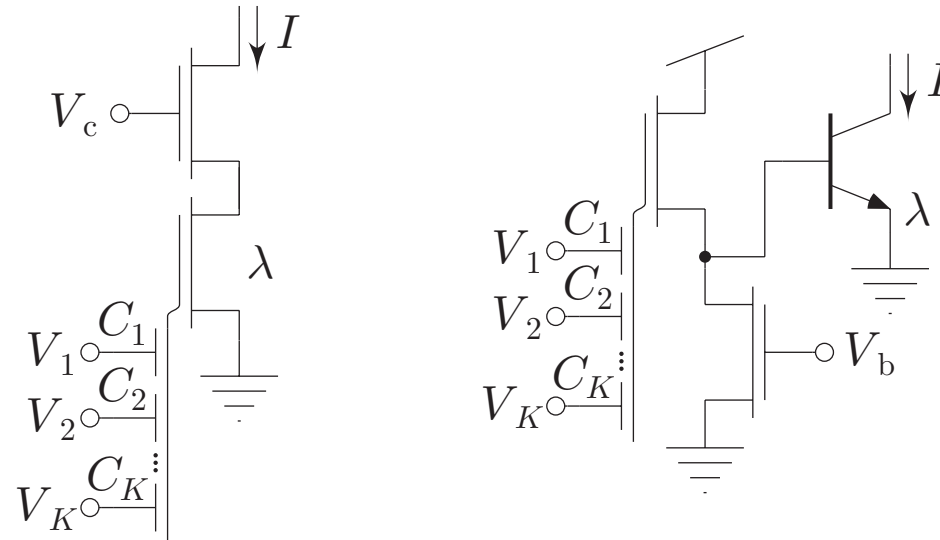Practical Floating-Gate MITE Implementations




Basic MITE Circuit Stages

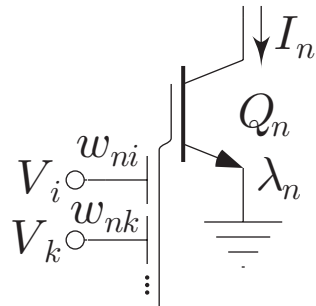


$$I_n \propto e^{w_{ni}V_i/U_T} e^{w_{nk}V_k/U_T}$$

Basic MITE Circuit Stages

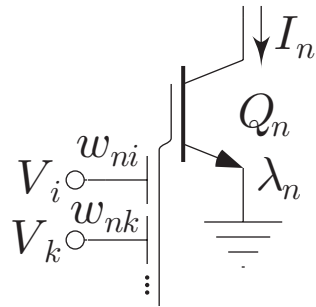

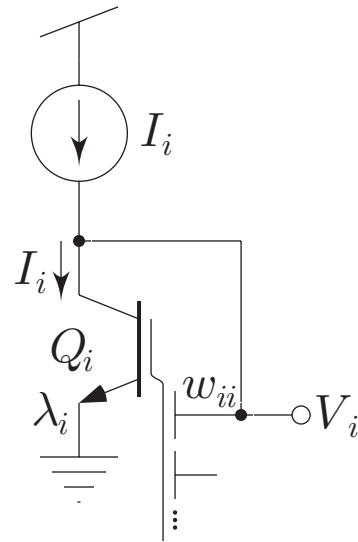
$$I_n \propto e^{w_{ni}V_i/U_T} e^{w_{nk}V_k/U_T}$$




$$V_i = \frac{U_T}{w_{ii}} \log I_i - \dots$$


Basic MITE Circuit Stages

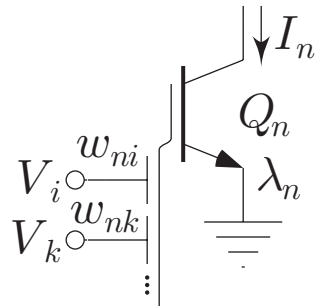
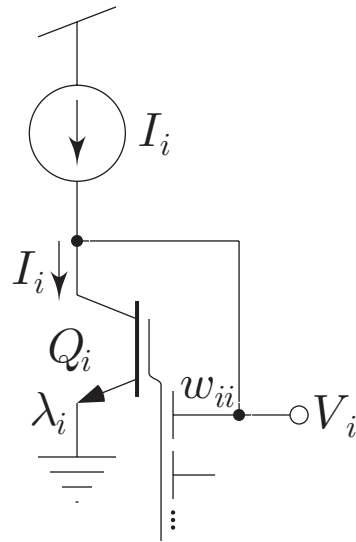
$$I_n \propto e^{w_{ni}V_i/U_T} e^{w_{nk}V_k/U_T}$$


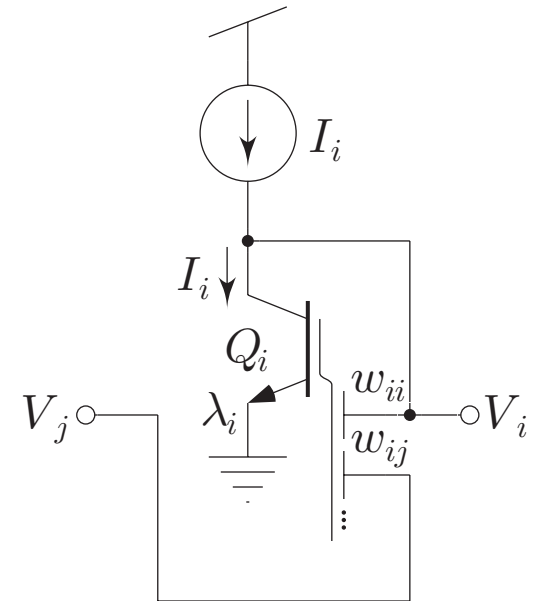
$$V_i = \frac{U_T}{w_{ii}} \log I_i - \dots$$



$$V_i = \frac{U_T}{w_{ii}} \log I_i - \frac{w_{ij}}{w_{ii}} V_j - \dots$$

Elementary MITE Networks


$$I_n \propto e^{w_{ni}V_i/U_T} e^{w_{nk}V_k/U_T}$$

$$\Rightarrow I_n \propto \exp\left(\frac{w_{ni}}{U_T} \left(\frac{U_T}{w_{ii}} \log I_i - \dots\right)\right)$$

$$\times \exp\left(\frac{w_{nk}}{U_T} \left(\frac{U_T}{w_{kk}} \log I_k - \dots\right)\right)$$

$$\Rightarrow I_n \propto e^{(w_{ni}/w_{ii}) \log I_i} e^{(w_{nk}/w_{kk}) \log I_k}$$
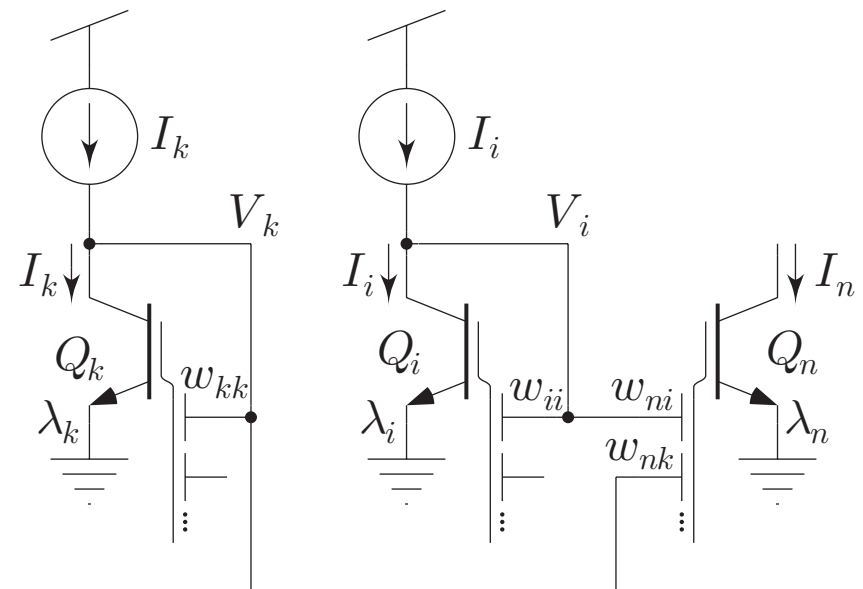
$$\Rightarrow I_n \propto I_i^{w_{ni}/w_{ii}} \times I_k^{w_{nk}/w_{kk}}$$




Elementary MITE Networks

$$I_n \propto e^{w_{ni}V_i/U_T}$$

$$\Rightarrow I_n \propto \exp\left(\frac{w_{ni}}{U_T}\left(\frac{U_T}{w_{ii}}\log I_i - \frac{w_{ij}}{w_{ii}}\left(\frac{U_T}{w_{jj}}\log I_j - \dots\right) - \dots\right)\right)$$

$$\Rightarrow I_n \propto e^{(w_{ni}/w_{ii})\log I_i} e^{-\left(w_{ni}w_{ij}/w_{ii}w_{jj}\right)\log I_j}$$
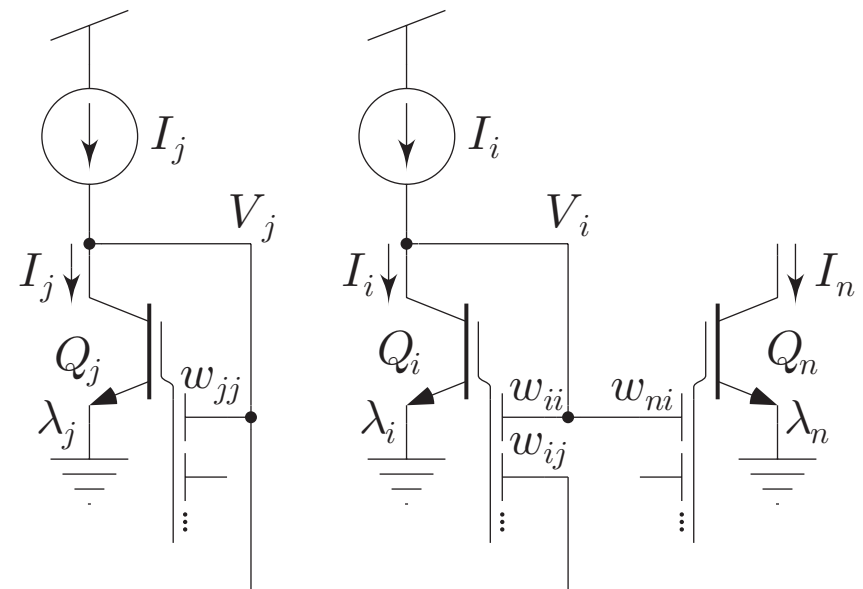
$$\Rightarrow I_n \propto \frac{I_i^{w_{ni}/w_{ii}}}{I_j^{w_{ni}w_{ij}/w_{ii}w_{jj}}}$$



Static MITE Network Synthesis: **Square-Root Circuit**

Synthesize a square-root circuit described by

$$z = \sqrt{x}, \quad \text{where } x > 0.$$

Static MITE Network Synthesis: **Square-Root Circuit**

Synthesize a square-root circuit described by

$$z = \sqrt{x}, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Static MITE Network Synthesis: **Square-Root Circuit**

Synthesize a square-root circuit described by

$$z = \sqrt{x}, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the relationship, we obtain

$$\frac{I_z}{I_1} = \sqrt{\frac{I_x}{I_1}}$$

Static MITE Network Synthesis: **Square-Root Circuit**

Synthesize a square-root circuit described by

$$z = \sqrt{x}, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the relationship, we obtain

$$\frac{I_z}{I_1} = \sqrt{\frac{I_x}{I_1}} \quad \Rightarrow \quad I_z = \sqrt{I_x I_1}$$

Static MITE Network Synthesis: **Square-Root Circuit**

Synthesize a square-root circuit described by

$$z = \sqrt{x}, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the relationship, we obtain


$$\frac{I_z}{I_1} = \sqrt{\frac{I_x}{I_1}} \quad \Rightarrow \quad I_z = \sqrt{I_x I_1} \quad \Rightarrow \quad I_z^2 = I_x I_1.$$

Static MITE Network Synthesis: Square-Root Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$


Static MITE Network Synthesis: Square-Root Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

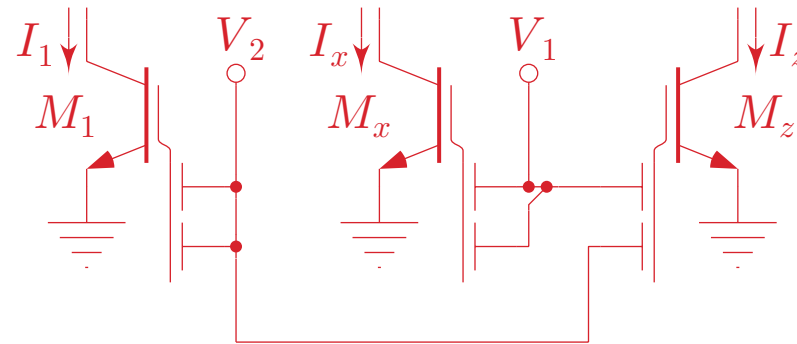


Static MITE Network Synthesis: Square-Root Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

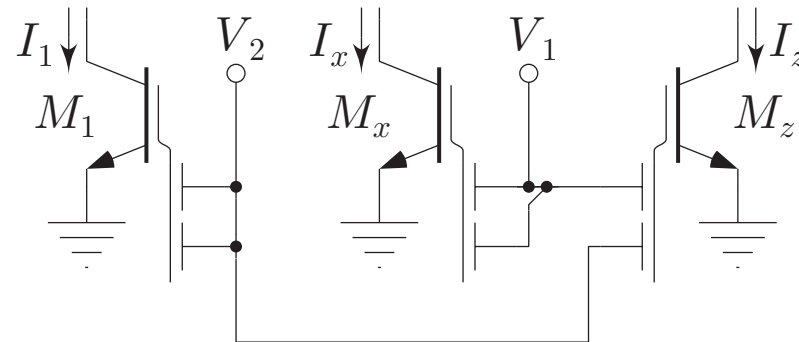


Static MITE Network Synthesis: Square-Root Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

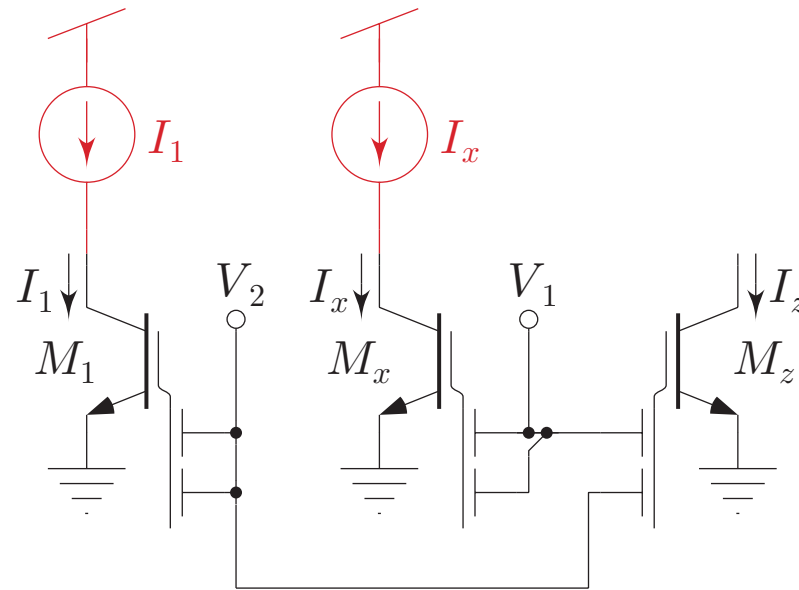


Static MITE Network Synthesis: Square-Root Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

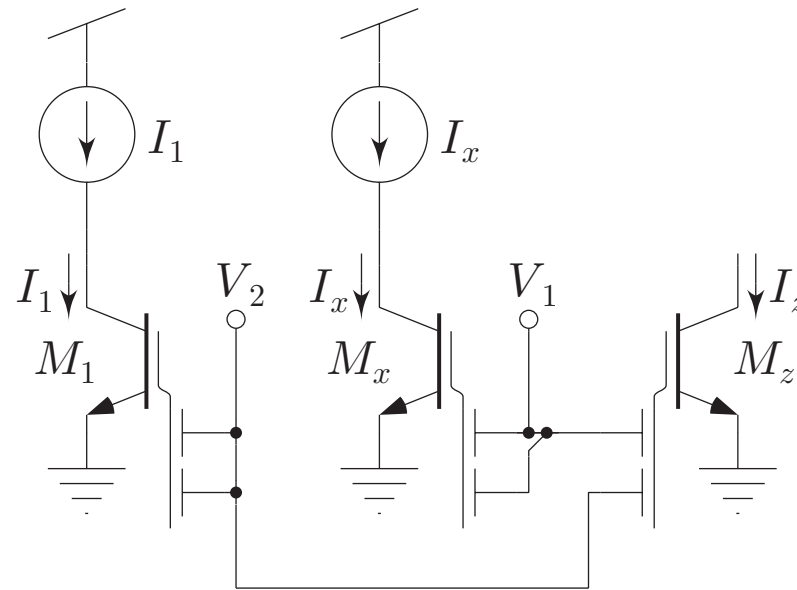


Static MITE Network Synthesis: Square-Root Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

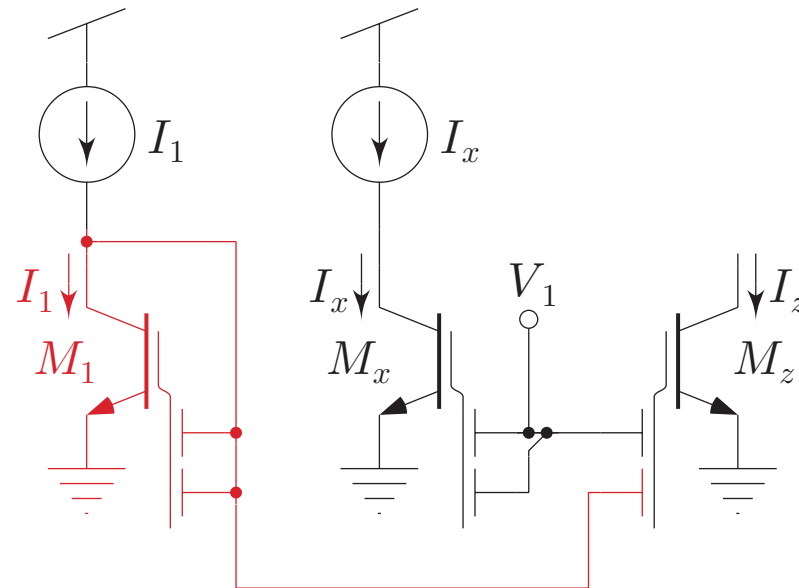


Static MITE Network Synthesis: Square-Root Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

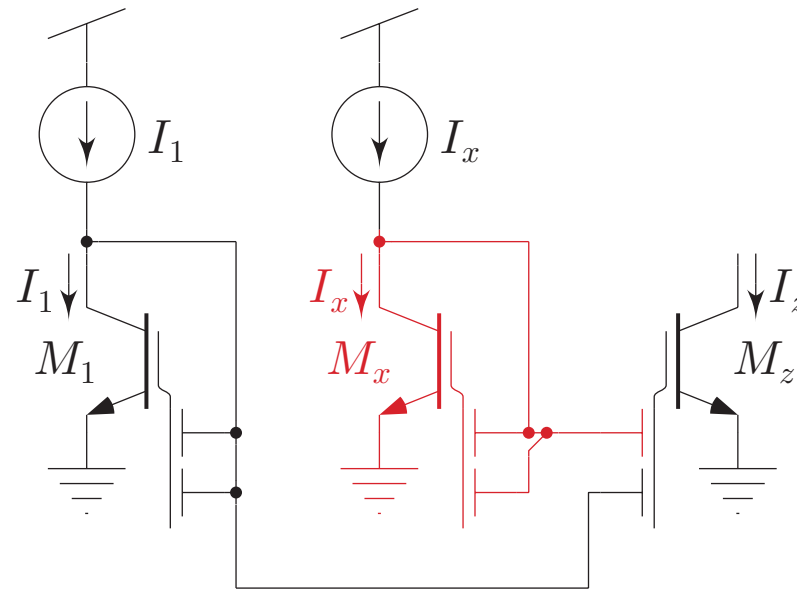


Static MITE Network Synthesis: Square-Root Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

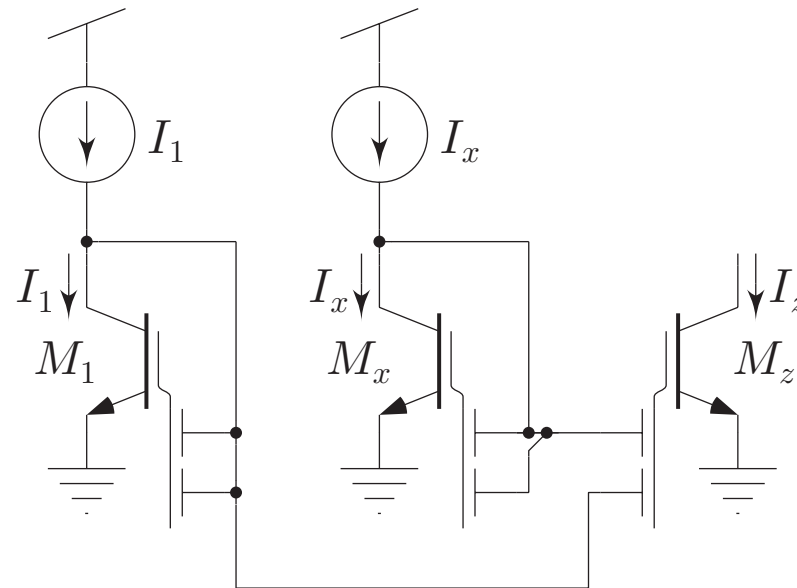

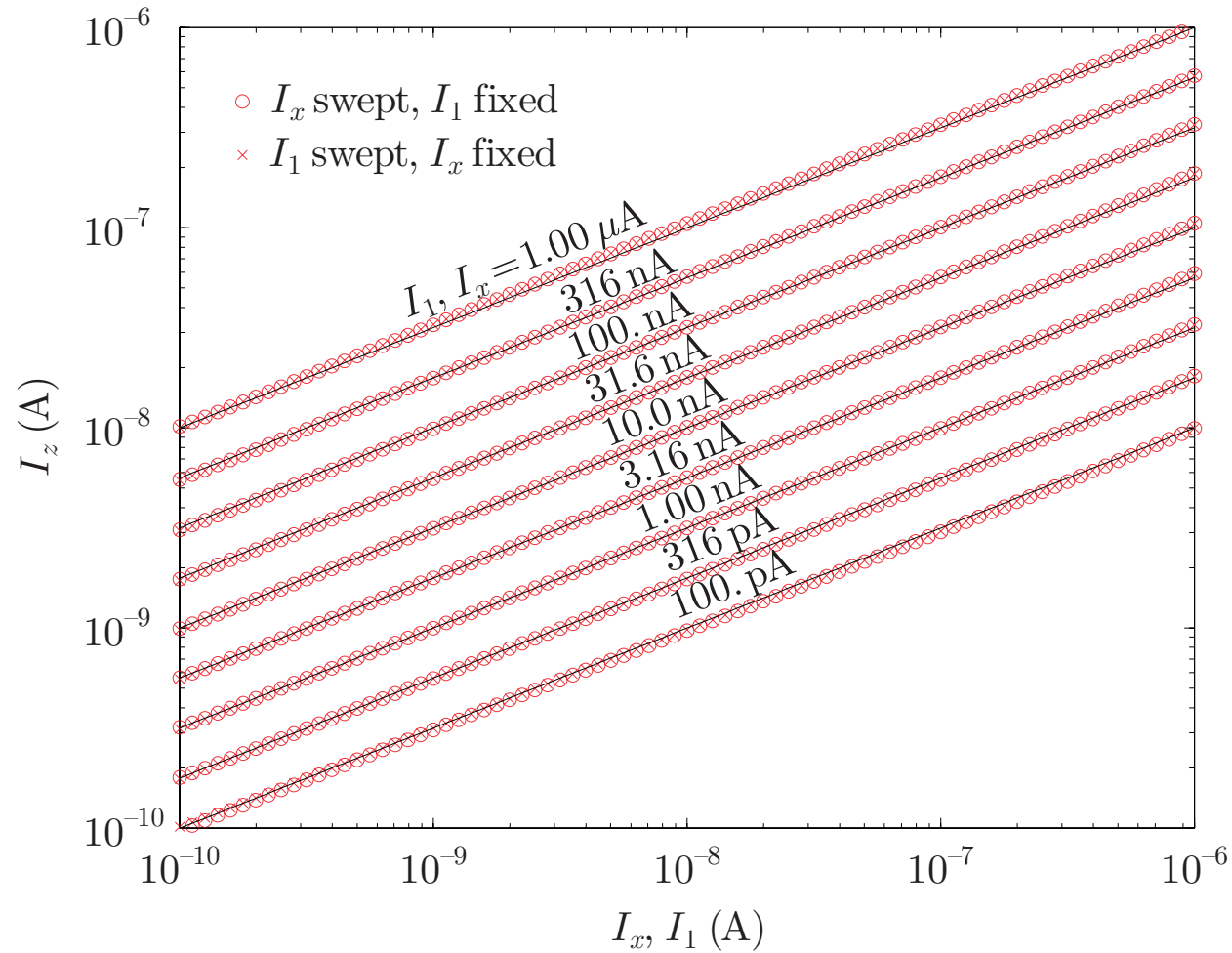Experimental Measurements: Square-Root Circuit



Static MITE Network Synthesis: Squaring Circuit

Synthesize a squaring circuit described by

$$x = z^2, \quad \text{where } x > 0.$$

Static MITE Network Synthesis: Squaring Circuit

Synthesize a squaring circuit described by

$$x = z^2, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Static MITE Network Synthesis: Squaring Circuit

Synthesize a squaring circuit described by

$$x = z^2, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the relationship, we obtain

$$\frac{I_x}{I_1} = \left(\frac{I_z}{I_1} \right)^2$$

Static MITE Network Synthesis: Squaring Circuit

Synthesize a squaring circuit described by

$$x = z^2, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the relationship, we obtain


$$\frac{I_x}{I_1} = \left(\frac{I_z}{I_1} \right)^2 \quad \Rightarrow \quad I_z^2 = I_x I_1.$$

Static MITE Network Synthesis: Squaring Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$


Static MITE Network Synthesis: Squaring Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

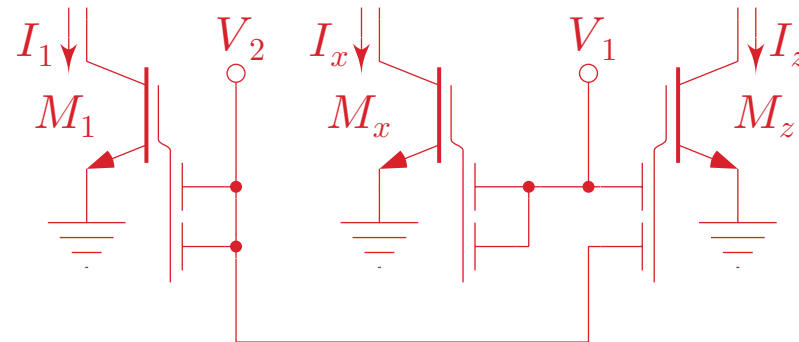


Static MITE Network Synthesis: Squaring Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

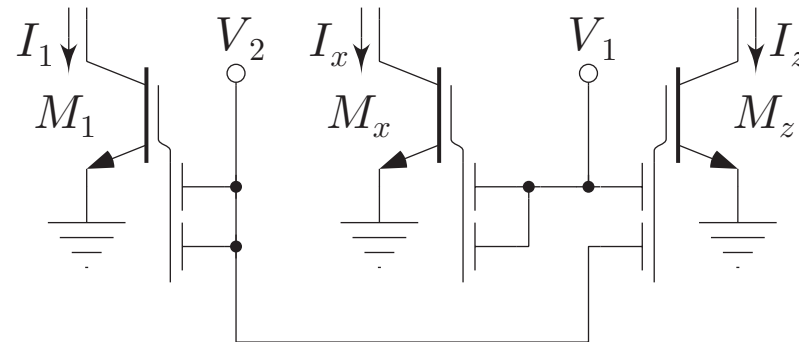


Static MITE Network Synthesis: Squaring Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

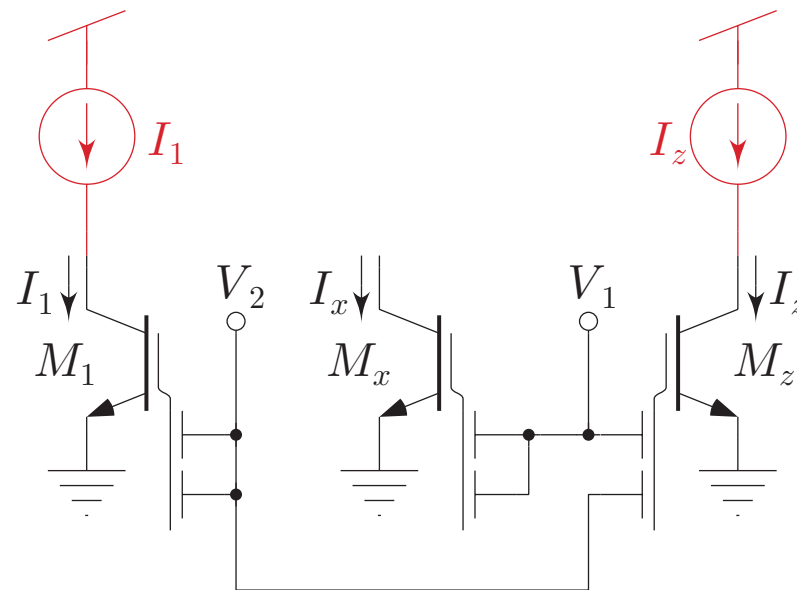


Static MITE Network Synthesis: Squaring Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

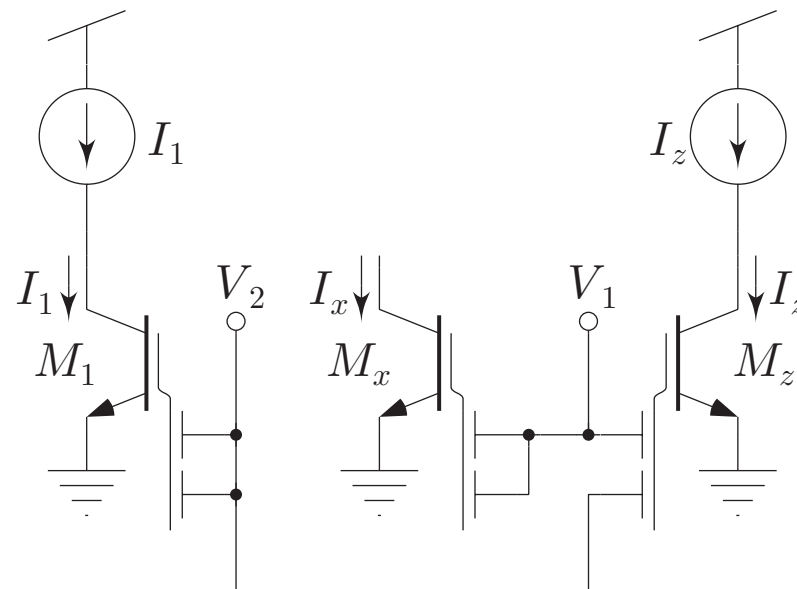


Static MITE Network Synthesis: Squaring Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

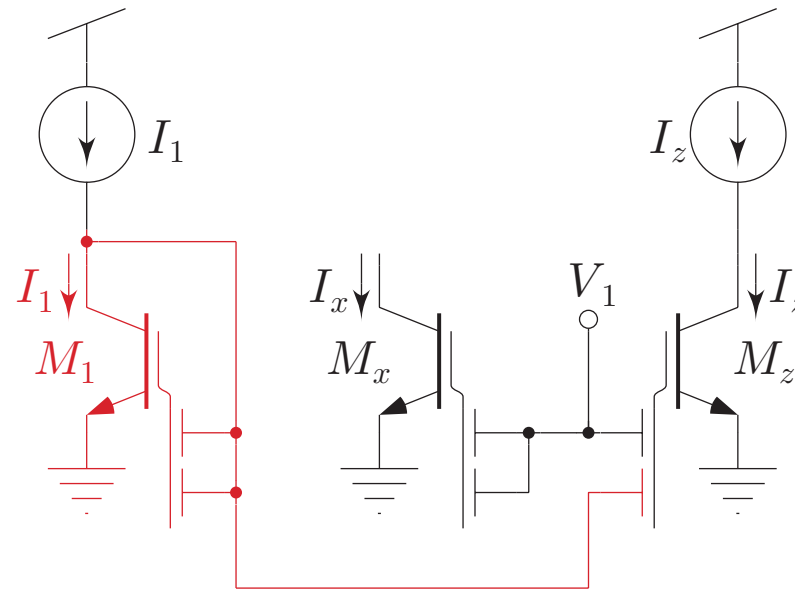


Static MITE Network Synthesis: Squaring Circuit

$$\text{TLP: } I_z^2 = I_x I_1$$

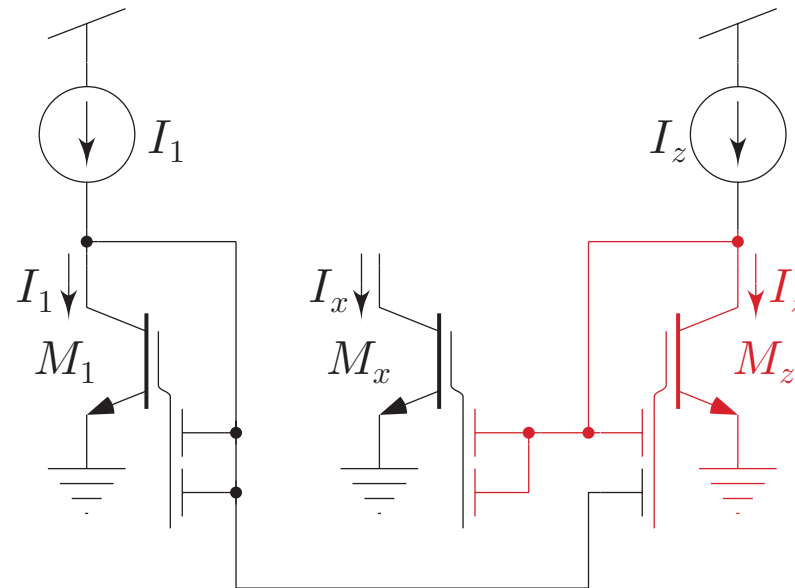


Static MITE Network Synthesis: Squaring Circuit


$$\text{TLP: } I_z^2 = I_x I_1$$

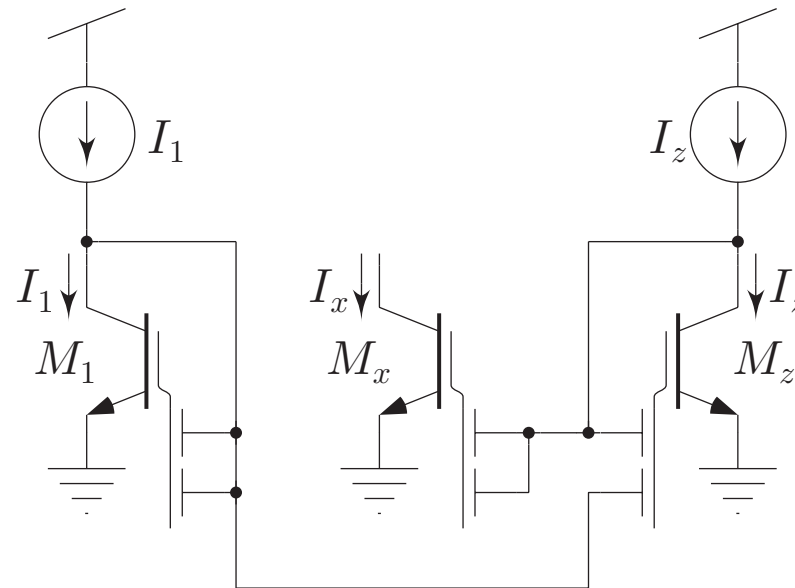

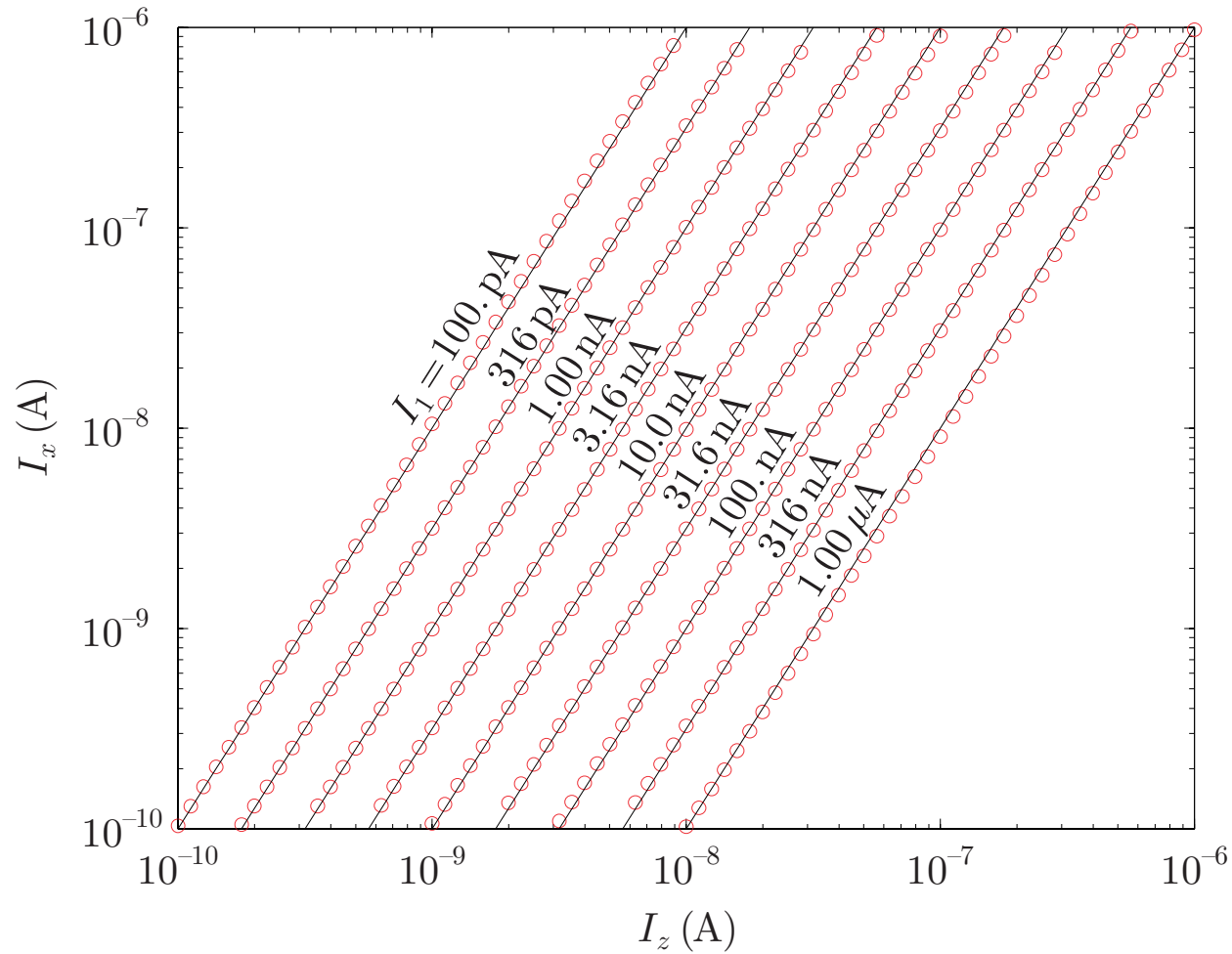
Experimental Measurements: Squaring Circuit



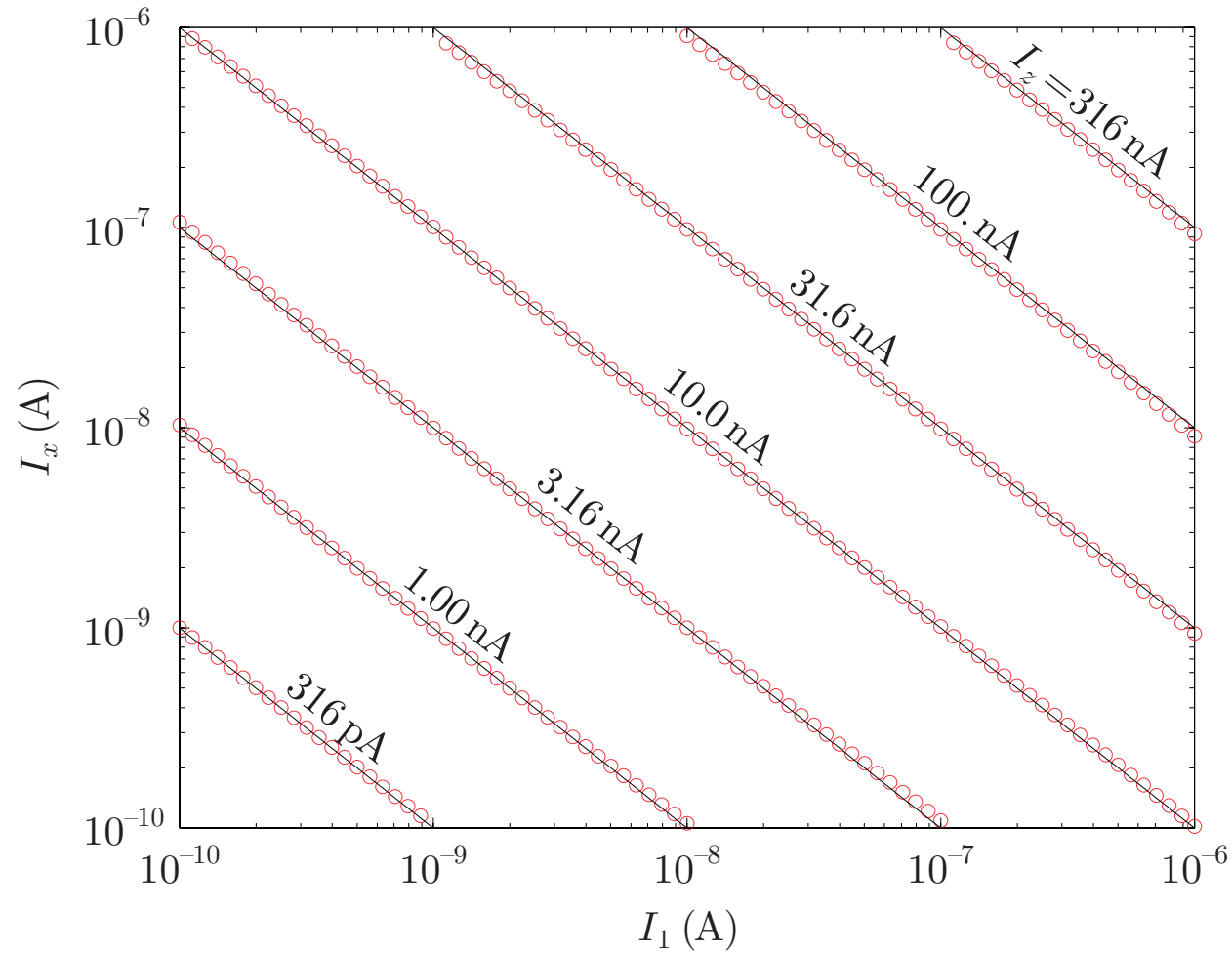
Experimental Measurements: Squaring Circuit



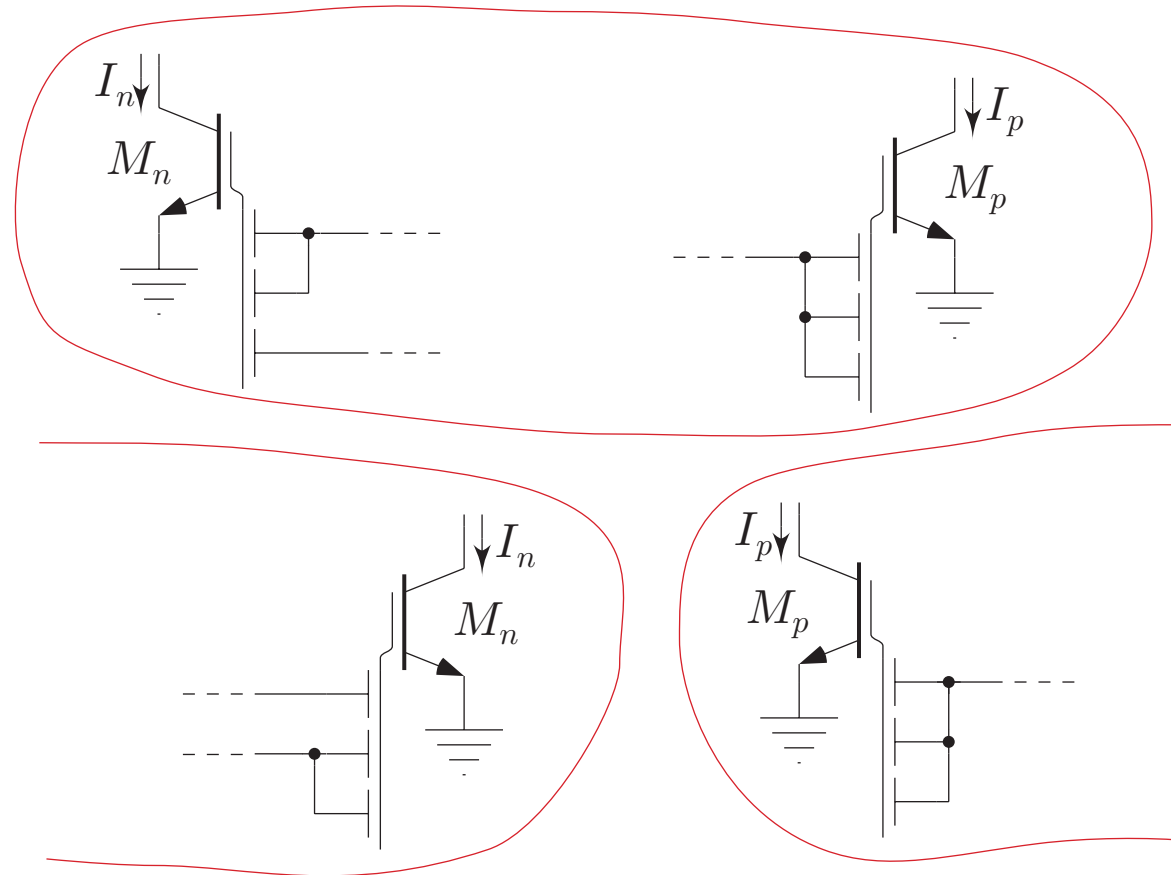
Static MITE Network Synthesis: Consolidation



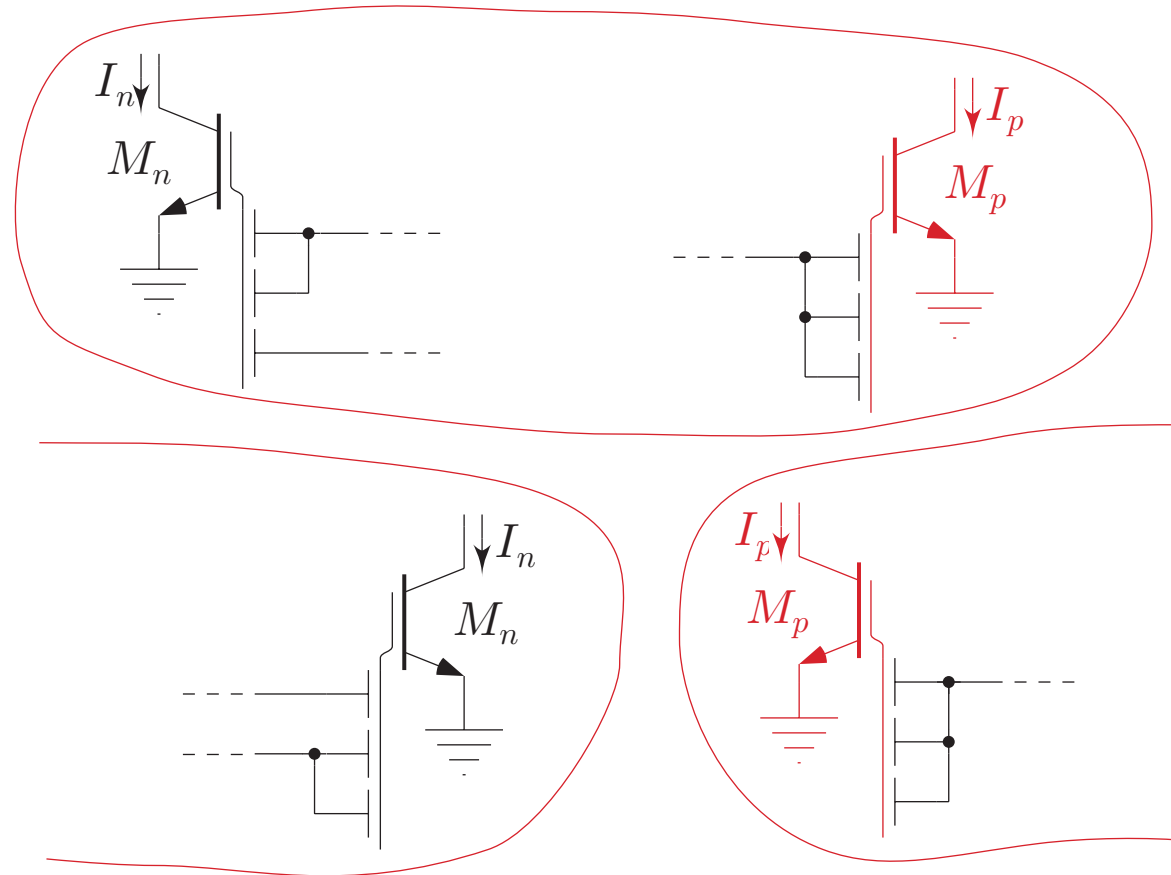
Static MITE Network Synthesis: Consolidation



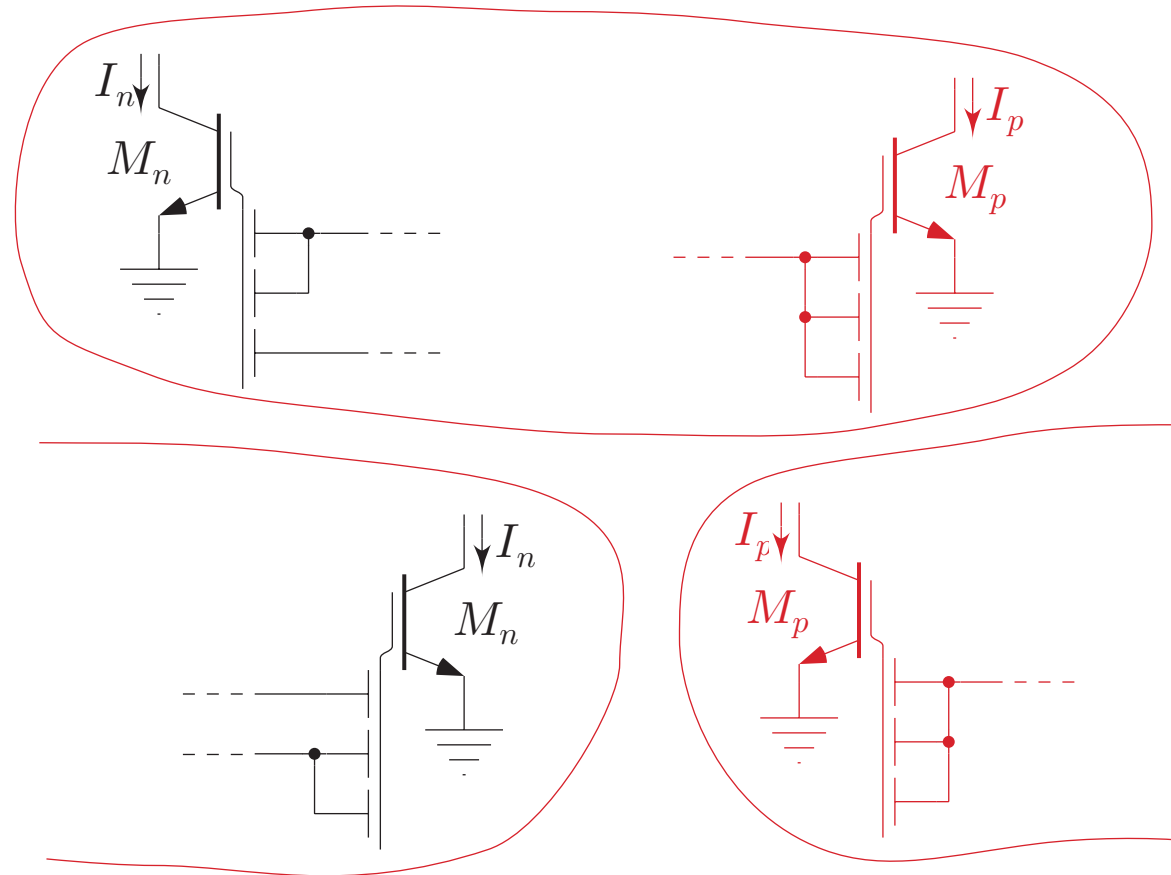
Static MITE Network Synthesis: Consolidation



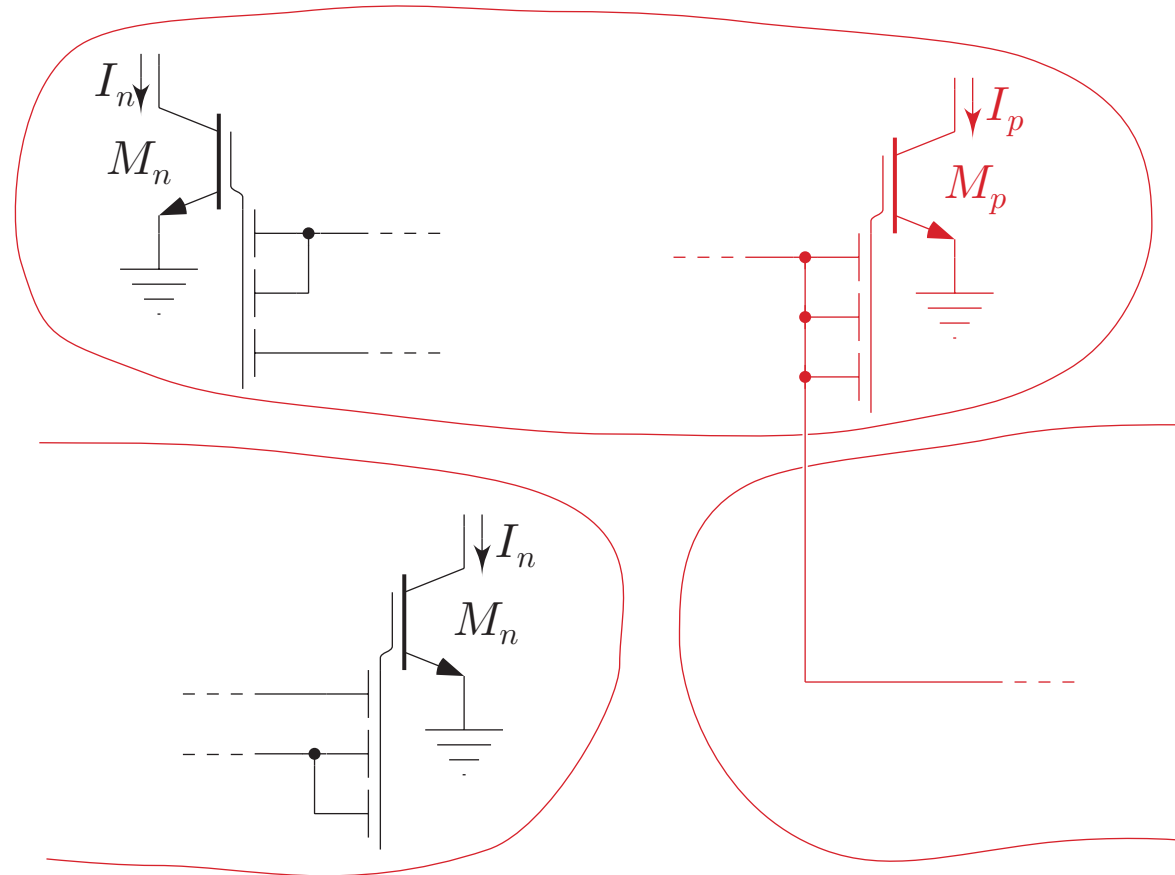
Static MITE Network Synthesis: Consolidation



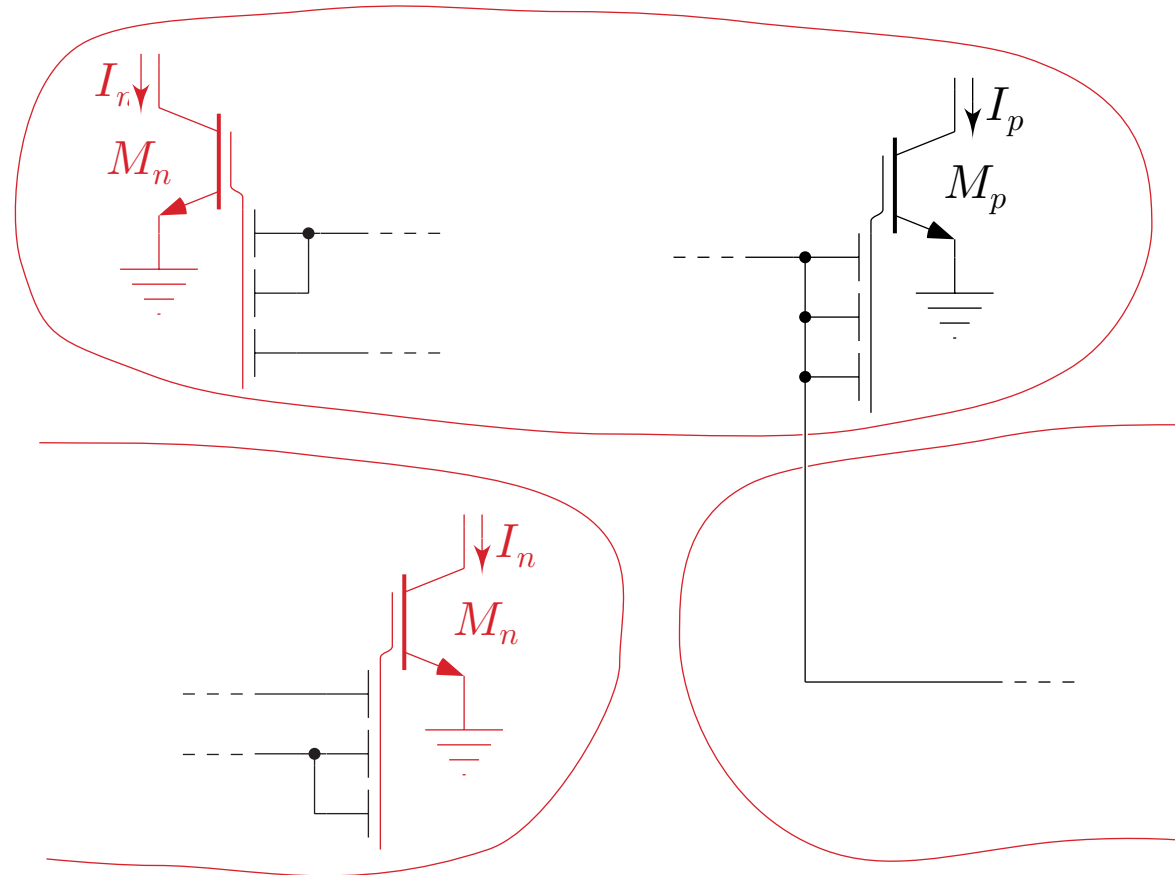
Static MITE Network Synthesis: Consolidation



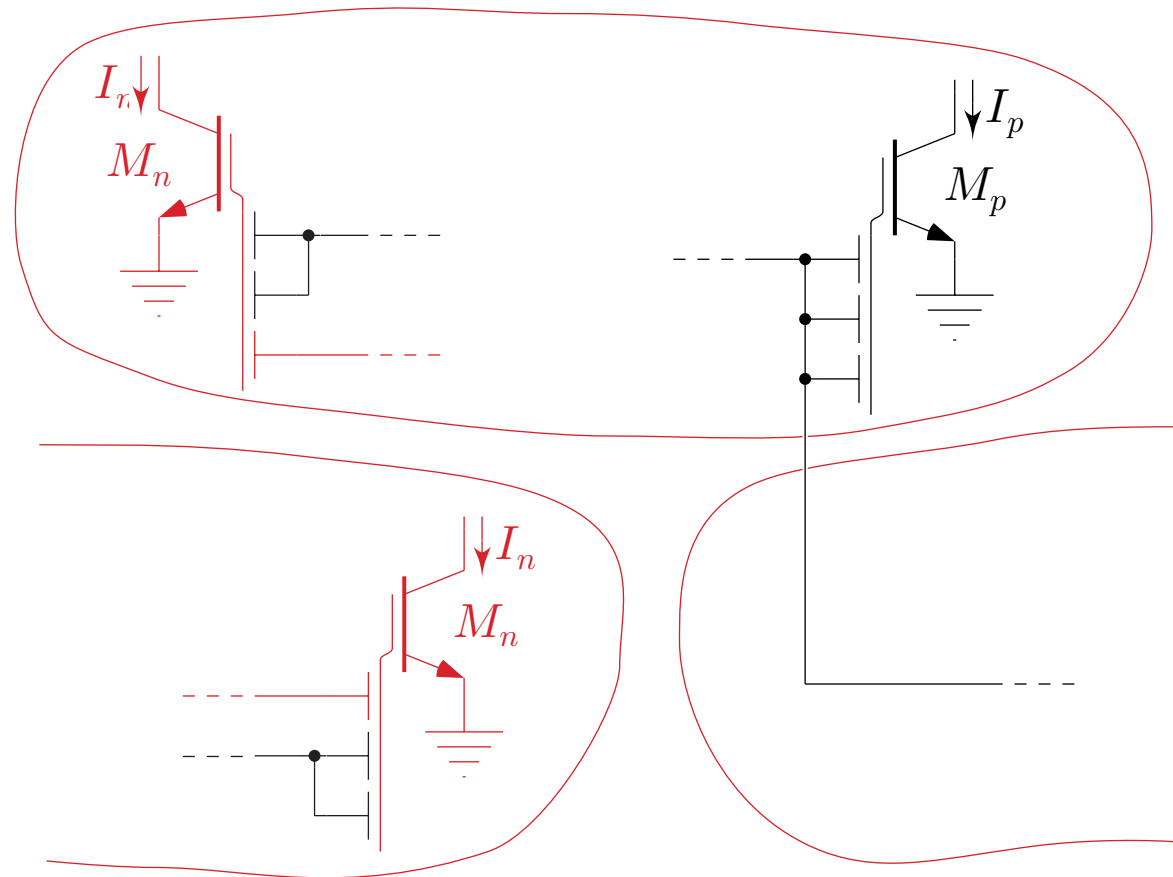
Static MITE Network Synthesis: Consolidation



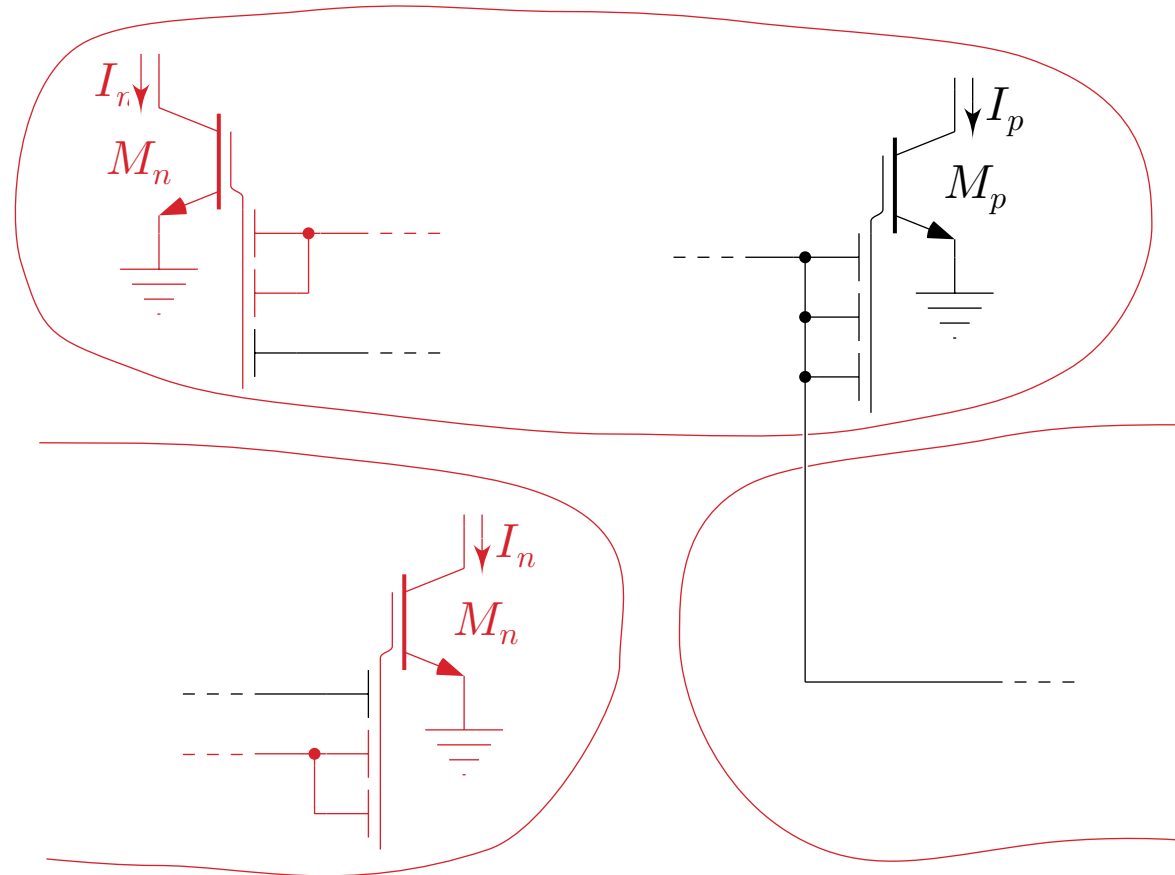
Static MITE Network Synthesis: Consolidation



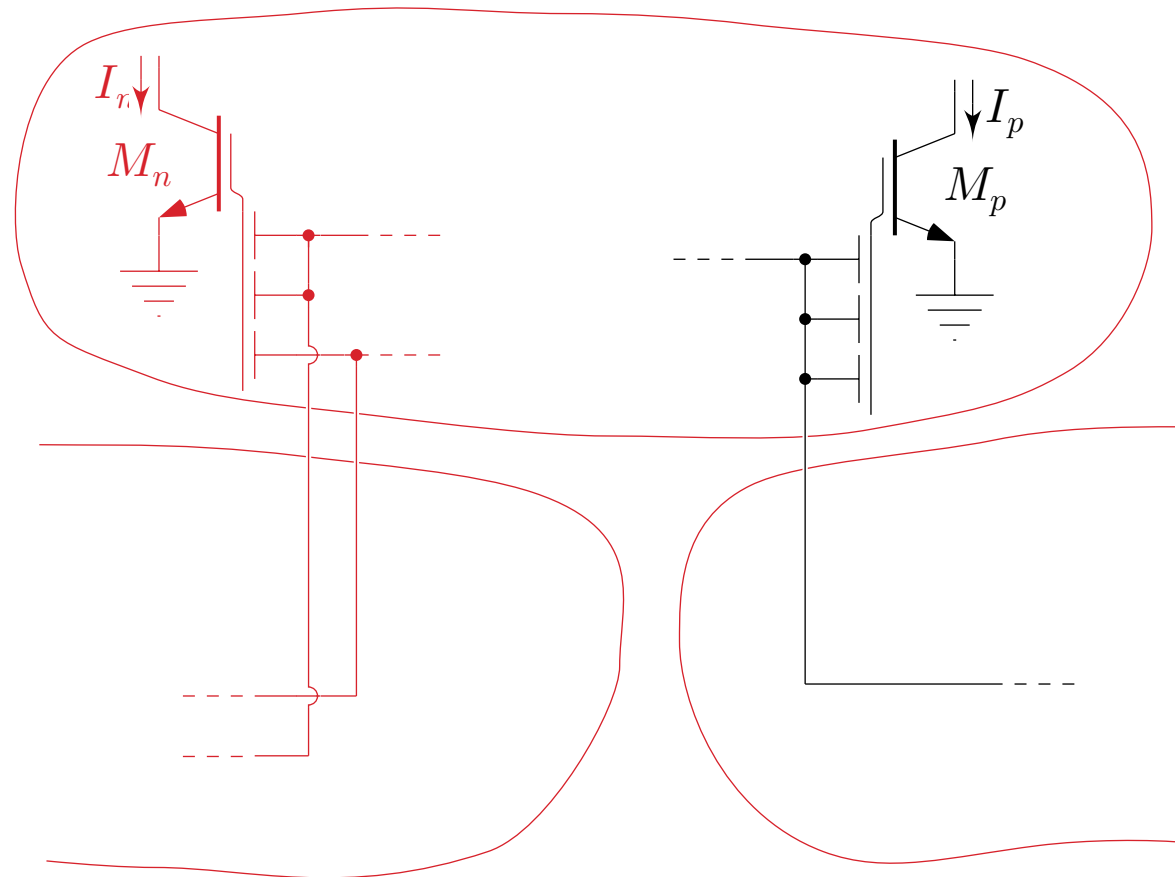Static MITE Network Synthesis: Consolidation



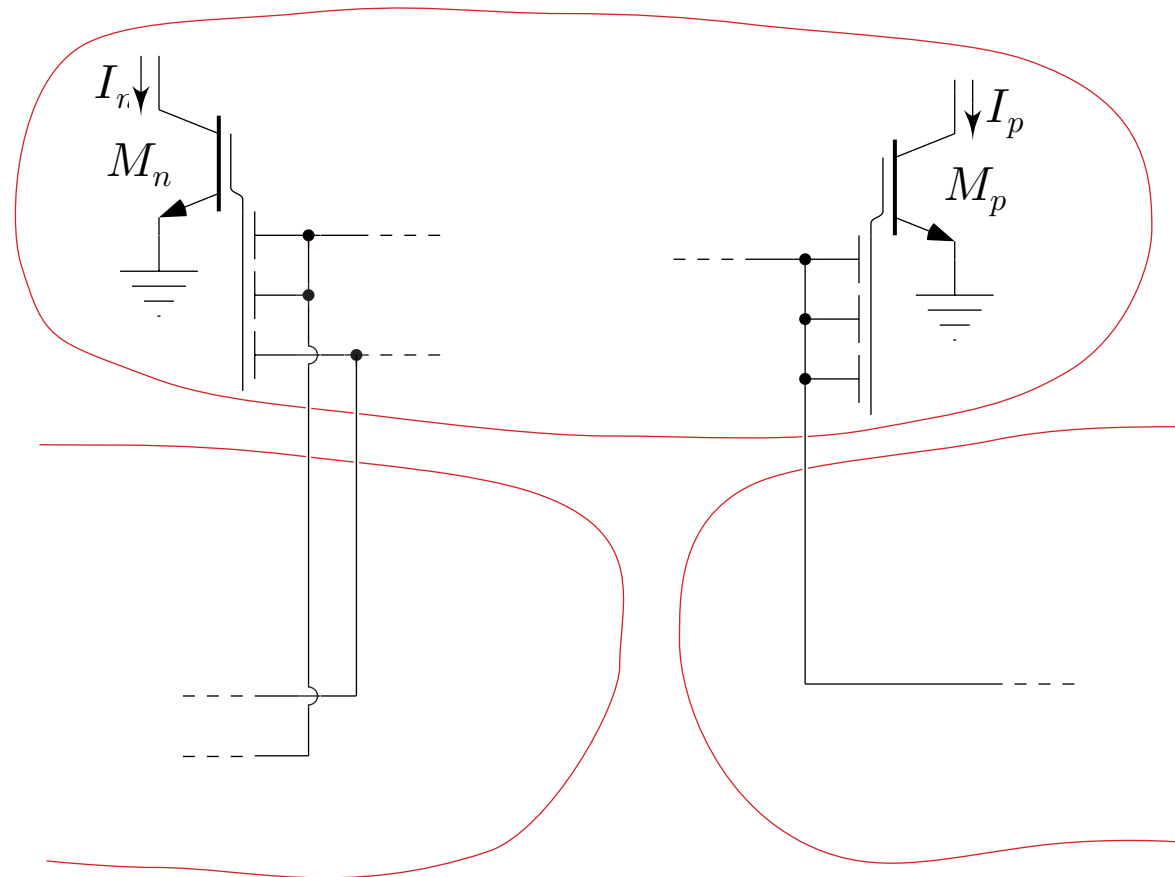Static MITE Network Synthesis: Consolidation



Static MITE Network Synthesis: **Vector Magnitude**

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

Static MITE Network Synthesis: **Vector Magnitude**

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

Static MITE Network Synthesis: **Vector Magnitude**

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

We substitute these into the original equation and rearrange to obtain

$$\frac{I_r}{I_1} = \sqrt{\left(\frac{I_x}{I_1}\right)^2 + \left(\frac{I_y}{I_1}\right)^2}$$

Static MITE Network Synthesis: **Vector Magnitude**

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

We substitute these into the original equation and rearrange to obtain

$$\frac{I_r}{I_1} = \sqrt{\left(\frac{I_x}{I_1}\right)^2 + \left(\frac{I_y}{I_1}\right)^2} \quad \Rightarrow \quad I_r^2 = I_x^2 + I_y^2$$

Static MITE Network Synthesis: **Vector Magnitude**

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

We substitute these into the original equation and rearrange to obtain

$$\frac{I_r}{I_1} = \sqrt{\left(\frac{I_x}{I_1}\right)^2 + \left(\frac{I_y}{I_1}\right)^2} \quad \Rightarrow \quad I_r^2 = I_x^2 + I_y^2 \quad \Rightarrow \quad I_r = \frac{I_x^2}{I_r} + \frac{I_y^2}{I_r}$$

Static MITE Network Synthesis: **Vector Magnitude**

Synthesize a two-dimensional vector-magnitude circuit implementing

$$r = \sqrt{x^2 + y^2}, \quad \text{where } x > 0 \quad \text{and} \quad y > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad r \equiv \frac{I_r}{I_1}.$$

We substitute these into the original equation and rearrange to obtain

$$\frac{I_r}{I_1} = \sqrt{\left(\frac{I_x}{I_1}\right)^2 + \left(\frac{I_y}{I_1}\right)^2} \quad \Rightarrow \quad I_r^2 = I_x^2 + I_y^2 \quad \Rightarrow \quad I_r = \underbrace{\frac{I_x}{I_r}}_{I_{r1}} + \underbrace{\frac{I_y}{I_r}}_{I_{r2}}$$

Static MITE Network Synthesis: **Vector Magnitude**


$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$

$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$

$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

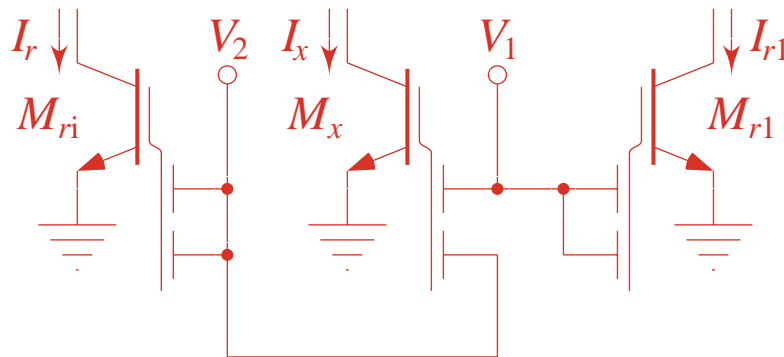


Static MITE Network Synthesis: **Vector Magnitude**

$$\text{TLP: } I_{r1}I_r = I_x^2$$

$$I_{r2}I_r = I_y^2$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

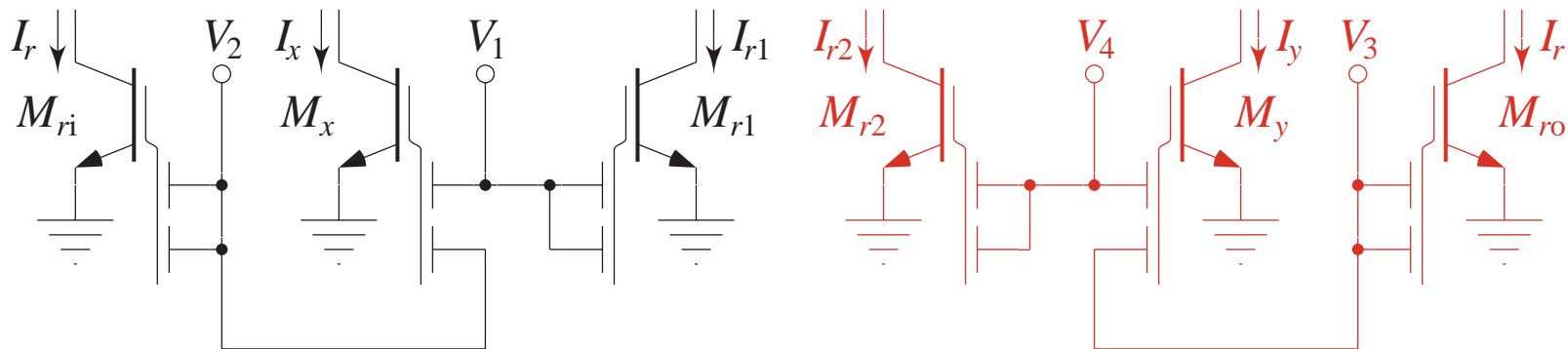

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

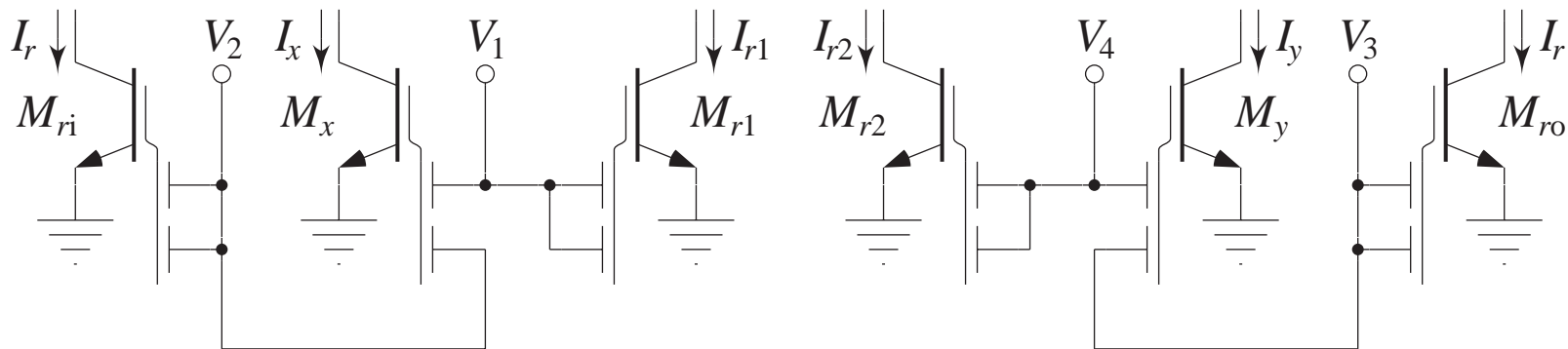

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

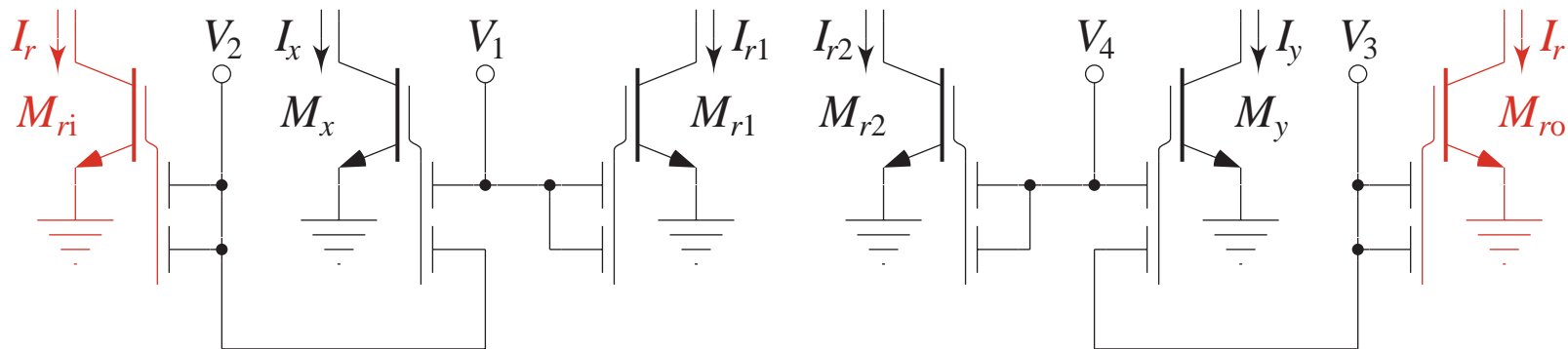

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

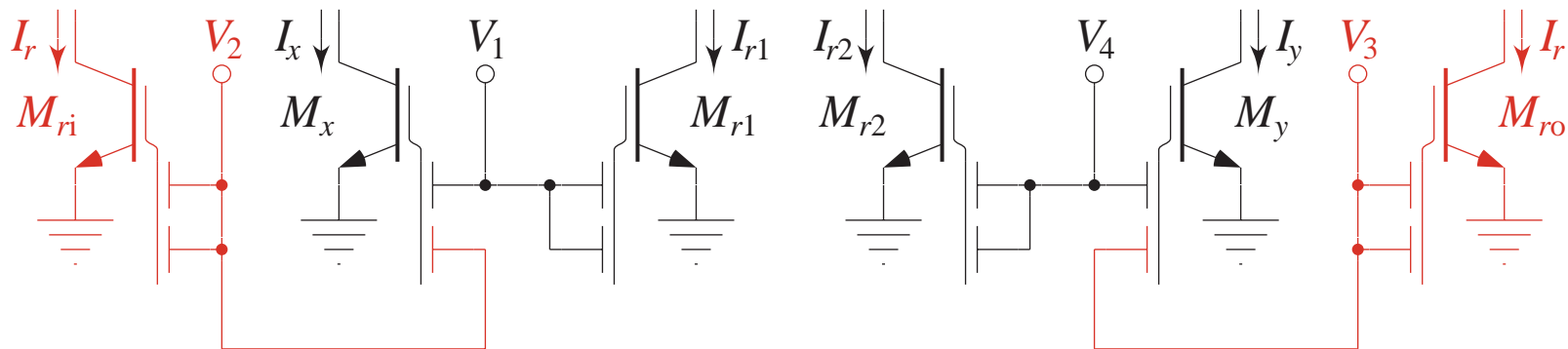

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

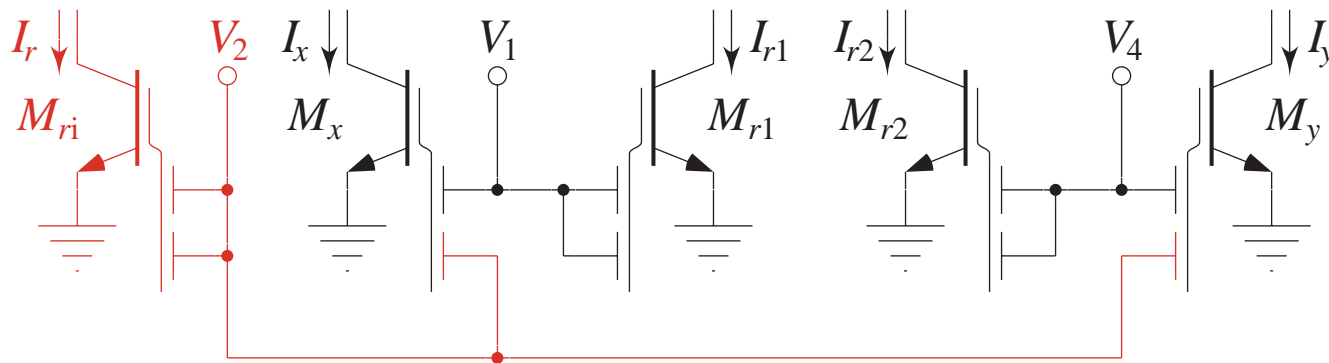

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

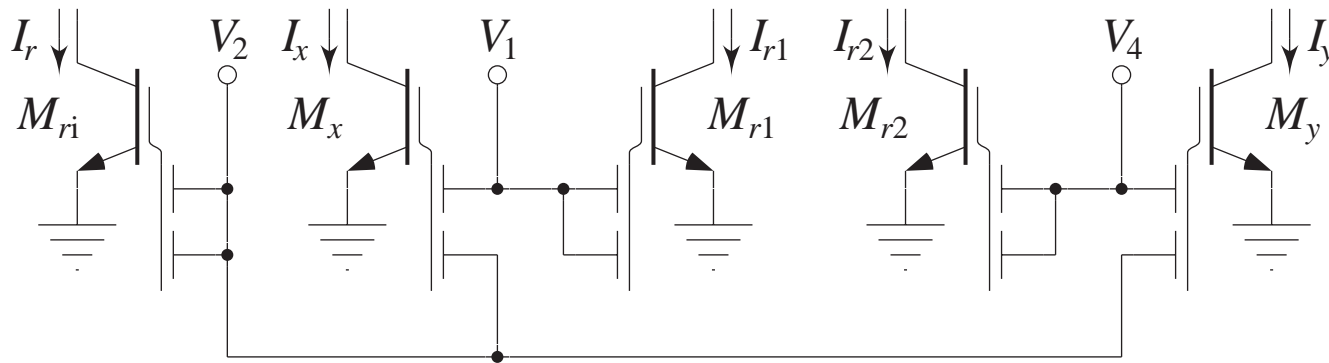

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

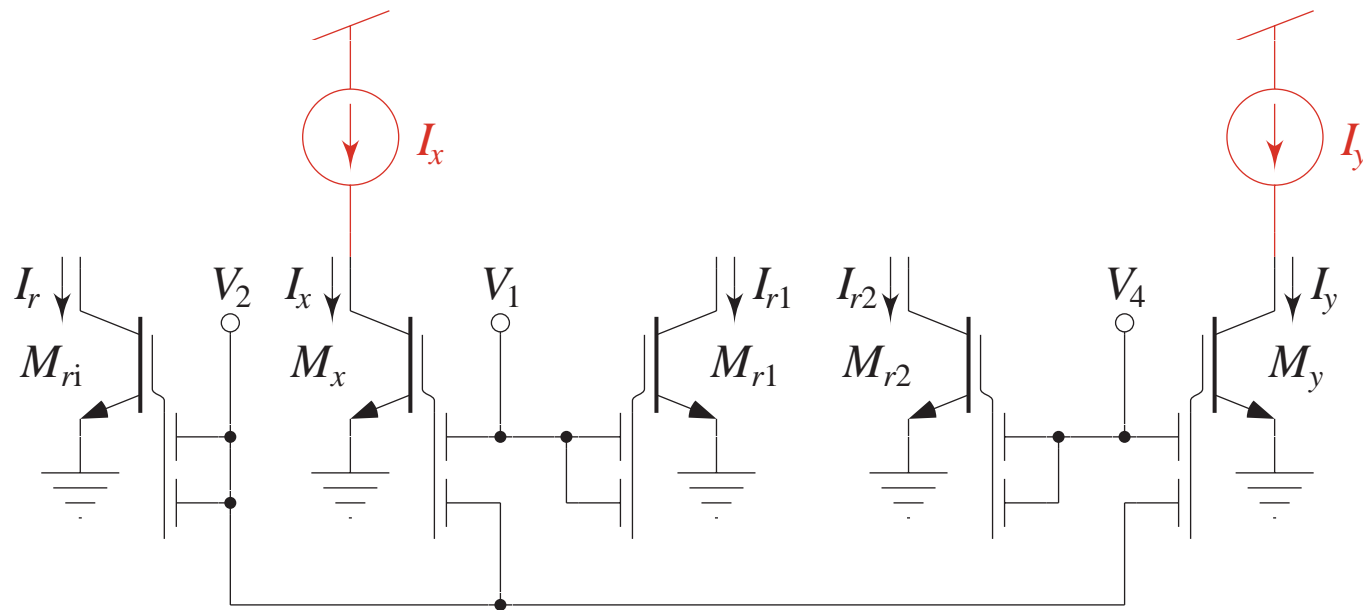

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

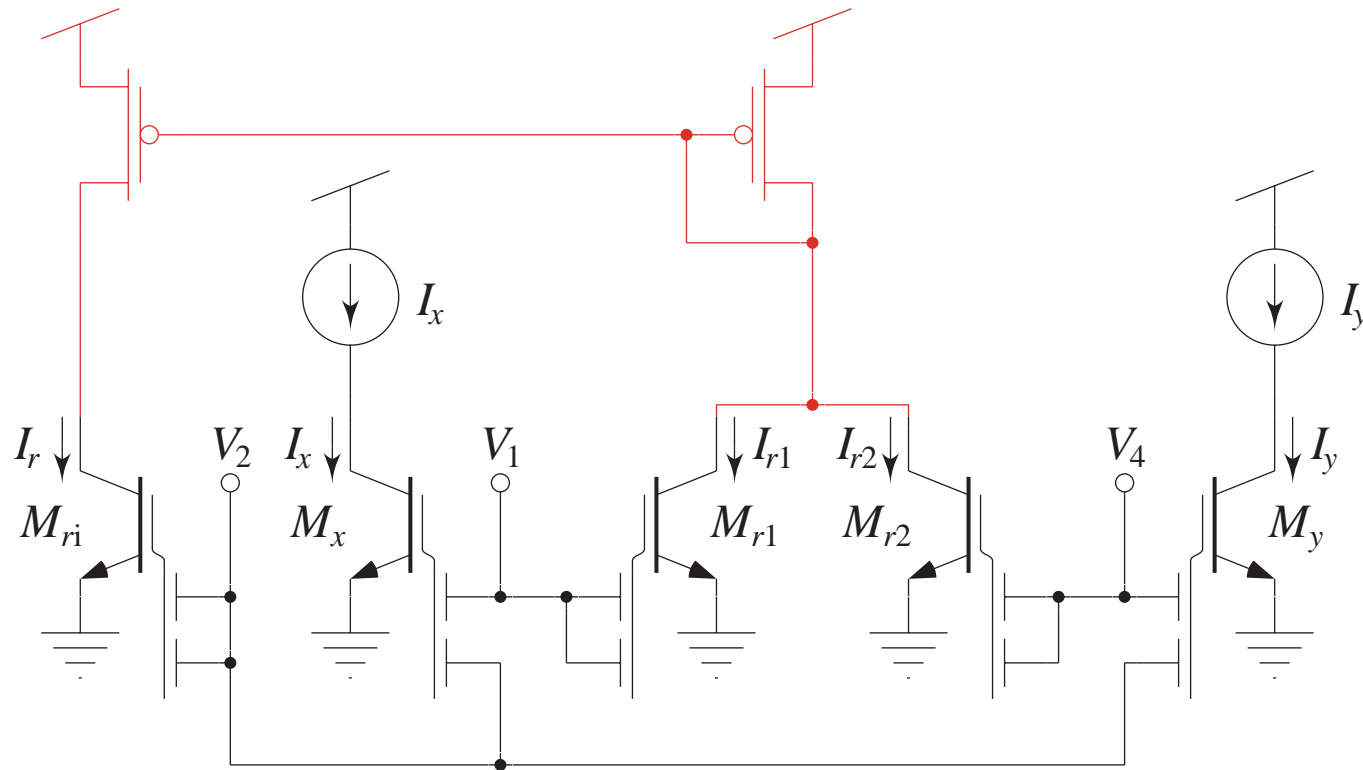

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

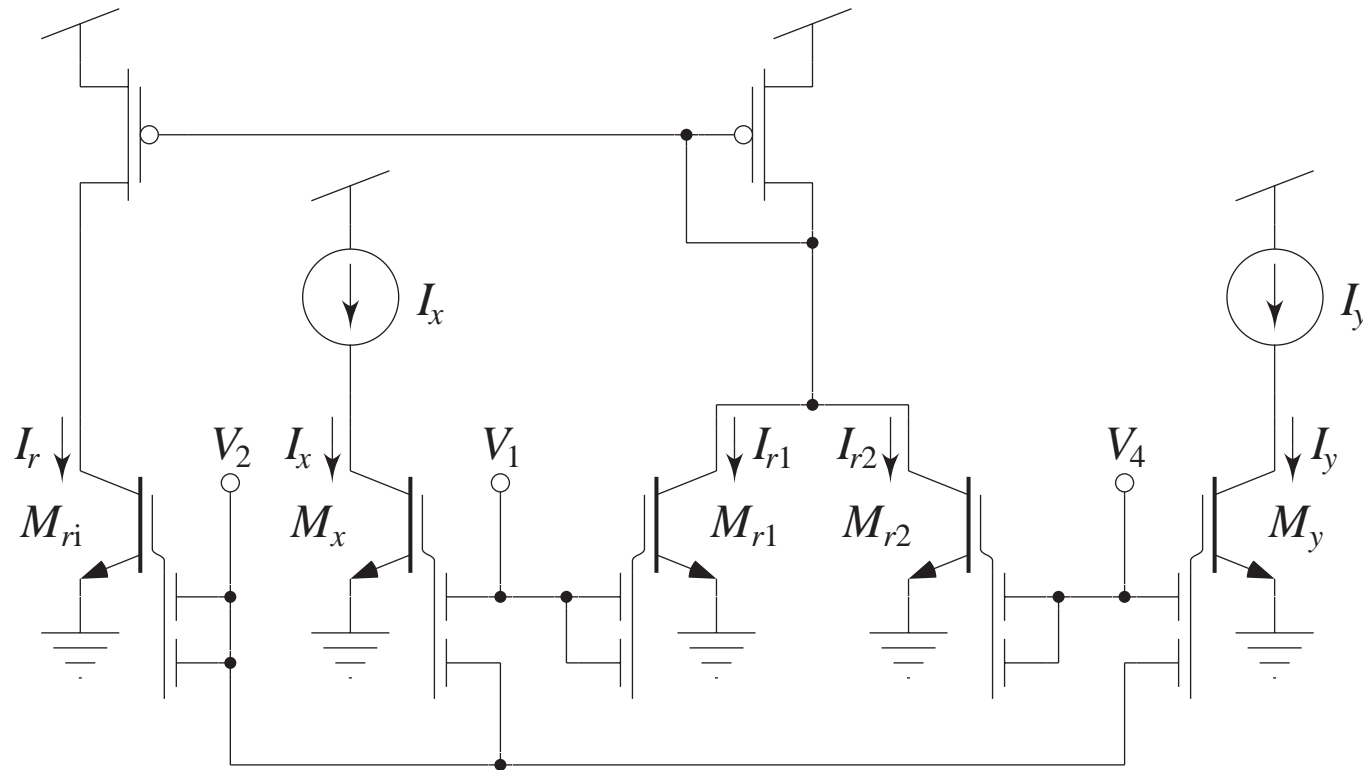

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

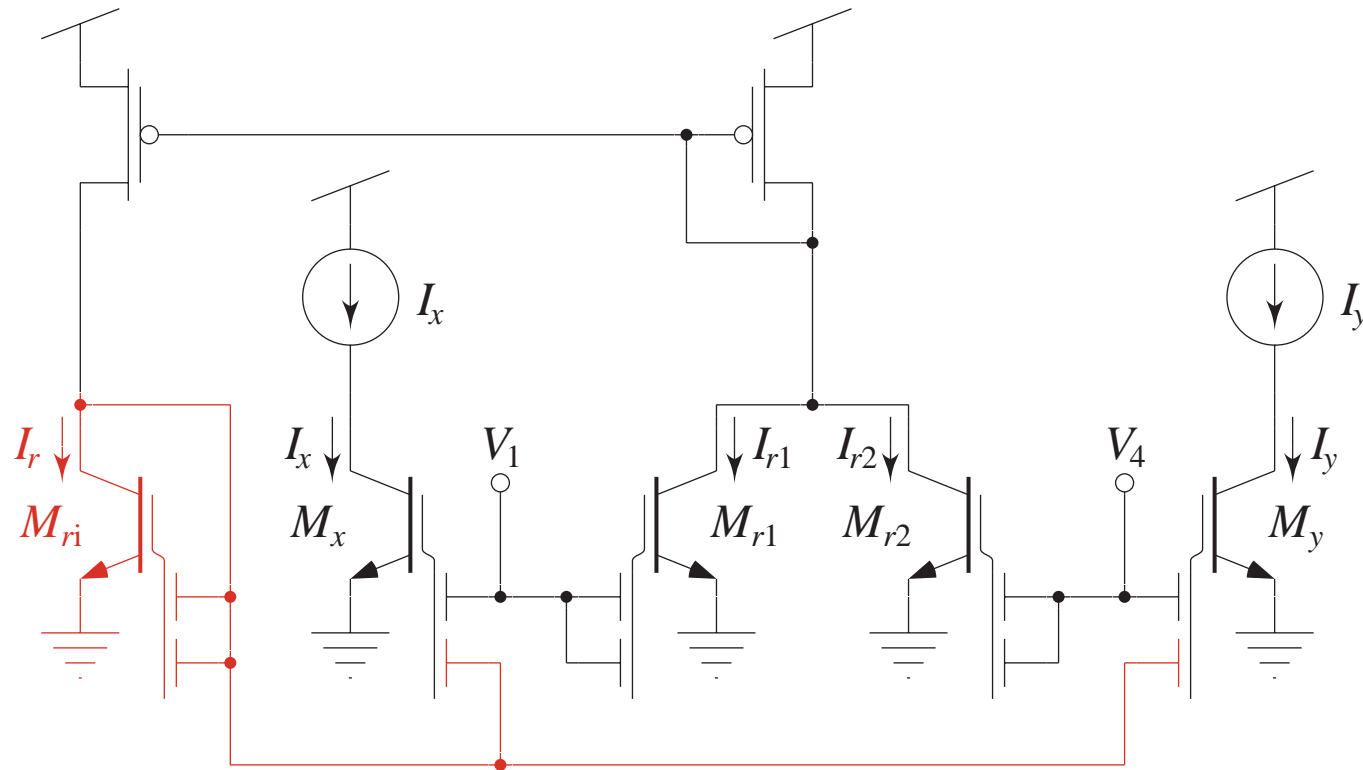

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

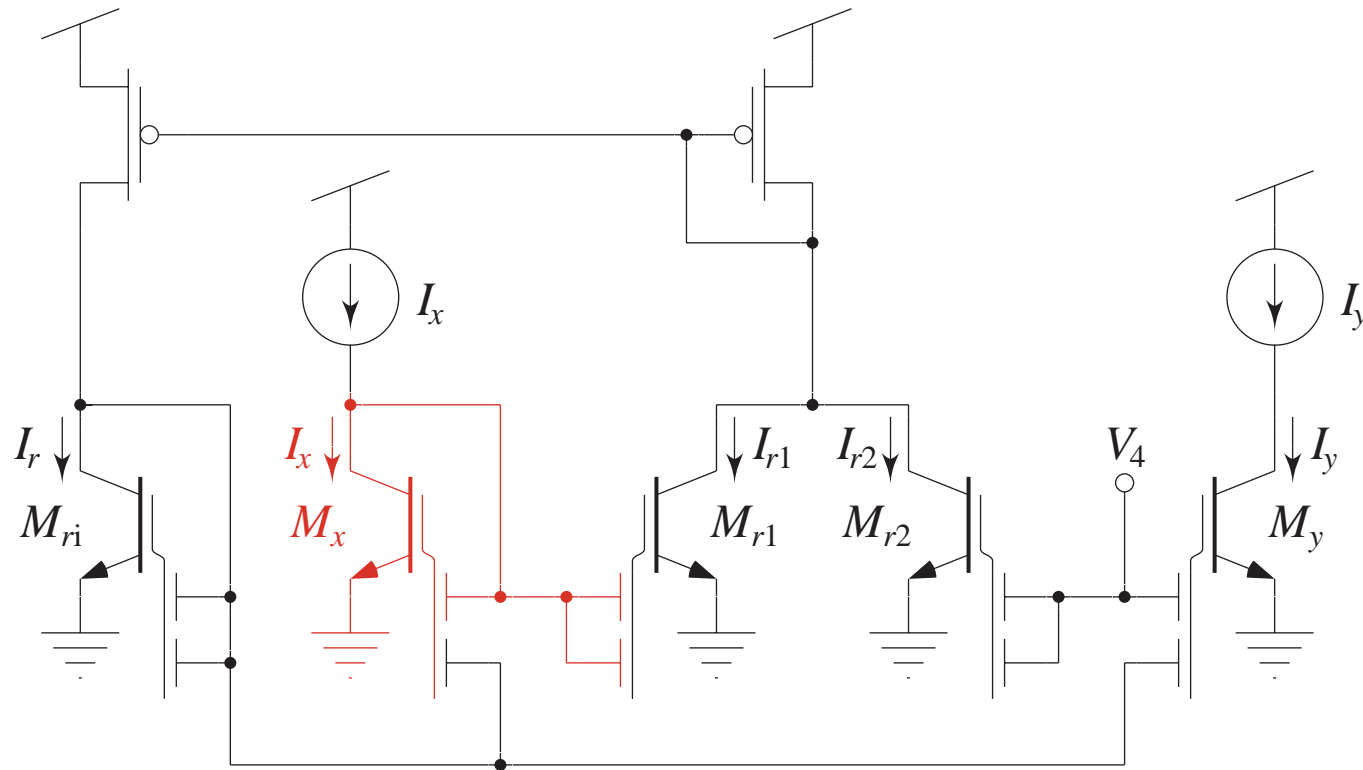

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

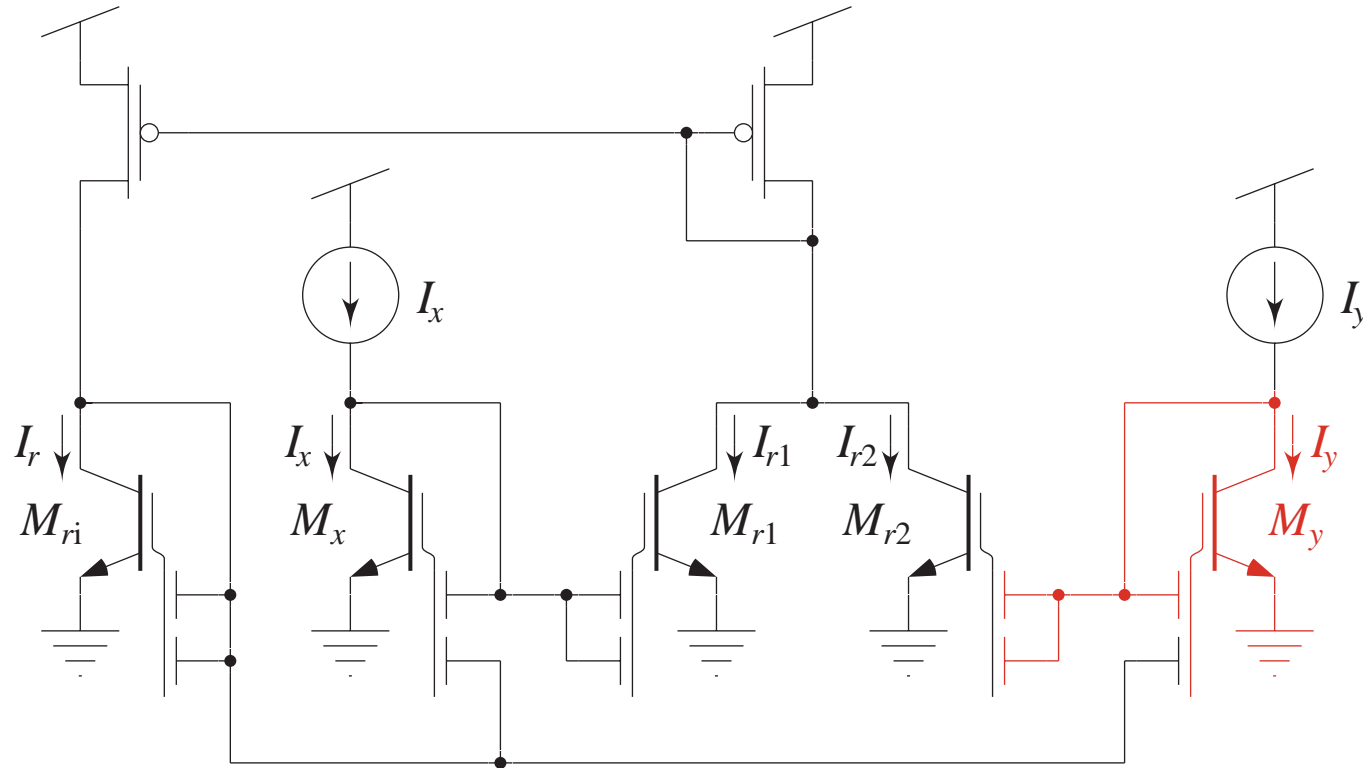

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

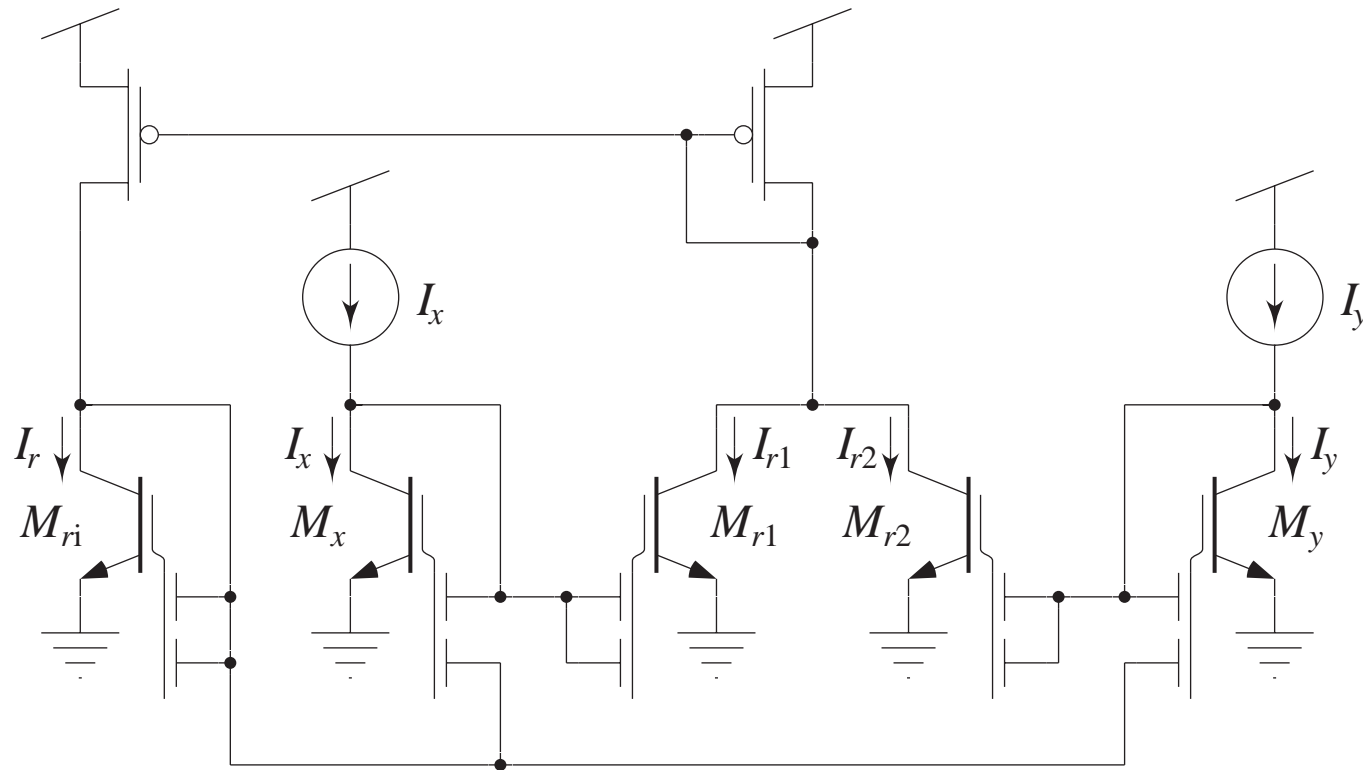

Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$


$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

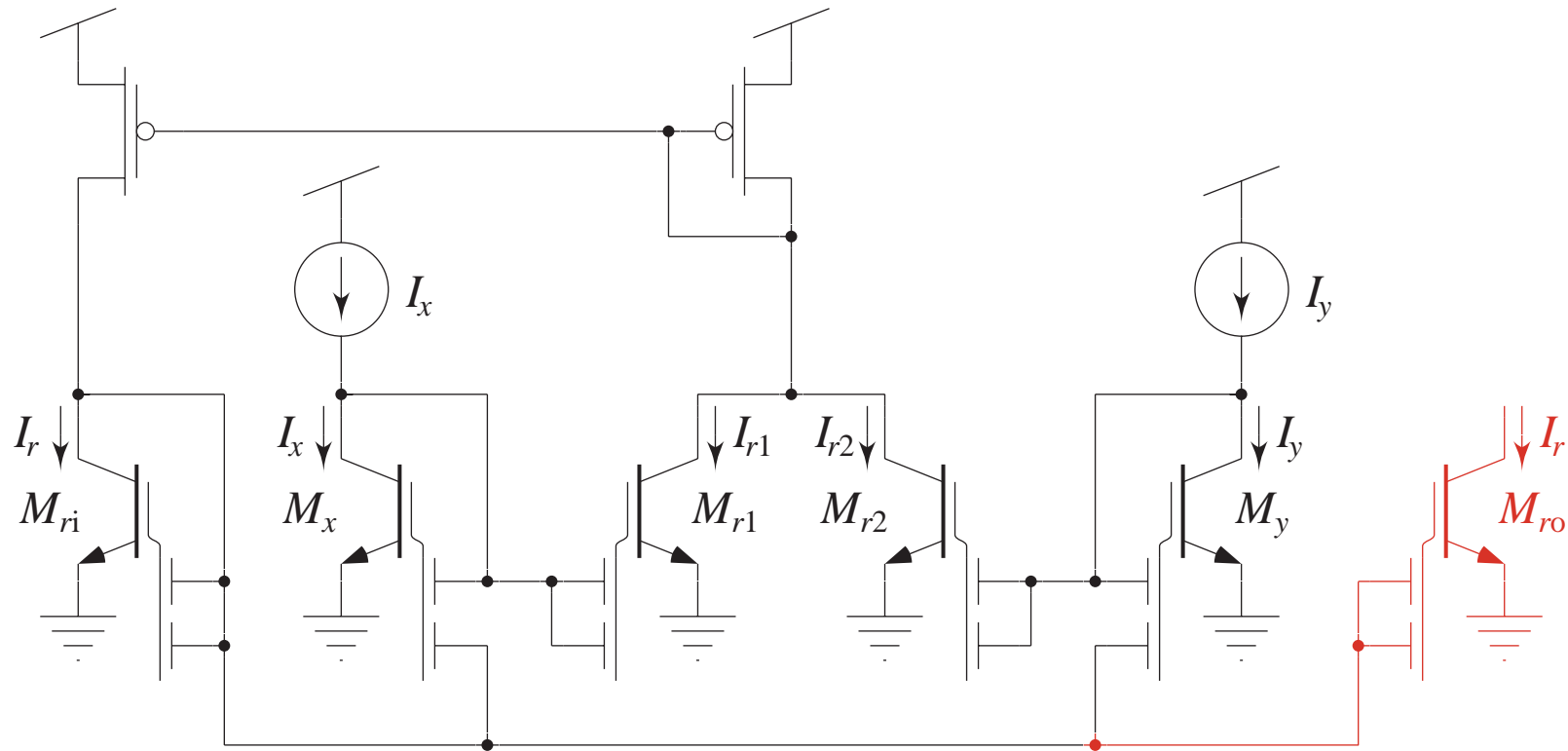


Static MITE Network Synthesis: **Vector Magnitude**

$$\begin{aligned} \text{TLP: } I_{r1}I_r &= I_x^2 \\ I_{r2}I_r &= I_y^2 \end{aligned}$$

$$\text{KCL: } I_r = I_{r1} + I_{r2}$$

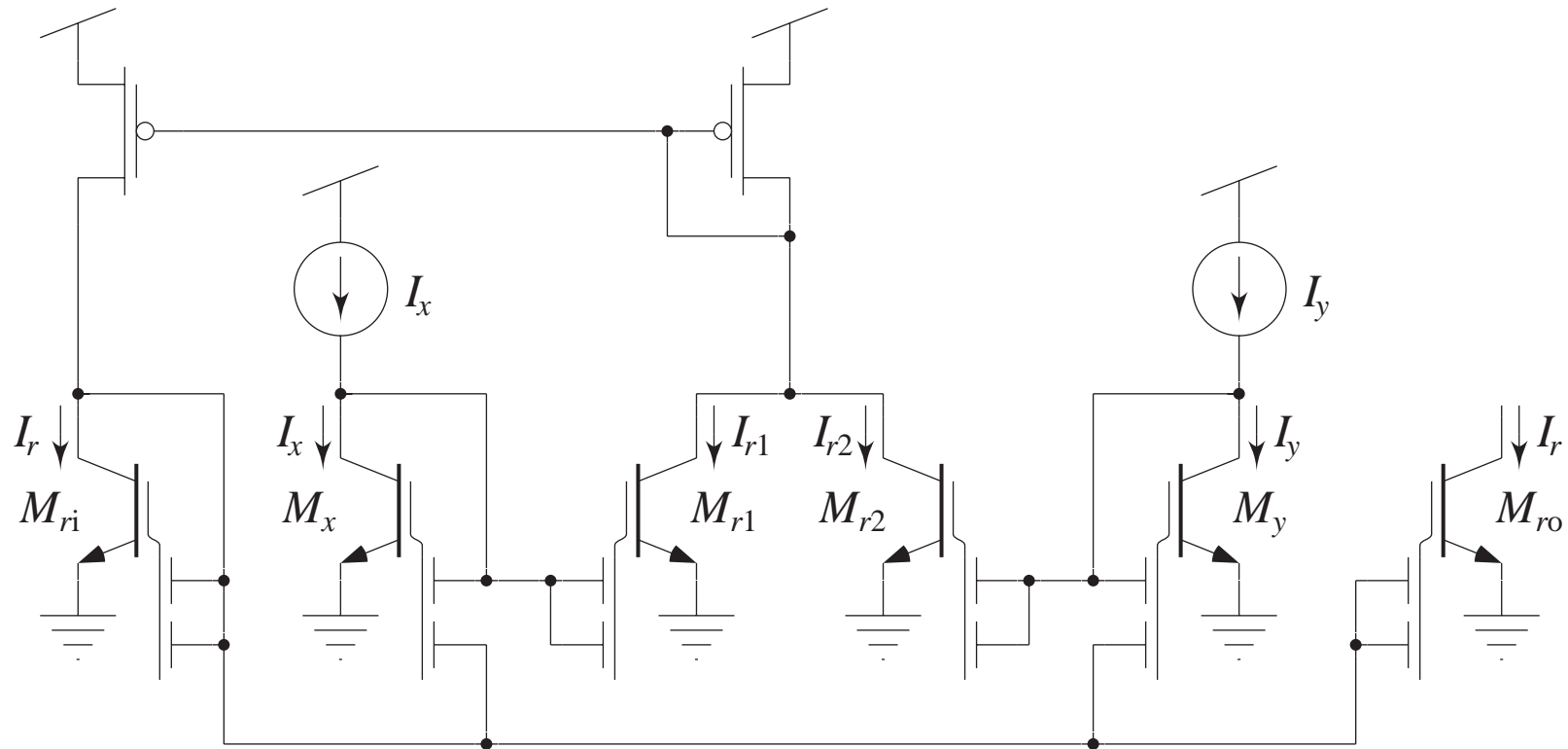

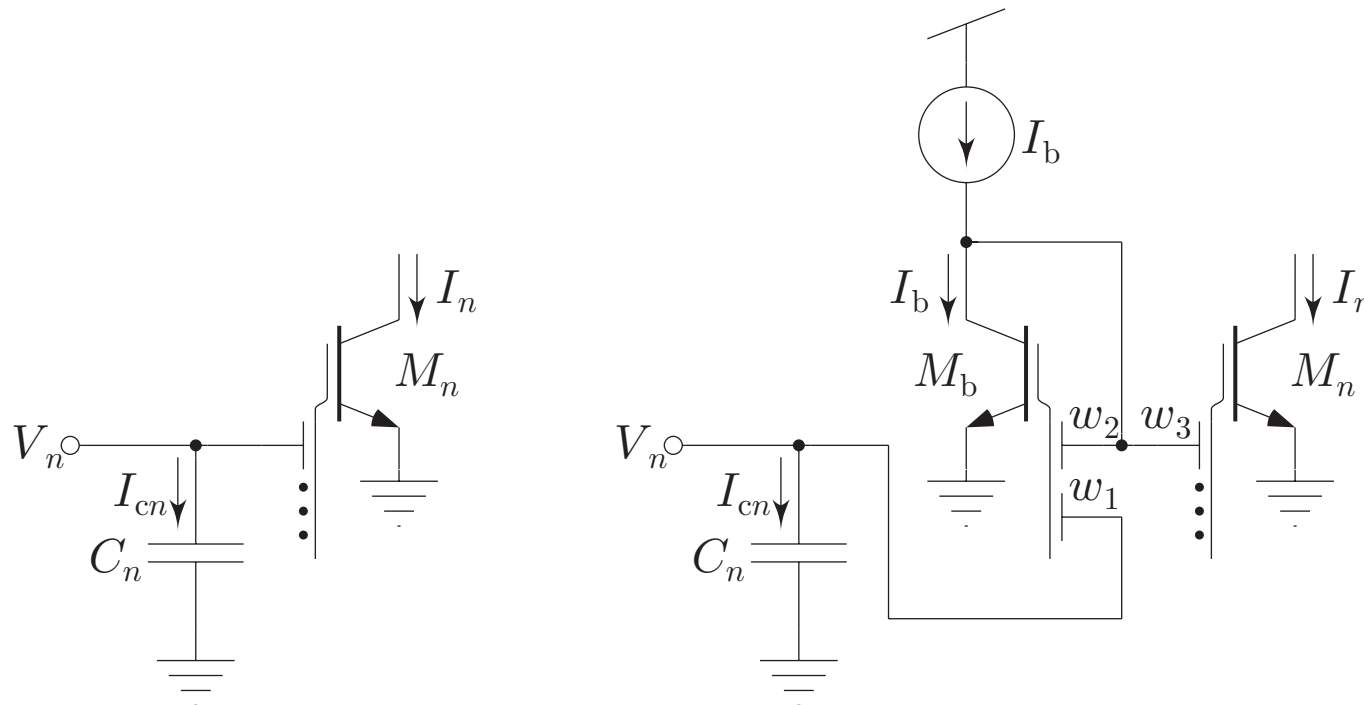Dynamic MITE Network Synthesis: Output Structures



$$I_n \propto e^{wV_n/U_T}$$

$$\frac{\partial I_n}{\partial V_n} = \frac{w}{U_T} I_n$$

$$I_n \propto e^{-wV_n/U_T}$$

$$\frac{\partial I_n}{\partial V_n} = -\frac{w}{U_T} I_n$$

Dynamic MITE Network Synthesis: **First-Order LPF**

Synthesize a first-order low-pass filter described by

$$\tau \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

Dynamic MITE Network Synthesis: **First-Order LPF**

Synthesize a first-order low-pass filter described by

$$\tau \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad y \equiv \frac{I_y}{I_1}.$$

Dynamic MITE Network Synthesis: **First-Order LPF**

Synthesize a first-order low-pass filter described by

$$\tau \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad y \equiv \frac{I_y}{I_1}.$$

Substituting these into the ODE, we obtain

$$\tau \frac{d}{dt} \left(\frac{I_y}{I_1} \right) + \frac{I_y}{I_1} = \frac{I_x}{I_1}$$

Dynamic MITE Network Synthesis: **First-Order LPF**

Synthesize a first-order low-pass filter described by

$$\tau \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1} \quad \text{and} \quad y \equiv \frac{I_y}{I_1}.$$

Substituting these into the ODE, we obtain

$$\tau \frac{d}{dt} \left(\frac{I_y}{I_1} \right) + \frac{I_y}{I_1} = \frac{I_x}{I_1} \quad \Rightarrow \quad \tau \frac{dI_y}{dt} + I_y = I_x.$$

Dynamic MITE Network Synthesis: **First-Order LPF**

To implement the time derivative, we introduce a log-compressed voltage state variable, V_y . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x$$

Dynamic MITE Network Synthesis: **First-Order LPF**

To implement the time derivative, we introduce a log-compressed voltage state variable, V_y . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Rightarrow \quad \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

Dynamic MITE Network Synthesis: **First-Order LPF**

To implement the time derivative, we introduce a log-compressed voltage state variable, V_y . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Rightarrow \quad \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

$$\Rightarrow -\frac{w\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y}$$

Dynamic MITE Network Synthesis: **First-Order LPF**

To implement the time derivative, we introduce a log-compressed voltage state variable, V_y . Using the chain rule, we can express the preceding equation as

$$\tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x \quad \Rightarrow \quad \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x$$

$$\Rightarrow -\frac{w\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} \quad \Rightarrow \quad -\frac{w\tau}{CU_T} \cdot C \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y}$$

Dynamic MITE Network Synthesis: **First-Order LPF**

To implement the time derivative, we introduce a log-compressed voltage state variable, V_y . Using the chain rule, we can express the preceding equation as

$$\begin{aligned} \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x &\implies \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x \\ \implies -\frac{w\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} &\implies -\underbrace{\frac{w\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C}_{I_c} \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} \end{aligned}$$

Dynamic MITE Network Synthesis: **First-Order LPF**

To implement the time derivative, we introduce a log-compressed voltage state variable, V_y . Using the chain rule, we can express the preceding equation as

$$\begin{aligned} \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x &\implies \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x \\ \implies -\frac{w\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} &\implies -\underbrace{\frac{w\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C \frac{dV_y}{dt}}_{I_c} + 1 = \frac{I_x}{I_y} \\ \implies -\frac{I_c}{I_\tau} + 1 = \frac{I_x}{I_y} \end{aligned}$$

Dynamic MITE Network Synthesis: **First-Order LPF**

To implement the time derivative, we introduce a log-compressed voltage state variable, V_y . Using the chain rule, we can express the preceding equation as

$$\begin{aligned} \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x &\implies \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x \\ \implies -\frac{w\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} &\implies -\underbrace{\frac{w\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C \frac{dV_y}{dt}}_{I_c} + 1 = \frac{I_x}{I_y} \\ \implies -\frac{I_c}{I_\tau} + 1 = \frac{I_x}{I_y} &\implies I_c - I_\tau = \frac{I_\tau I_x}{I_y}. \end{aligned}$$

Dynamic MITE Network Synthesis: **First-Order LPF**

To implement the time derivative, we introduce a log-compressed voltage state variable, V_y . Using the chain rule, we can express the preceding equation as


$$\begin{aligned} \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} + I_y = I_x &\implies \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} + I_y = I_x \\ \implies -\frac{w\tau}{U_T} \cdot \frac{dV_y}{dt} + 1 = \frac{I_x}{I_y} &\implies -\underbrace{\frac{w\tau}{CU_T}}_{1/I_\tau} \cdot \underbrace{C \frac{dV_y}{dt}}_{I_c} + 1 = \frac{I_x}{I_y} \\ \implies -\frac{I_c}{I_\tau} + 1 = \frac{I_x}{I_y} &\implies I_c - I_\tau = \underbrace{\frac{I_\tau I_x}{I_y}}_{I_p} \end{aligned}$$

Dynamic MITE Network Synthesis: **First-Order LPF**

$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$


Dynamic MITE Network Synthesis: **First-Order LPF**
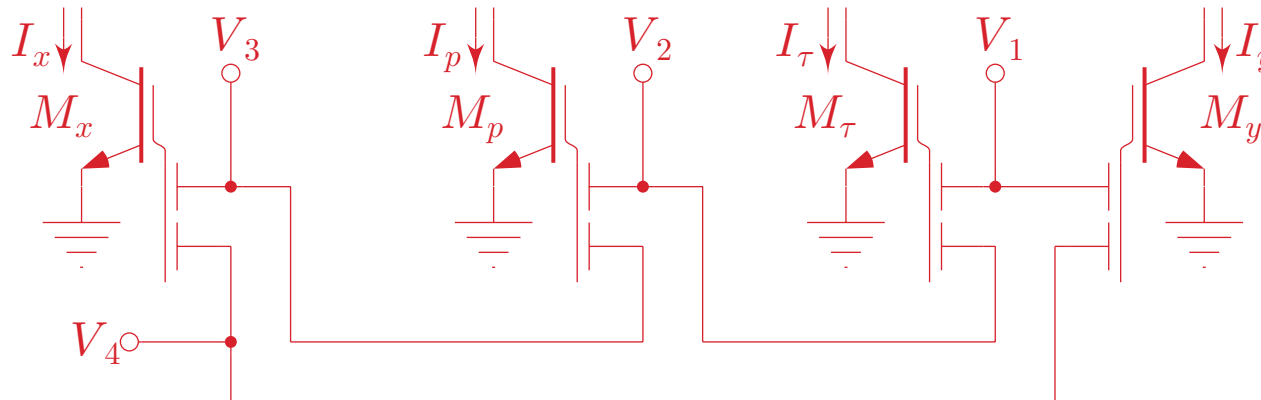
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
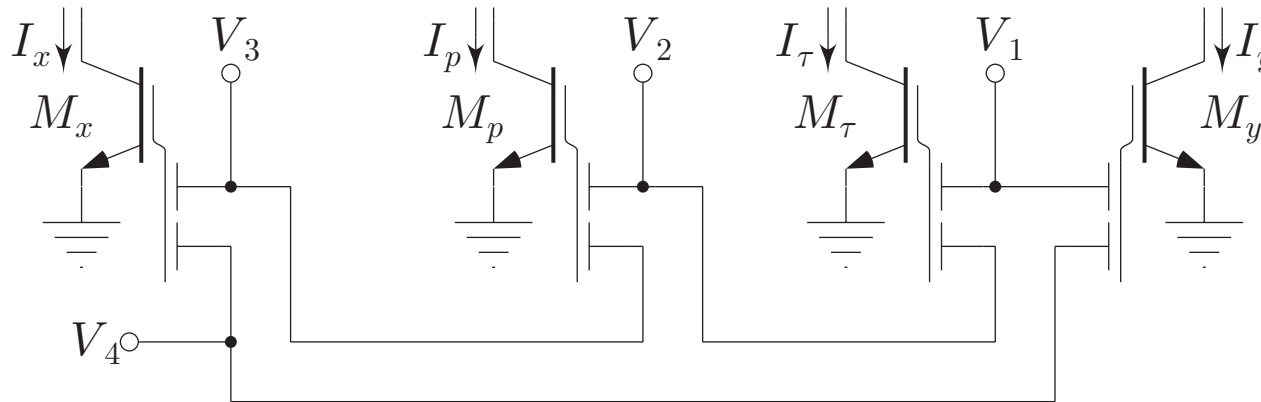
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
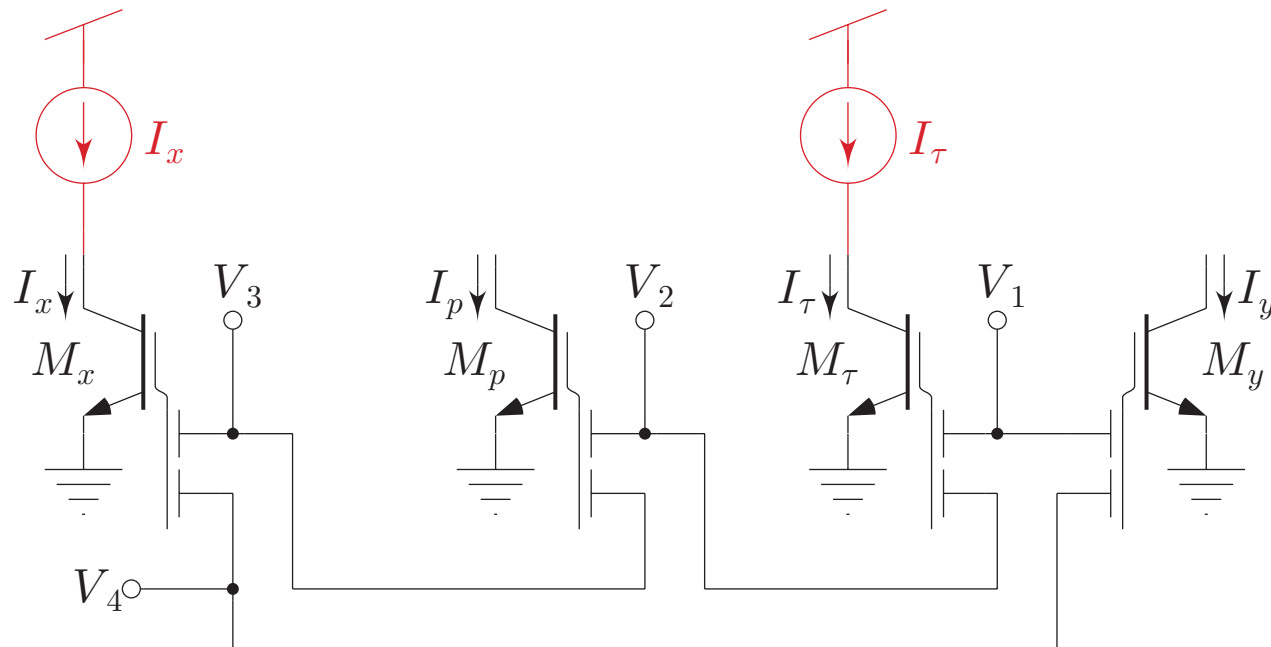
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
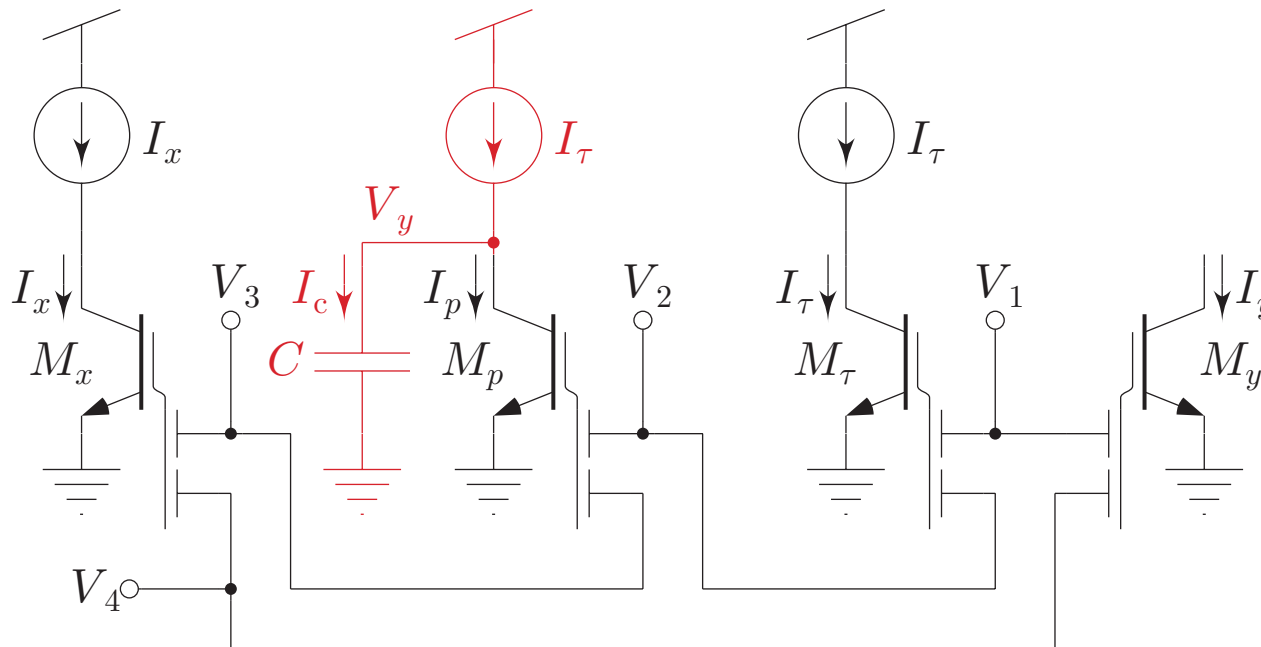
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
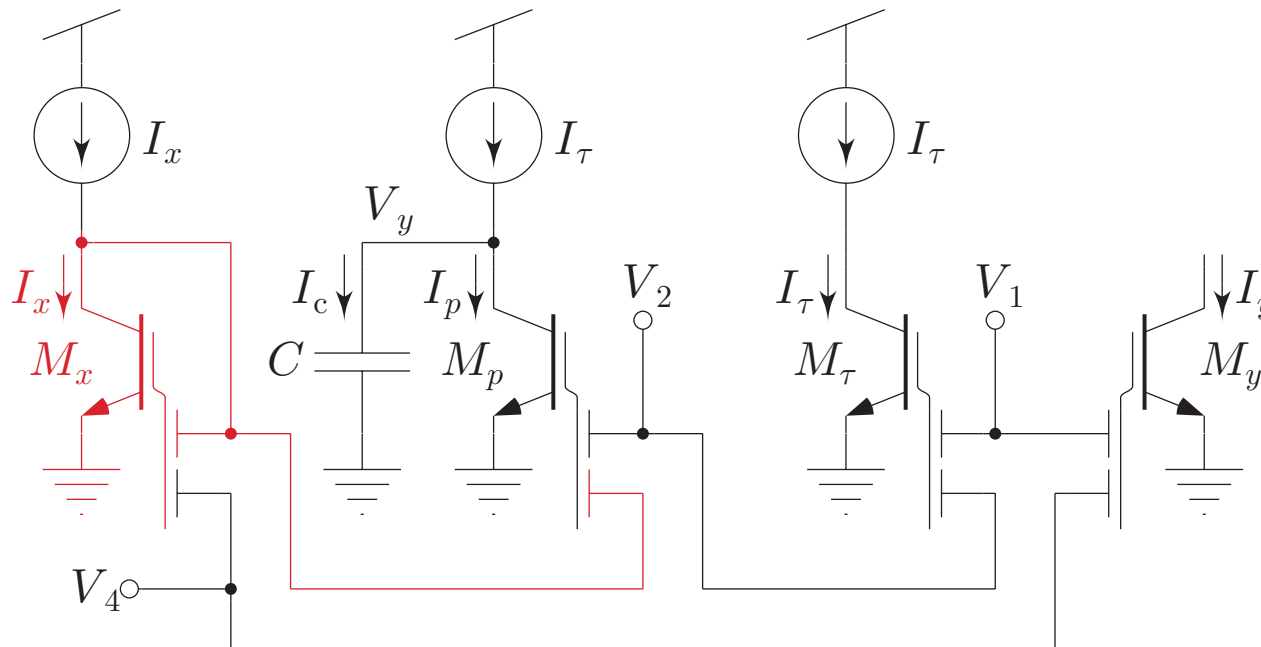
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
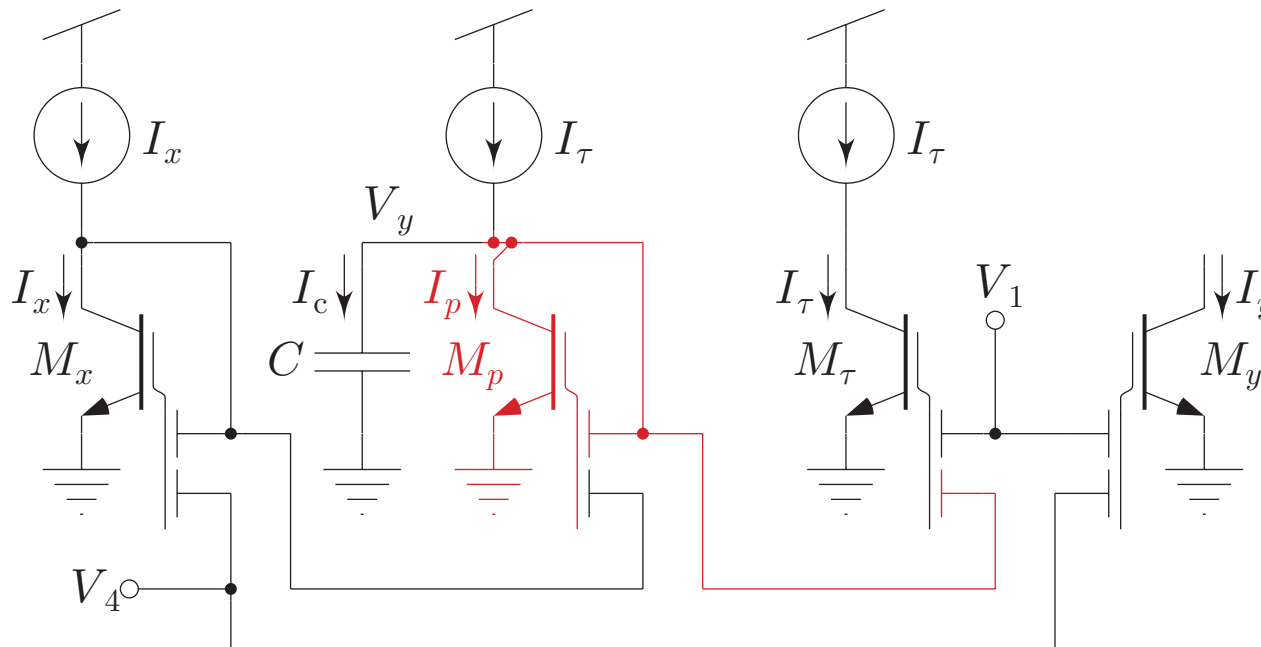
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
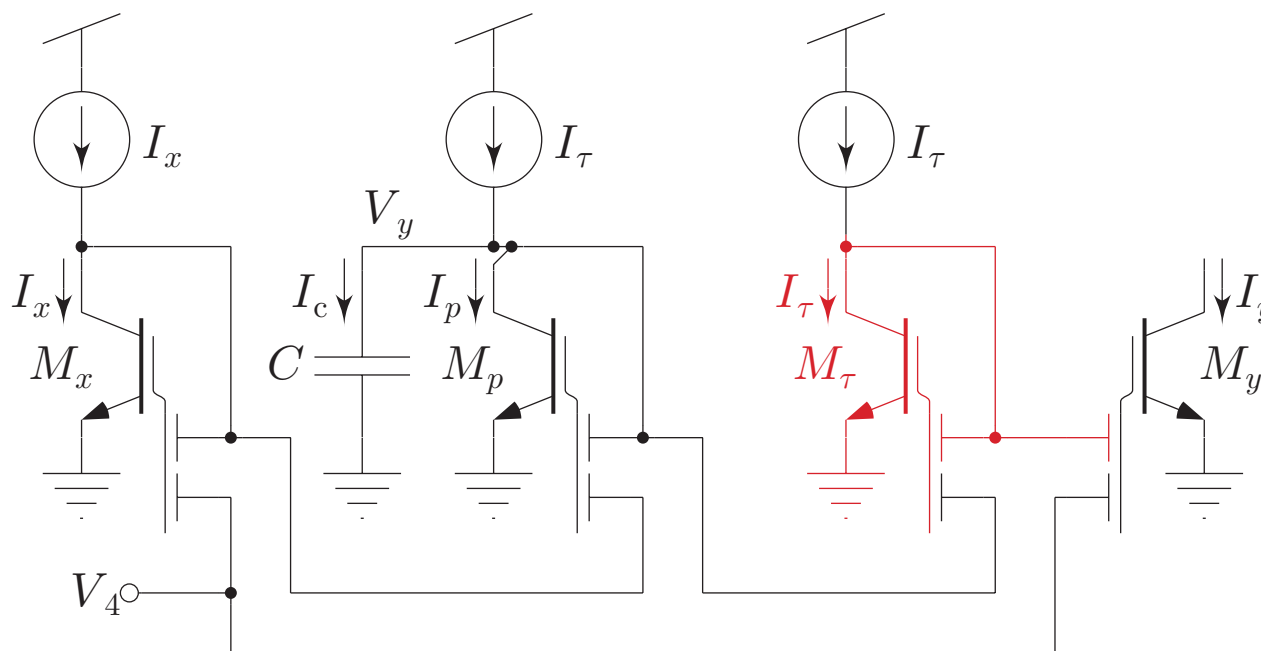
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
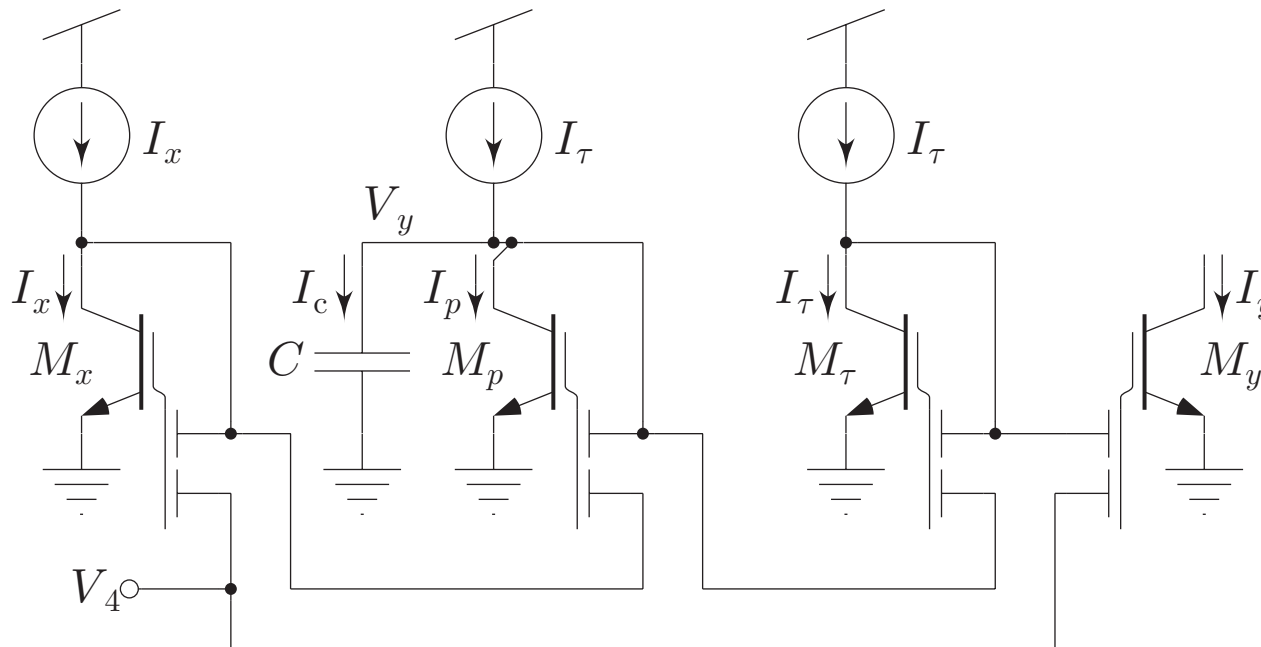
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
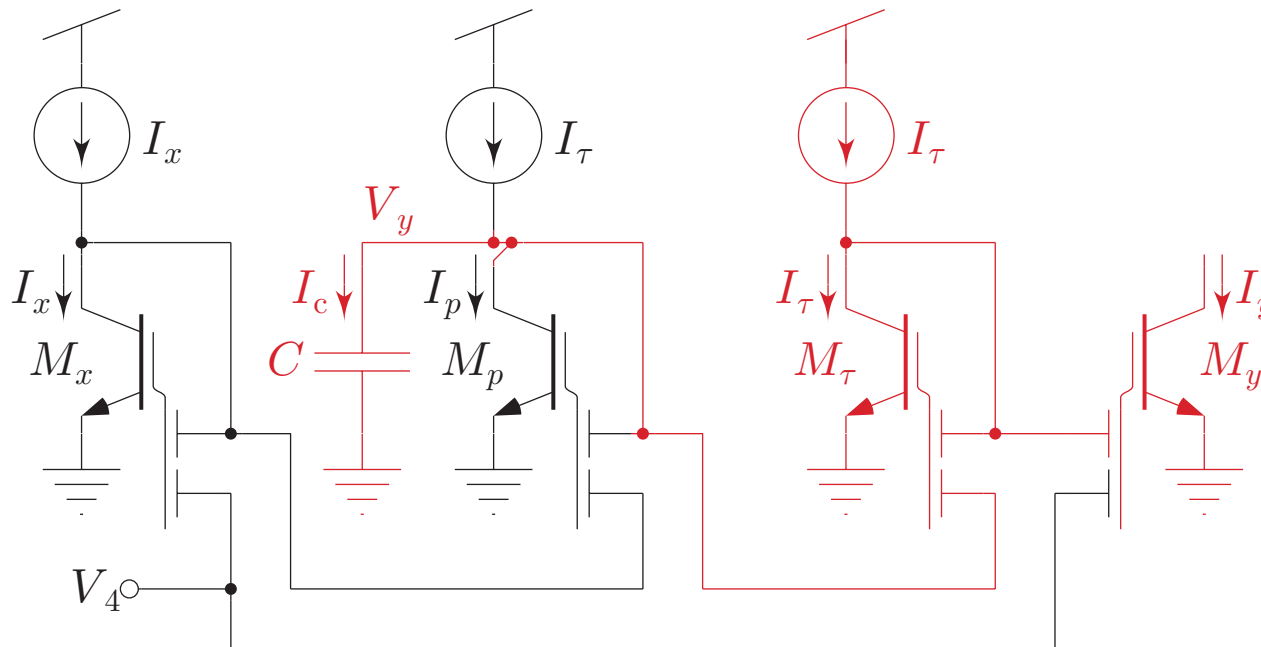
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$




Dynamic MITE Network Synthesis: **First-Order LPF**
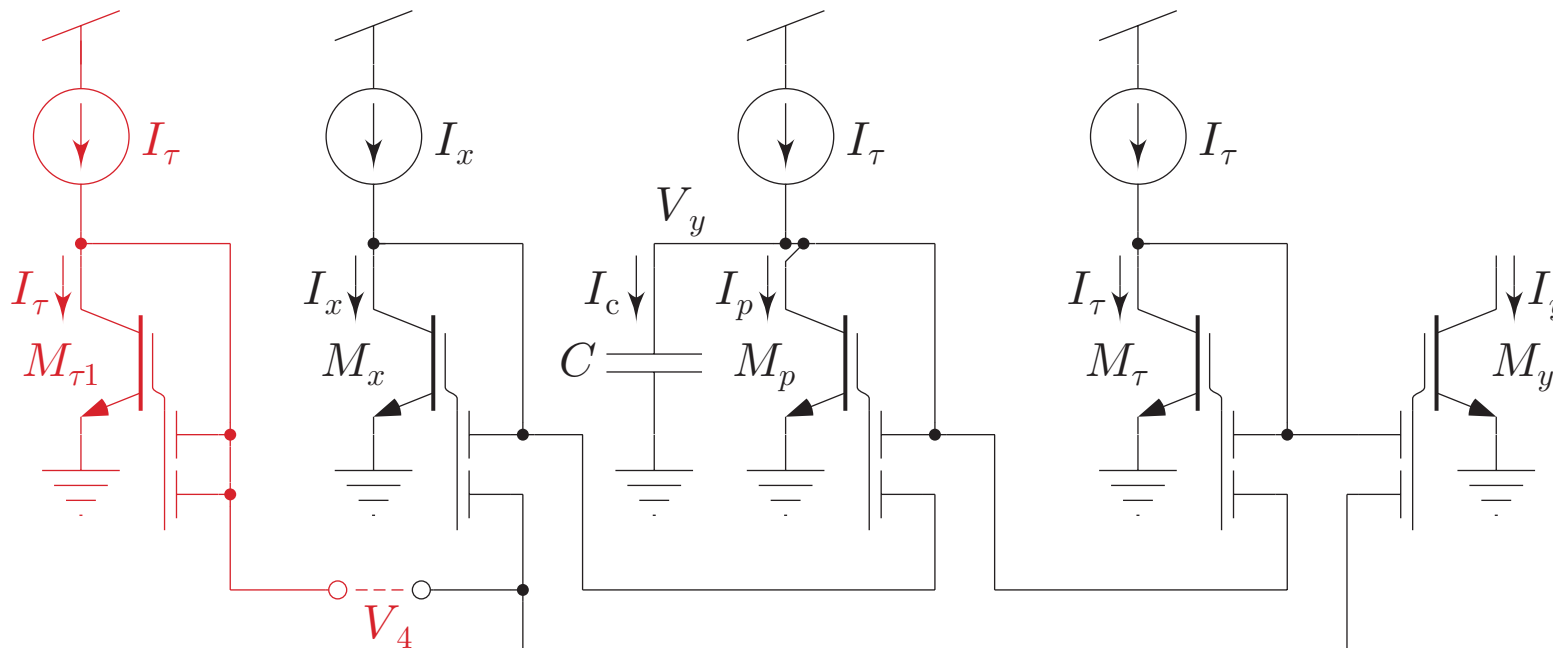
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$



Dynamic MITE Network Synthesis: **First-Order LPF**
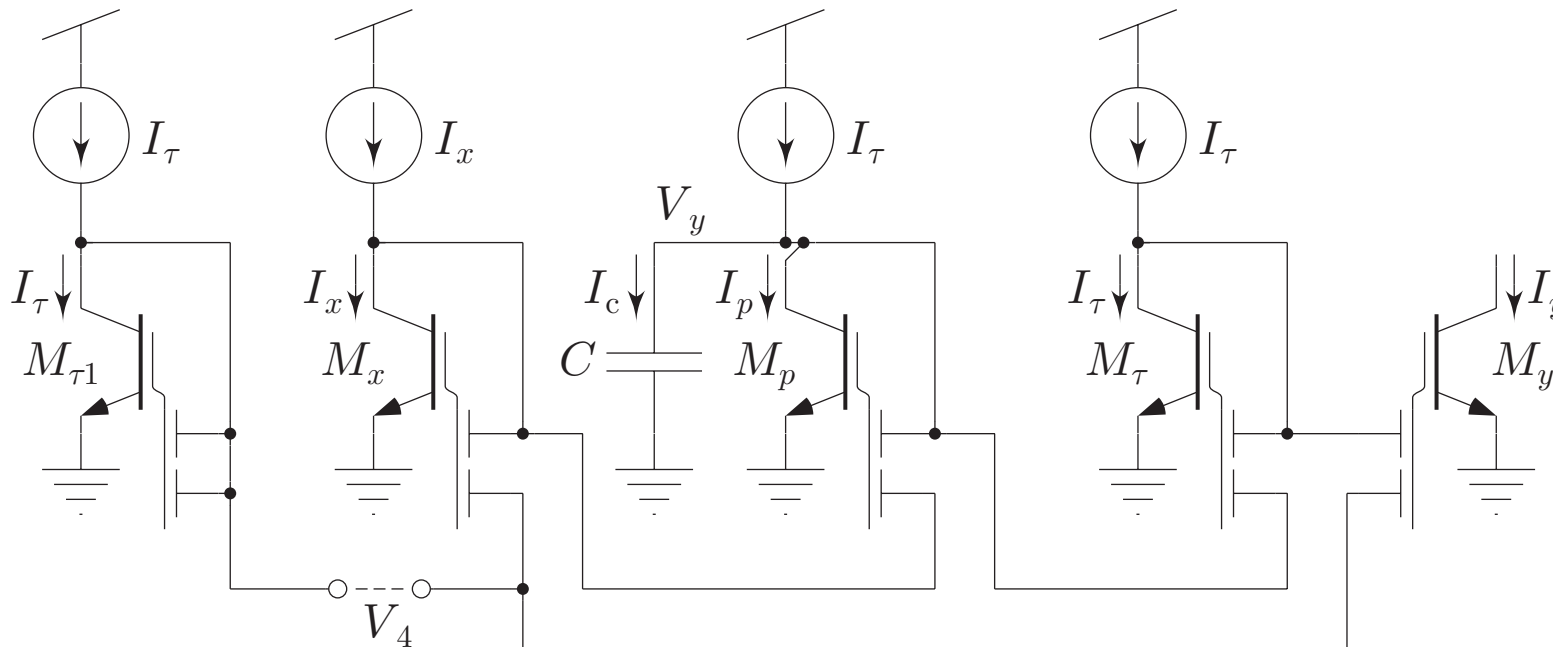
$$\text{TLP: } I_p I_y = I_x I_\tau \quad \text{KCL: } I_p + I_c = I_\tau$$



Dynamic MITE Network Synthesis: **Second-Order LPF**

Synthesize a second-order low-pass filter described by

$$\tau^2 \frac{d^2 y}{dt^2} + \frac{\tau}{Q} \cdot \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

Synthesize a second-order low-pass filter described by

$$\tau^2 \frac{d^2 y}{dt^2} + \frac{\tau}{Q} \cdot \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We can decompose this second-order ODE into two coupled first-order ODEs as

$$\tau \frac{d}{dt} \left(\tau \frac{dy}{dt} + \frac{y}{Q} \right) + y = x$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

Synthesize a second-order low-pass filter described by

$$\tau^2 \frac{d^2 y}{dt^2} + \frac{\tau}{Q} \cdot \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We can decompose this second-order ODE into two coupled first-order ODEs as

$$\tau \frac{d}{dt} \left(\underbrace{\tau \frac{dy}{dt} + \frac{y}{Q}}_z \right) + y = x$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

Synthesize a second-order low-pass filter described by

$$\tau^2 \frac{d^2 y}{dt^2} + \frac{\tau}{Q} \cdot \frac{dy}{dt} + y = x, \quad \text{where } x > 0.$$

We can decompose this second-order ODE into two coupled first-order ODEs as

$$\tau \frac{d}{dt} \left(\underbrace{\tau \frac{dy}{dt} + \frac{y}{Q}}_z \right) + y = x \quad \Longrightarrow \quad \begin{cases} \tau \frac{dz}{dt} = x - y \\ \tau \frac{dy}{dt} = z - \frac{y}{Q} \end{cases}$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the pair of ODEs, we obtain

$$\left\{ \begin{array}{l} \tau \frac{d}{dt} \left(\frac{I_z}{I_1} \right) = \frac{I_x}{I_1} - \frac{I_y}{I_1} \\ \tau \frac{d}{dt} \left(\frac{I_y}{I_1} \right) = \frac{I_z}{I_1} - \frac{1}{Q} \cdot \frac{I_y}{I_1} \end{array} \right.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

We represent each signal as a ratio of a signal current to the unit current:

$$x \equiv \frac{I_x}{I_1}, \quad y \equiv \frac{I_y}{I_1}, \quad \text{and} \quad z \equiv \frac{I_z}{I_1}.$$

Substituting these into the pair of ODEs, we obtain

$$\left\{ \begin{array}{l} \tau \frac{d}{dt} \left(\frac{I_z}{I_1} \right) = \frac{I_x}{I_1} - \frac{I_y}{I_1} \\ \tau \frac{d}{dt} \left(\frac{I_y}{I_1} \right) = \frac{I_z}{I_1} - \frac{1}{Q} \cdot \frac{I_y}{I_1} \end{array} \right. \implies \left\{ \begin{array}{l} \tau \frac{dI_z}{dt} = I_x - I_y \\ \tau \frac{dI_y}{dt} = I_z - \frac{I_y}{Q}. \end{array} \right.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

To implement the time derivatives, we introduce log-compressed voltage state variables, V_z and V_y . Using the chain rule, we can express the preceding pair of equations as

$$\left\{ \begin{array}{l} \tau \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} = I_x - I_y \\ \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} = I_z - \frac{I_y}{Q} \end{array} \right.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

To implement the time derivatives, we introduce log-compressed voltage state variables, V_z and V_y . Using the chain rule, we can express the preceding pair of equations as

$$\left\{ \begin{array}{l} \tau \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} = I_x - I_y \\ \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} = I_z - \frac{I_y}{Q} \end{array} \right. \implies \left\{ \begin{array}{l} \tau \left(-\frac{w}{U_T} I_z \right) \frac{dV_z}{dt} = I_x - I_y \\ \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} = I_z - \frac{I_y}{Q} \end{array} \right.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

To implement the time derivatives, we introduce log-compressed voltage state variables, V_z and V_y . Using the chain rule, we can express the preceding pair of equations as

$$\left\{ \begin{array}{l} \tau \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} = I_x - I_y \\ \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} = I_z - \frac{I_y}{Q} \end{array} \right. \implies \left\{ \begin{array}{l} \tau \left(-\frac{w}{U_T} I_z \right) \frac{dV_z}{dt} = I_x - I_y \\ \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} = I_z - \frac{I_y}{Q} \end{array} \right.$$

$$\implies \left\{ \begin{array}{l} \frac{w\tau}{U_T} \cdot \frac{dV_z}{dt} = \frac{I_y}{I_z} - \frac{I_x}{I_z} \\ \frac{w\tau}{U_T} \cdot \frac{dV_y}{dt} = \frac{1}{Q} - \frac{I_z}{I_y} \end{array} \right.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

To implement the time derivatives, we introduce log-compressed voltage state variables, V_z and V_y . Using the chain rule, we can express the preceding pair of equations as

$$\left\{ \begin{array}{l} \tau \frac{\partial I_z}{\partial V_z} \cdot \frac{dV_z}{dt} = I_x - I_y \\ \tau \frac{\partial I_y}{\partial V_y} \cdot \frac{dV_y}{dt} = I_z - \frac{I_y}{Q} \end{array} \right. \implies \left\{ \begin{array}{l} \tau \left(-\frac{w}{U_T} I_z \right) \frac{dV_z}{dt} = I_x - I_y \\ \tau \left(-\frac{w}{U_T} I_y \right) \frac{dV_y}{dt} = I_z - \frac{I_y}{Q} \end{array} \right.$$

$$\implies \left\{ \begin{array}{l} \frac{w\tau}{U_T} \cdot \frac{dV_z}{dt} = \frac{I_y}{I_z} - \frac{I_x}{I_z} \\ \frac{w\tau}{U_T} \cdot \frac{dV_y}{dt} = \frac{1}{Q} - \frac{I_z}{I_y} \end{array} \right. \implies \left\{ \begin{array}{l} \frac{w\tau}{CU_T} \cdot C \frac{dV_z}{dt} = \frac{I_y}{I_z} - \frac{I_x}{I_z} \\ \frac{w\tau}{CU_T} \cdot C \frac{dV_y}{dt} = \frac{1}{Q} - \frac{I_z}{I_y} \end{array} \right.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

By introducing

$$I_\tau \equiv \frac{CU_T}{w\tau}, \quad I_{cz} \equiv C \frac{dV_z}{dt}, \quad \text{and} \quad I_{cy} \equiv C \frac{dV_y}{dt},$$

we can express this pair of equations as

$$\left\{ \begin{array}{l} \frac{I_{cz}}{I_\tau} = \frac{I_y}{I_z} - \frac{I_x}{I_z} \\ \frac{I_{cy}}{I_\tau} = \frac{1}{Q} - \frac{I_z}{I_y} \end{array} \right.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

By introducing

$$I_\tau \equiv \frac{CU_T}{w\tau}, \quad I_{cz} \equiv C \frac{dV_z}{dt}, \quad \text{and} \quad I_{cy} \equiv C \frac{dV_y}{dt},$$

we can express this pair of equations as

$$\left\{ \begin{array}{l} \frac{I_{cz}}{I_\tau} = \frac{I_y}{I_z} - \frac{I_x}{I_z} \\ \frac{I_{cy}}{I_\tau} = \frac{1}{Q} - \frac{I_z}{I_y} \end{array} \right. \implies \left\{ \begin{array}{l} I_{cz} = \frac{I_y I_\tau}{I_z} - \frac{I_x I_\tau}{I_z} \\ I_{cy} = \frac{I_\tau}{Q} - \frac{I_z I_\tau}{I_y} \end{array} \right.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

By introducing

$$I_\tau \equiv \frac{CU_T}{w\tau}, \quad I_{cz} \equiv C \frac{dV_z}{dt}, \quad \text{and} \quad I_{cy} \equiv C \frac{dV_y}{dt},$$

we can express this pair of equations as

$$\left\{ \begin{array}{l} \frac{I_{cz}}{I_\tau} = \frac{I_y}{I_z} - \frac{I_x}{I_z} \\ \frac{I_{cy}}{I_\tau} = \frac{1}{Q} - \frac{I_z}{I_y} \end{array} \right. \Rightarrow \left\{ \begin{array}{l} I_{cz} = \frac{I_y I_\tau}{I_z} - \frac{I_x I_\tau}{I_z} \\ I_{cy} = \frac{I_\tau}{Q} - \frac{I_z I_\tau}{I_y} \end{array} \right. \Rightarrow \left\{ \begin{array}{l} I_{cz} = I_w - I_{pz} \\ I_{cy} = \frac{I_\tau}{Q} - I_{py}, \end{array} \right.$$

where we have further introduced

$$I_w \equiv \frac{I_y I_\tau}{I_z}, \quad I_{pz} \equiv \frac{I_x I_\tau}{I_z}, \quad \text{and} \quad I_{py} \equiv \frac{I_z I_\tau}{I_y}.$$

Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$
$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$
$$I_{py} + I_{cy} = I_\tau / Q$$


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

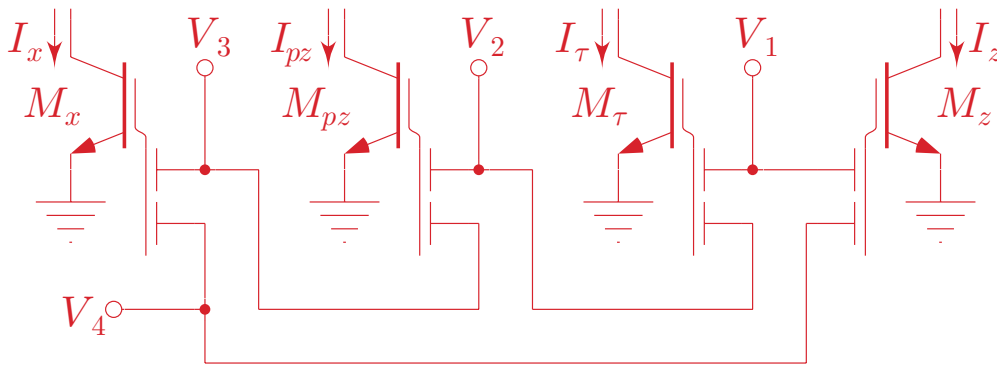

Dynamic MITE Network Synthesis: **Second-Order LPF**



$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

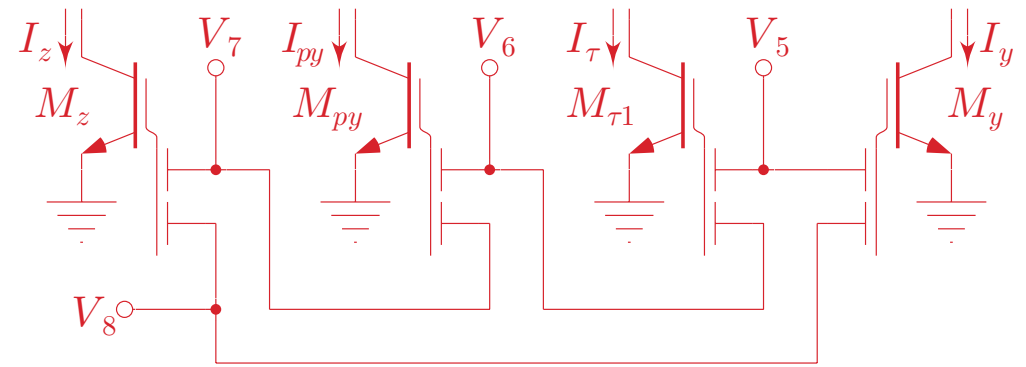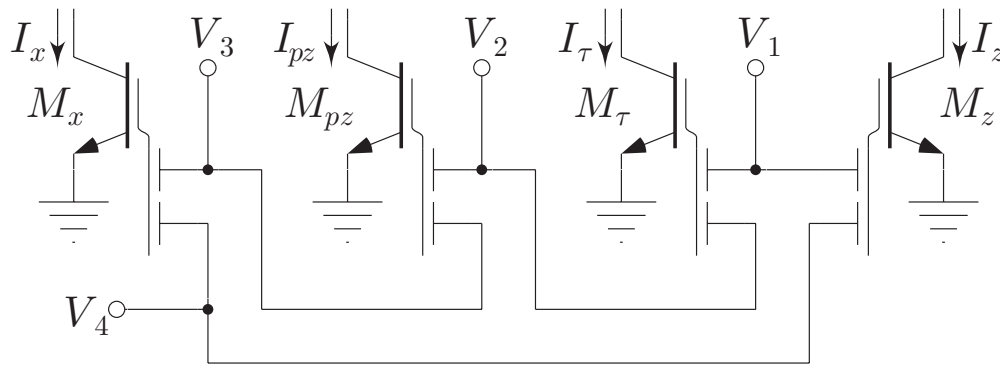


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

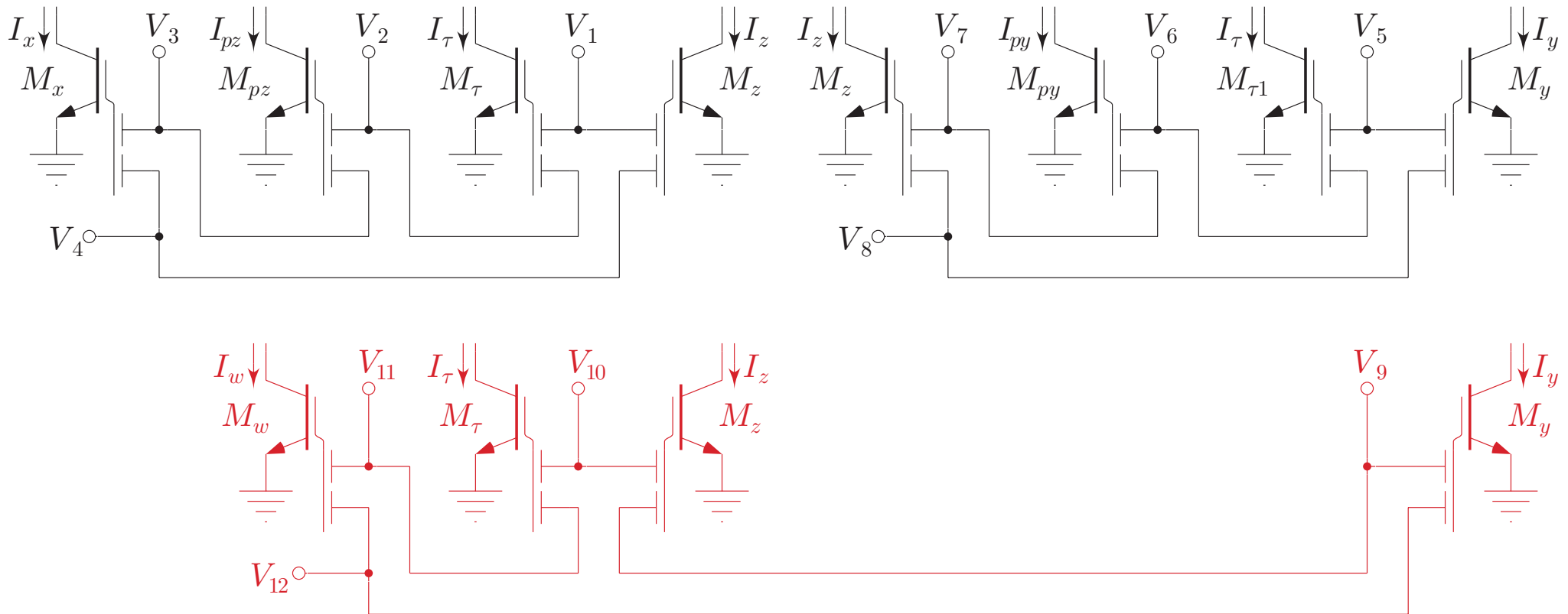

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

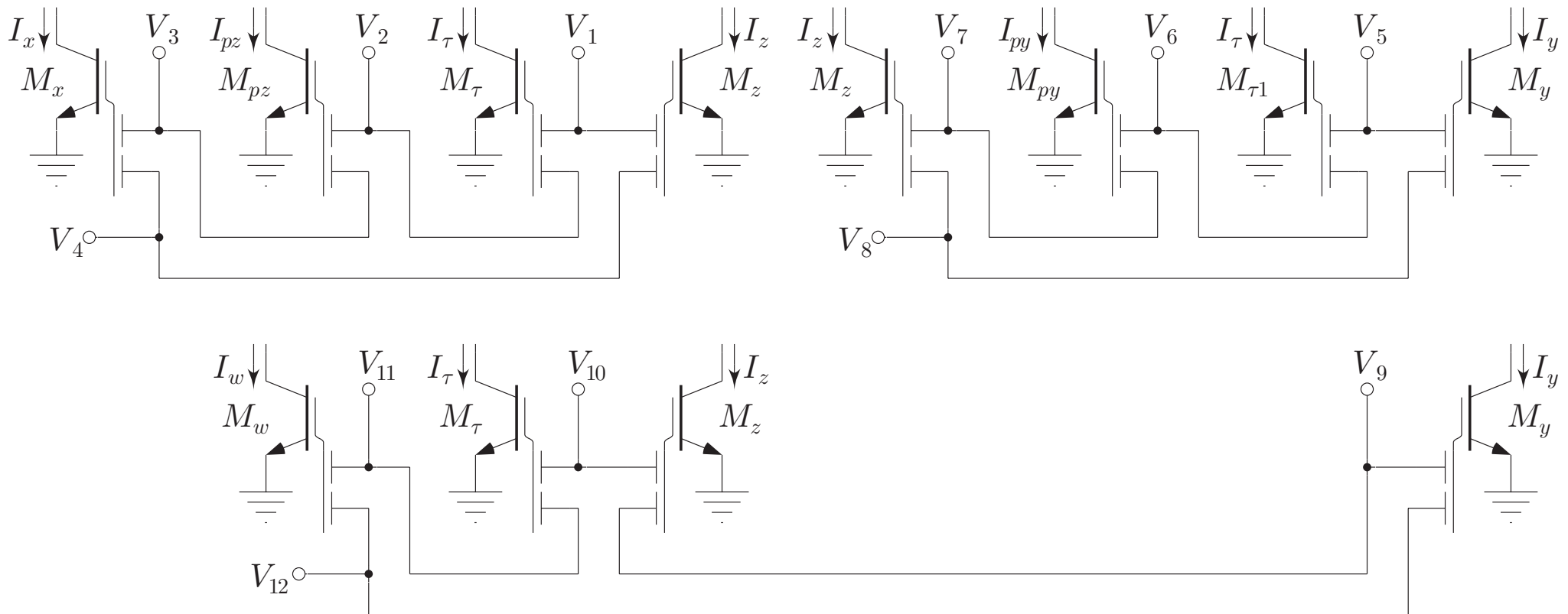

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

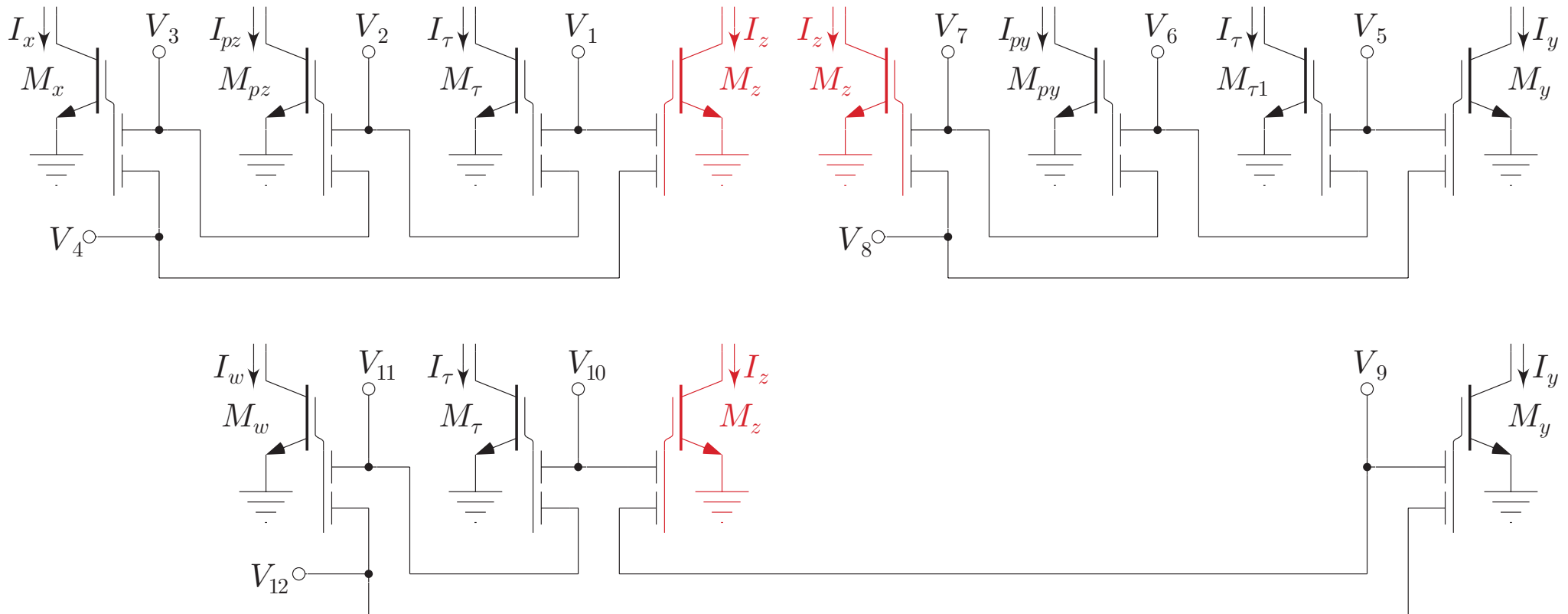

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

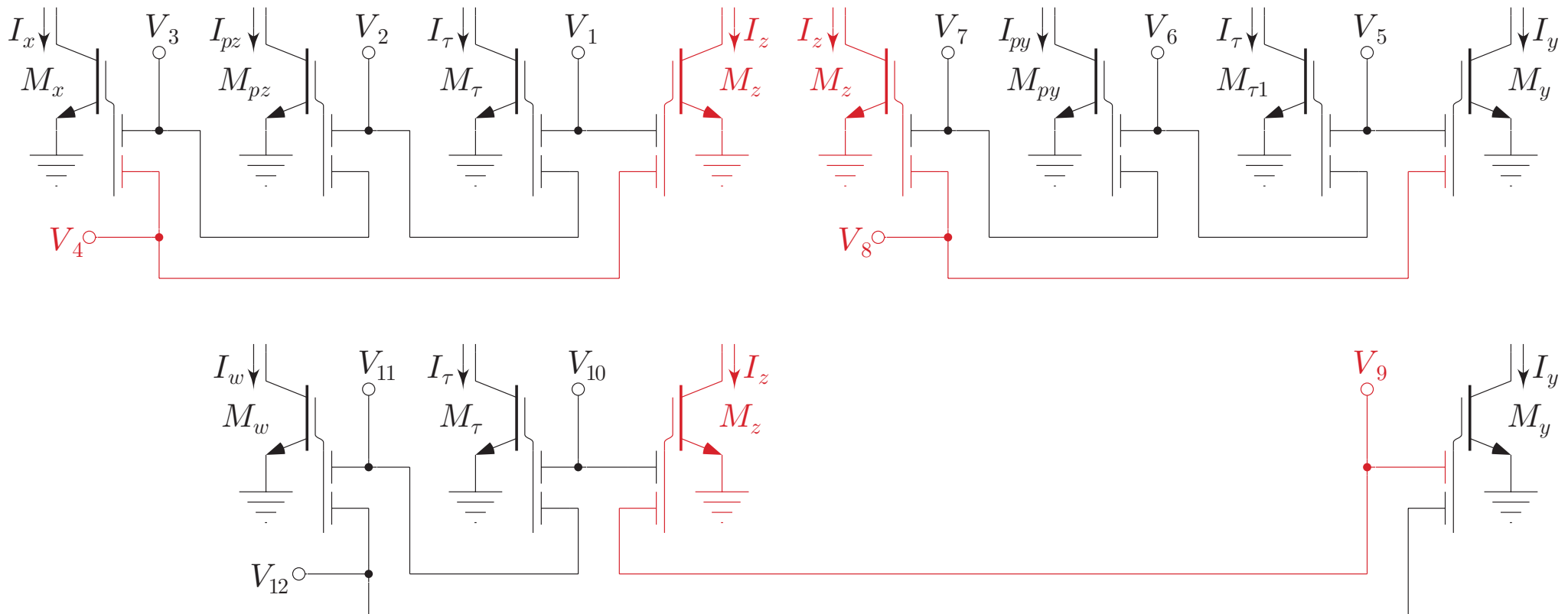

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

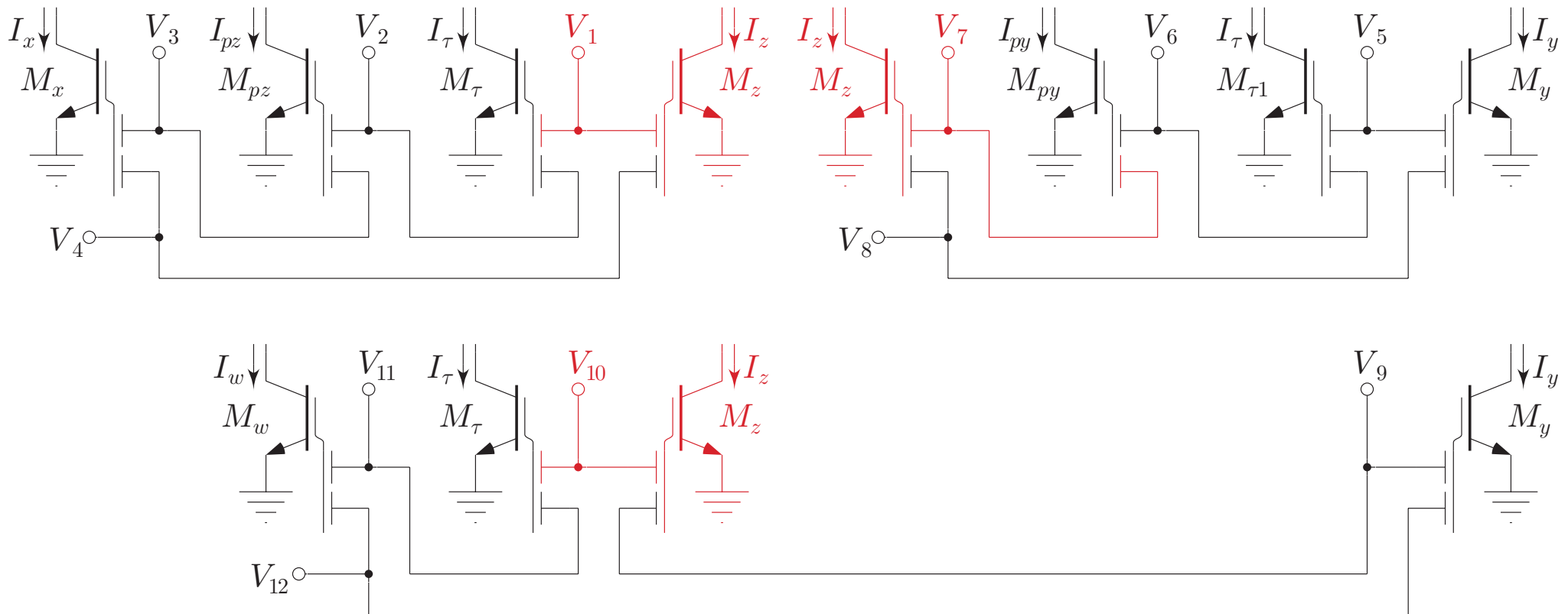


Dynamic MITE Network Synthesis: **Second-Order LPF**

TLP: $I_z I_{pz} = I_x I_\tau$
 $I_z I_w = I_y I_\tau$

$I_y I_{py} = I_z I_\tau$

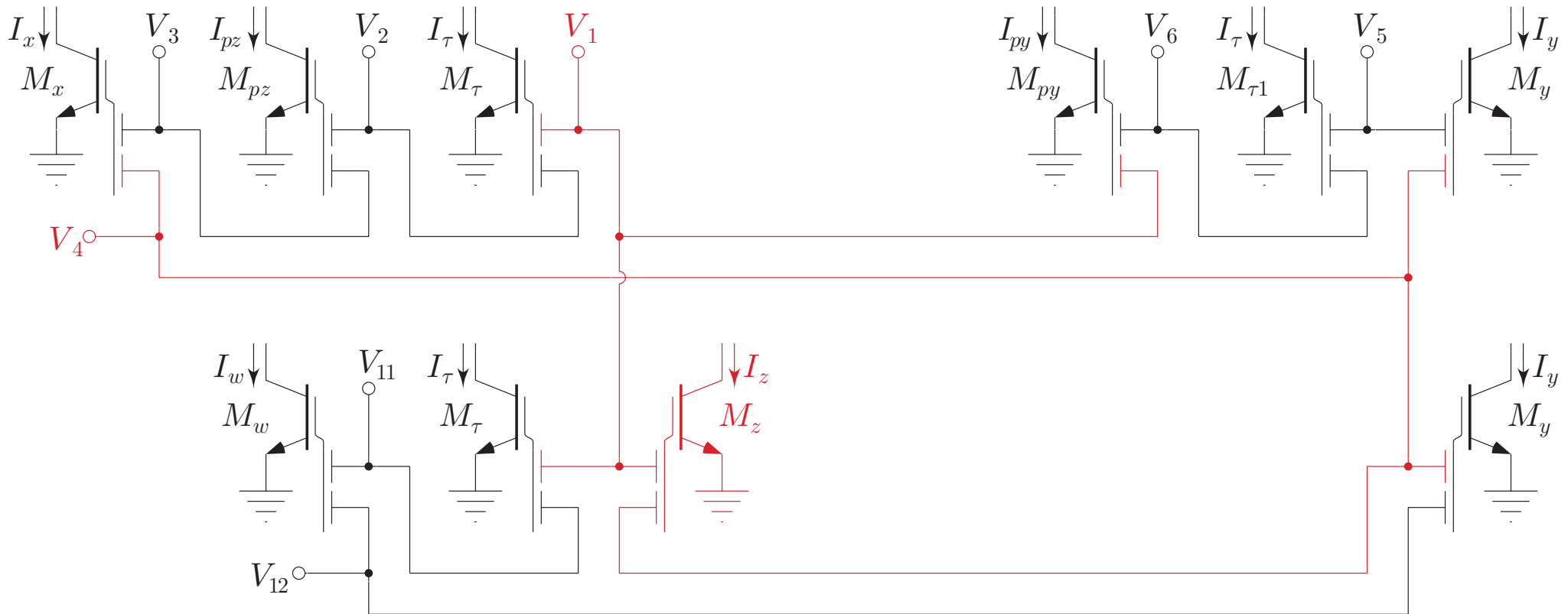KCL: $I_{pz} + I_{cz} = I_w$
 $I_{py} + I_{cy} = I_\tau / Q$




Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

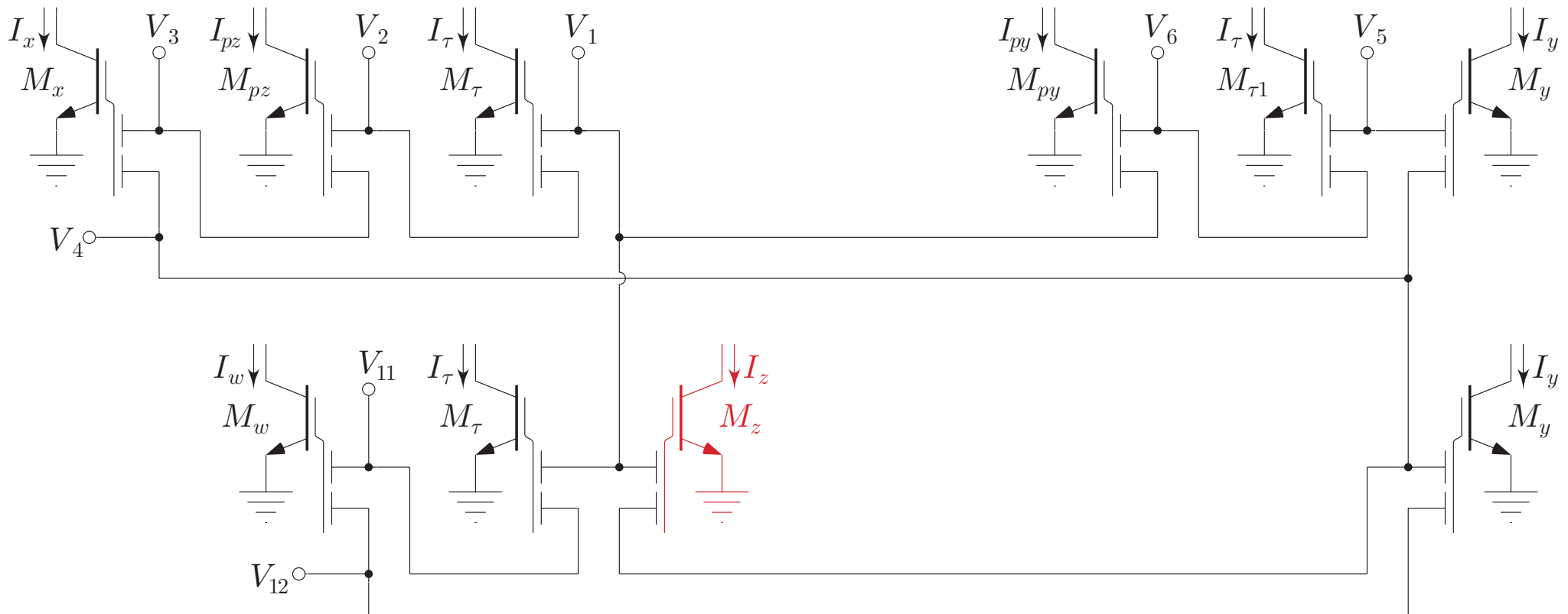


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

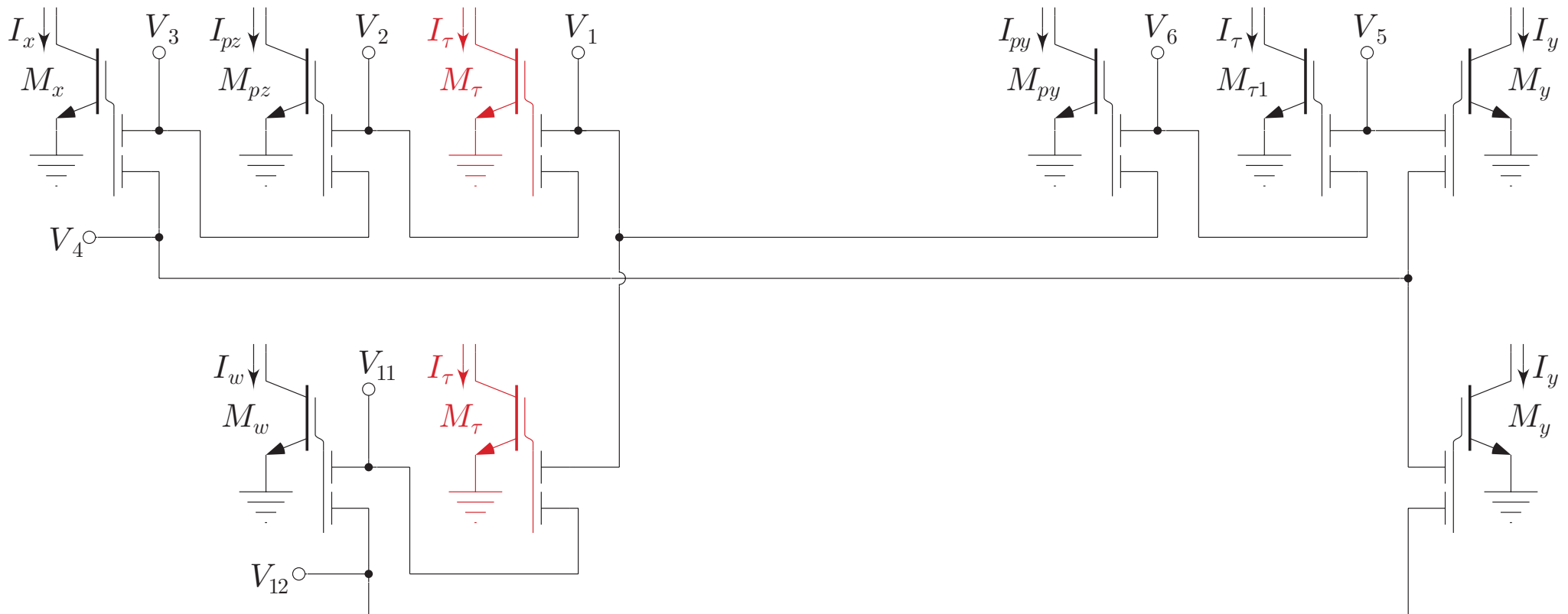


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

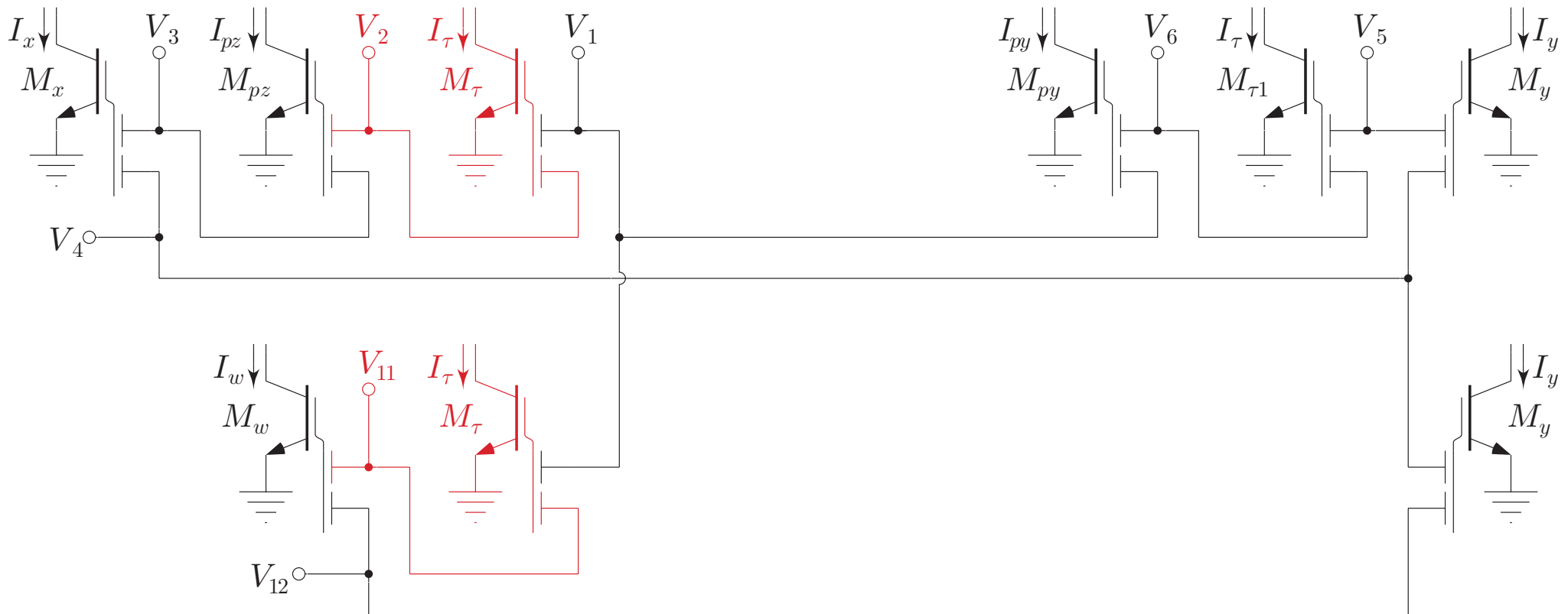


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

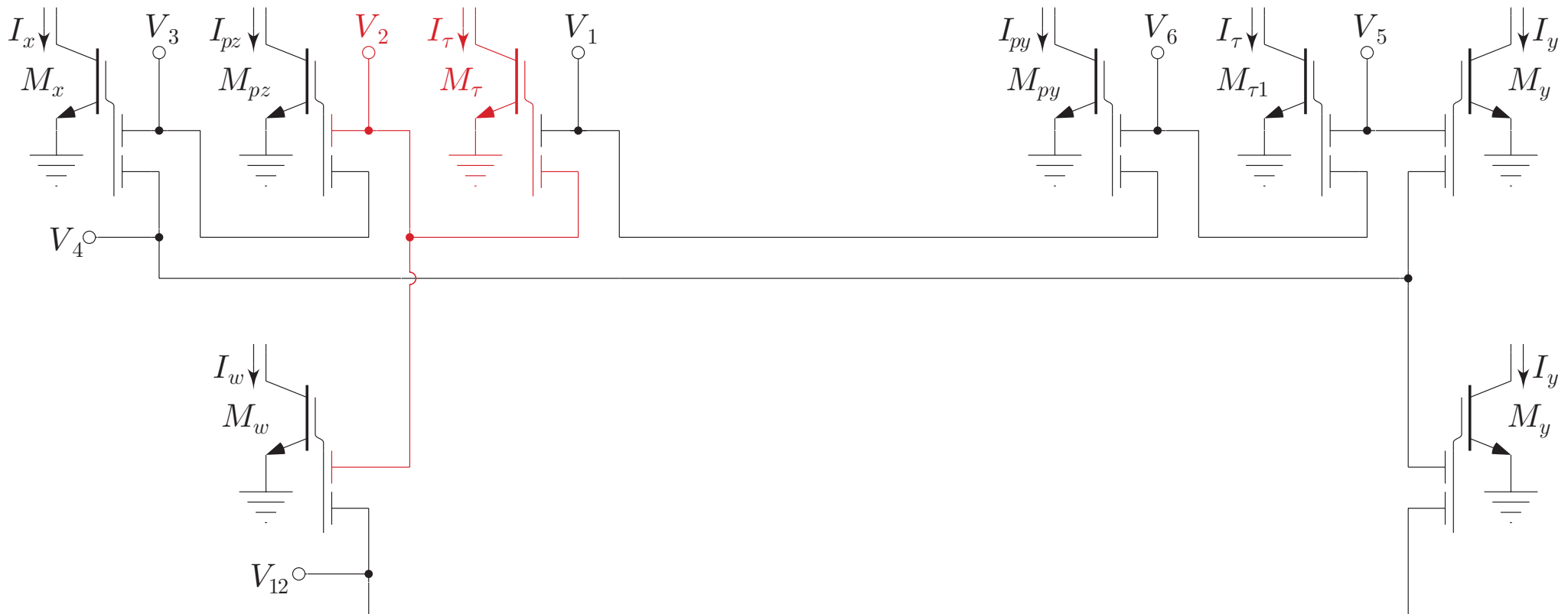


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

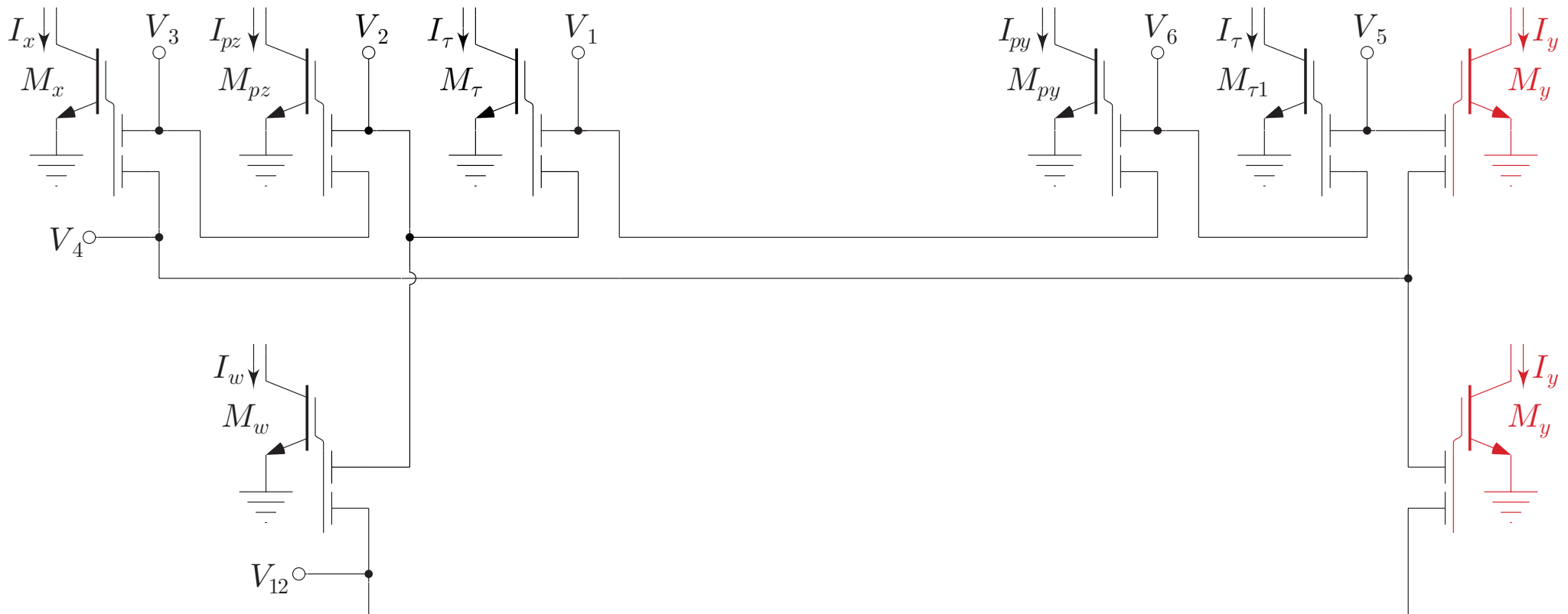


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

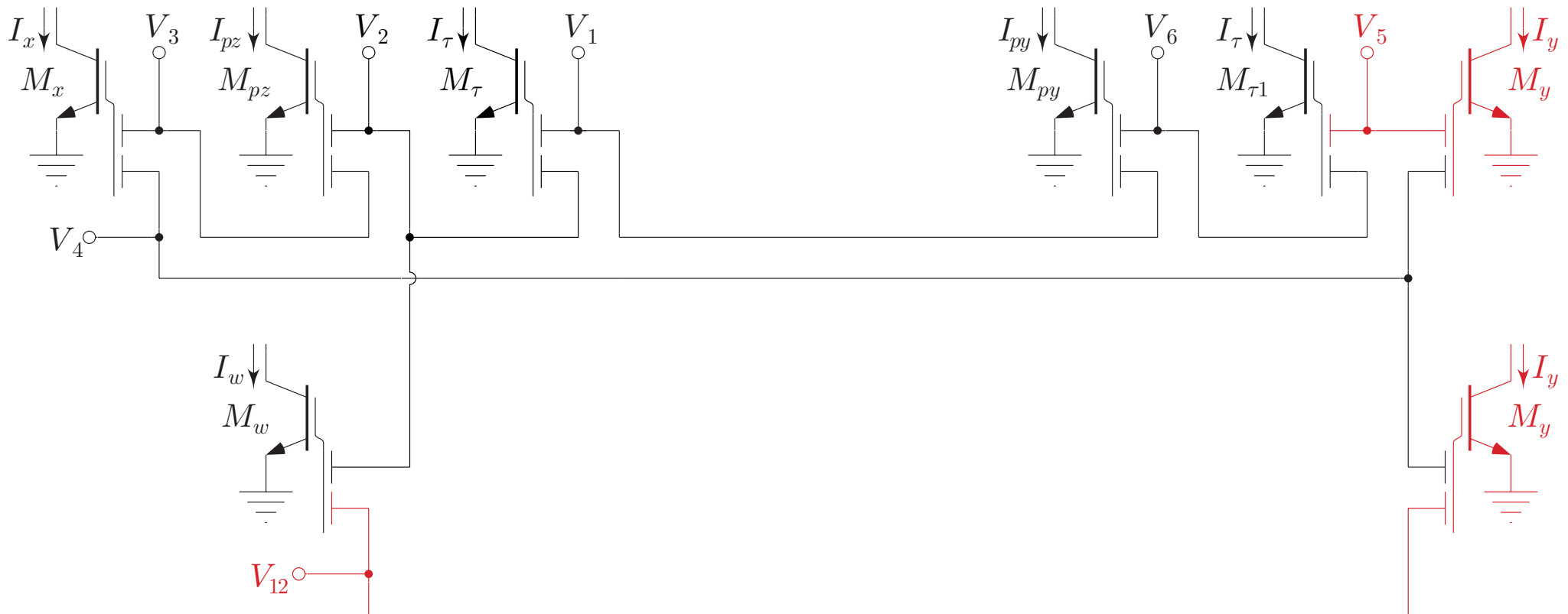


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

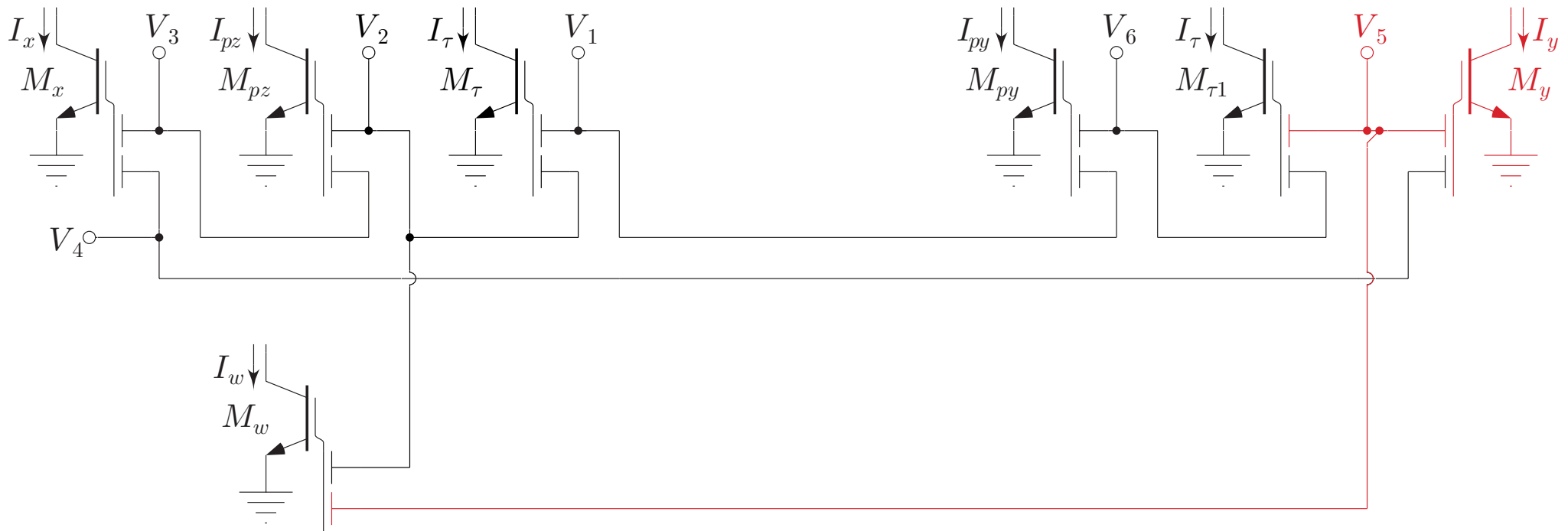


Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau \quad I_y I_{py} = I_z I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

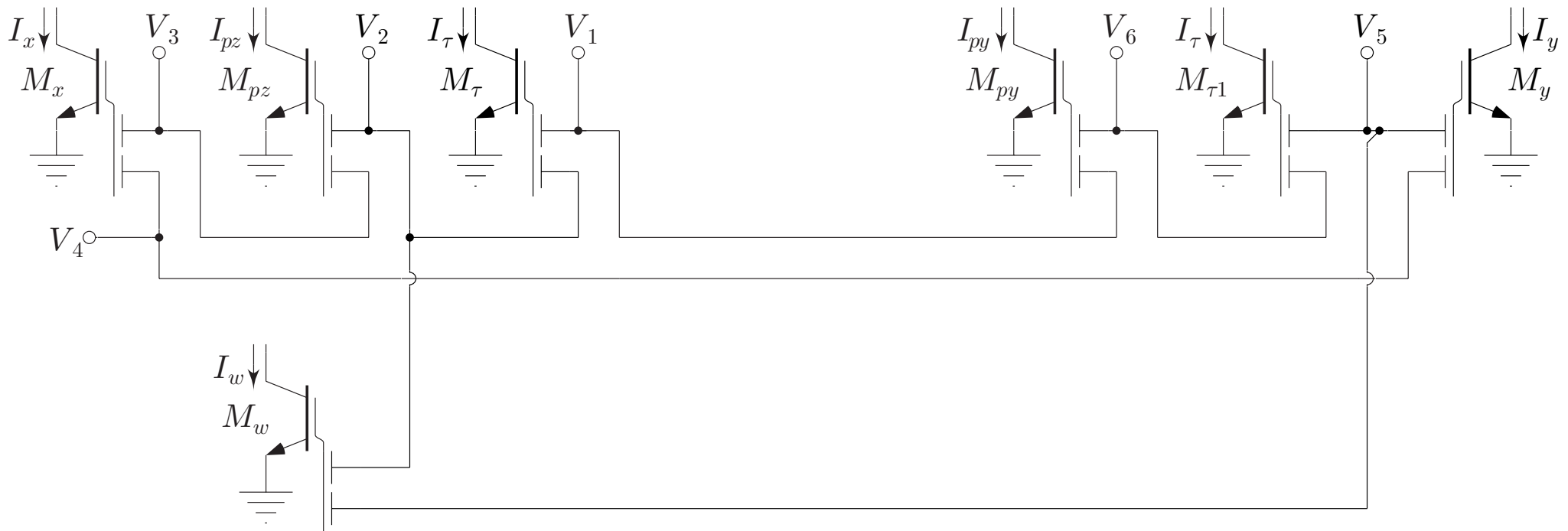

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

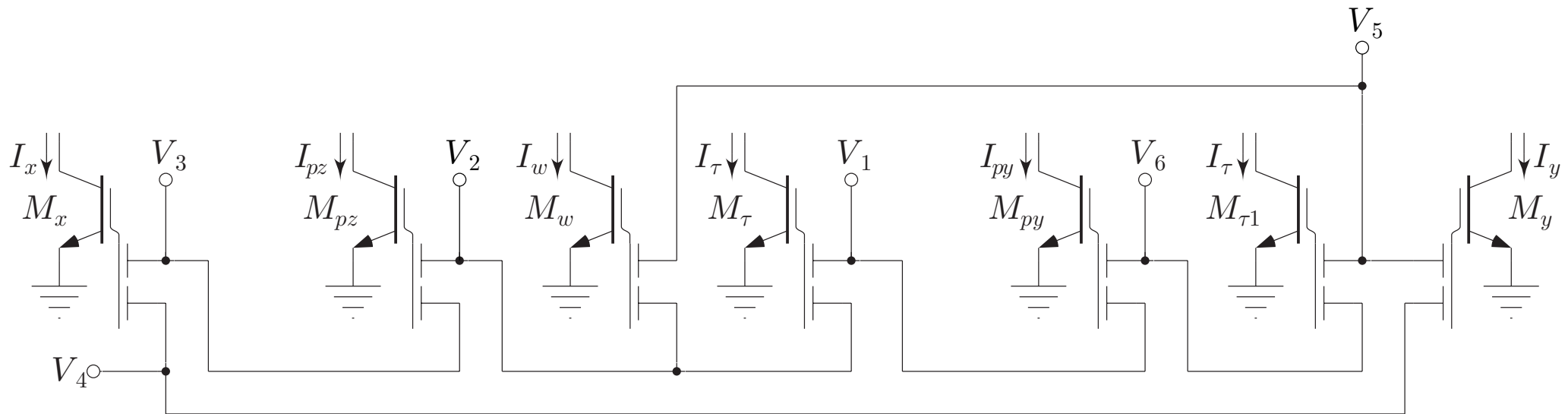

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

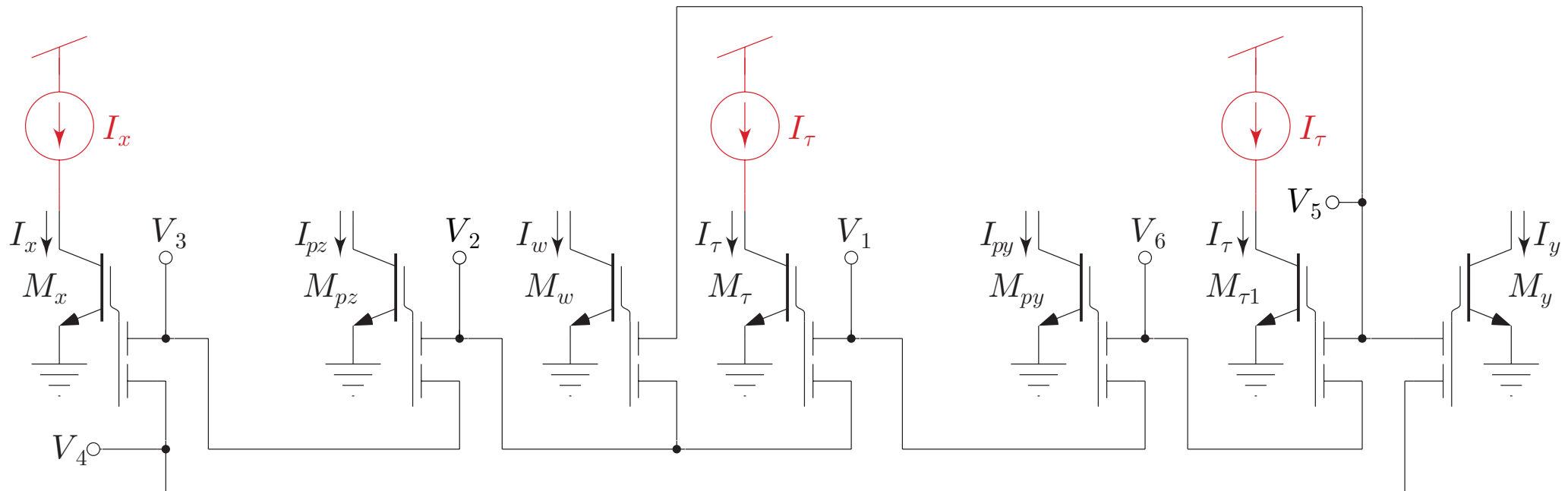

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

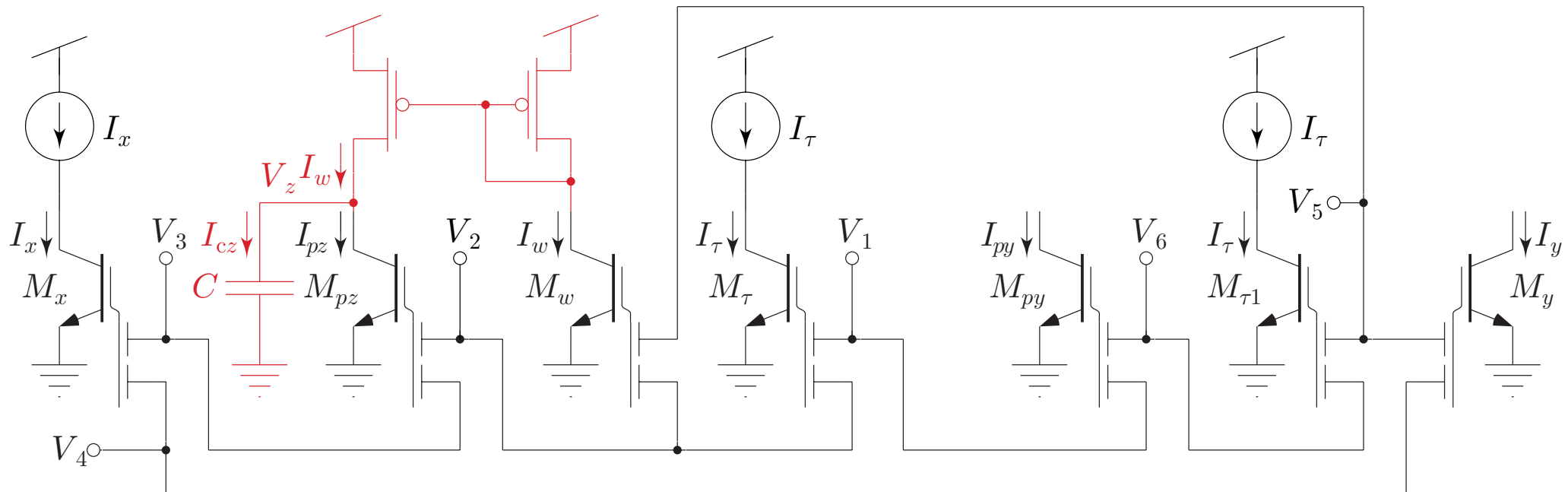

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

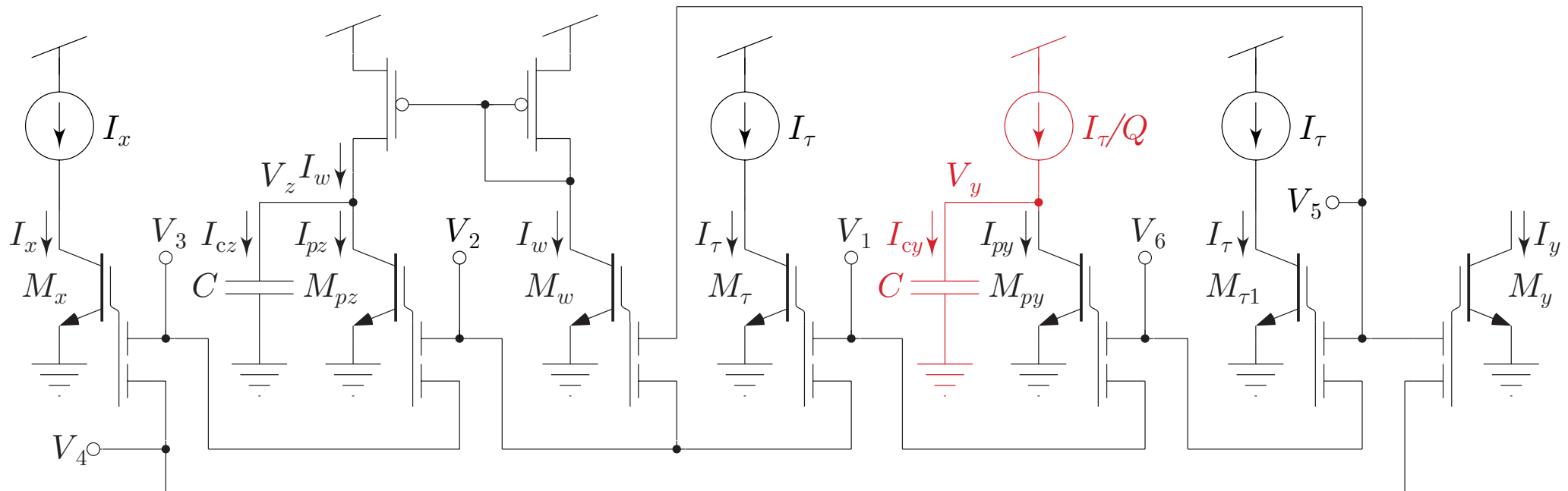

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

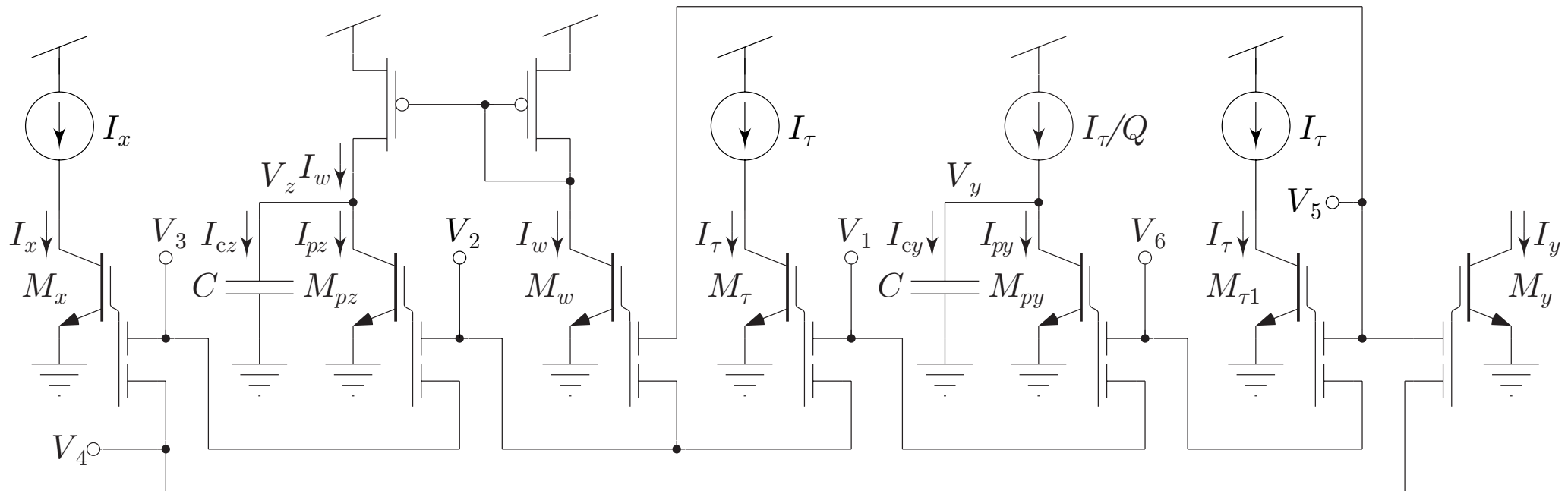

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

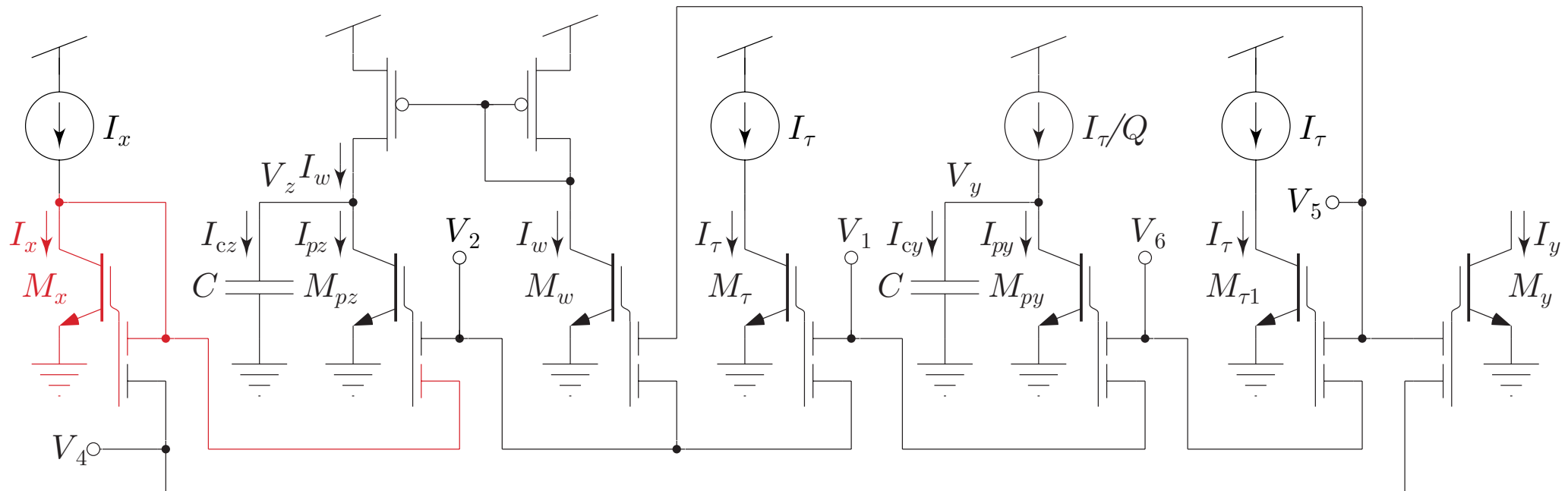

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

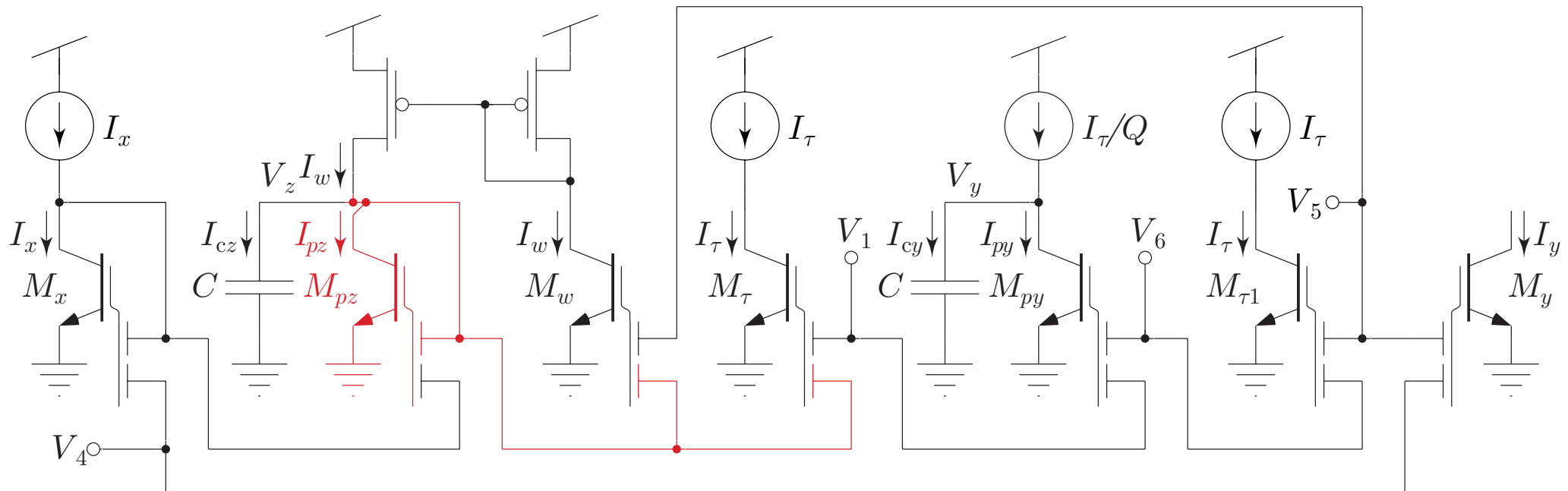

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

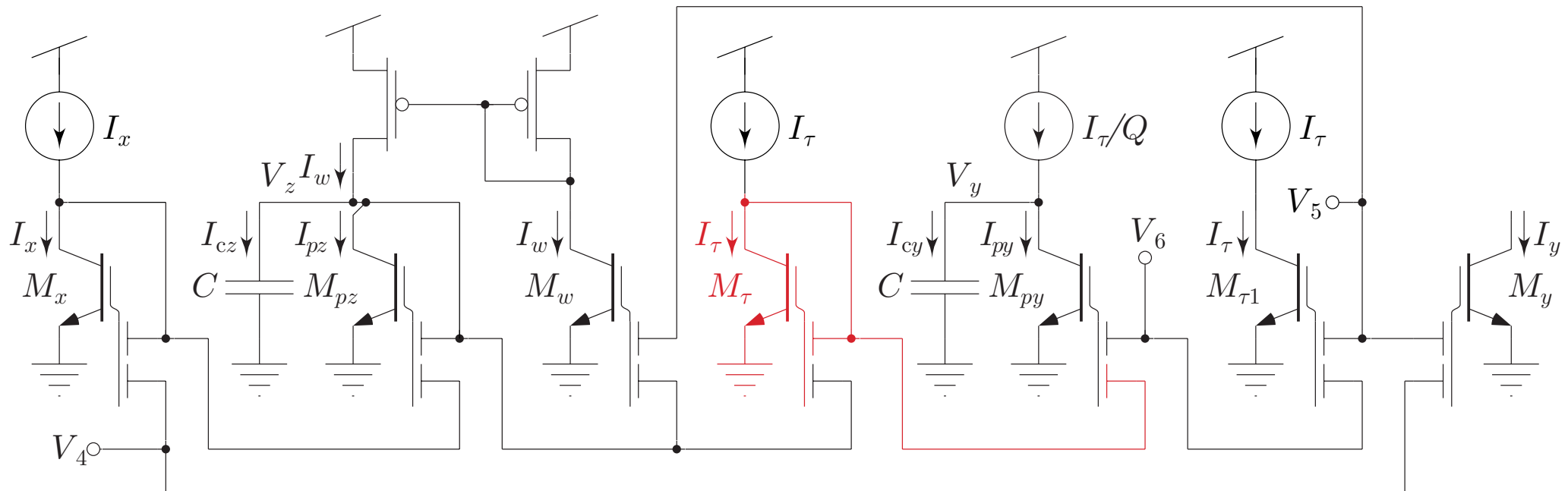

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

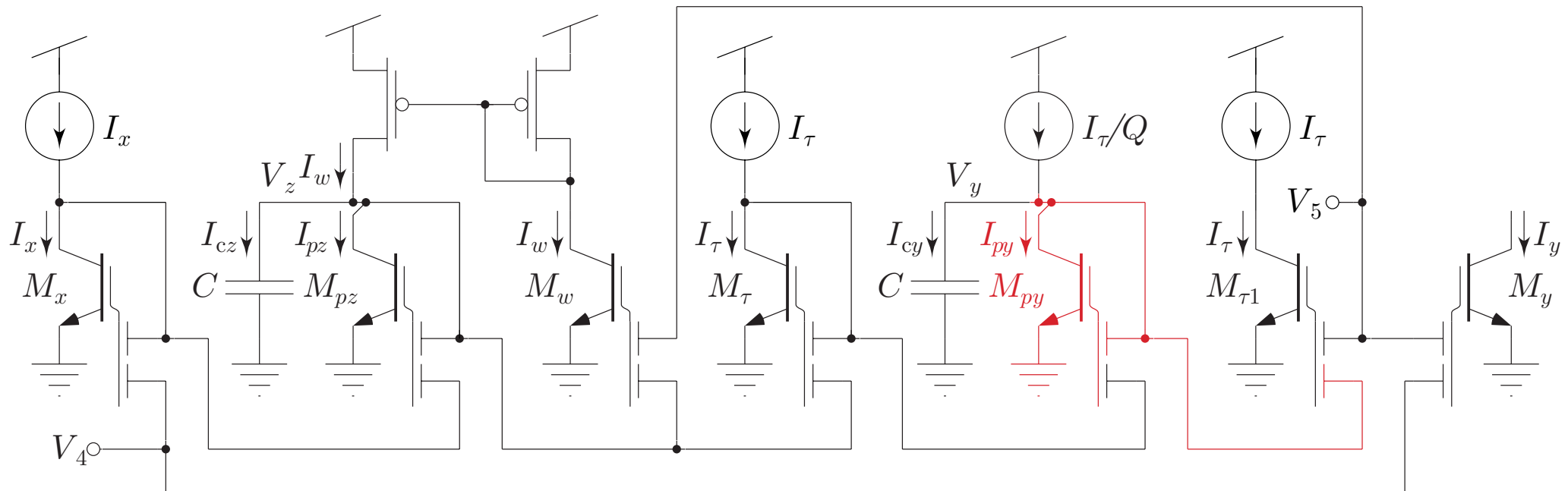

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

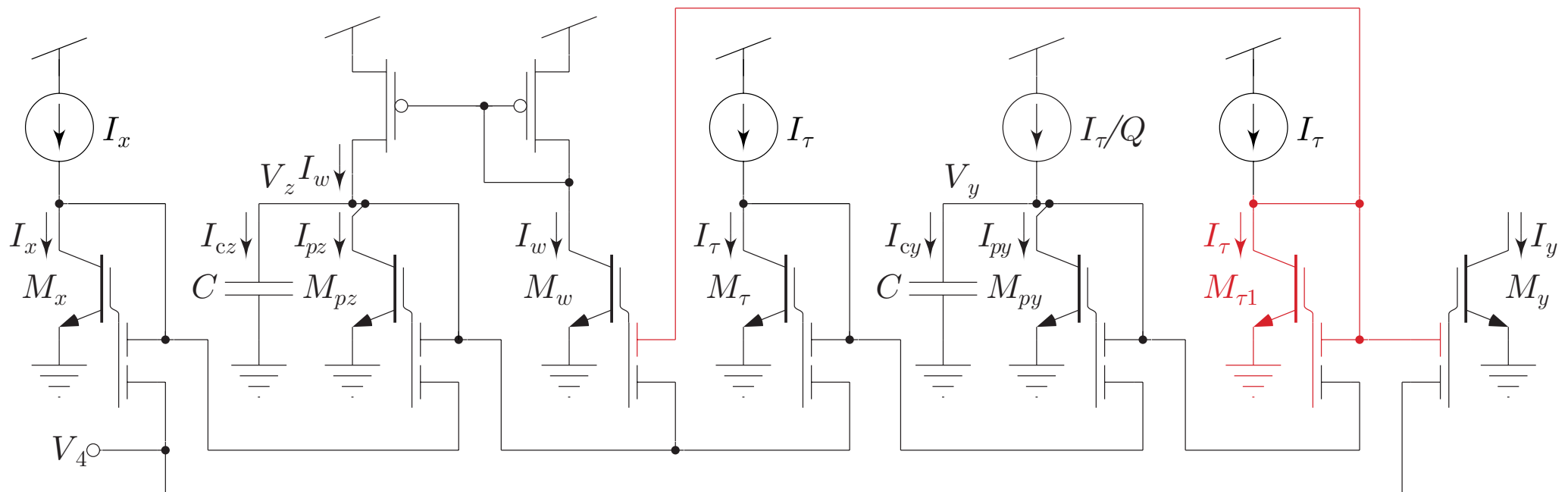

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

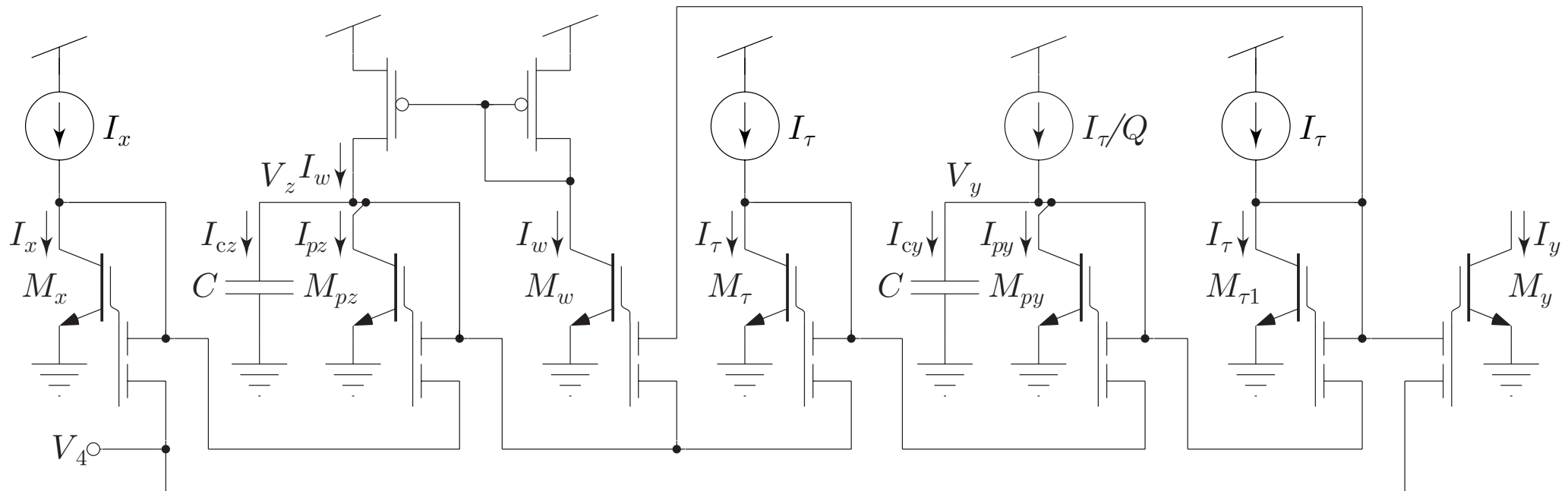

Dynamic MITE Network Synthesis: **Second-Order LPF**


$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

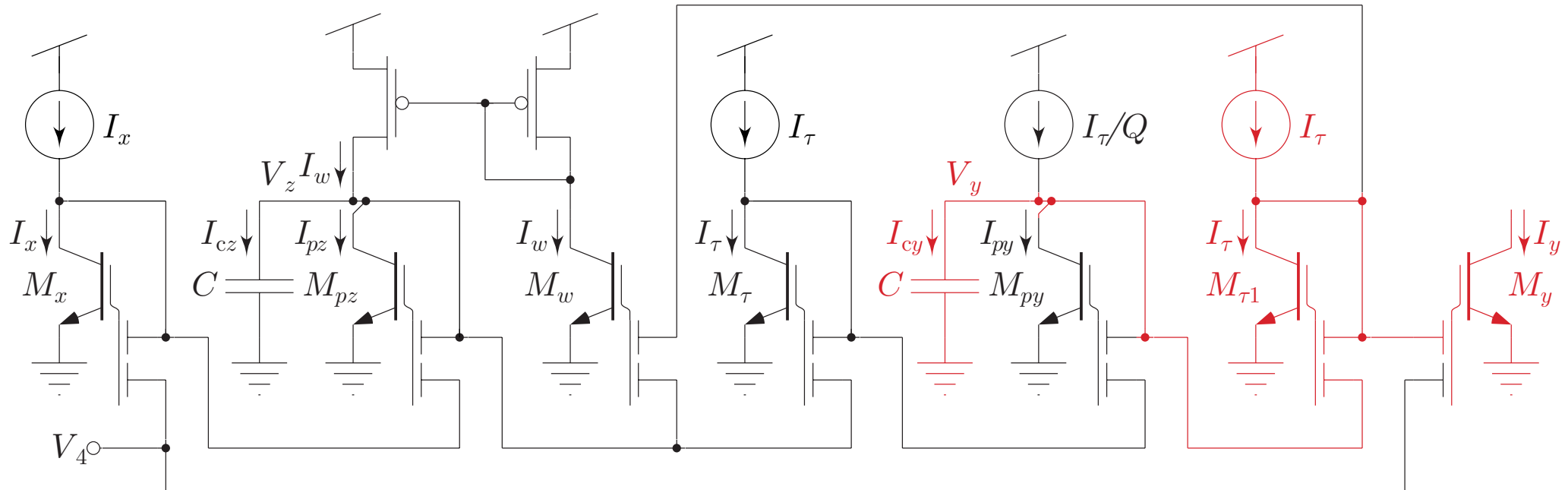

Dynamic MITE Network Synthesis: **Second-Order LPF**

$$\text{TLP: } I_z I_{pz} = I_x I_\tau$$

$$I_z I_w = I_y I_\tau$$

$$I_y I_{py} = I_z I_\tau$$

$$\text{KCL: } I_{pz} + I_{cz} = I_w$$

$$I_{py} + I_{cy} = I_\tau / Q$$

