



MAD VLSI

CIRCUITS & SYSTEMS LAB

Mixed Analog-Digital VLSI Circuits & Systems Laboratory

Our research presently revolves around two major themes:

- Devising new circuit techniques to facilitate the development of low-power/low-voltage analog and mixed-signal systems.
- Developing structured synthesis methodologies that will shorten the design time for complex analog and mixed-signal systems.


Low-Voltage Topologies for Analog and Mixed-Signal Circuits in Nanoscale CMOS

Bradley A. Minch

Mixed Analog-Digital VLSI Circuits and Systems Laboratory
School of Electrical and Computer Engineering
Cornell University
Ithaca, NY 14853–5401



minch@ece.cornell.edu
<http://people.ece.cornell.edu/minch>

The Double-Gate MOS Transistor

 



- ▶ The double-gate MOS transistor is perhaps the most promising device structure for scaling L down to 20 nm.
- ▶ Similar to fully-depleted SOI structure, but back gate provides better control over the potential in the silicon body, reducing short-channel effects.
- ▶ In principle, we can use V_F and V_B independently for signal or biasing inputs \Rightarrow new topologies possible!

Conventional MOS Differential Pairs

  

- ▶ The differential pair is widely used as an input stage for operational amplifiers, comparators, mixers, and many other circuits.
- ▶ This circuit does not function well with a low power-supply voltage, because transistor M_b shuts off if V_1 and V_2 get too close to the appropriate rail.


Conventional MOS Differential Pairs

  

Differential-pair intuition:

- ▶ $I_1 = f(g(V_1, -V))$ and $I_2 = f(g(V_2, -V))$, where f is expansive and g is quasilinear.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.

Capacitive Voltage Dividers

 


$$-C_1(V_1 - V) - C_2(V_2 - V) = Q$$

$$\Rightarrow (C_1 + C_2)V = C_1V_1 + C_2V_2 + Q$$

$$\Rightarrow V = \frac{C_1}{C_1 + C_2} V_1 + \frac{C_2}{C_1 + C_2} V_2 + \frac{Q}{C_1 + C_2}$$


- ▶ The voltage on the middle node is a weighted sum of the two input voltages.
- ▶ If node V is really floating, then the inputs couple into the floating node all the way down to DC!
- ▶ The charge Q linearly offsets the V . The charge can be adjusted either optically or electronically.

Floating-Gate MOS Transistors

 

- ▶ The capacitors C_1 and C_2 are called *control gates*.
- ▶ If floating-gate voltage, V , is a weighted sum of the control-gate voltages.
- ▶ The floating-gate charge, Q , can be thought of as giving us a programmable threshold voltage.

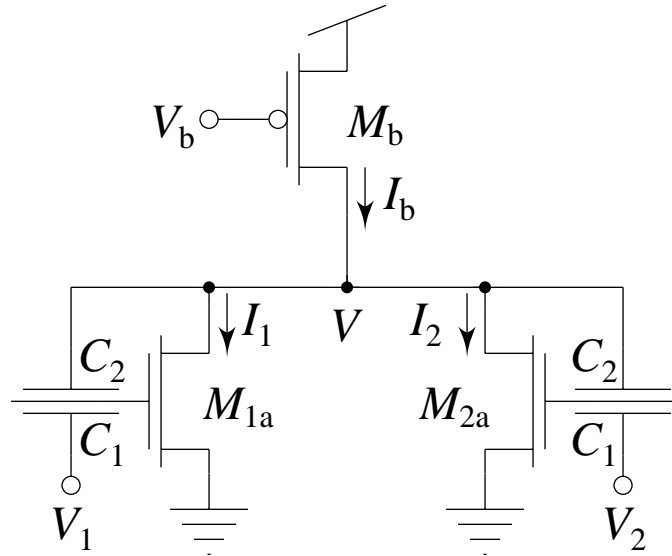
An **Inverted** Floating-Gate Differential Pair



Differential-pair intuition:

- ▶ $I_1 = f(g(V_1, V))$ and $I_2 = f(g(V_2, V))$, where f is expansive and g is quasilinear.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.

 An **Inverted** Floating-Gate Differential Pair




Differential-pair intuition:

- ▶ $I_1 = f(g(V_1, V))$ and $I_2 = f(g(V_2, V))$, where f is expansive and g is quasilinear.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.

Sign reversal permits us to *invert* V w.r.t. the normal diffpair.

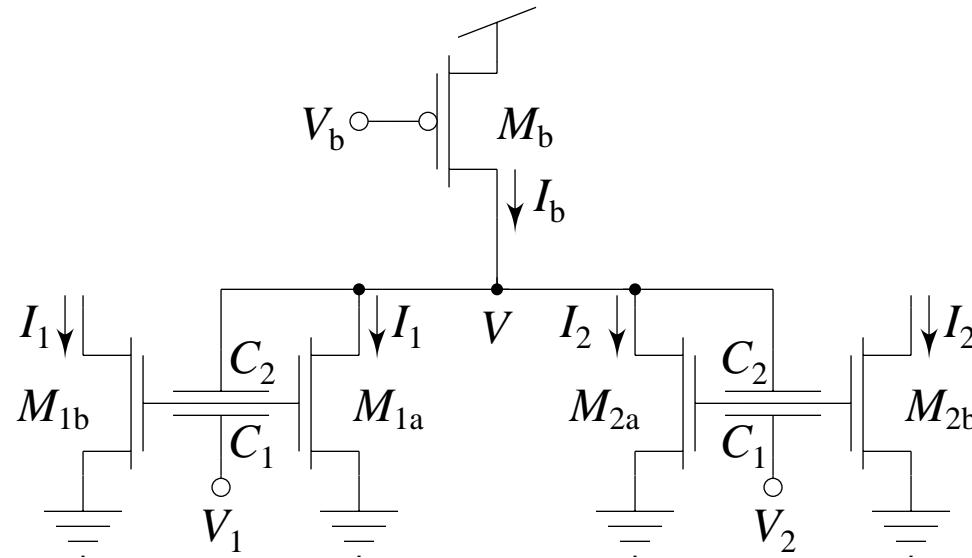An **Inverted** Floating-Gate Differential Pair




Differential-pair intuition:

- ▶ $I_1 = f(g(V_1, V))$ and $I_2 = f(g(V_2, V))$, where f is expansive and g is quasilinear.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.

M_{1b} and M_{2b} provide mirror copies of I_1 and I_2 .

 An **Inverted** Floating-Gate Differential Pair




Differential-pair intuition:

- ▶ $I_1 = f(g(V_1, V))$ and $I_2 = f(g(V_2, V))$, where f is expansive and g is quasilinear.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.


M_{1c} and M_{2c} mitigate the C_{gd} 's of transistors M_{1b} and M_{2b} .

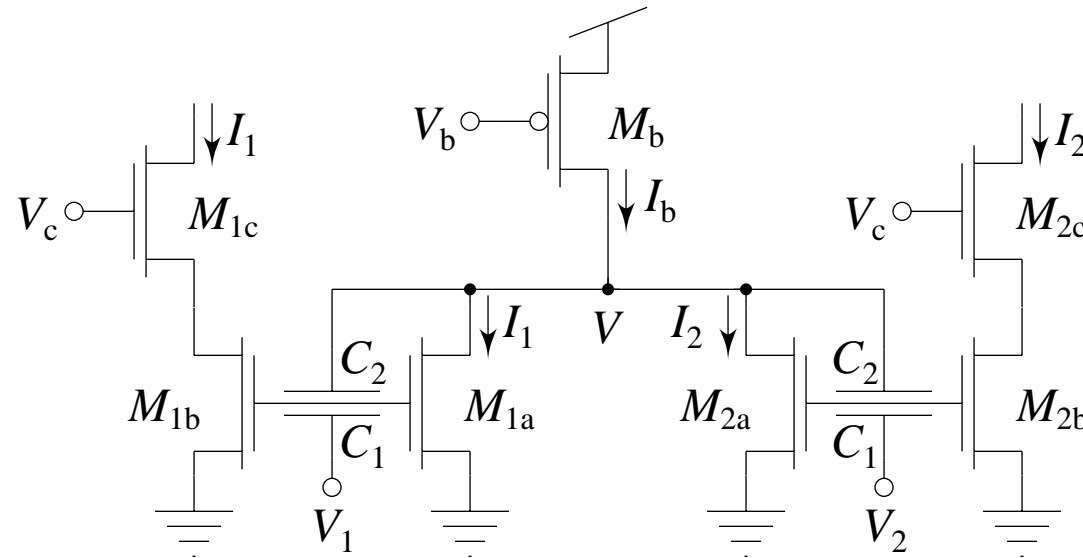An **Inverted** Floating-Gate Differential Pair




- ▶ C_1 sets the linear range and transconductance gain.
- ▶ C_2 controls by how much V changes in response to changes in either V_{cm} or I_b .
- ▶ Input and output voltage ranges are from rail-to-rail.
- ▶ Transconductance gain nearly constant with V_{cm} .

 
Output Currents vs. V_{dm} ($I_b = 316 \text{ pA}$)



 
Output Currents vs. V_{dm} ($I_b = 31.6 \mu A$)




Transconductance Gain vs. V_{cm}

 

Common-Mode Output Current vs. V_{out}

 

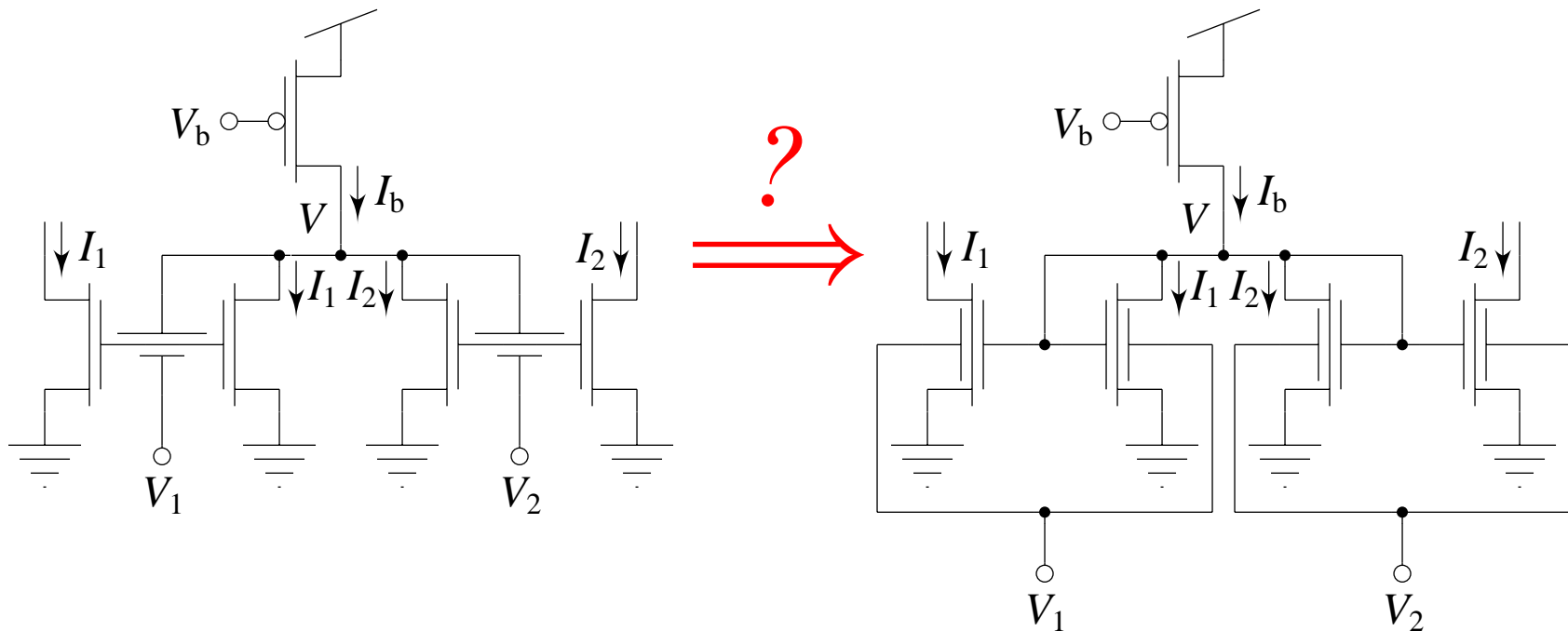A Double-Gate MOS Inverted Differential Pair?



► Requirements for DGMOS version to be feasible:

- Independent front and back gates
- V_1 and V affect I_1 in a similar manner
- V_2 and V affect I_2 in a similar manner
- V transconductance larger than V_1 and V_2
- V_1 , V_2 , and $V \geq$ ground