
Synthesis of Multiple-Input Tanslinear Element Log-Domain Filters

Bradley A. Minch


Laboratory of Analogical Information Processing
School of Electrical Engineering
Cornell University
Ithaca, NY 14853–5401

minch@ee.cornell.edu
<http://www.ee.cornell.edu/~minch>



The Multiple-Input Translinear Element

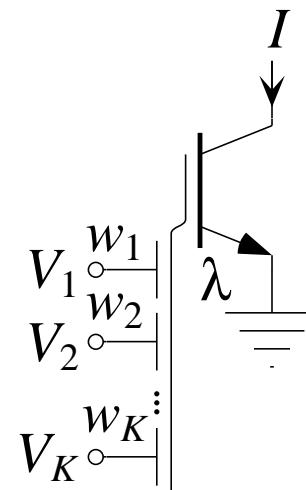
$$I = I_s \exp \left[\sum_{k=1}^K \frac{w_k V_k}{U_T} \right]$$




- The MITE has K *trans*conductances, each of which is *linear* in the output current, I :

$$\begin{aligned} g_k &= \frac{\partial I}{\partial V_k} \\ &= \frac{w_k}{U_T} I_s \exp \left[\sum_{k=1}^K \frac{w_k V_k}{U_T} \right] \\ &= \frac{w_k}{U_T} I \end{aligned}$$


MITE Implementations

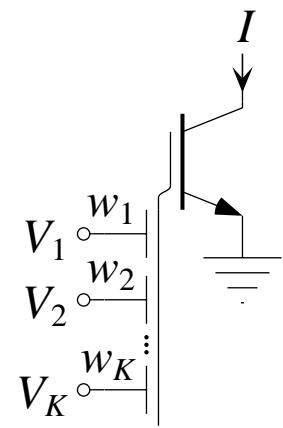


MITE Implementations

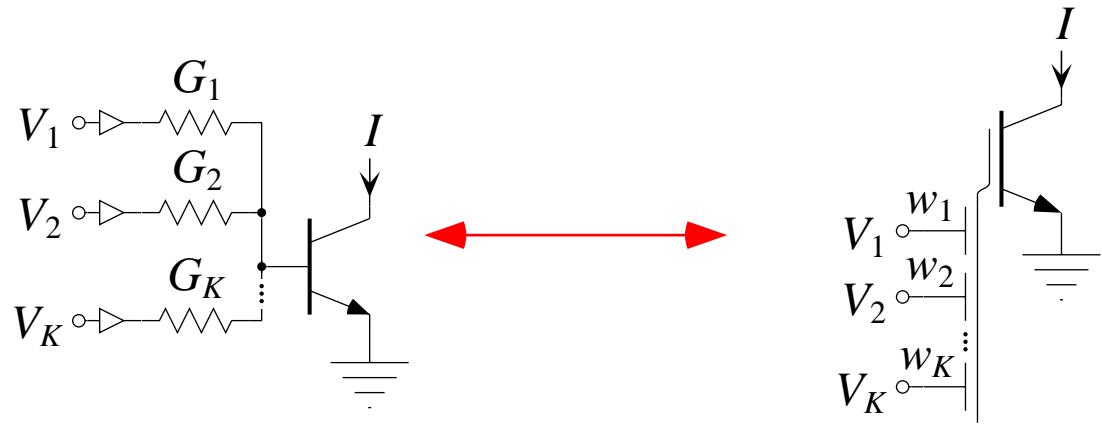


MITE Implementations

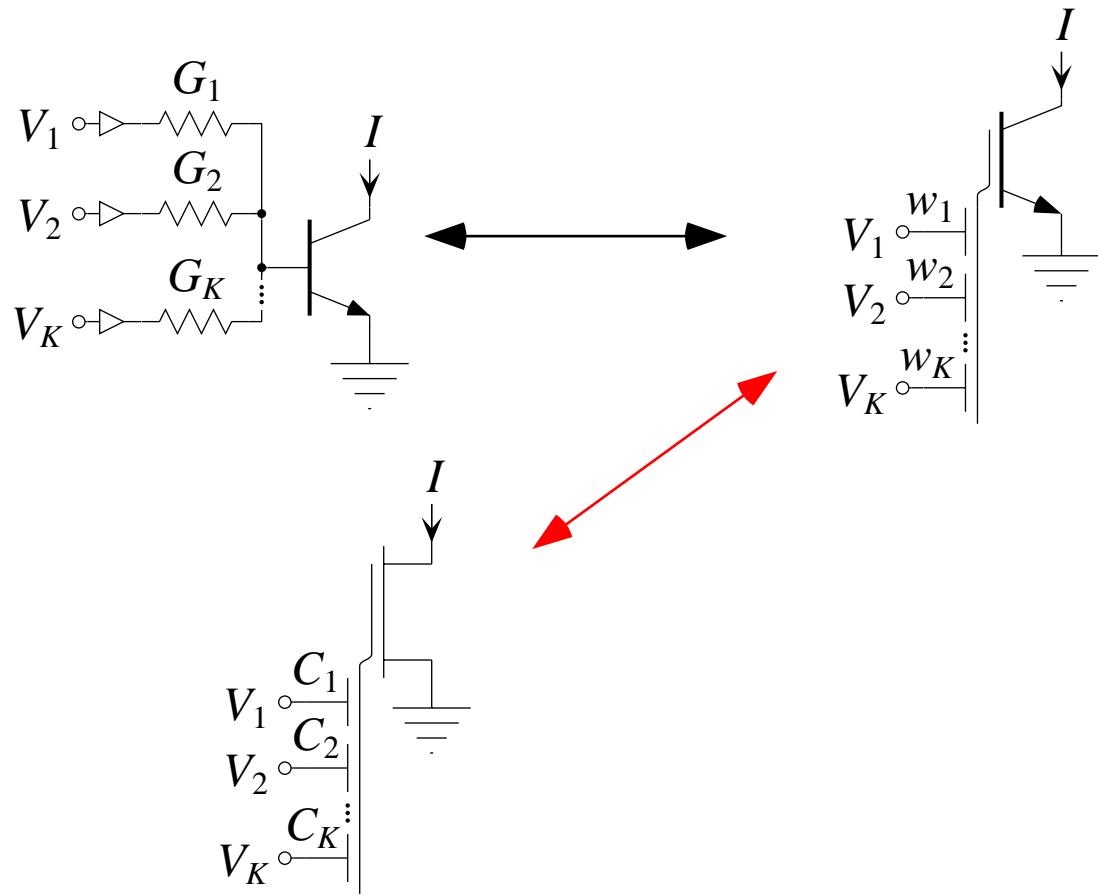


MITE Implementations

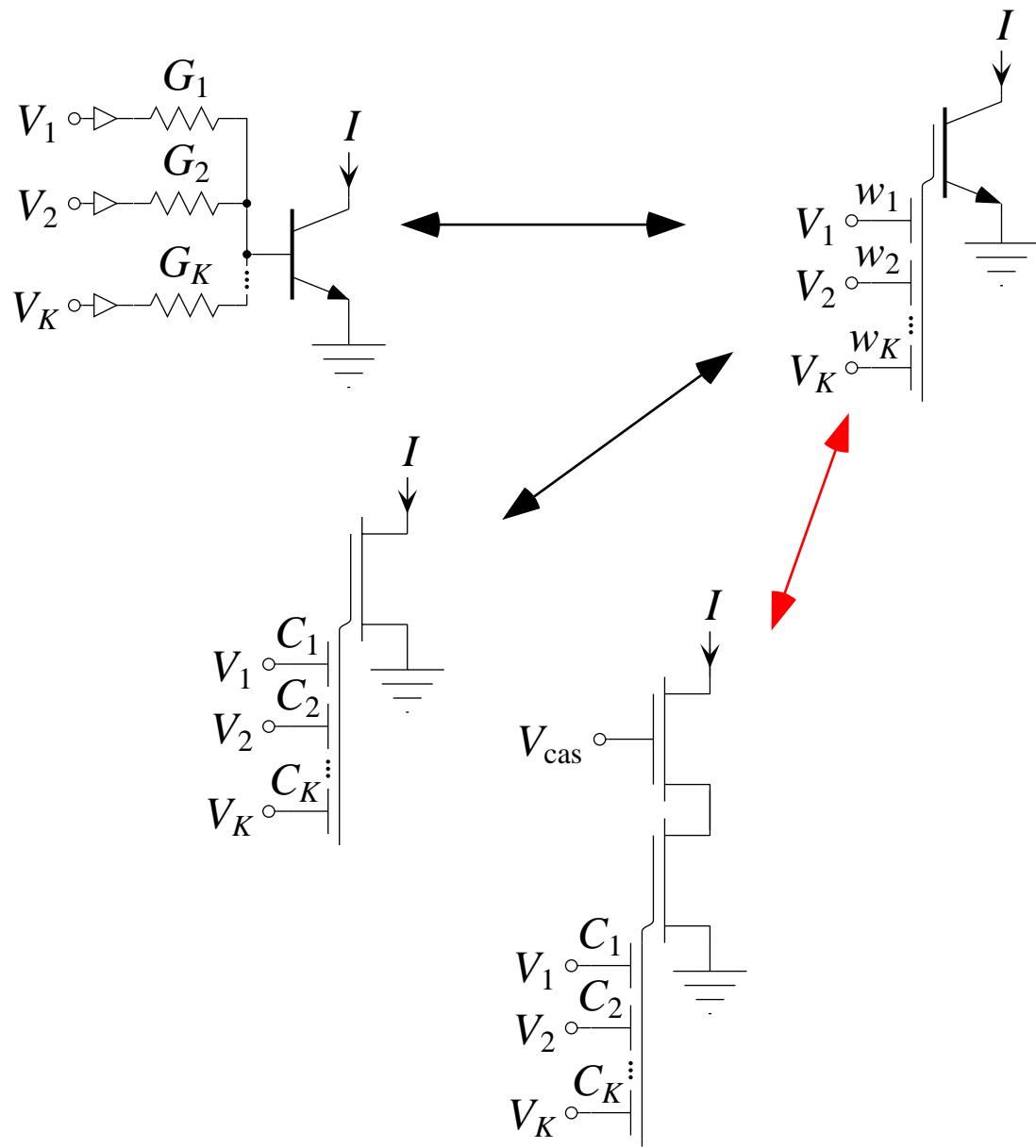


MITE Implementations

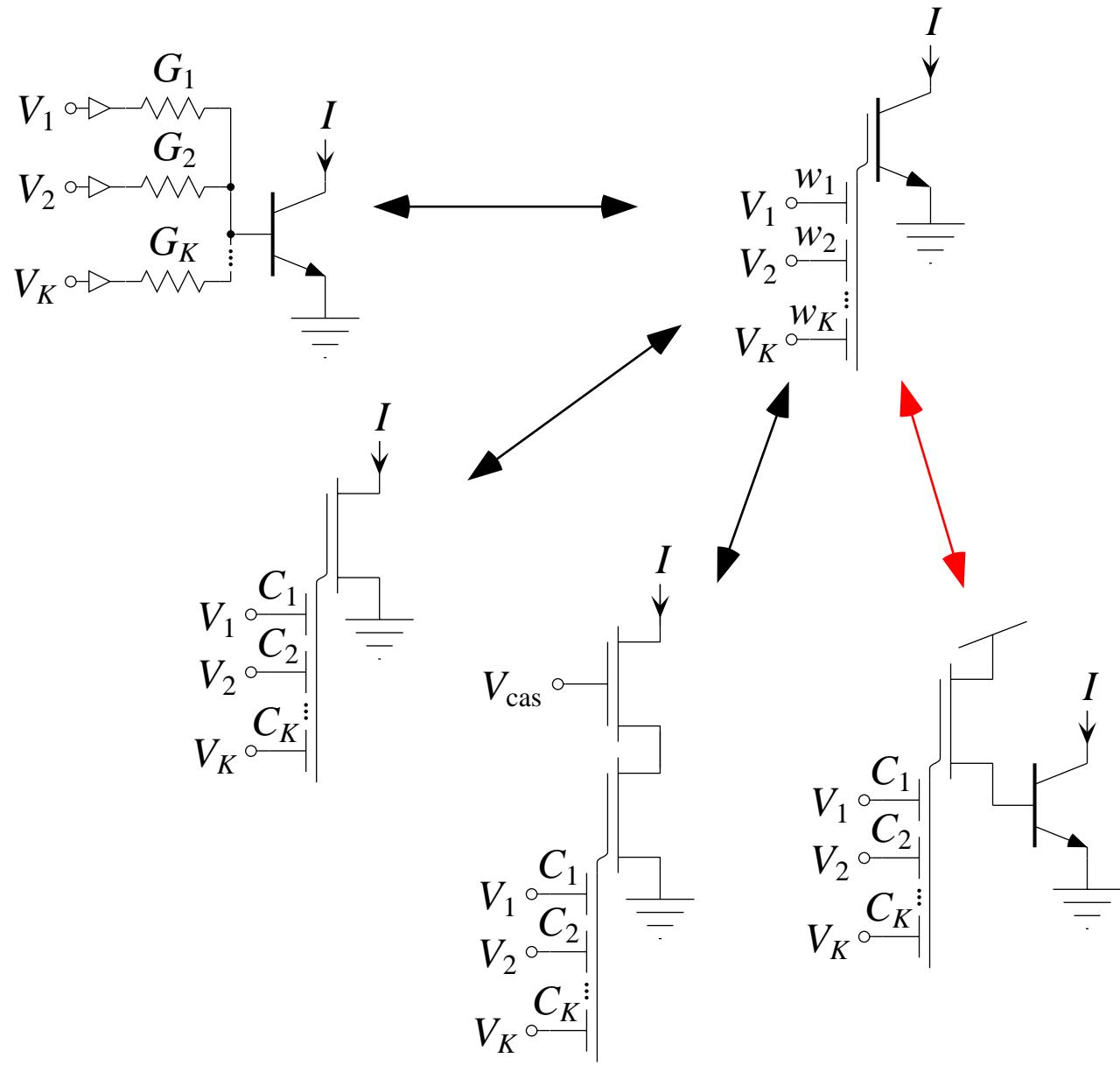


MITE Implementations

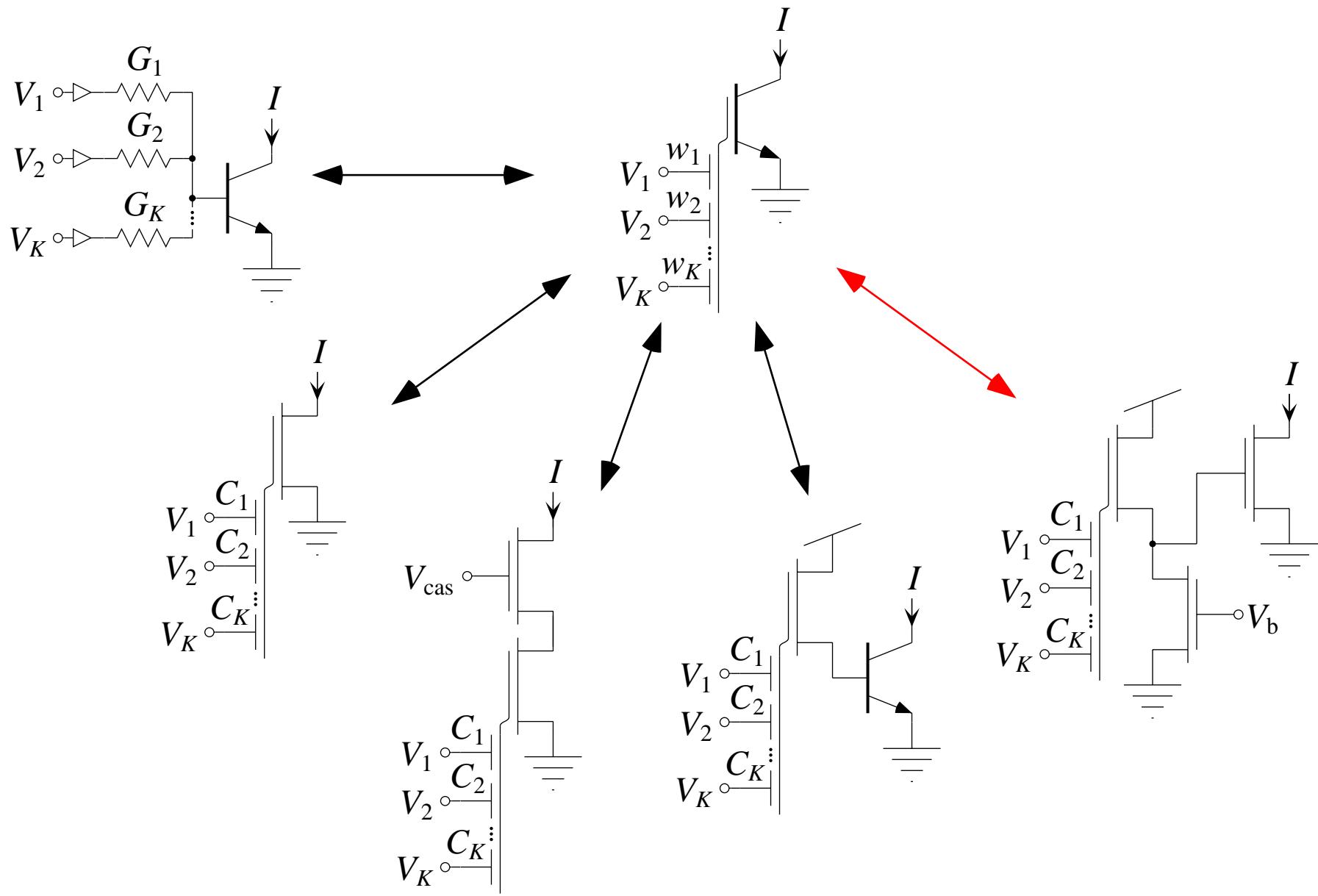


MITE Implementations

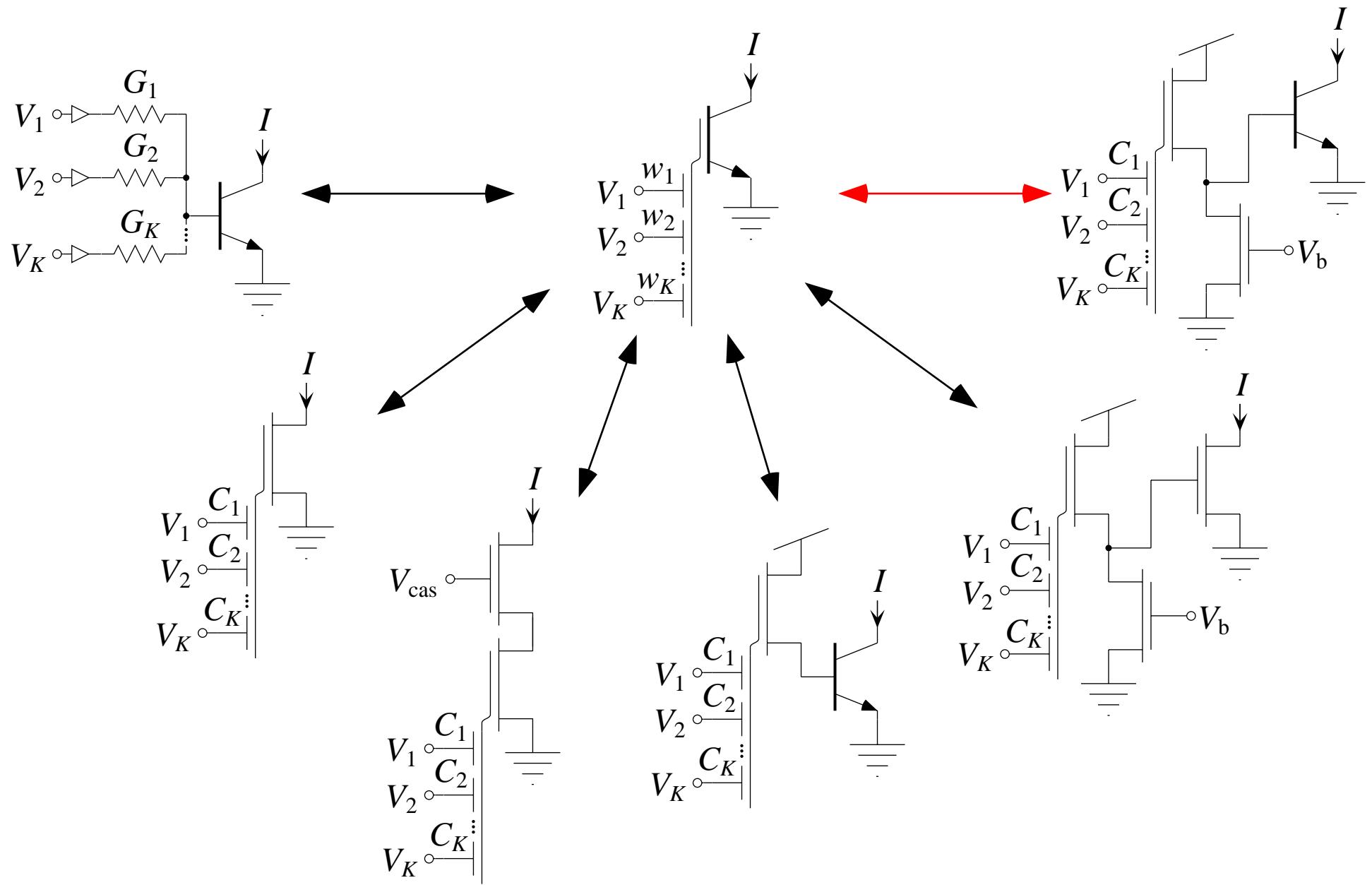

MITE Implementations

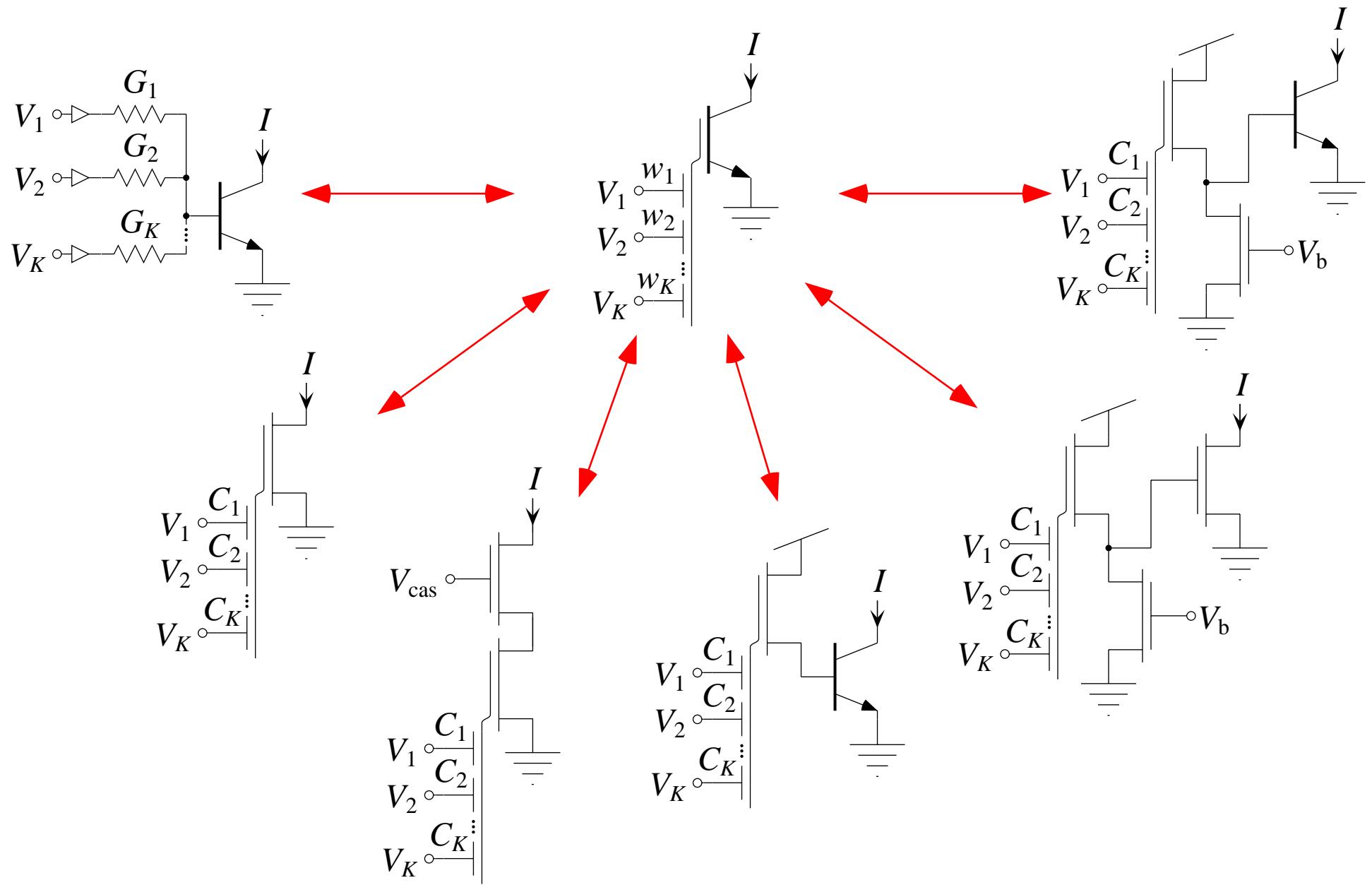

MITE Log-Domain Filters: Building Block

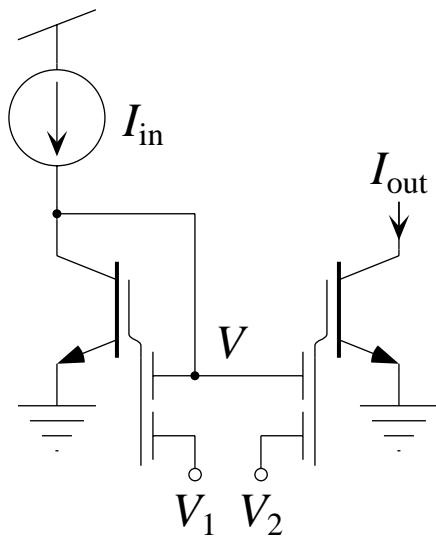


$$I_{\text{in}} = I_s e^{w(V+V_1)/U_T}$$

$$I_{\text{out}} = I_s e^{w(V+V_2)/U_T}$$

$$\Rightarrow \frac{I_{\text{out}}}{I_{\text{in}}} = \frac{\cancel{I_s} \cancel{e^{wV/U_T}}}{\cancel{I_s} \cancel{e^{wV/U_T}}} \frac{e^{wV_2/U_T}}{e^{wV_1/U_T}}$$

$$\Rightarrow \boxed{I_{\text{out}} = I_{\text{in}} e^{w(V_2 - V_1)/U_T}}$$

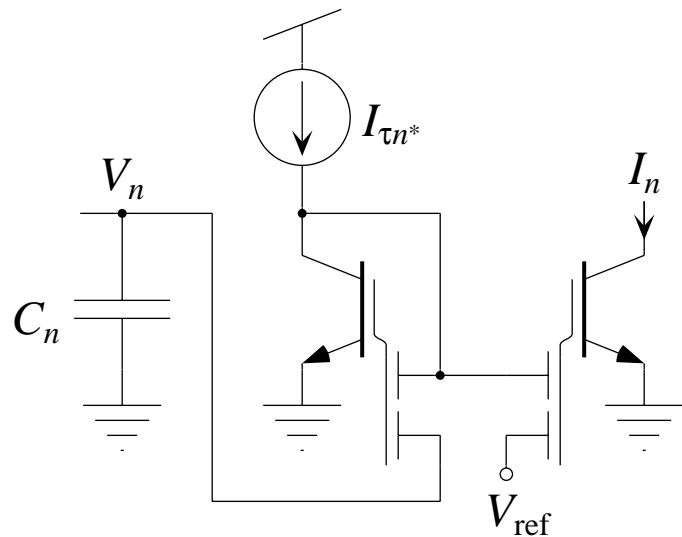MITE Log-Domain Filters: Output Structure



$$\tau_n = \frac{C_n U_T}{w I_{\tau n}}$$



$$I_n = I_{\tau n^*} e^{w(V_{\text{ref}} - V_n)/U_T}$$

$$\frac{dV_n}{dt} = -\frac{U_T}{w} \frac{1}{I_n} \frac{dI_n}{dt}$$

$$\tau_n \frac{dI_n}{dt} = \dots$$

Note: n^* is the index of the state that is excited by the external input.


MITE Log-Domain Filters: Diagonal Terms

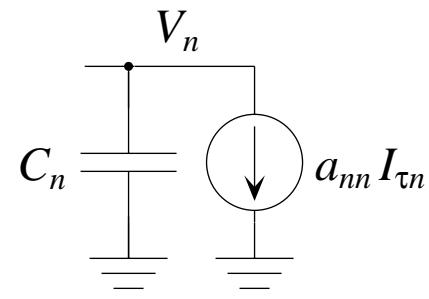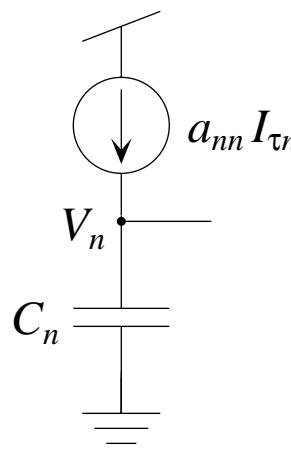

$$\tau_n \frac{dI_n}{dt} = \dots - a_{nn} I_n - \dots$$

$$\tau_n \frac{dI_n}{dt} = \dots + a_{nn} I_n - \dots$$


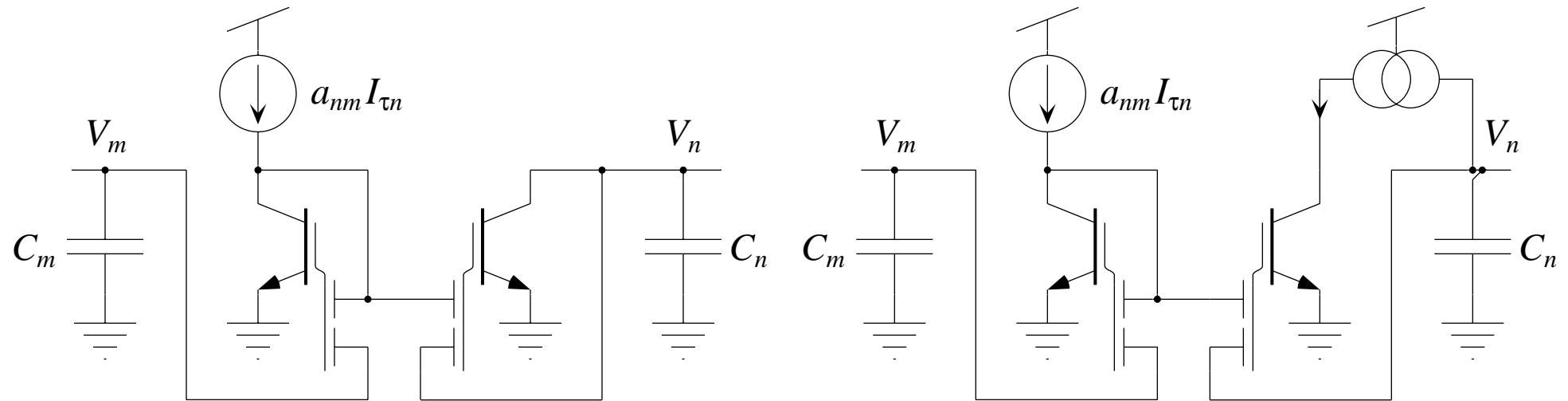
MITE Log-Domain Filters: Off-Diagonal Terms



$$\tau_n \frac{dI_n}{dt} = \dots + a_{nm} I_m - \dots$$

$$\tau_n \frac{dI_n}{dt} = \dots - a_{nm} I_m - \dots$$


MITE Log-Domain Filters: Input Structure

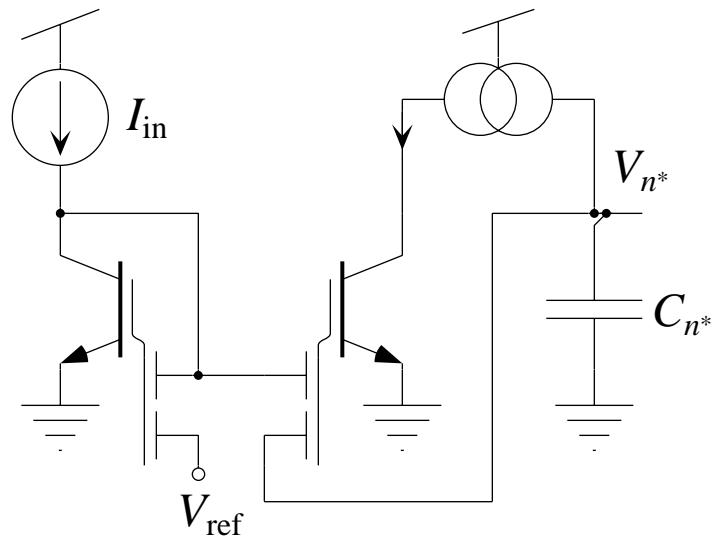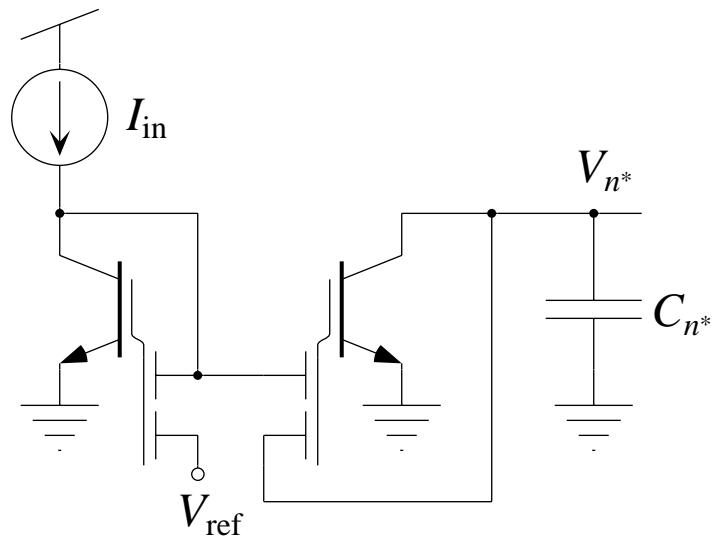

$$\tau_n \frac{dI_n}{dt} = \dots + I_{\text{in}} - \dots$$

$$\tau_n \frac{dI_n}{dt} = \dots - I_{\text{in}} - \dots$$

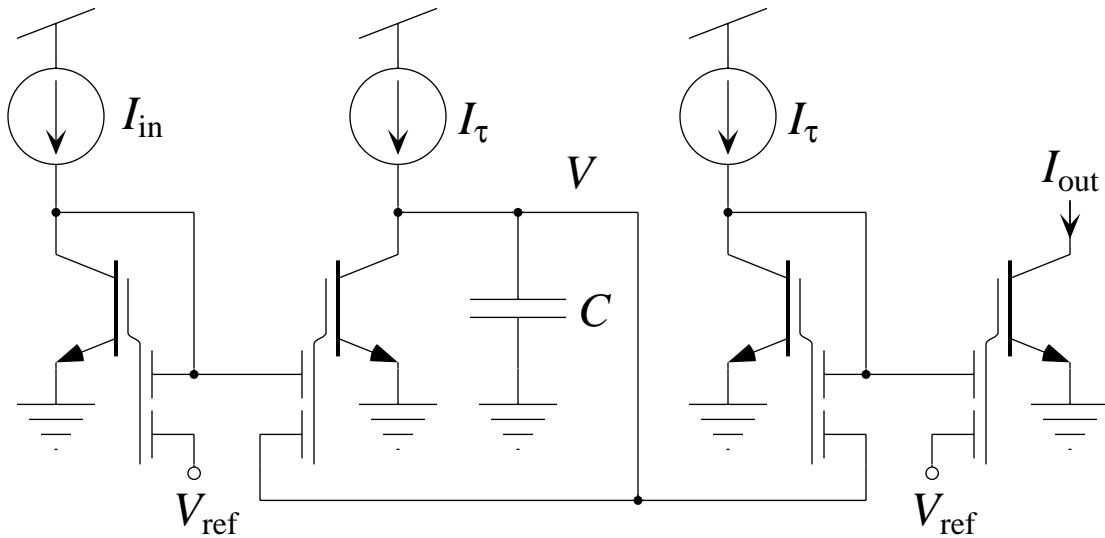MITE Log-Domain Filters: First-Order Low-Pass Filter



$$I_{\text{out}} = I_{\tau} e^{w(V_{\text{ref}} - V)/U_T}$$


$$\Rightarrow \frac{dV}{dt} = -\frac{U_T}{w} \frac{1}{I_{\text{out}}} \frac{dI_{\text{out}}}{dt} \quad \text{and} \quad e^{w(V - V_{\text{ref}})/U_T} = \frac{I_{\tau}}{I_{\text{out}}}$$

$$\text{KCL} \Rightarrow C \frac{dV}{dt} = I_{\tau} - I_{\text{in}} e^{w(V - V_{\text{ref}})/U_T}$$

$$\Rightarrow -\frac{CU_T}{w} \frac{1}{I_{\text{out}}} \frac{dI_{\text{out}}}{dt} = I_{\tau} - I_{\text{in}} \frac{I_{\tau}}{I_{\text{out}}}$$

$$\tau \equiv \frac{CU_T}{wI_{\tau}} \Rightarrow \boxed{\tau \frac{dI_{\text{out}}}{dt} + I_{\text{out}} = I_{\text{in}}}$$

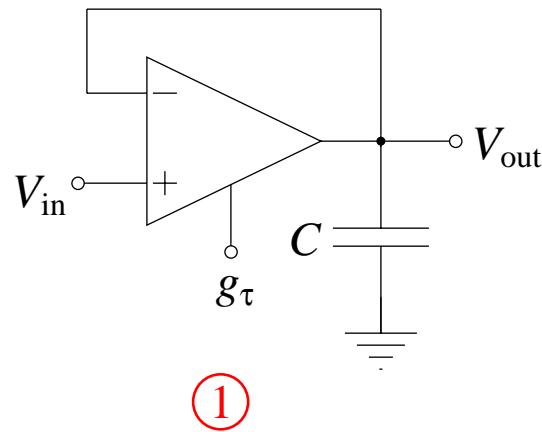
MITE Log-Domain Filter Synthesis: First-Order Low-Pass Filter




$$② \quad C \frac{dV_{\text{out}}}{dt} = g_{\tau} (V_{\text{in}} - V_{\text{out}})$$

$$③ \quad \tau \frac{dV_{\text{out}}}{dt} = V_{\text{in}} - V_{\text{out}}$$
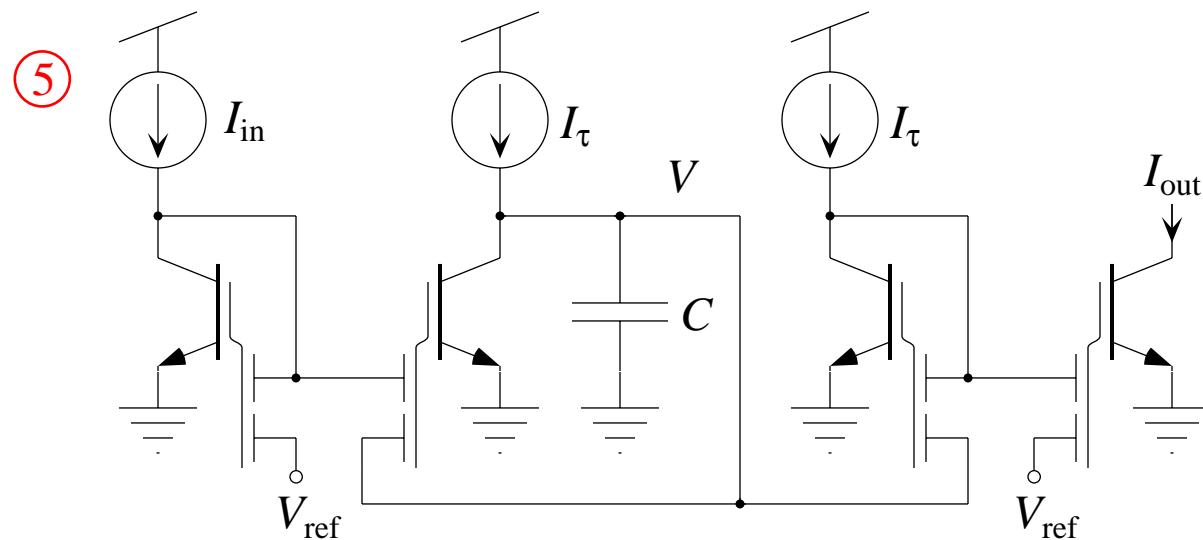
$$④ \quad \tau \frac{dI_{\text{out}}}{dt} = I_{\text{in}} - I_{\text{out}}$$



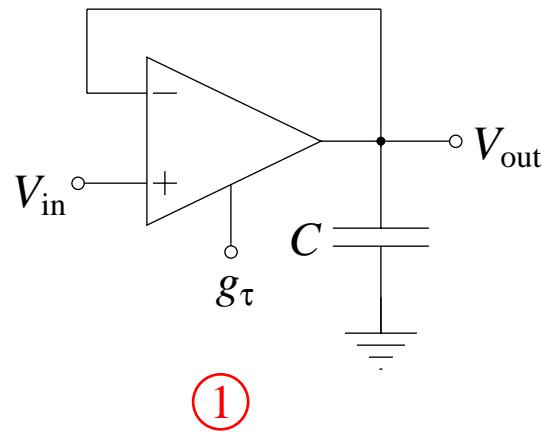
MITE Log-Domain Filter Synthesis: First-Order Low-Pass Filter




$$② \quad C \frac{dV_{\text{out}}}{dt} = g_{\tau} (V_{\text{in}} - V_{\text{out}})$$

$$③ \quad \tau \frac{dV_{\text{out}}}{dt} = V_{\text{in}} - V_{\text{out}}$$
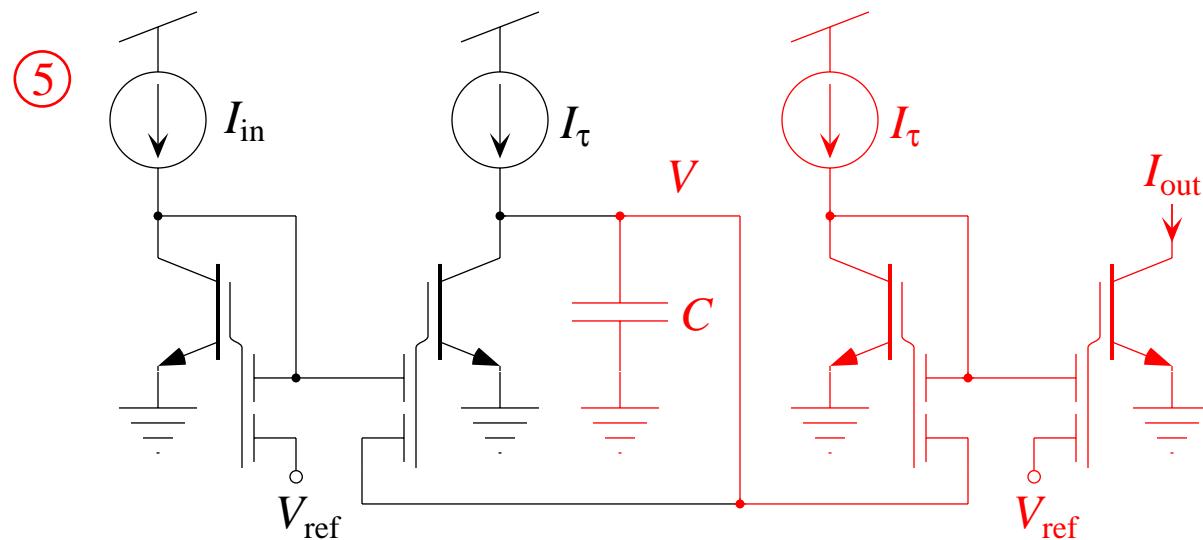
$$④ \quad \tau \frac{dI_{\text{out}}}{dt} = I_{\text{in}} - I_{\text{out}}$$



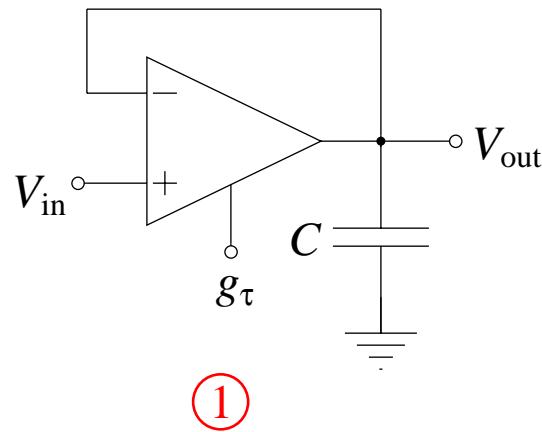
MITE Log-Domain Filter Synthesis: First-Order Low-Pass Filter




$$② \quad C \frac{dV_{\text{out}}}{dt} = g_{\tau} (V_{\text{in}} - V_{\text{out}})$$

$$③ \quad \tau \frac{dV_{\text{out}}}{dt} = V_{\text{in}} - V_{\text{out}}$$
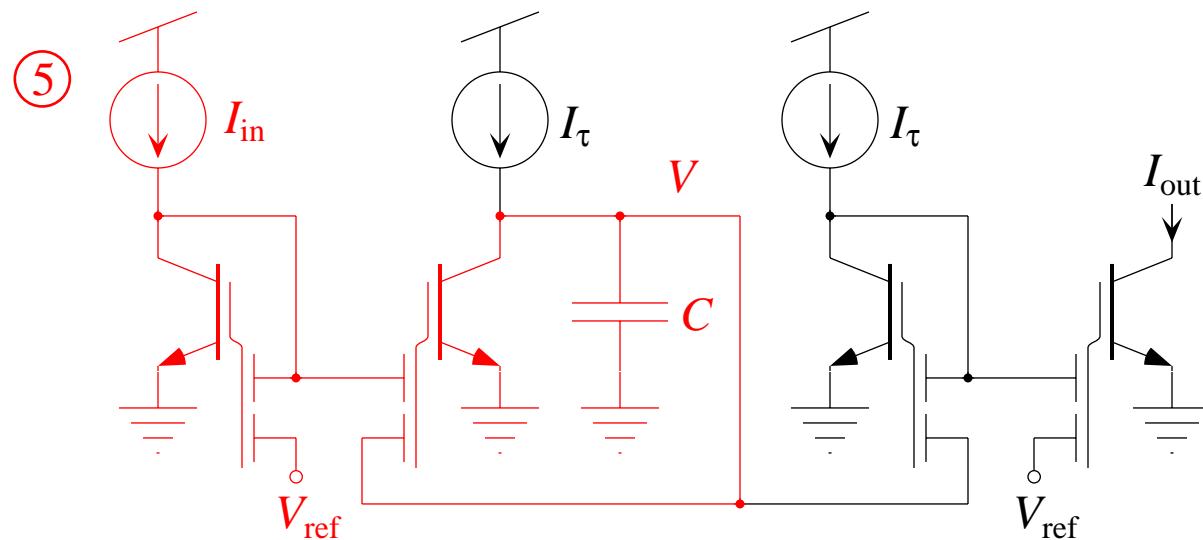
$$④ \quad \tau \frac{dI_{\text{out}}}{dt} = I_{\text{in}} - I_{\text{out}}$$



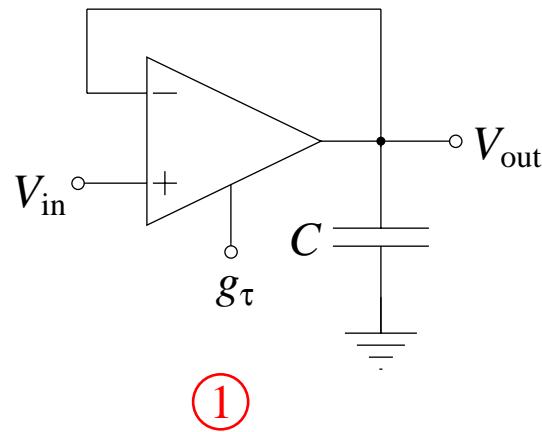
MITE Log-Domain Filter Synthesis: First-Order Low-Pass Filter




$$② \quad C \frac{dV_{\text{out}}}{dt} = g_{\tau} (V_{\text{in}} - V_{\text{out}})$$

$$③ \quad \tau \frac{dV_{\text{out}}}{dt} = V_{\text{in}} - V_{\text{out}}$$
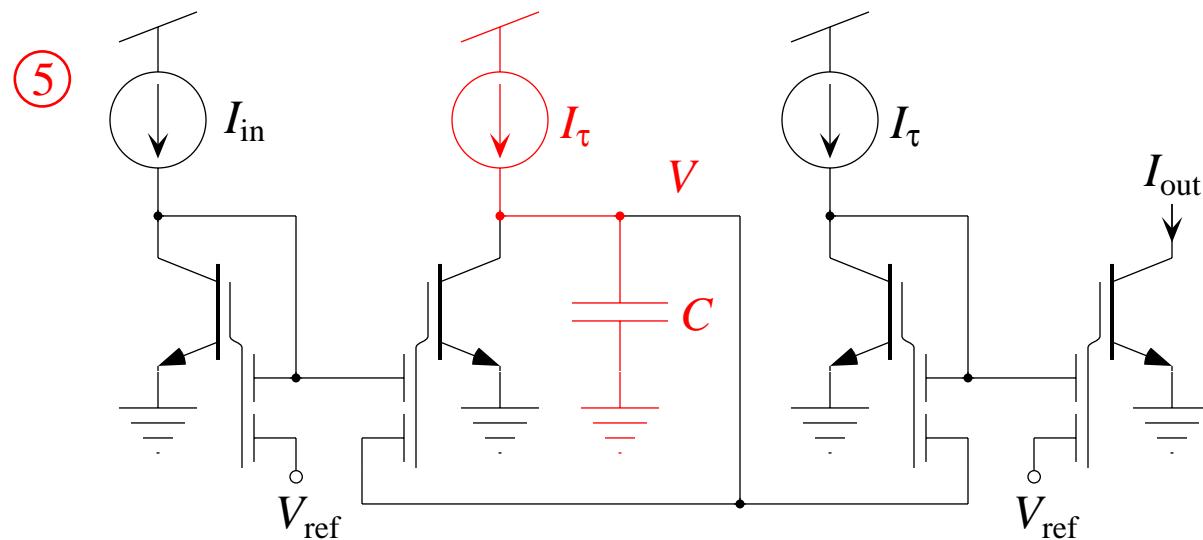
$$④ \quad \tau \frac{dI_{\text{out}}}{dt} = I_{\text{in}} - I_{\text{out}}$$




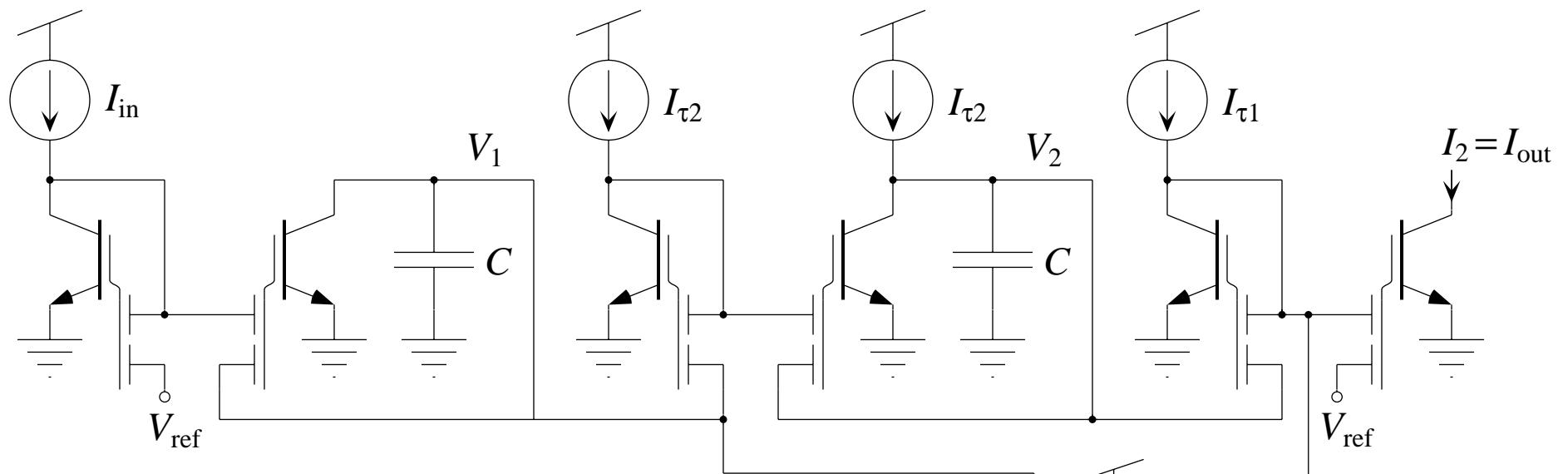MITE Log-Domain Filter: Second-Order Low-Pass Filter




$$H(s) = \frac{I_{\text{out}}(s)}{I_{\text{in}}(s)} = \frac{1}{1 + \tau_1 s + \tau_1 \tau_2 s^2} = \frac{1}{1 + \frac{\tau s}{Q} + (\tau s)^2}$$
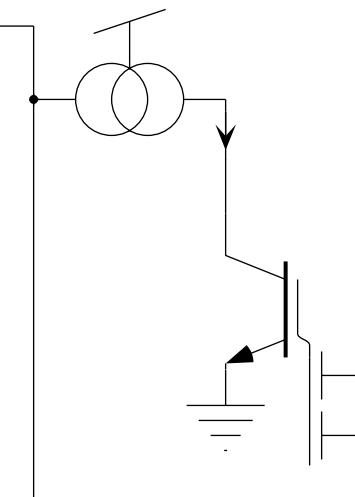
$$\tau_1 = \frac{C U_T}{w I_{\tau_1}} \quad \tau_2 = \frac{C U_T}{w I_{\tau_2}} \quad \tau \equiv \sqrt{\tau_1 \tau_2} \quad Q \equiv \sqrt{\frac{\tau_2}{\tau_1}}$$



MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter

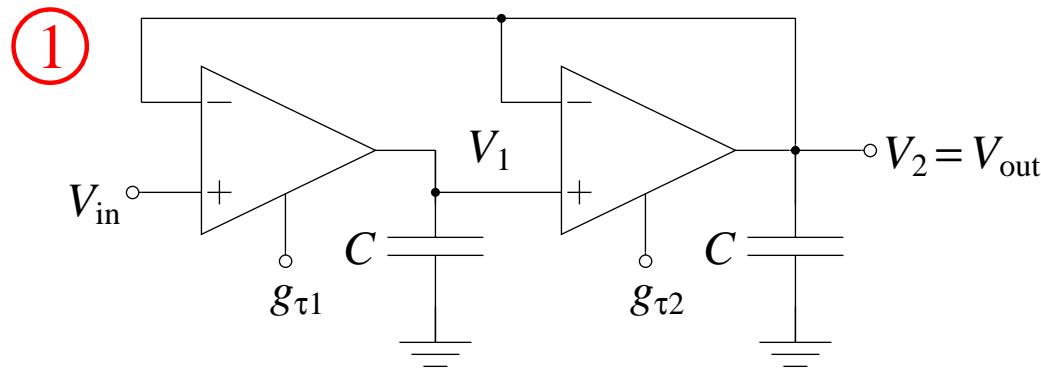
$$\textcircled{2} \begin{cases} C \frac{dV_1}{dt} = g_{\tau 1} (V_{\text{in}} - V_2) \\ C \frac{dV_2}{dt} = g_{\tau 2} (V_1 - V_2) \end{cases}$$




$$\textcircled{3} \begin{cases} \tau_1 \frac{dV_1}{dt} = V_{\text{in}} - V_2 \\ \tau_2 \frac{dV_2}{dt} = V_1 - V_2 \end{cases}$$

$$\textcircled{4} \begin{cases} \tau_1 \frac{dI_1}{dt} = I_{\text{in}} - I_2 \\ \tau_2 \frac{dI_2}{dt} = I_1 - I_2 \end{cases}$$

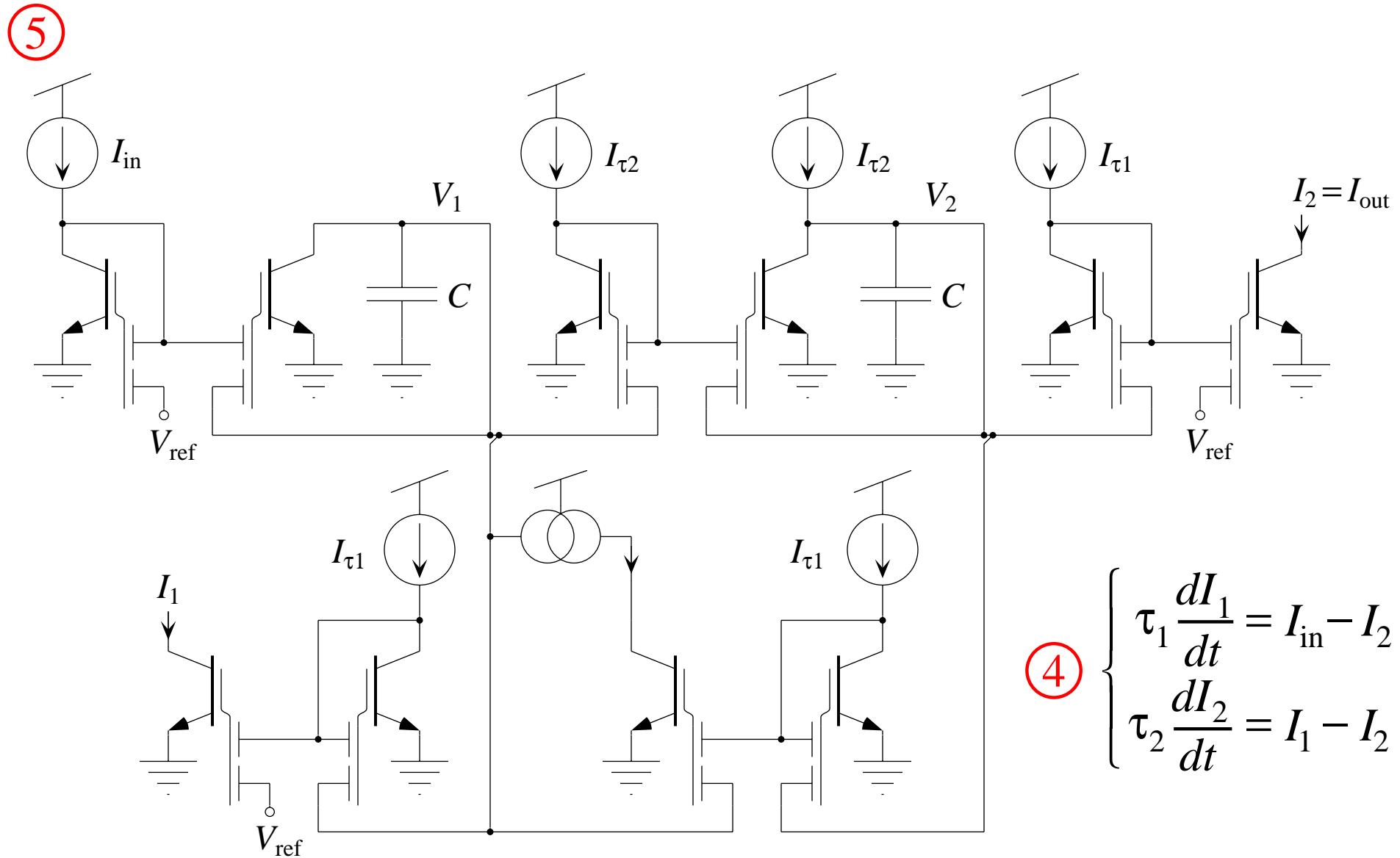
MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter



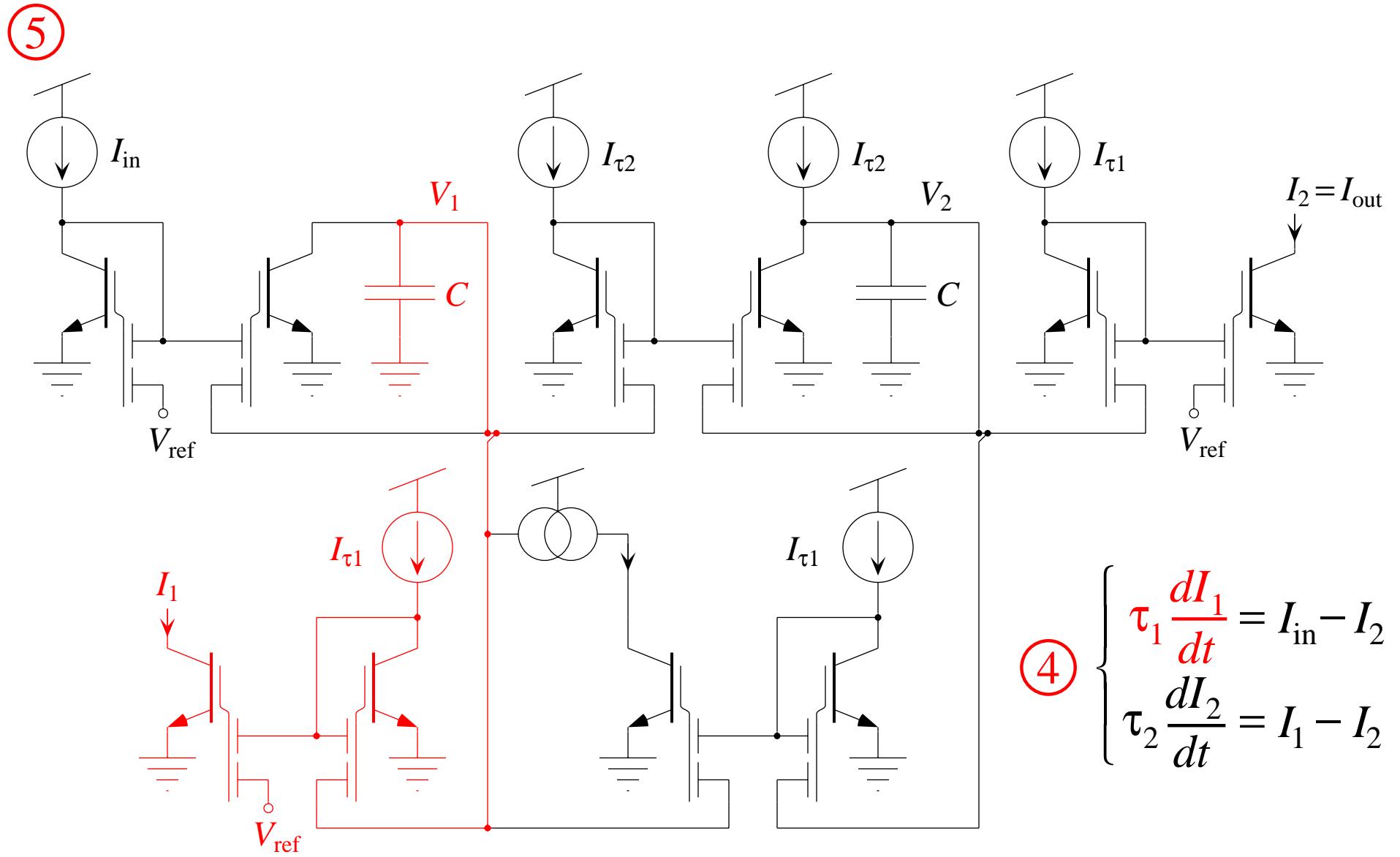
MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter



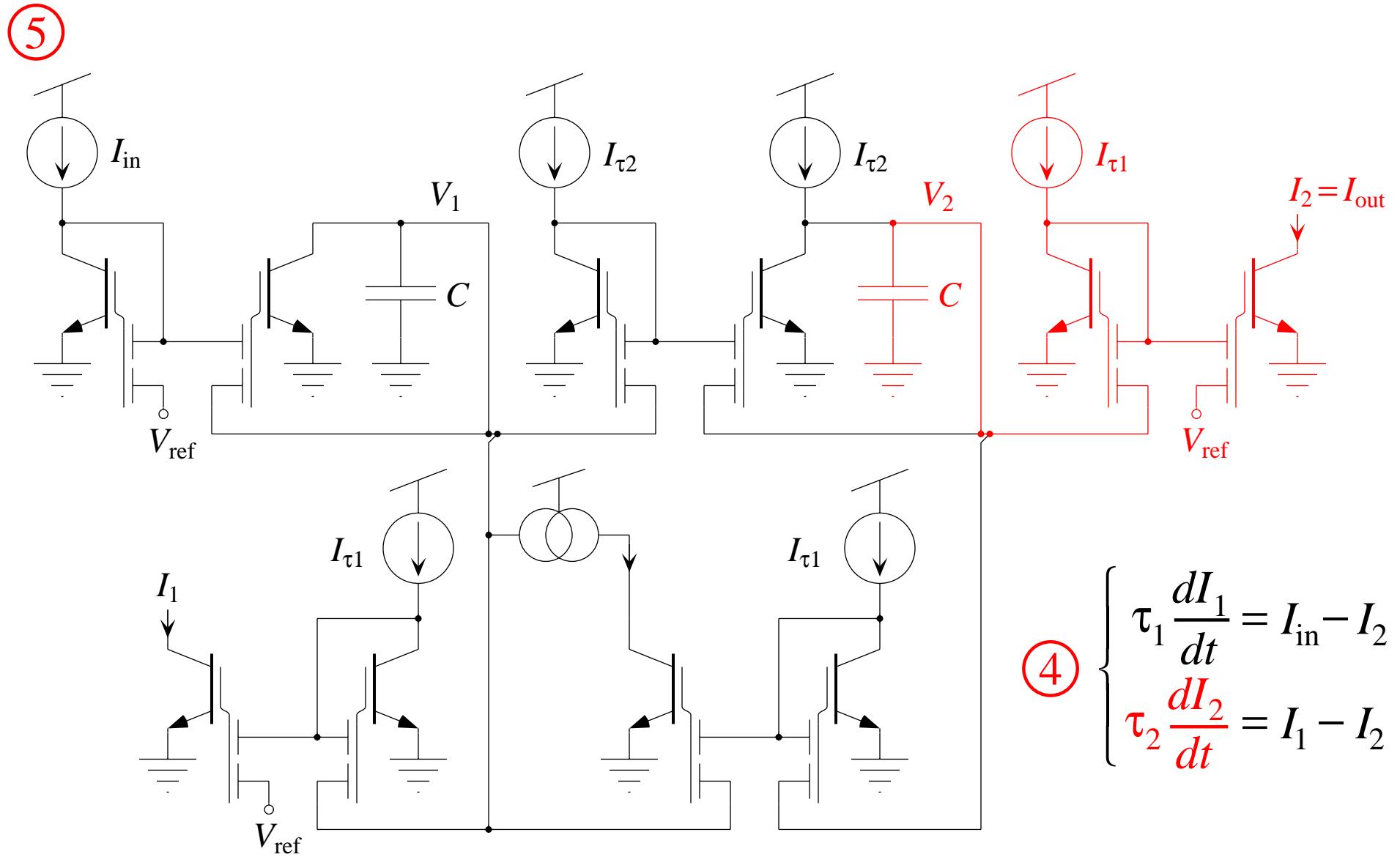
MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter



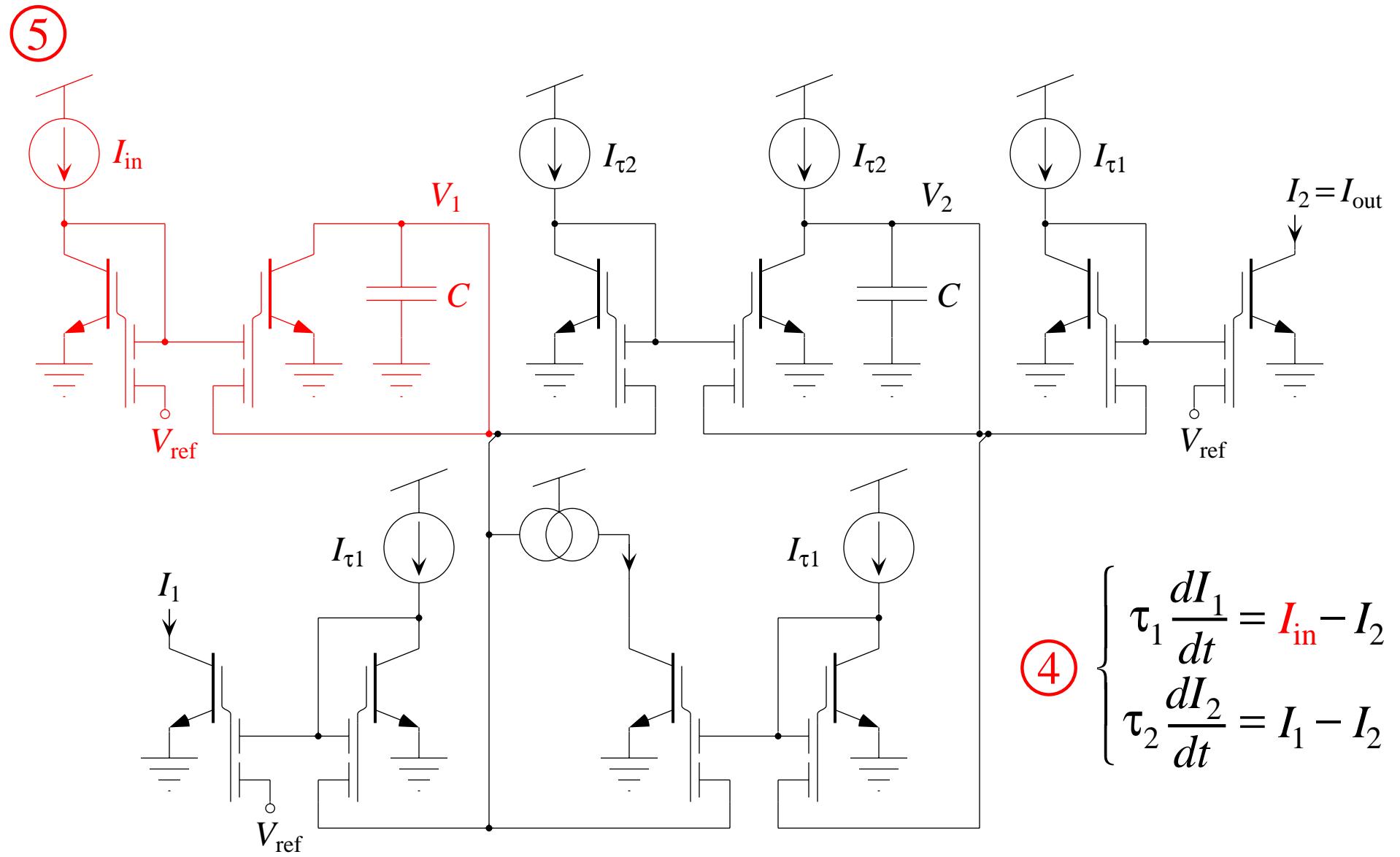
MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter



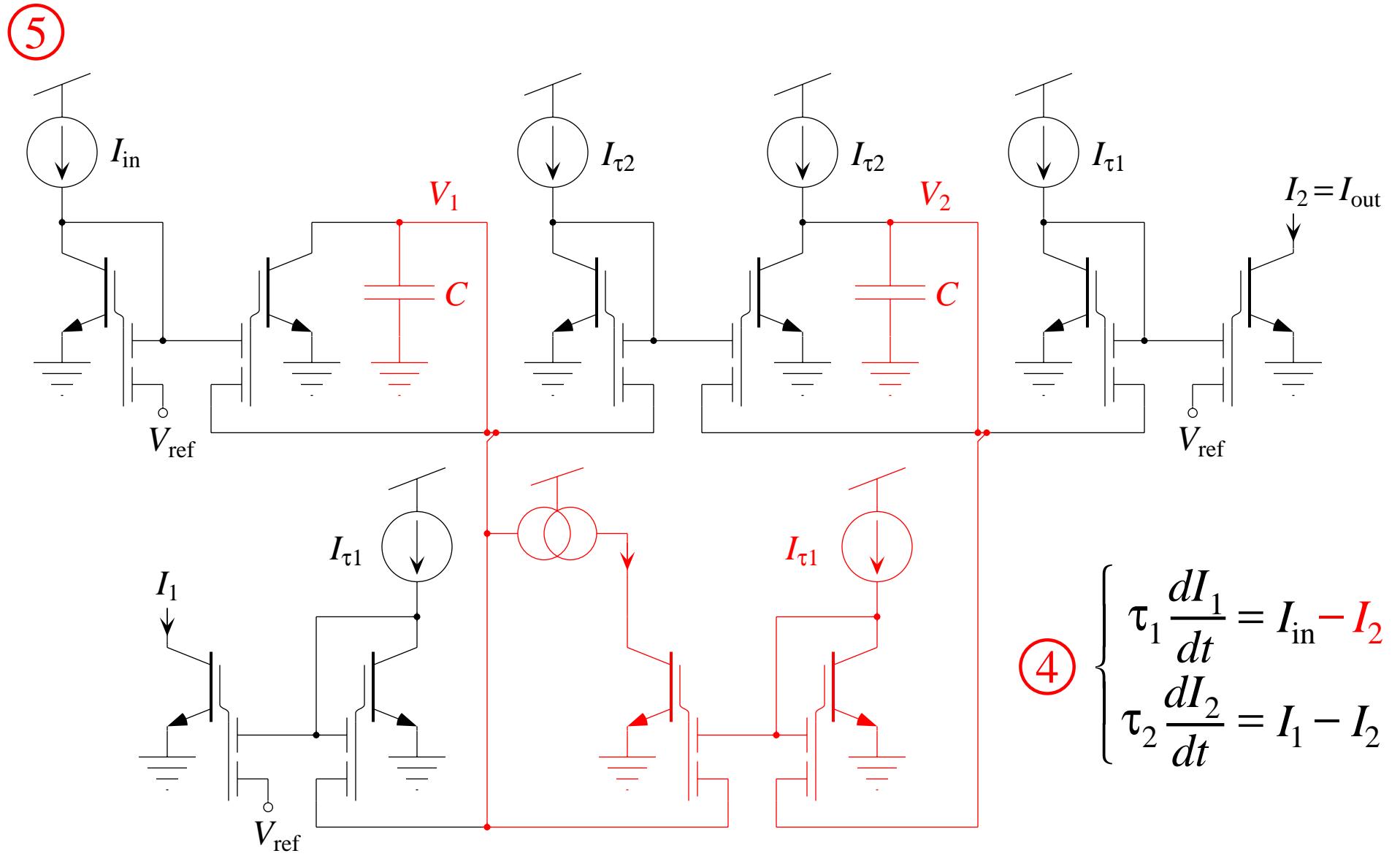
MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter



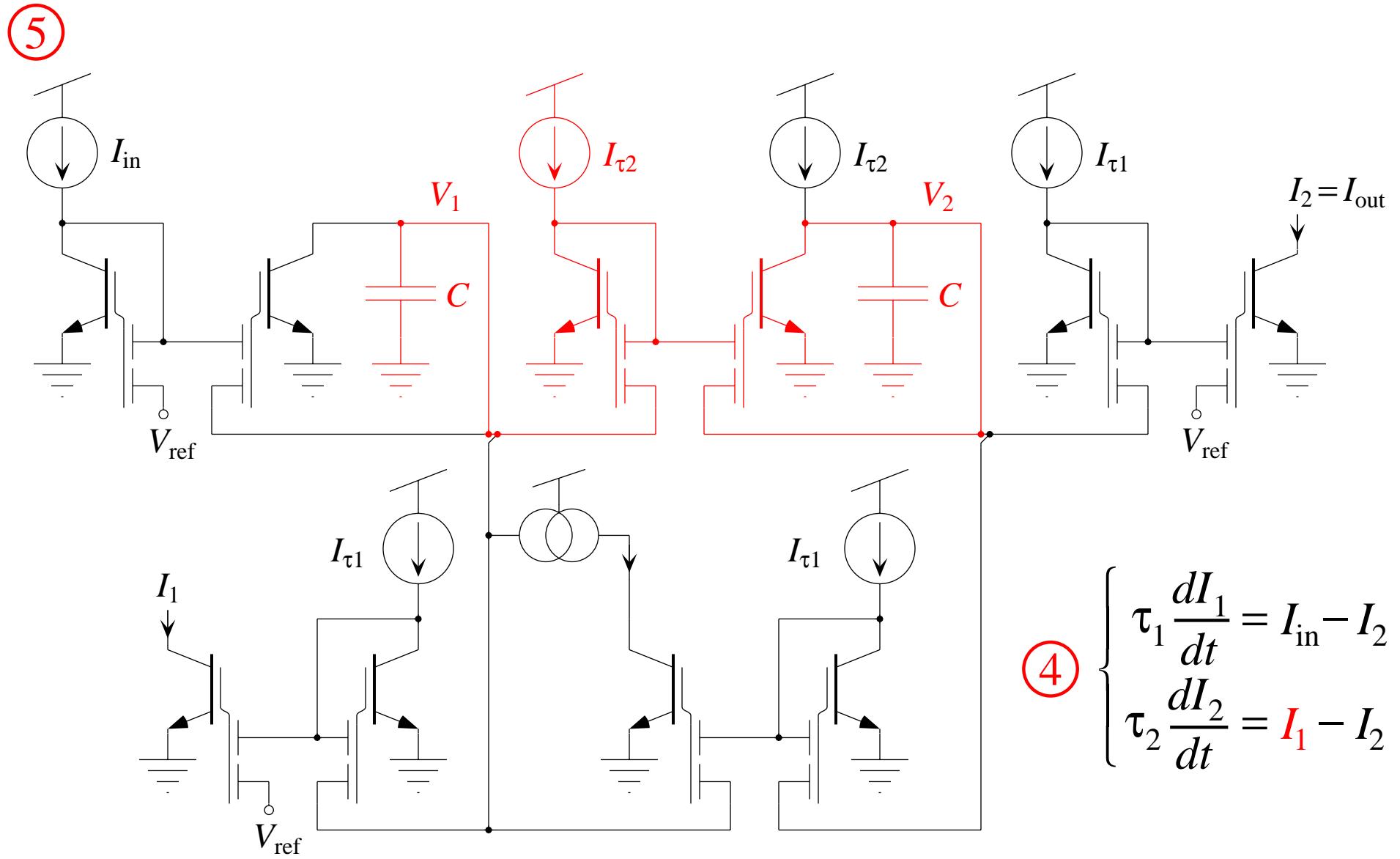MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter




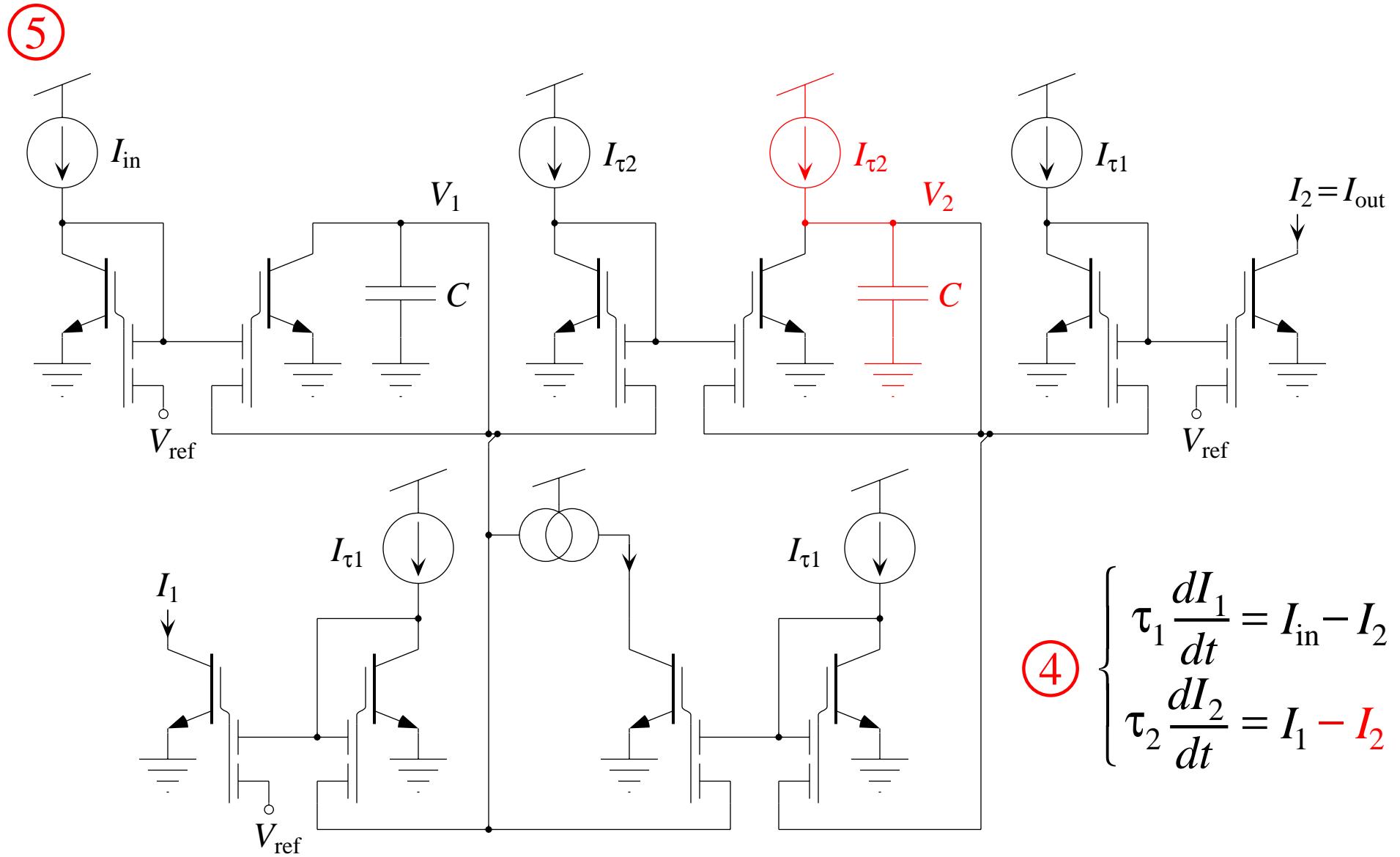MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter




MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter


⑥

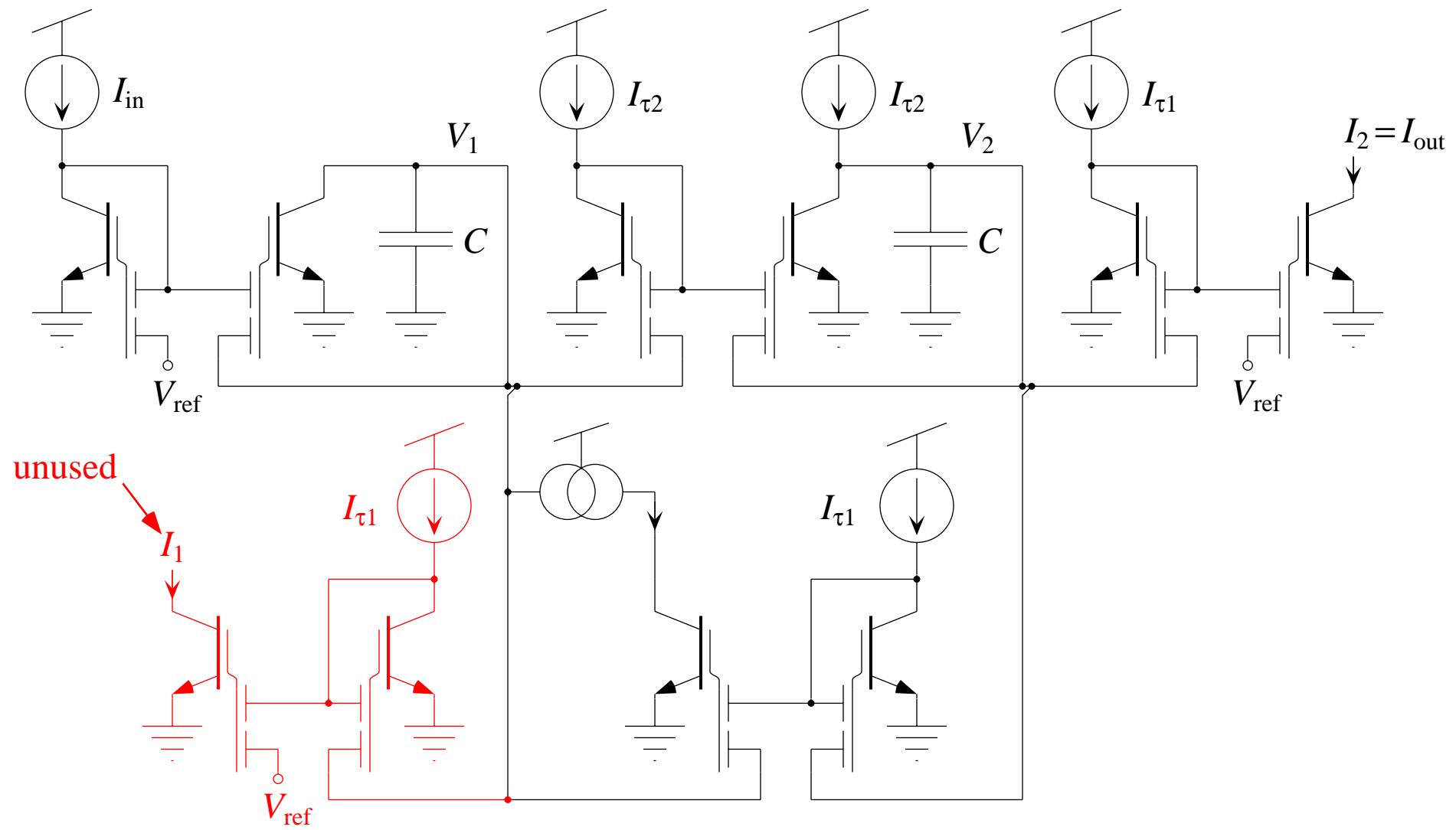

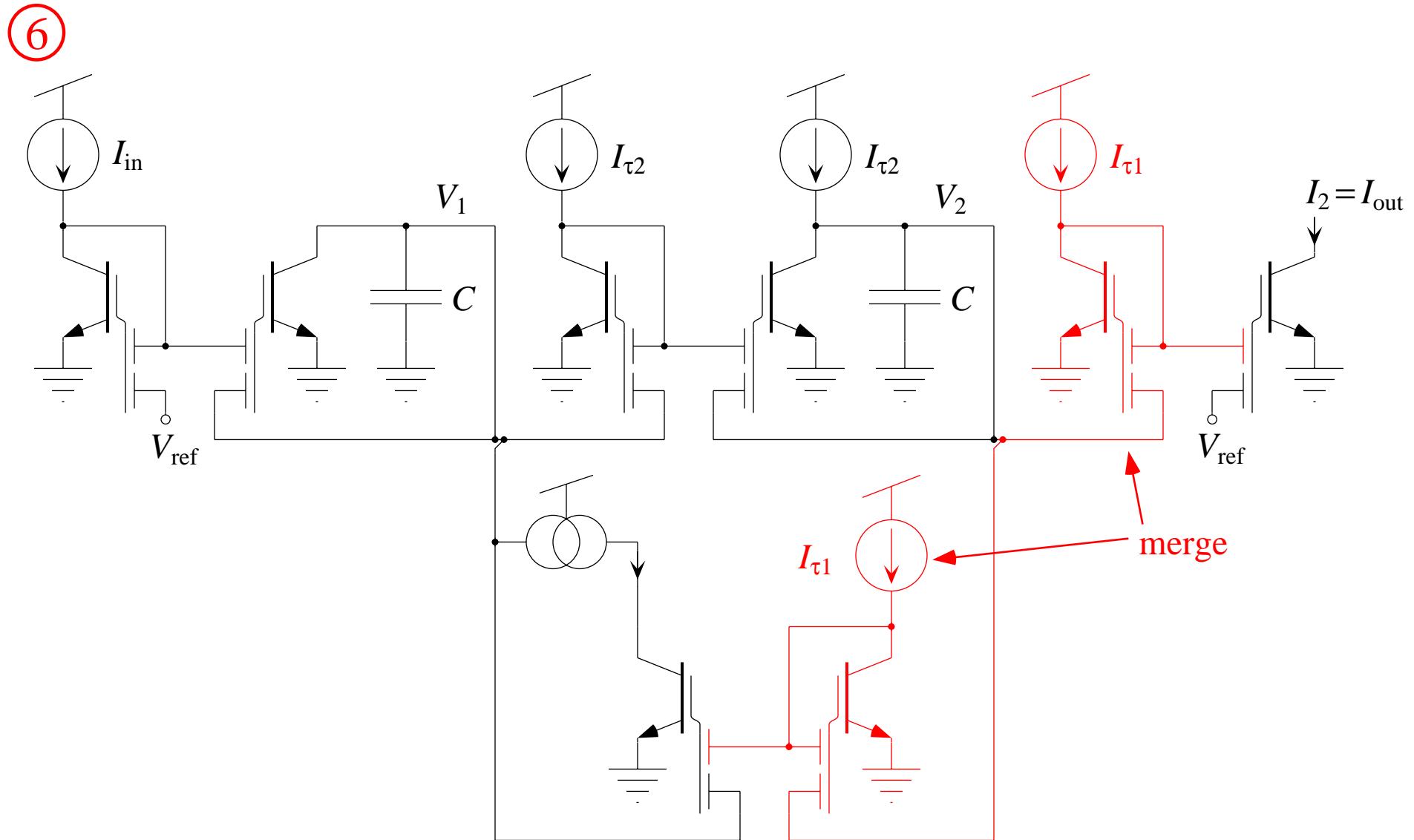
MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter



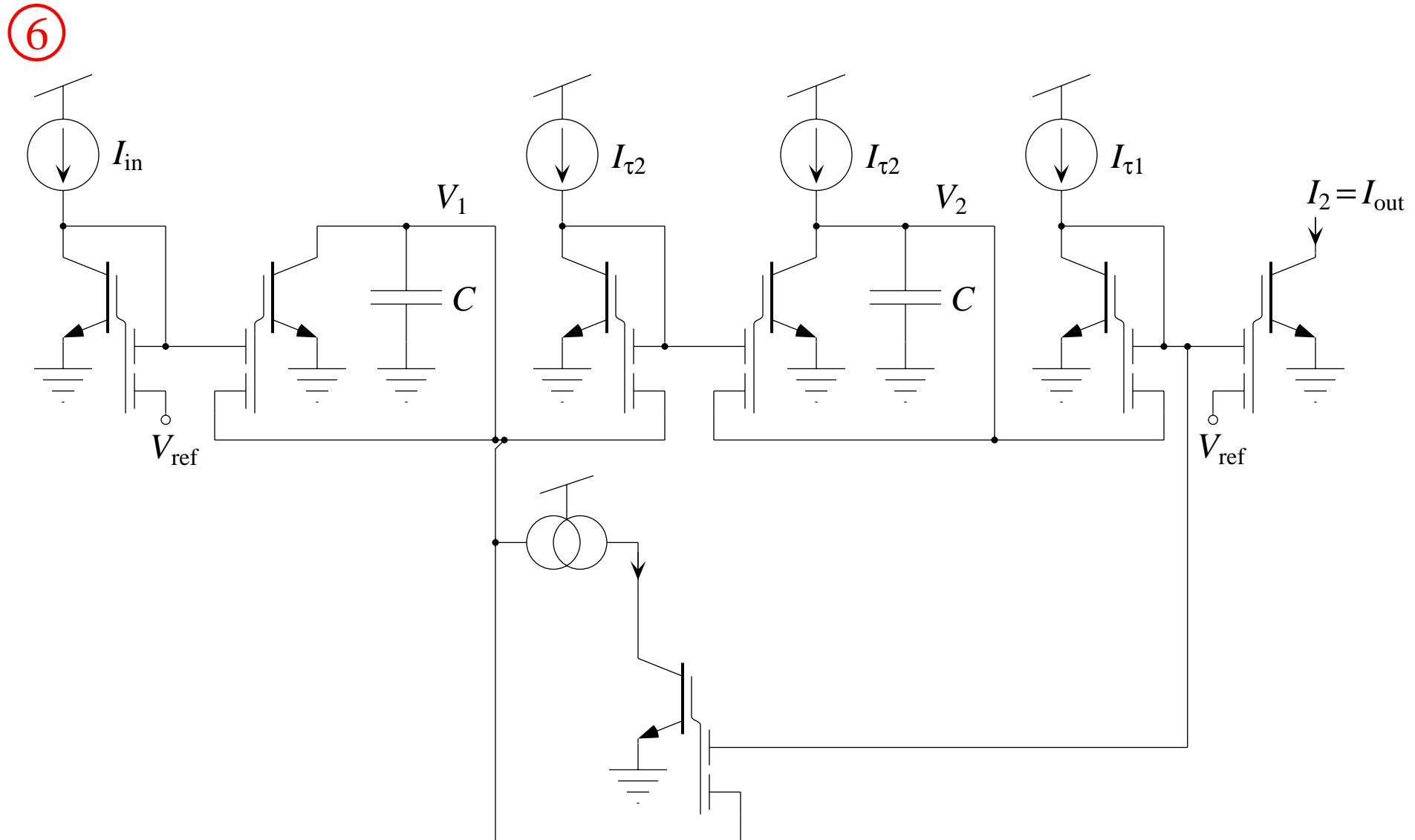MITE Log-Domain Filter Synthesis: Second-Order Low-Pass Filter




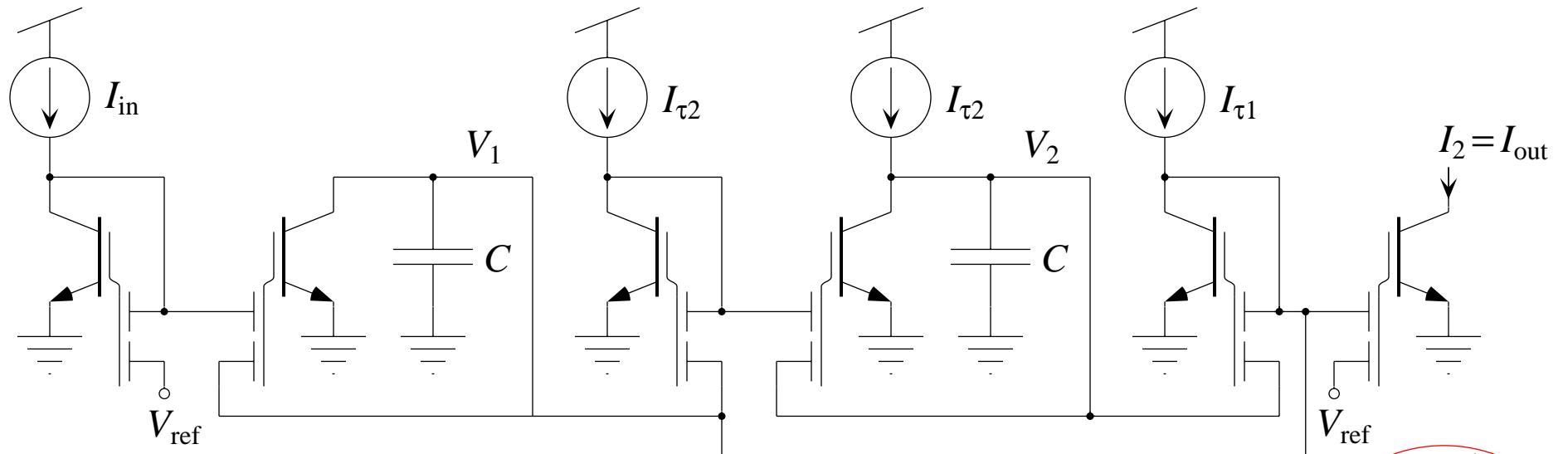MITE Log-Domain Filters : Second-Order Low-Pass Filter




$$H(s) = \frac{I_{\text{out}}(s)}{I_{\text{in}}(s)} = \frac{1}{1 + \tau_1 s + \tau_1 \tau_2 s^2} = \frac{1}{1 + \frac{\tau s}{Q} + (\tau s)^2}$$
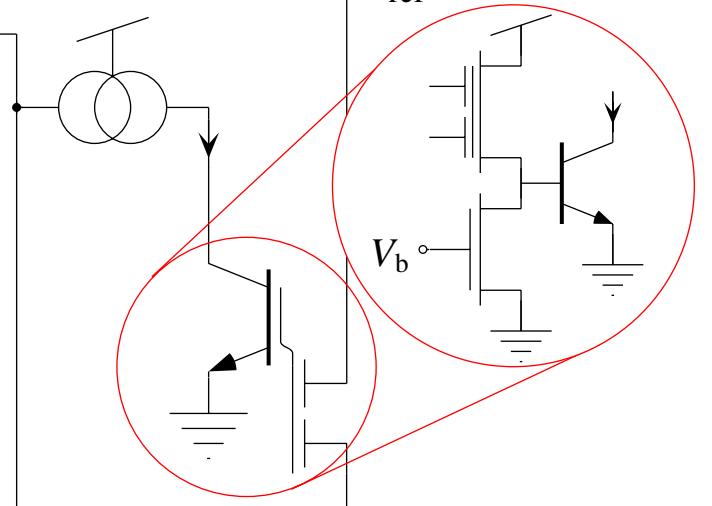
$$\tau_1 = \frac{C U_T}{w I_{\tau_1}} \quad \tau_2 = \frac{C U_T}{w I_{\tau_2}} \quad \tau \equiv \sqrt{\tau_1 \tau_2} \quad Q \equiv \sqrt{\frac{\tau_2}{\tau_1}}$$



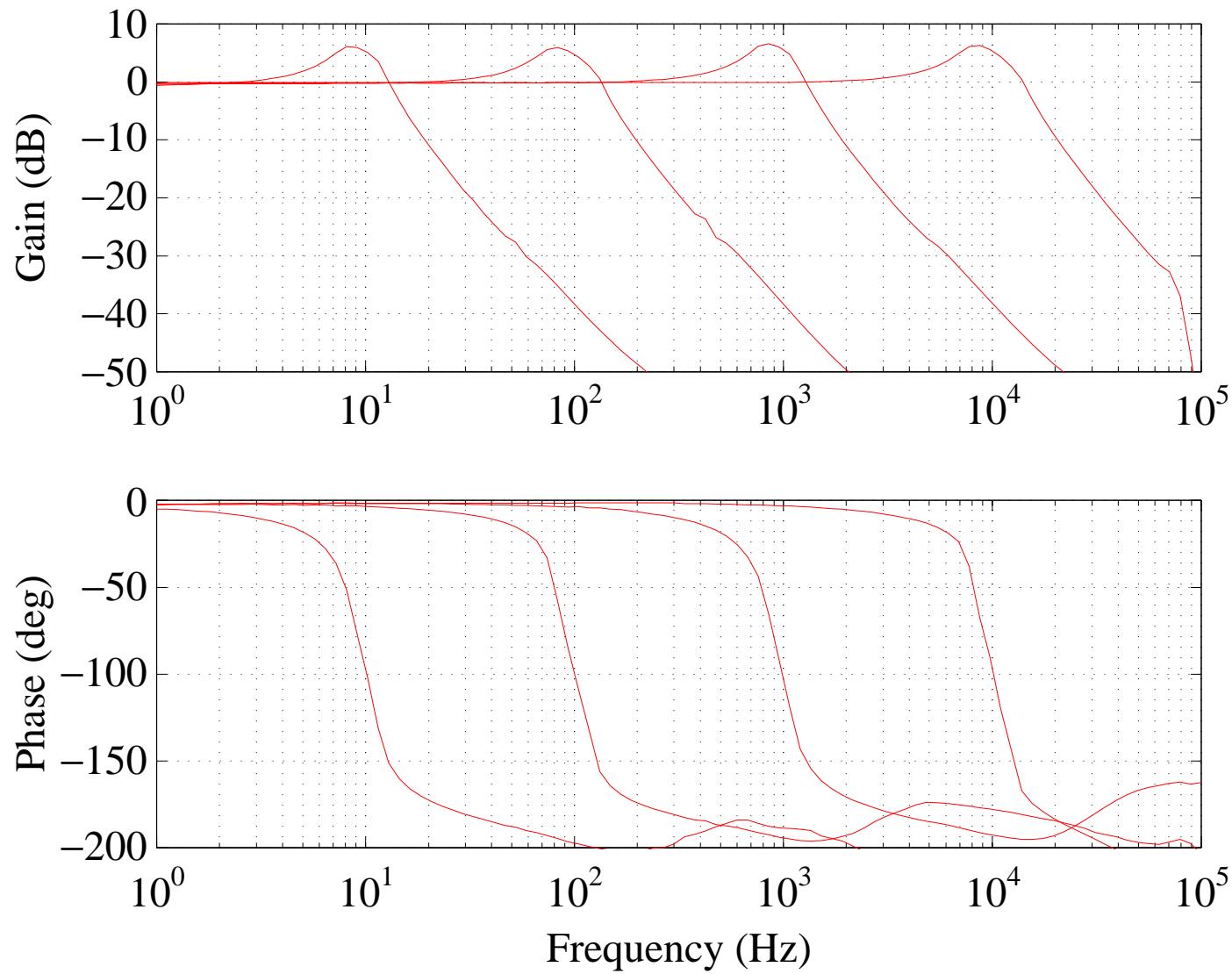MITE Second-Order Low-Pass Log-Domain Filter: Tuning τ



MITE Second-Order Low-Pass Log-Domain Filter: Tuning Q

