

Synthesis of Dynamic **M**ultiple-**I**nput **T**ranslinear **E**lement Networks


Bradley A. Minch

School of Electrical and Computer Engineering
Cornell University
Ithaca, NY 14853-5401

minch@ee.cornell.edu
<http://www.ee.cornell.edu/~minch>

The Multiple-Input Translinear Element

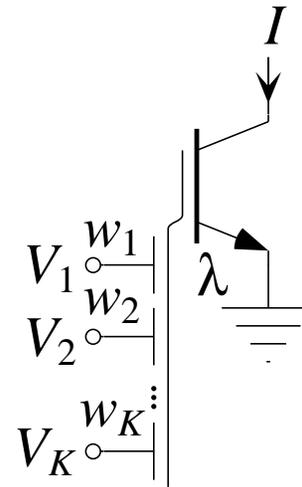
$$I = \lambda I_s \exp \left[\sum_{k=1}^K \frac{w_k V_k}{U_T} \right]$$



- ▶ The MITE has K *trans*conductances, each of which is *linear* in the output current, I :

$$\begin{aligned} g_k &= \frac{\partial I}{\partial V_k} \\ &= \frac{w_k}{U_T} \lambda I_s \exp \left[\sum_{k=1}^K \frac{w_k V_k}{U_T} \right] \\ &= \frac{w_k}{U_T} I \end{aligned}$$


MITE Implementations

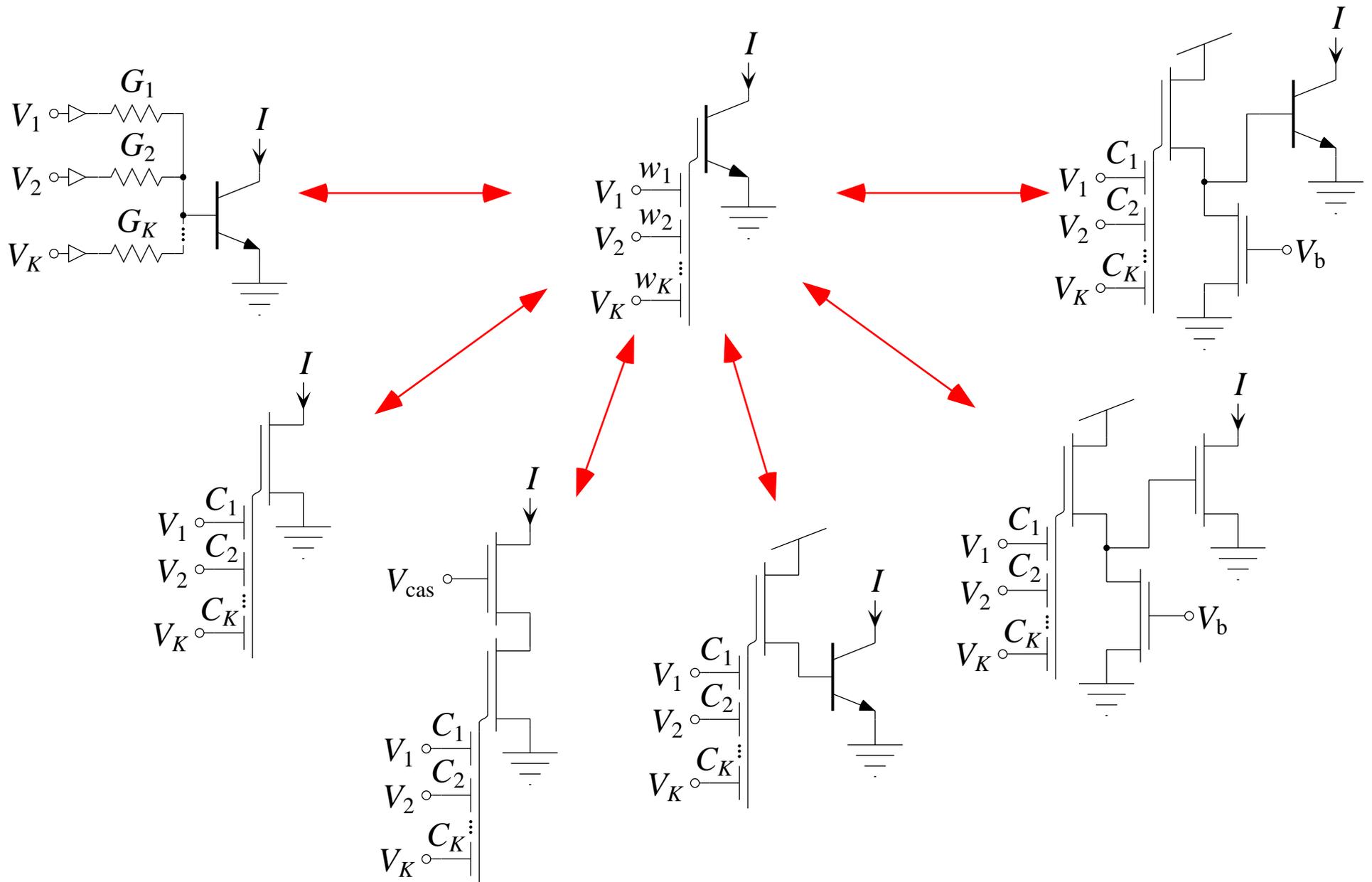

Basic MITE Configurations: Voltage-In, Current-Out

$$I_n \propto \exp\left[\frac{w_{ni}V_i + w_{nk}V_k + \dots}{U_T}\right]$$

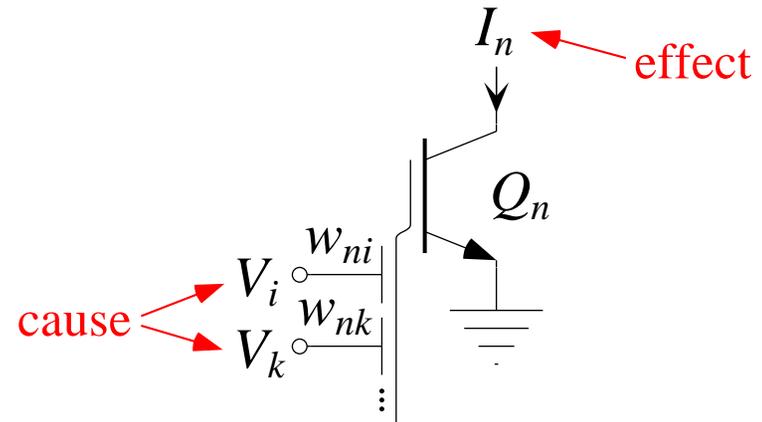
$$\Rightarrow I_n \propto \exp\left[\frac{w_{ni}V_i}{U_T}\right] \exp\left[\frac{w_{nk}V_k}{U_T}\right]$$



Basic MITE Configurations: Current-In, Voltage-Out

$$I_i \propto \exp\left[\frac{w_{ii} V_i + \dots}{U_T}\right]$$

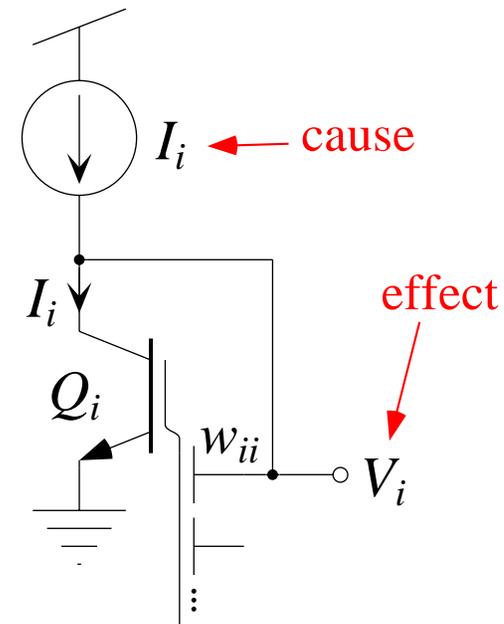
$$\Rightarrow V_i = \frac{U_T}{w_{ii}} \log I_i - \dots$$




Basic MITE Configurations: Voltage-In, Voltage-Out

$$I_i \propto \exp\left[\frac{w_{ii} V_i + w_{ij} V_j + \dots}{U_T}\right]$$
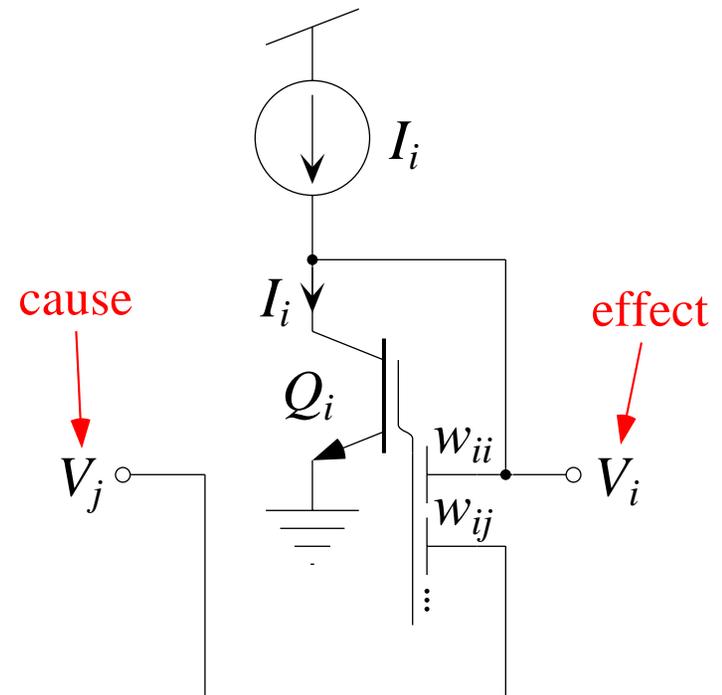
$$\Rightarrow V_i = \frac{U_T}{w_{ii}} \log I_i - \frac{w_{ij}}{w_{ii}} V_j - \dots$$



Static MITE Networks: Power-Law Circuits

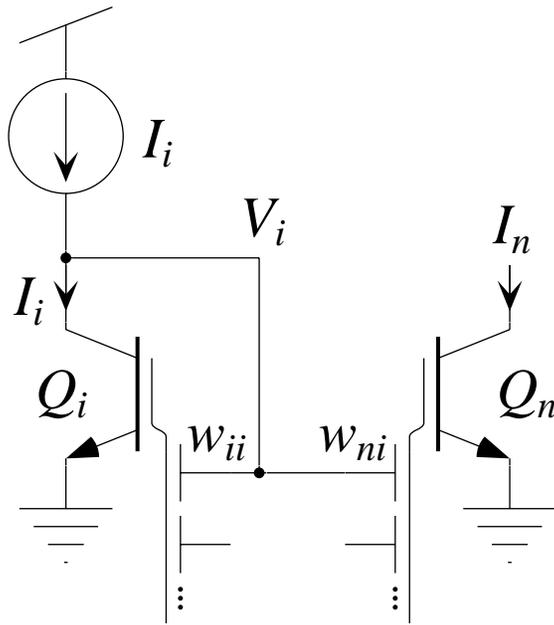


$$I_n \propto \exp\left[\frac{w_{ni} V_i + \dots}{U_T}\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{w_{ni}}{U_T} \left(\frac{U_T}{w_{ii}} \log I_i - \dots\right)\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{\cancel{U_T} w_{ni}}{\cancel{U_T} w_{ii}} \log I_i\right]$$

$$\Rightarrow I_n \propto I_i^{\frac{w_{ni}}{w_{ii}}}$$

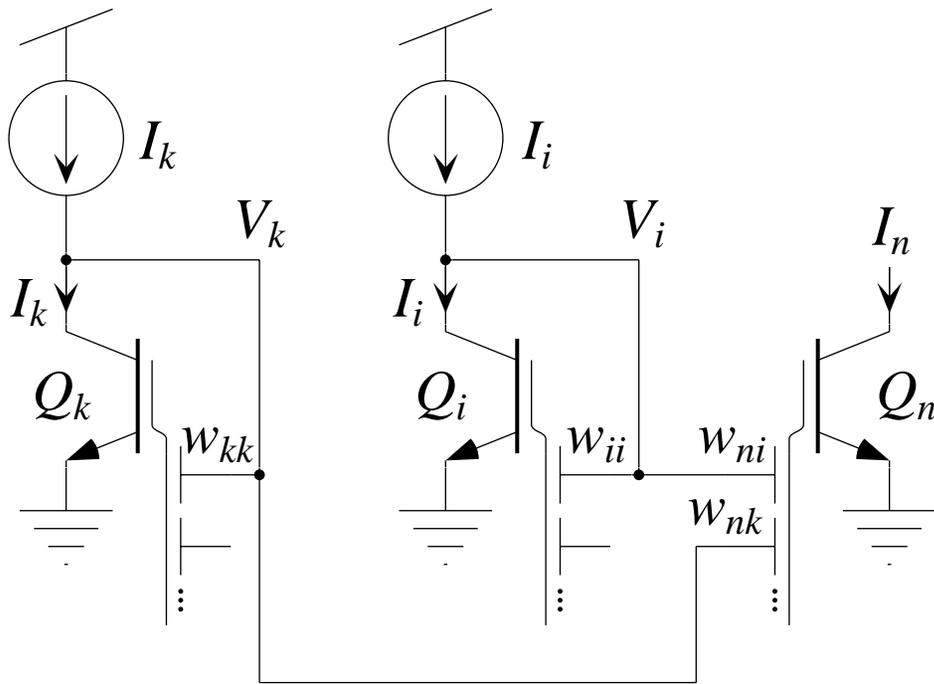Static MITE Networks: Product-of-Power-Law Circuits




$$I_n \propto \exp\left[\frac{w_{ni} V_i}{U_T}\right] \exp\left[\frac{w_{nk} V_k}{U_T}\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{w_{ni}}{U_T} \left(\frac{U_T}{w_{ii}} \log I_i - \dots\right)\right] \times \exp\left[\frac{w_{nk}}{U_T} \left(\frac{U_T}{w_{kk}} \log I_k - \dots\right)\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{\cancel{U_T} w_{ni}}{\cancel{U_T} w_{ii}} \log I_i\right] \times \exp\left[\frac{\cancel{U_T} w_{nk}}{\cancel{U_T} w_{kk}} \log I_k\right]$$

$$\Rightarrow I_n \propto I_i^{\frac{w_{ni}}{w_{ii}}} \times I_k^{\frac{w_{nk}}{w_{kk}}}$$

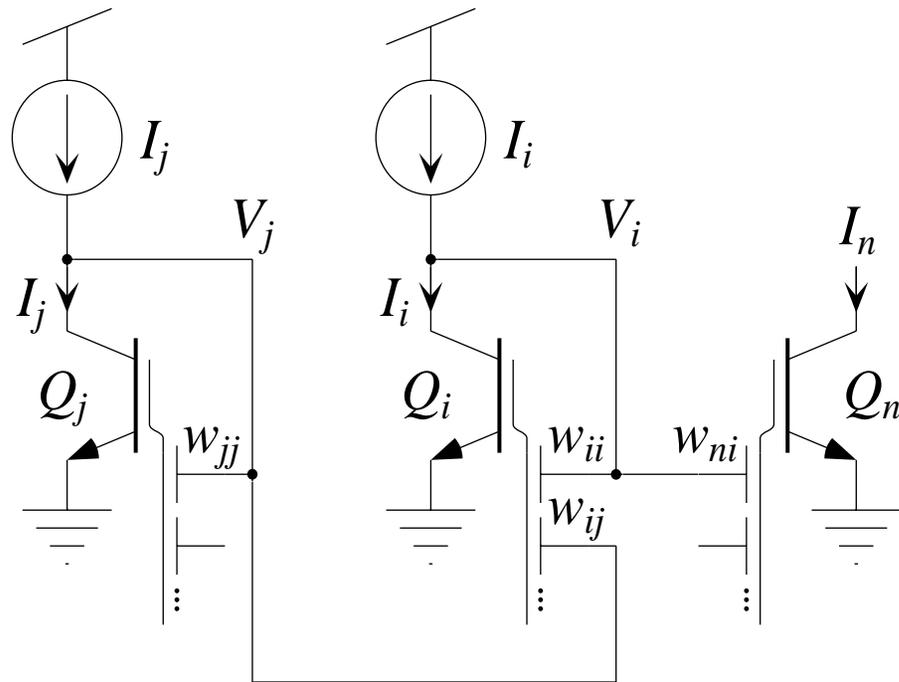Static MITE Networks: Quotient-of-Power-Law Circuits




$$I_n \propto \exp\left[\frac{w_{ni} V_i + \dots}{U_T}\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{w_{ni}}{U_T} \left(\frac{U_T}{w_{ii}} \log I_i - \frac{w_{ij}}{w_{ii}} \left(\frac{U_T}{w_{jj}} \log I_j - \dots \right) \dots \right)\right]$$

$$\Rightarrow I_n \propto \exp\left[\frac{\cancel{U_T} w_{ni}}{\cancel{U_T} w_{ii}} \log I_i\right] \times \exp\left[-\frac{\cancel{U_T} w_{ni} w_{ij}}{\cancel{U_T} w_{ii} w_{jj}} \log I_j\right]$$

$$\Rightarrow I_n \propto I_i^{\frac{w_{ni}}{w_{ii}}} \times I_j^{-\frac{w_{ni} w_{ij}}{w_{ii} w_{jj}}} \Rightarrow I_n \propto I_i^{\frac{w_{ni}}{w_{ii}}} \div I_j^{\frac{w_{ni} w_{ij}}{w_{ii} w_{jj}}}$$

Static MITE Networks: Square-Root

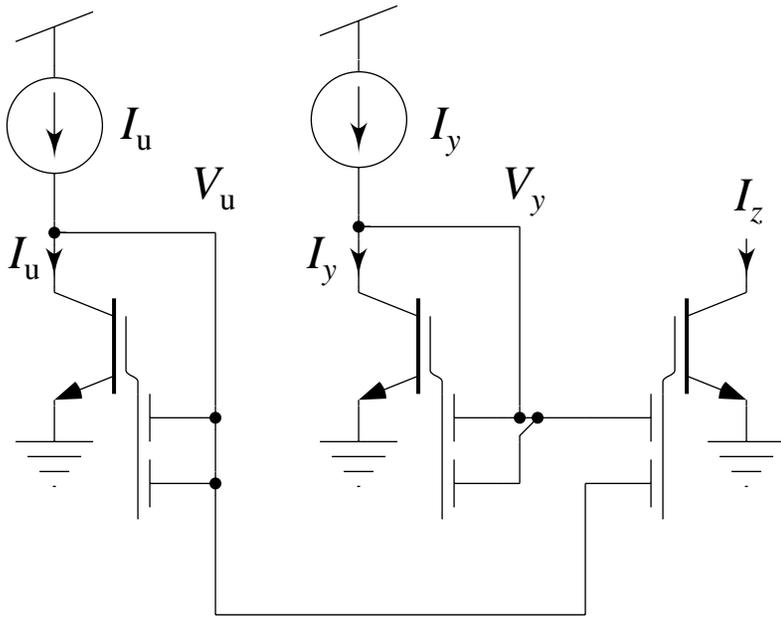


$$I_u = \lambda I_s e^{2wV_u/U_T} \Rightarrow \frac{wV_u}{U_T} = \log \sqrt{\frac{I_u}{\lambda I_s}}$$

$$I_y = \lambda I_s e^{2wV_y/U_T} \Rightarrow \frac{wV_y}{U_T} = \log \sqrt{\frac{I_y}{\lambda I_s}}$$



$$I_z = \lambda I_s e^{w(V_y + V_u)/U_T} = \lambda I_s e^{\log \sqrt{I_y/\lambda I_s} + \log \sqrt{I_u/\lambda I_s}}$$

$$\Rightarrow I_z = \sqrt{I_y I_u} \Rightarrow \underbrace{\left(\frac{I_z}{I_u}\right)}_z = \sqrt{\underbrace{\frac{I_y}{I_u}}_y} \Rightarrow \boxed{z = \sqrt{y}}$$


MITE Networks: Geometric Mean

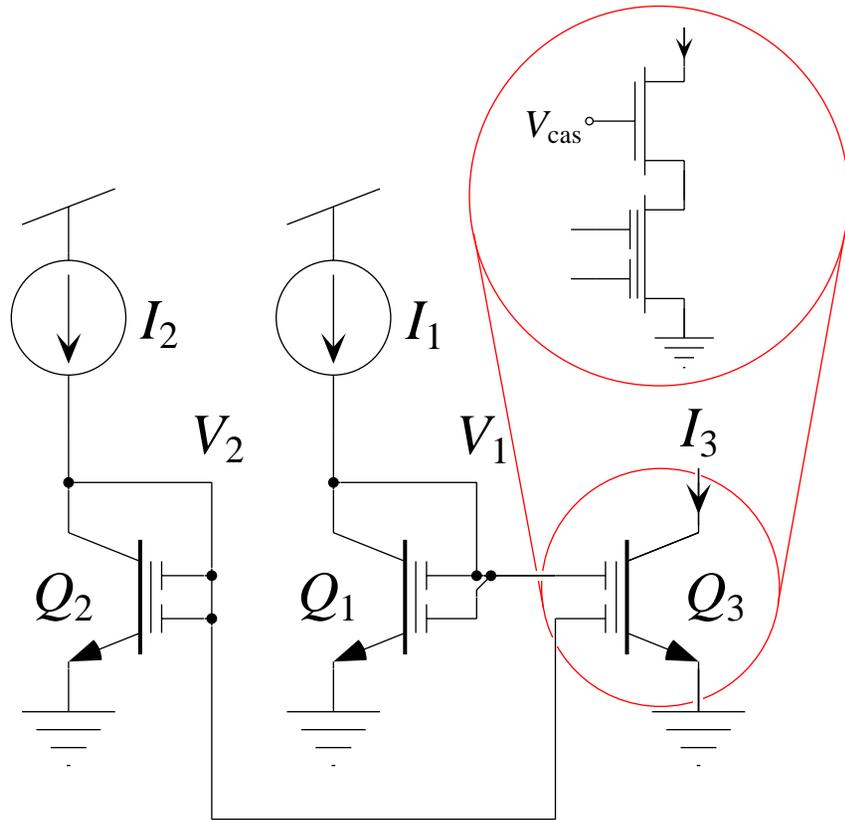

$$I_3 = \sqrt{I_1 I_2}$$

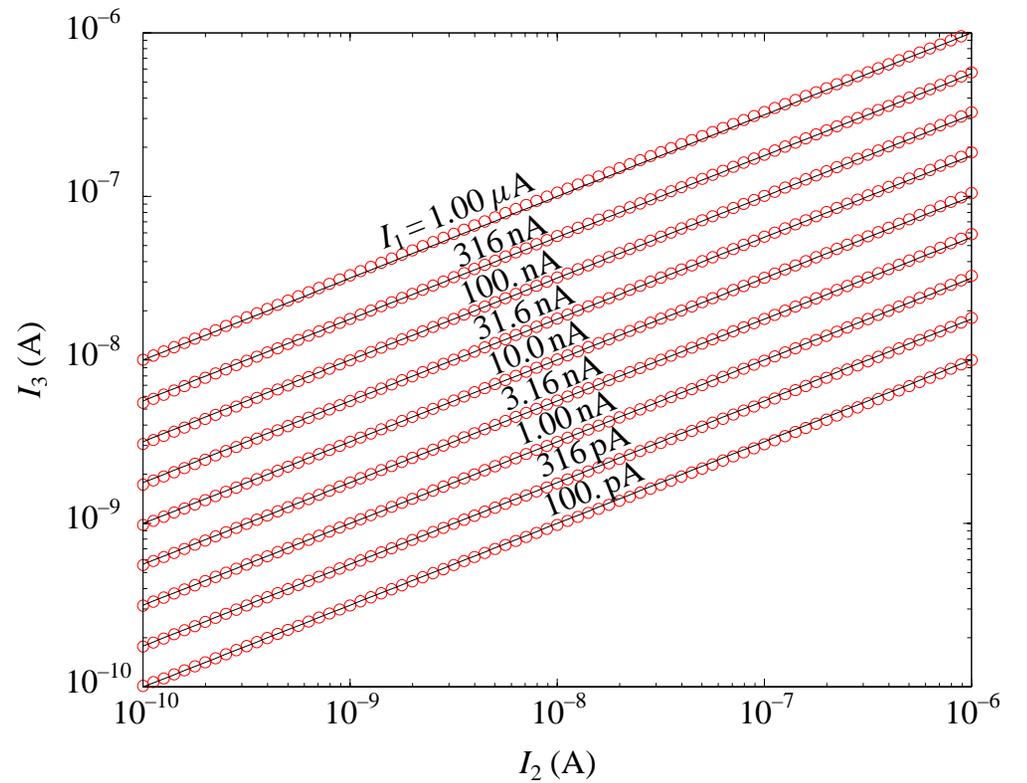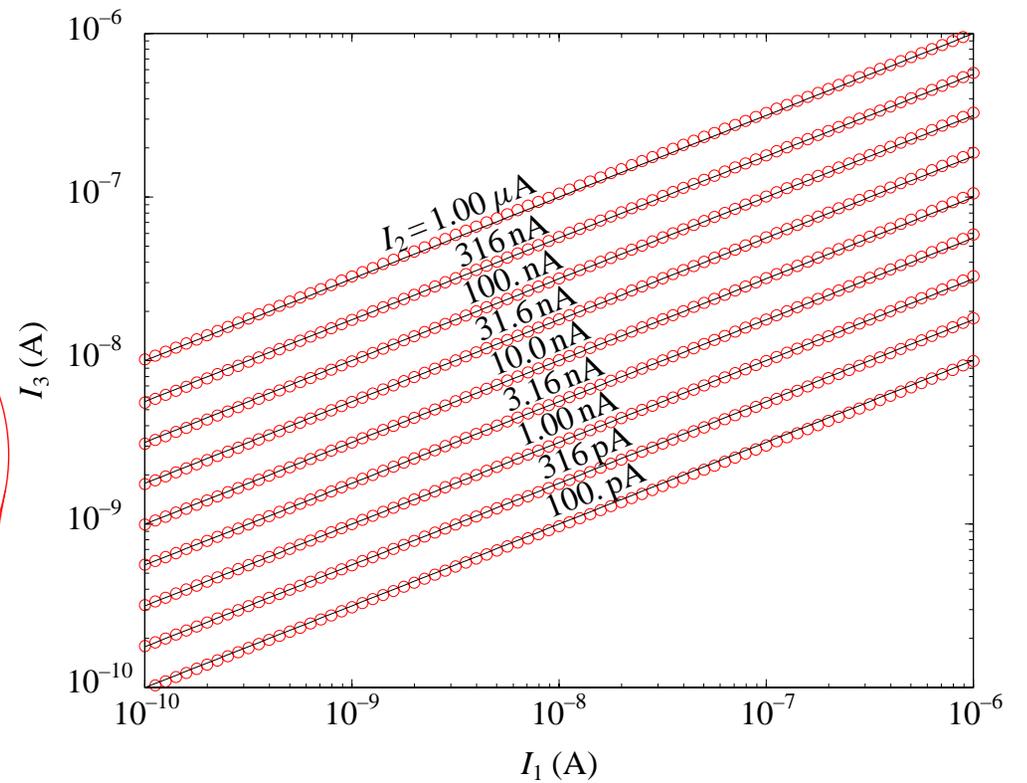

Static MITE Networks: Square

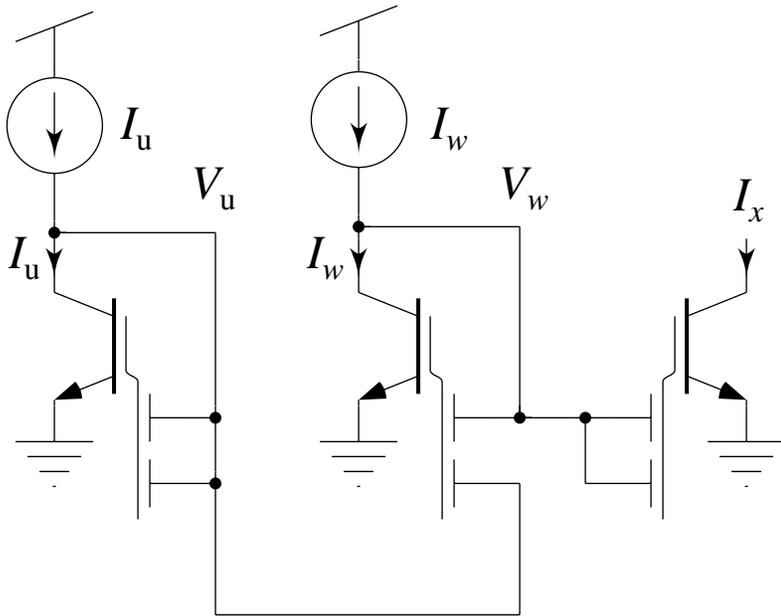

$$I_u = \lambda I_s e^{2wV_u/U_T} \Rightarrow \frac{wV_u}{U_T} = \log \sqrt{\frac{I_u}{\lambda I_s}}$$


$$I_w = \lambda I_s e^{w(V_w + V_u)/U_T} = \lambda I_s e^{wV_w/U_T} e^{\log \sqrt{I_u/\lambda I_s}}$$

$$\Rightarrow \frac{wV_w}{U_T} = \log \frac{I_w}{\sqrt{\lambda I_s I_u}}$$



$$I_x = \lambda I_s e^{2wV_w/U_T} = \lambda I_s e^{2 \log I_w / \sqrt{\lambda I_s I_u}} = \frac{I_w^2}{I_u}$$

$$\Rightarrow \underbrace{\left(\frac{I_x}{I_u} \right)}_x = \underbrace{\left(\frac{I_w}{I_u} \right)}_w^2 \Rightarrow \boxed{x = w^2}$$


MITE Networks: Square/Reciprocal

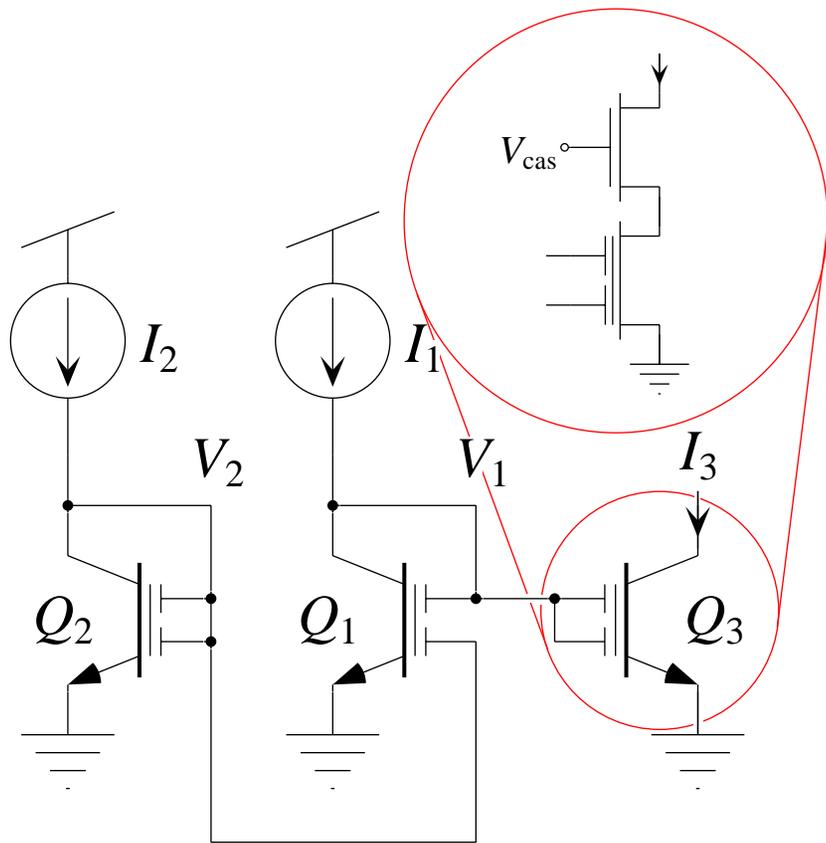



$$I_3 = \frac{I_1^2}{I_2}$$

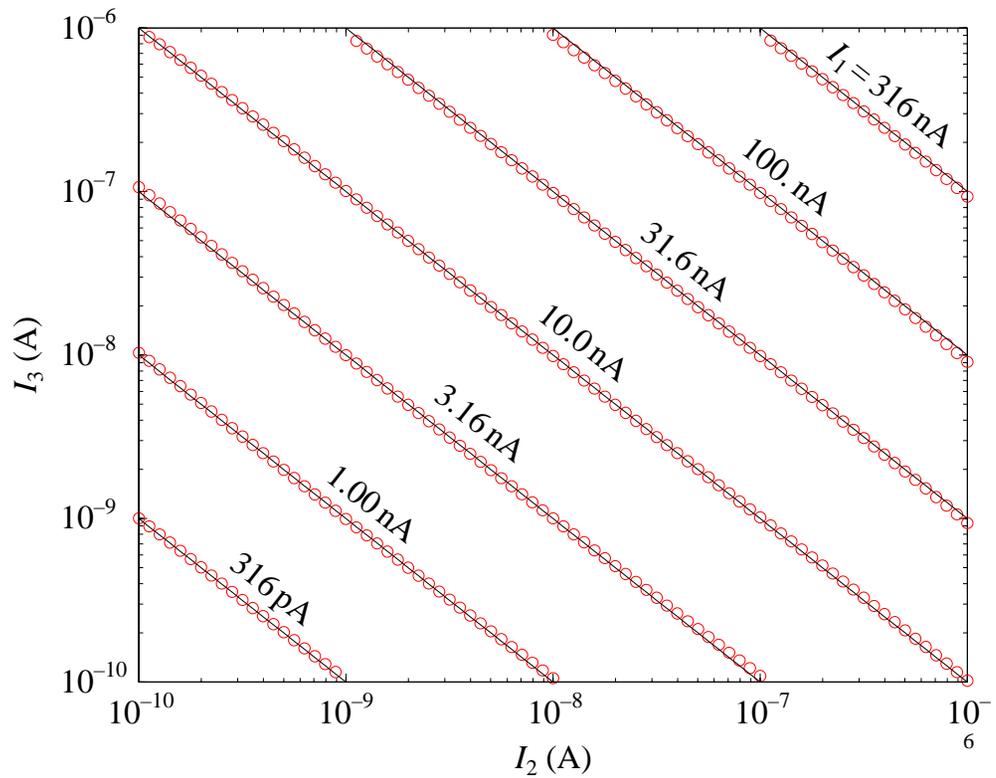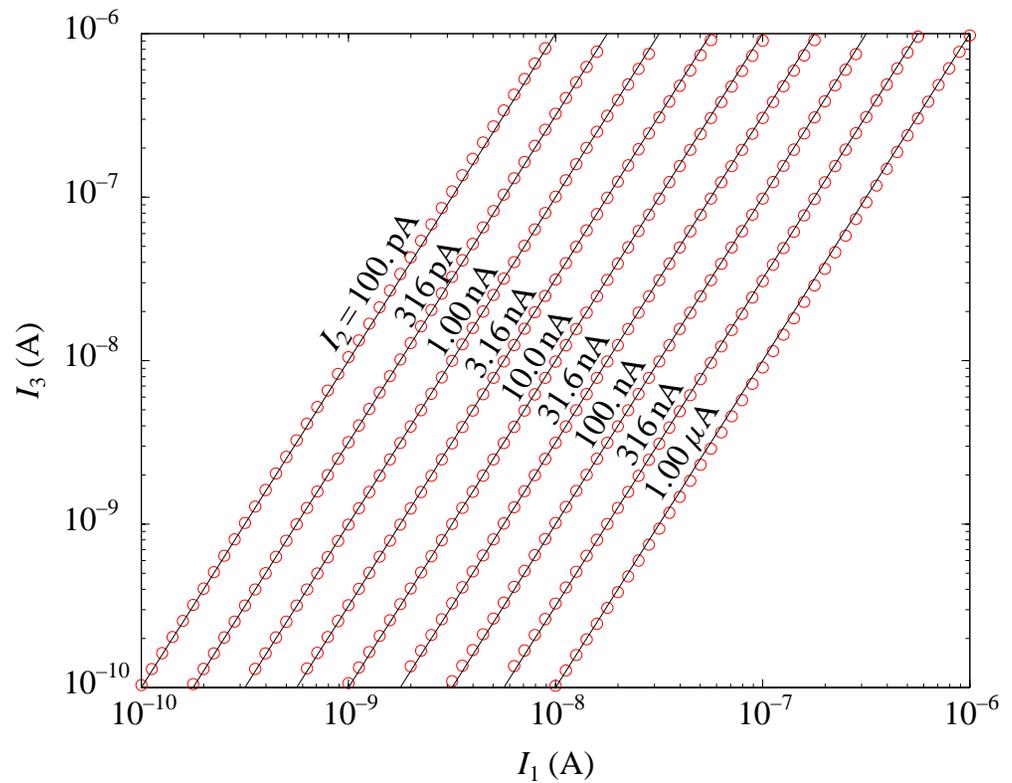


MITE Networks: Square/Reciprocal

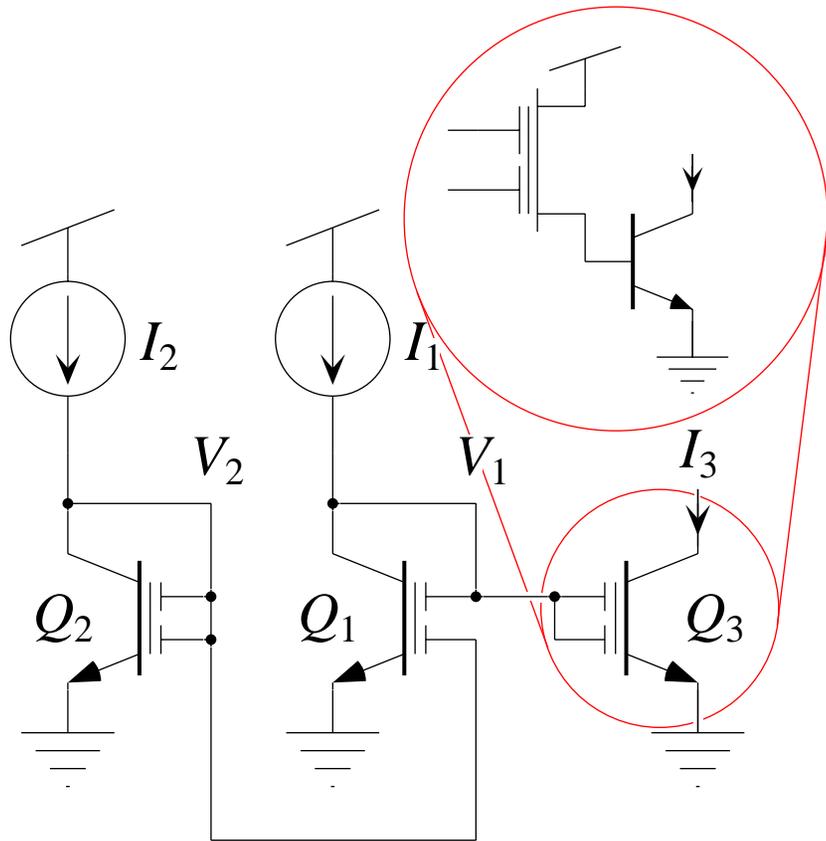



$$I_3 = \frac{I_1^2}{I_2}$$

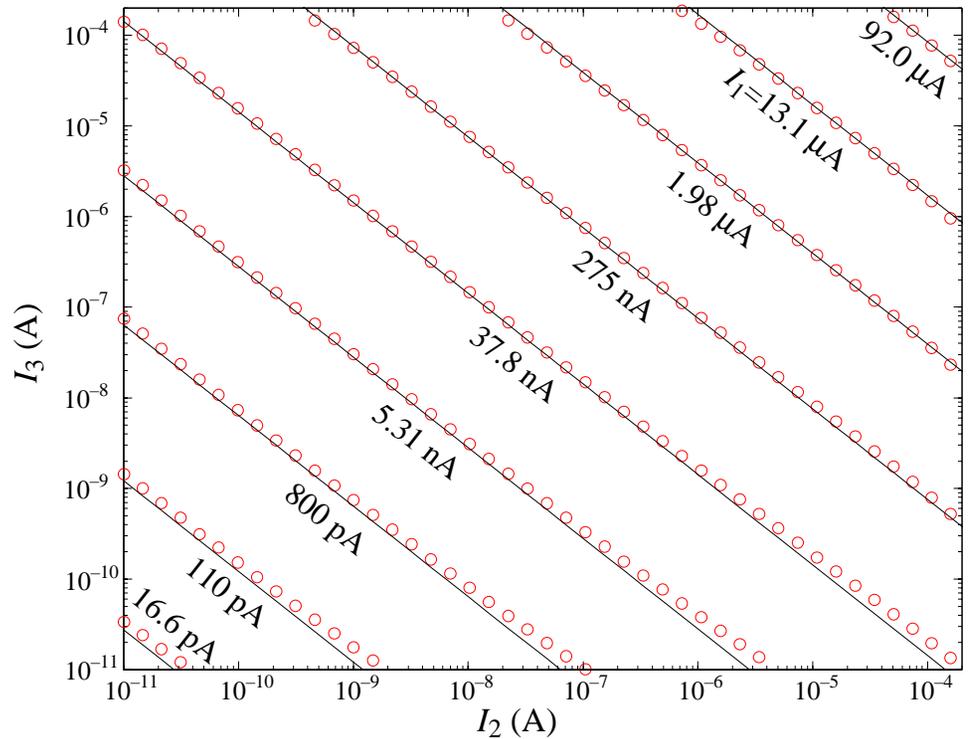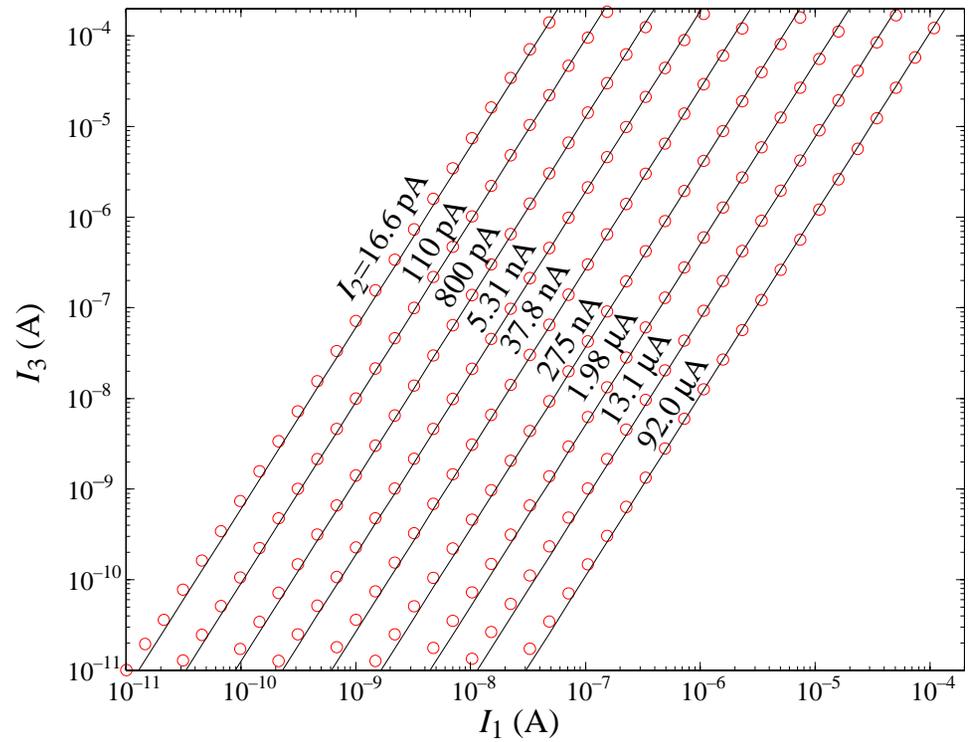


MITE Networks: Multiply/Reciprocal

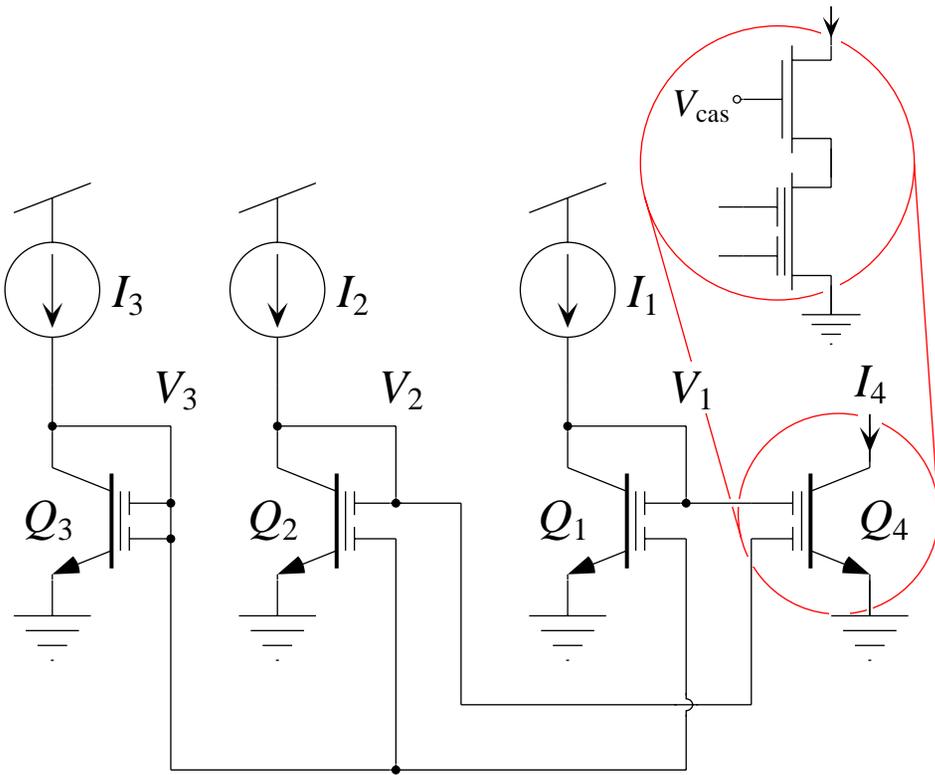

$$I_4 = \frac{I_1 I_2}{I_3}$$

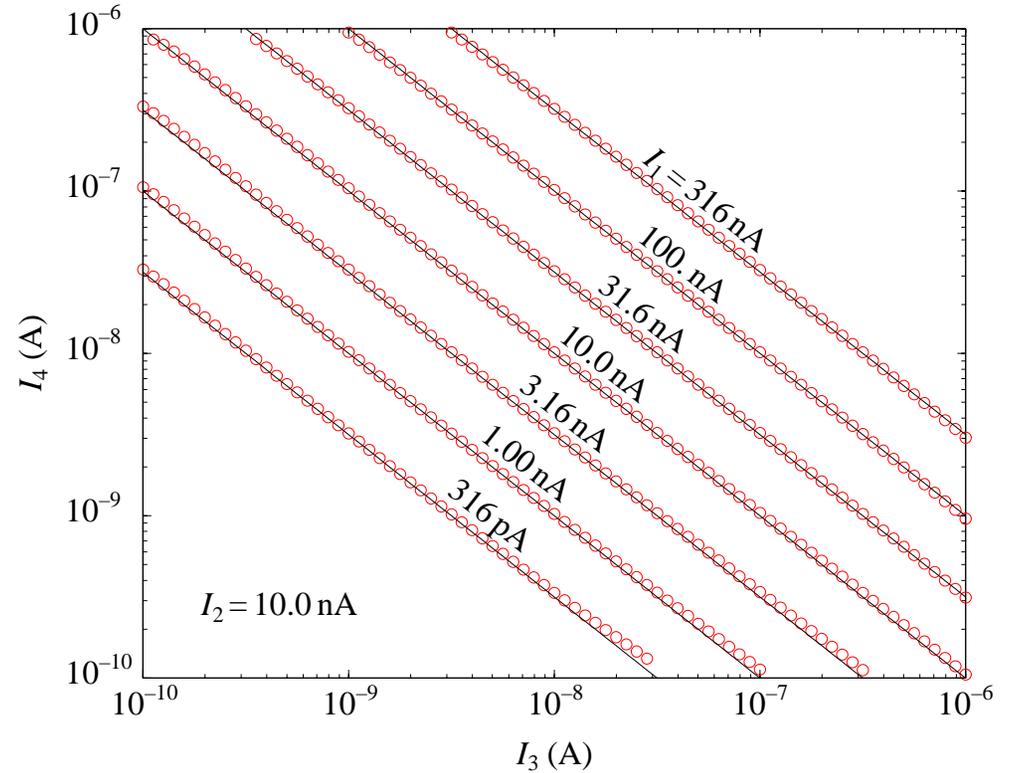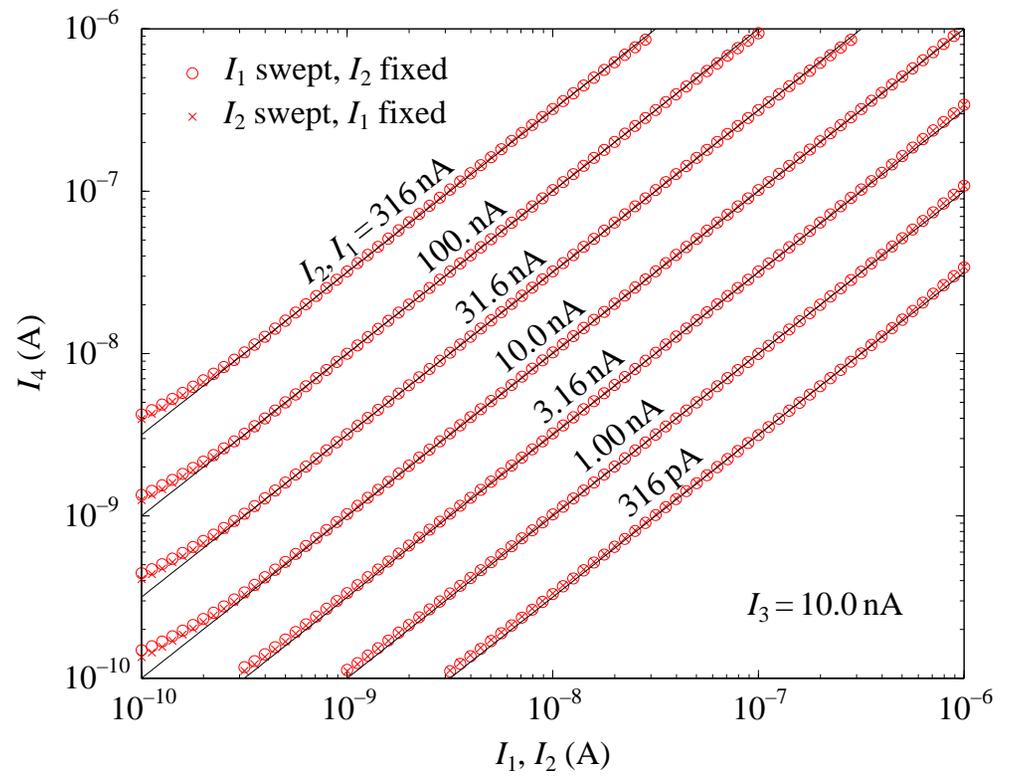

Static MITE Networks: Augmentation

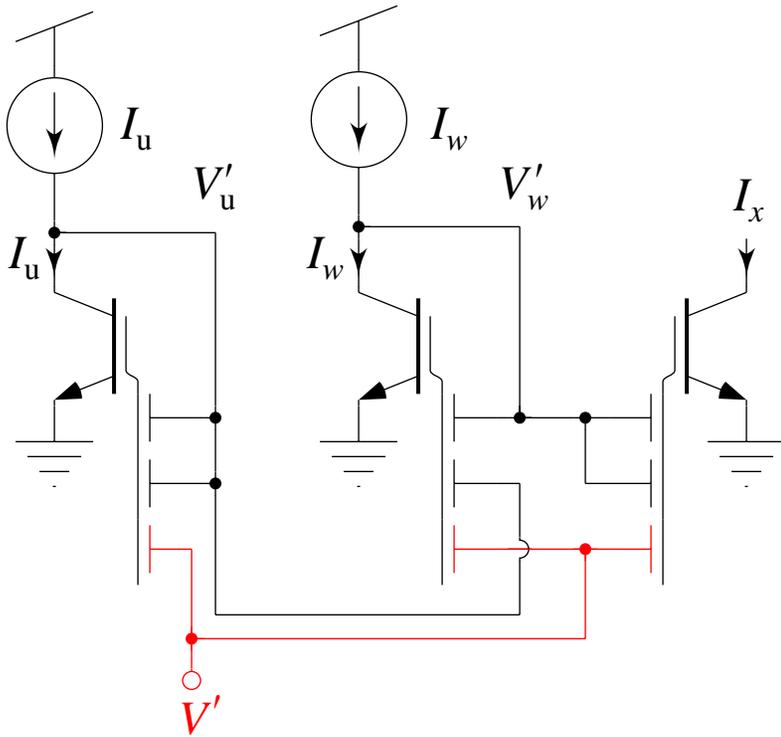

$$\text{Let } \lambda' \equiv \lambda e^{wV'/U_T}$$

$$I_u = \lambda' I_s e^{2wV'_u/U_T} \Rightarrow \frac{wV'_u}{U_T} = \log \sqrt{\frac{I_u}{\lambda' I_s}}$$

$$I_w = \lambda' I_s e^{w(V'_w + V'_u)/U_T} = \lambda' I_s e^{wV'_w/U_T} e^{\log \sqrt{I_u/\lambda' I_s}}$$


$$\Rightarrow \frac{wV'_w}{U_T} = \log \frac{I_w}{\sqrt{\lambda' I_s I_u}}$$

$$I_x = \lambda' I_s e^{2wV'_w/U_T} = \lambda' I_s e^{2 \log I_w / \sqrt{\lambda' I_s I_u}} = \frac{I_w^2}{I_u}$$

$$\Rightarrow \underbrace{\left(\frac{I_x}{I_u} \right)}_x = \underbrace{\left(\frac{I_w}{I_u} \right)}_w^2 \Rightarrow \boxed{x = w^2}$$

\Rightarrow Relationship holds regardless of V'

Static MITE Networks: Augmentation

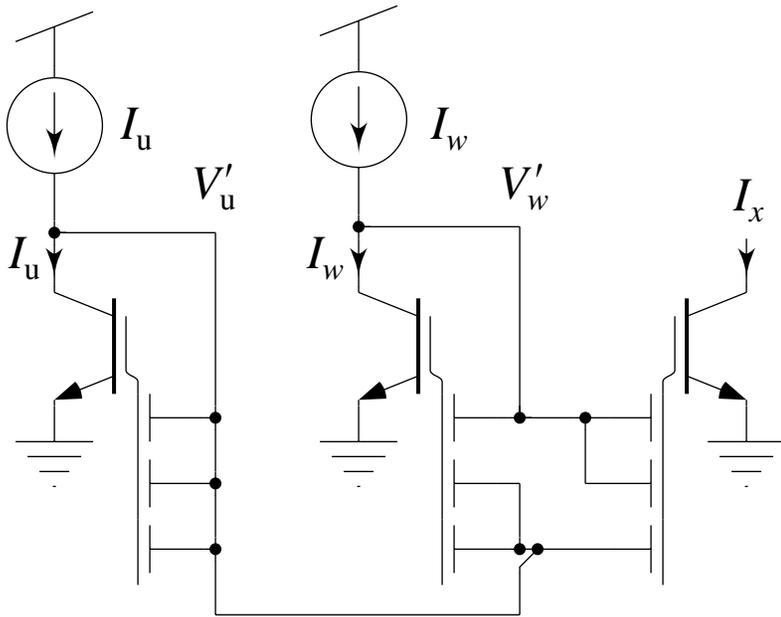


⇒ We can connect V'_u and V' together without changing the function of the MITE network...

Caveat emptor! To avoid the creation of (positive) feedback loops, choose a MITE that only has self connections.

If we had connected V'_w and V' , we would have introduced a positive feedback loop into the MITE network.

MITE Log-Domain Filters: Building Block

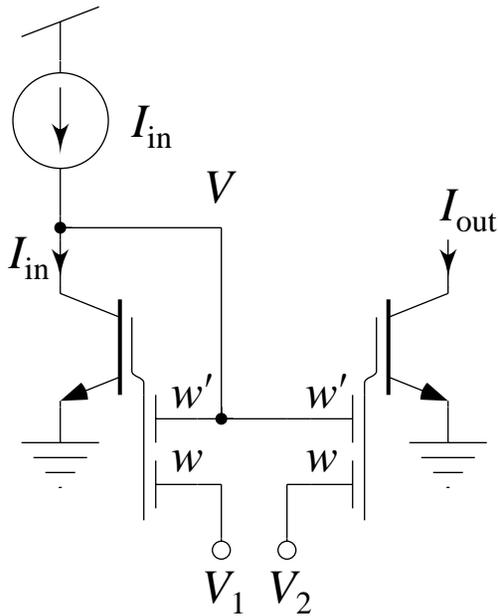


$$I_{\text{in}} = \lambda I_s e^{(w'V + wV_1)/U_T}$$

$$I_{\text{out}} = \lambda I_s e^{(w'V + wV_2)/U_T}$$

$$\Rightarrow \frac{I_{\text{out}}}{I_{\text{in}}} = \frac{\cancel{\lambda I_s} e^{w'V/U_T} e^{wV_2/U_T}}{\cancel{\lambda I_s} e^{w'V/U_T} e^{wV_1/U_T}}$$

$$\Rightarrow I_{\text{out}} = I_{\text{in}} e^{w(V_2 - V_1)/U_T}$$

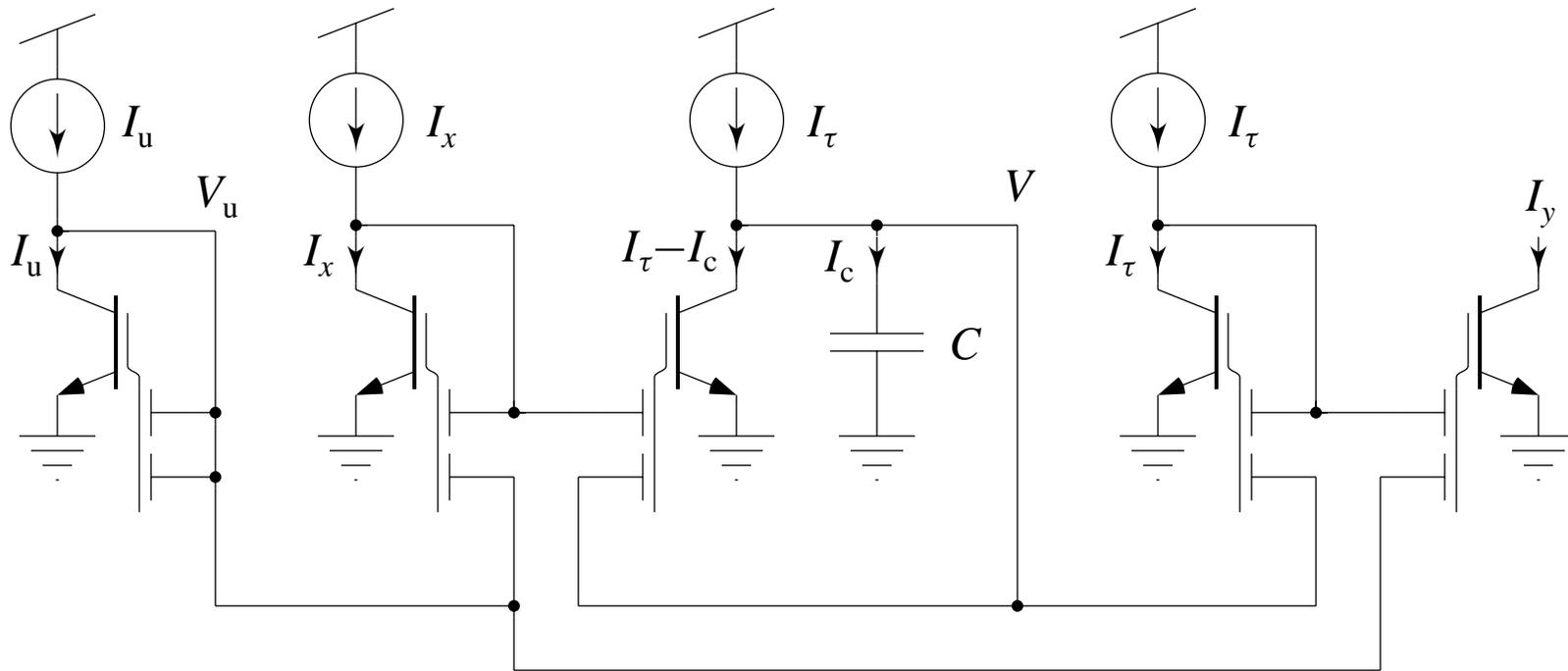MITE Log-Domain Filters: First-Order Low-Pass




$$I_y = I_\tau e^{w(V_u - V)/U_T} \Rightarrow e^{w(V - V_u)/U_T} = \frac{I_\tau}{I_y} \quad \text{and} \quad \frac{dV}{dt} = -\frac{U_T}{wI_y} \frac{dI_y}{dt}$$

$$\text{KCL} \Rightarrow C \frac{dV}{dt} = I_\tau - I_x e^{w(V - V_u)/U_T} \Rightarrow -\frac{CU_T}{wI_y} \frac{dI_y}{dt} = I_\tau - I_x \frac{I_\tau}{I_y}$$

$$\Rightarrow \frac{CU_T}{wI_\tau} \frac{dI_y}{dt} + I_y = I_x \Rightarrow \underbrace{\frac{CU_T}{wI_\tau}}_{\tau} \underbrace{\frac{d}{dt} \left(\frac{I_y}{I_u} \right)}_y + \underbrace{\left(\frac{I_y}{I_u} \right)}_y = \underbrace{\left(\frac{I_x}{I_u} \right)}_x \Rightarrow \boxed{\tau \frac{dy}{dt} + y = x}$$

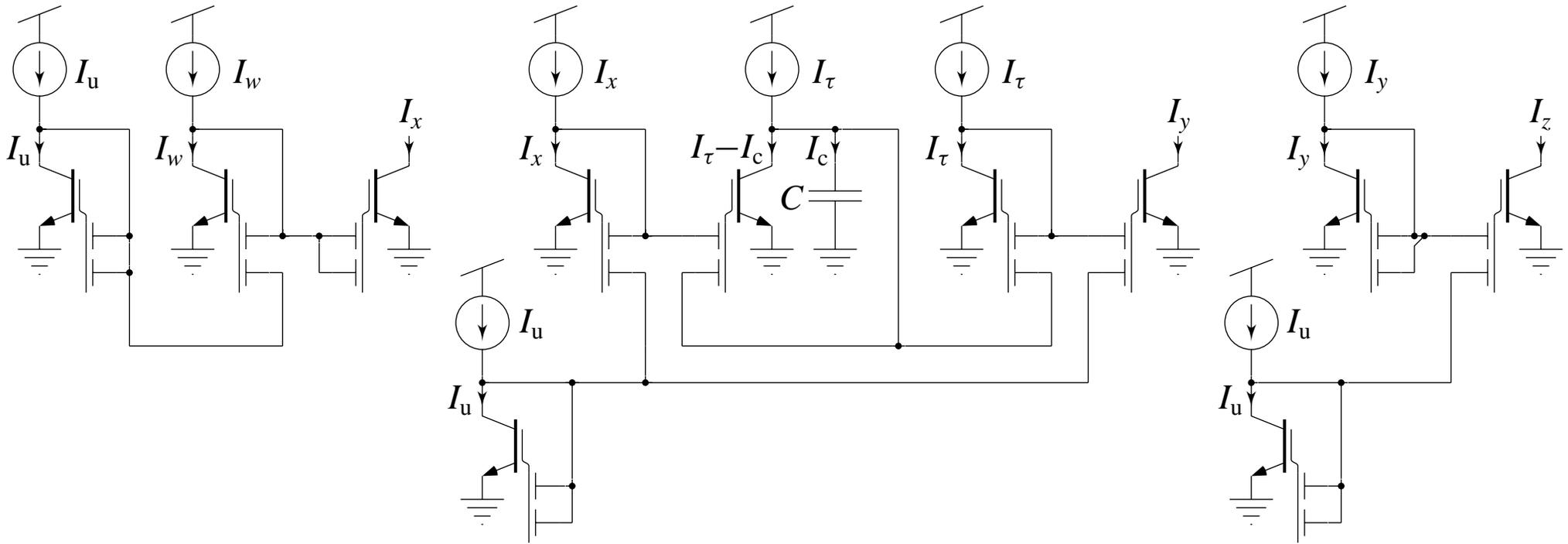Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter




$$x = w^2$$

$$\tau \frac{dy}{dt} + y = x$$

$$z = \sqrt{y}$$

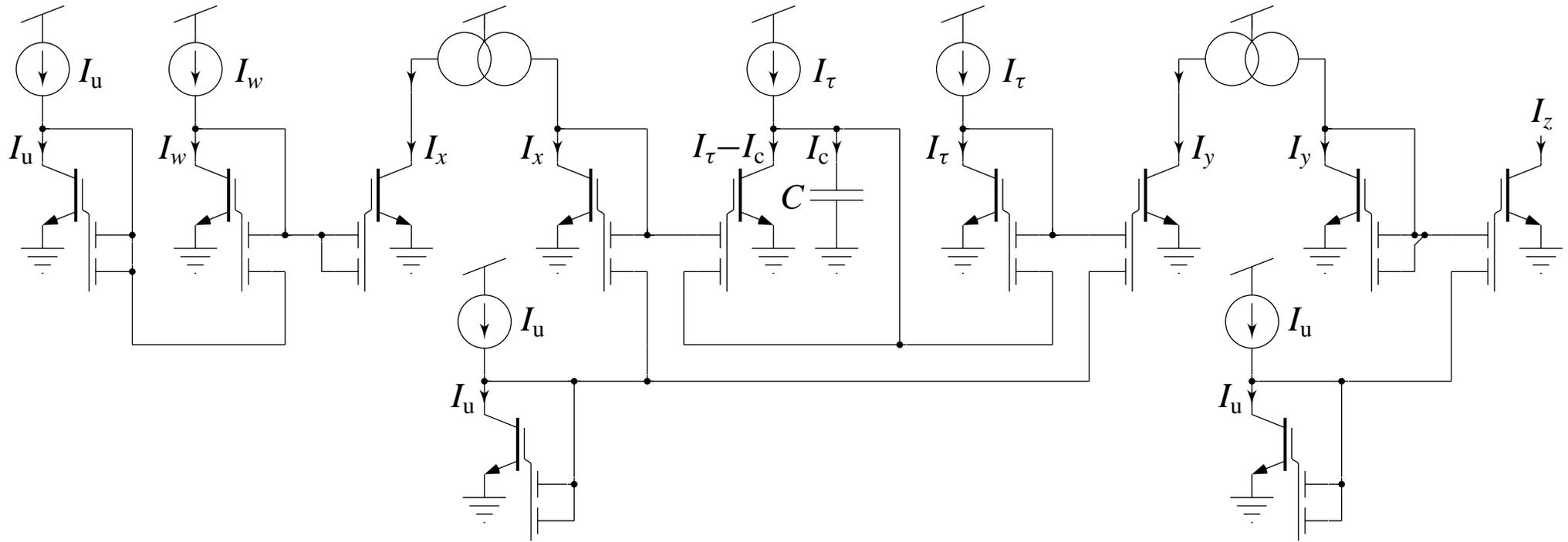Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter




$$x = w^2$$

$$\tau \frac{dy}{dt} + y = x$$

$$z = \sqrt{y}$$

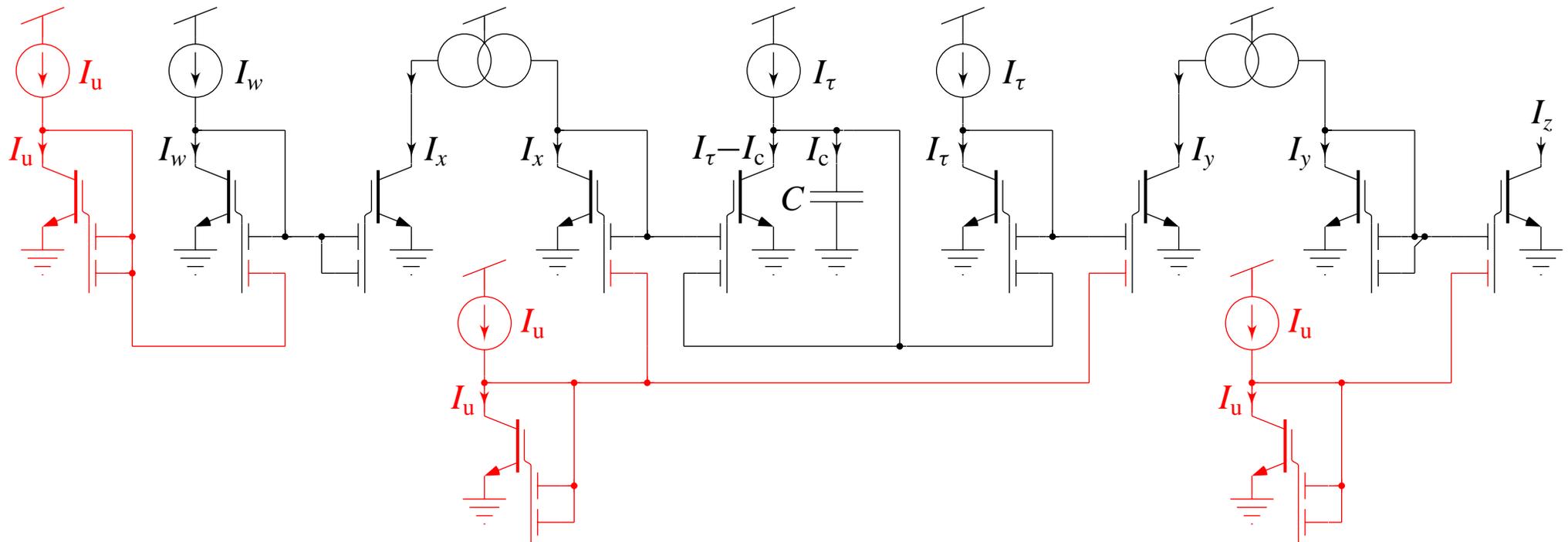Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter




$$x = w^2$$

$$\tau \frac{dy}{dt} + y = x$$

$$z = \sqrt{y}$$

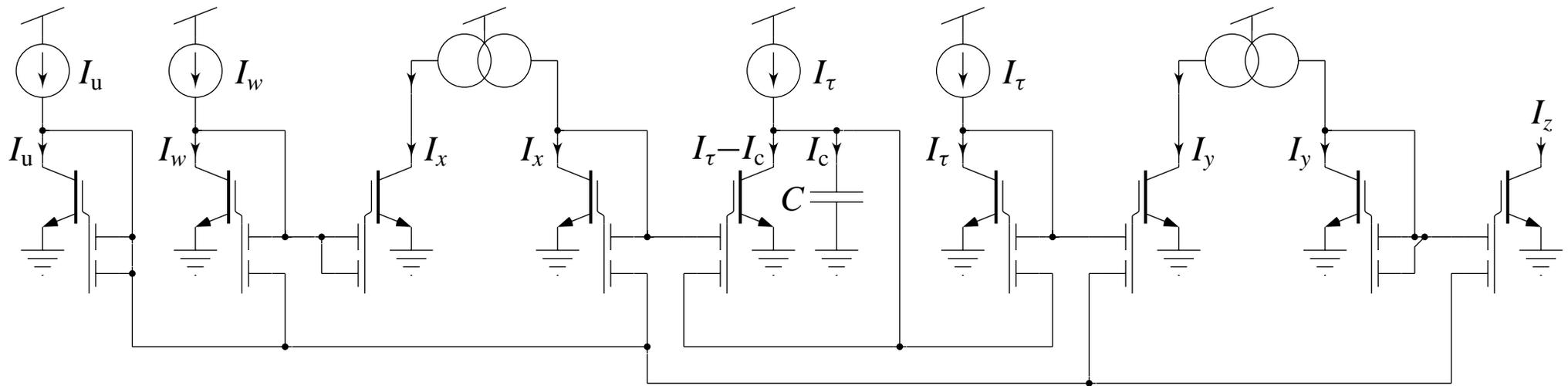Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter




$$x = w^2$$

$$\tau \frac{dy}{dt} + y = x$$

$$z = \sqrt{y}$$

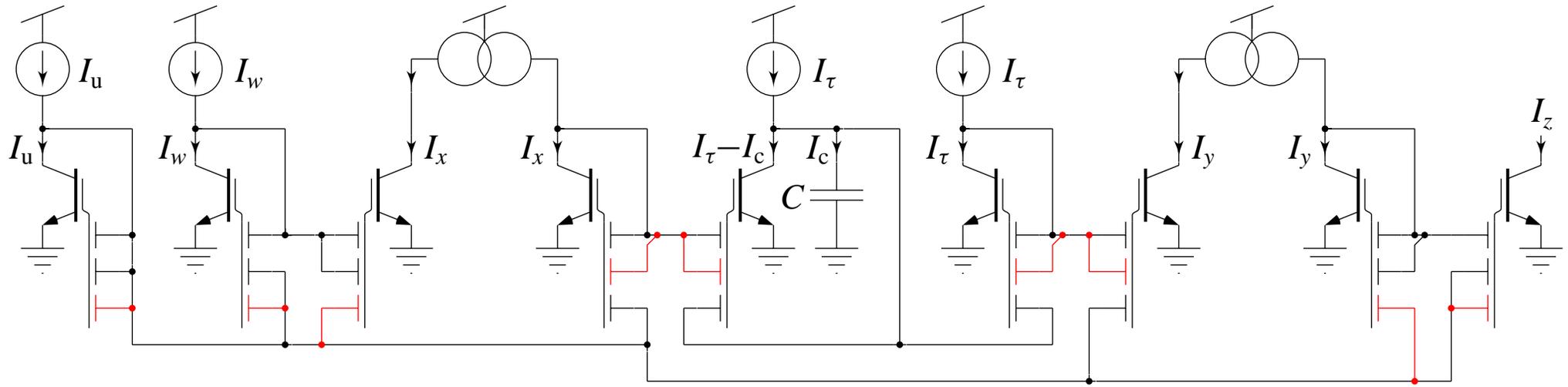Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter




$$x = w^2$$

$$\tau \frac{dy}{dt} + y = x$$

$$z = \sqrt{y}$$

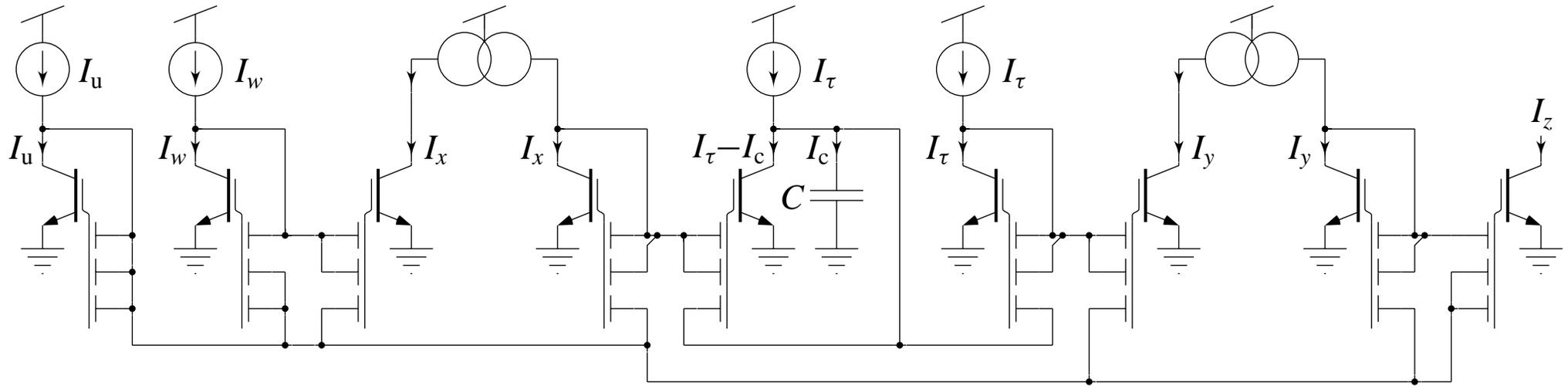Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter




$$x = w^2$$

$$\tau \frac{dy}{dt} + y = x$$

$$z = \sqrt{y}$$

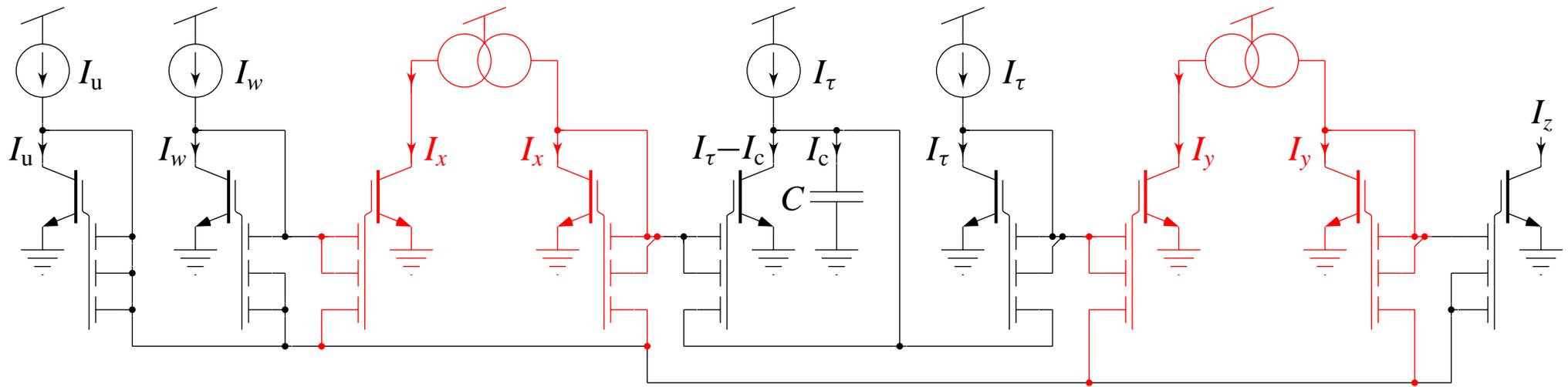Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter




$$x = w^2$$

$$\tau \frac{dy}{dt} + y = x$$


$$z = \sqrt{y}$$

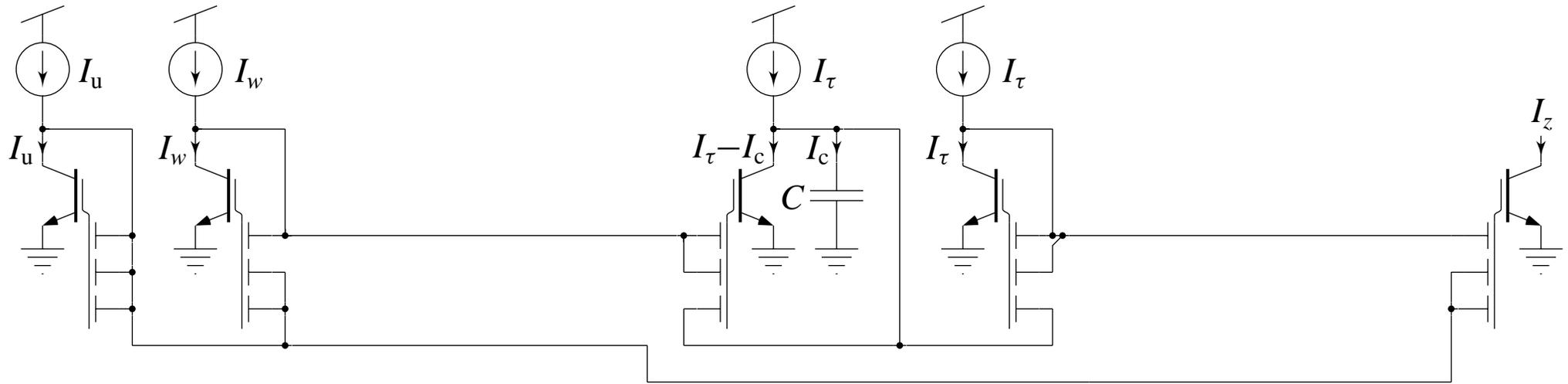Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter



$$\left(2\tau \frac{dz}{dt} + z\right)z = w^2$$

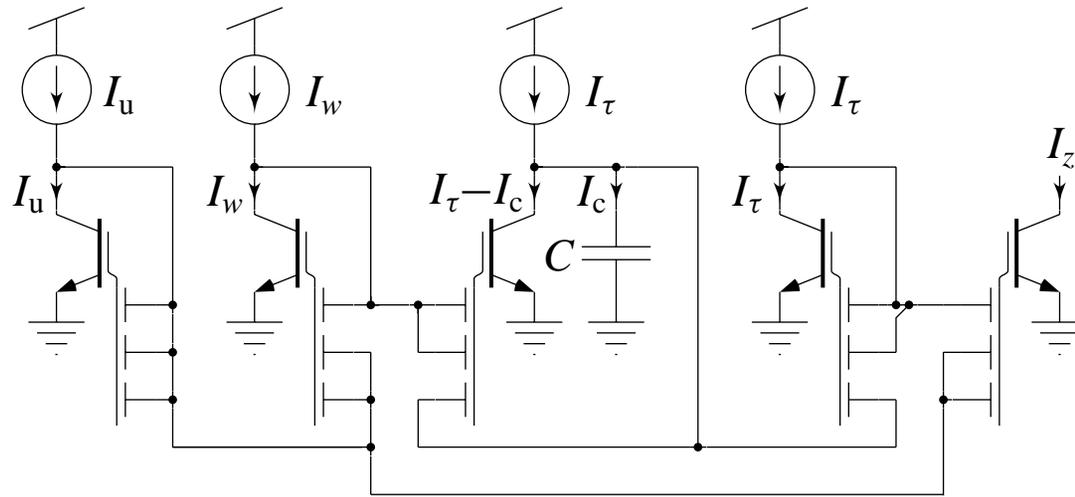Synthesis of **Dynamic MITE Networks**: RMS-to-DC Converter



$$\left(2\tau \frac{dz}{dt} + z\right)z = w^2$$