

A Simple Way to Extend the Common-Mode Input-Voltage Range of the MOS Differential Pair

Bradley A. Minch

Mixed Analog-Digital VLSI Circuits and Systems Lab

Cornell University

Ithaca, NY 14853–5401


minch@ece.cornell.edu

August 5, 2002




Extending the Common-Mode Input Range of the Differential Pair

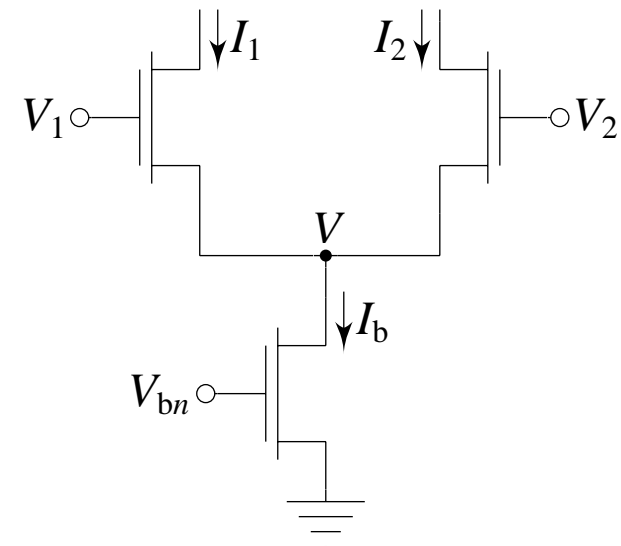- The humble differential pair is used widely in many analog integrated circuits.




Extending the Common-Mode Input Range of the Differential Pair

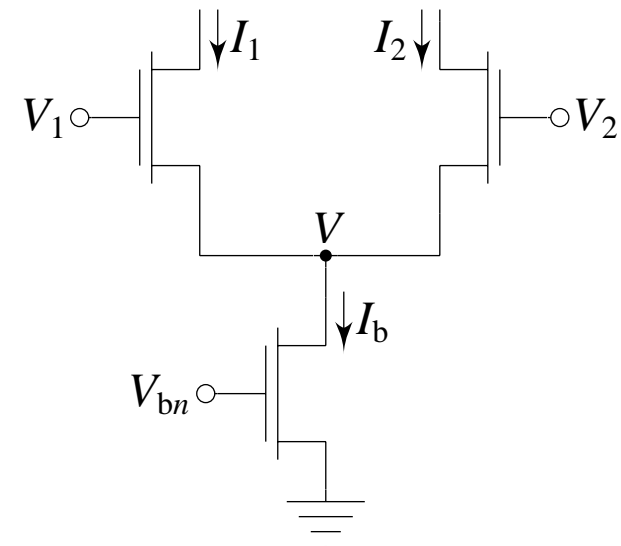- The humble differential pair is used widely in many analog integrated circuits.
- The secret of its success lies in its ability to keep $I_1 + I_2$ equal to I_b via direct series feedback.




Extending the Common-Mode Input Range of the Differential Pair

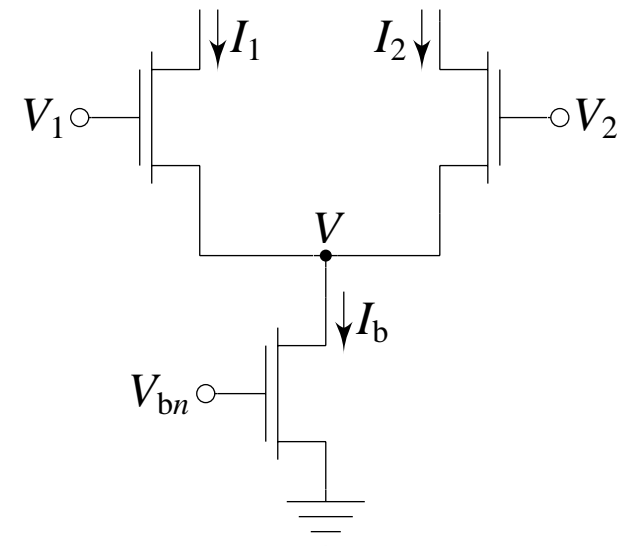- The humble differential pair is used widely in many analog integrated circuits.
- The secret of its success lies in its ability to keep $I_1 + I_2$ equal to I_b via direct series feedback.
- This venerable circuit starts to have headroom problems as the power supply voltage shrinks.




Extending the Common-Mode Input Range of the Differential Pair

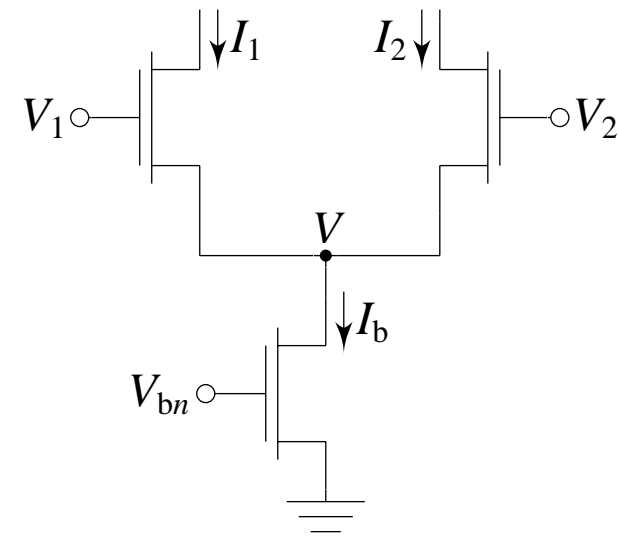- The humble differential pair is used widely in many analog integrated circuits.
- The secret of its success lies in its ability to keep $I_1 + I_2$ equal to I_b via direct series feedback.
- This venerable circuit starts to have headroom problems as the power supply voltage shrinks.
- The n MOS diff pair has a lower limit on V_{cm} of about a diode drop plus a saturation voltage.




Extending the Common-Mode Input Range of the Differential Pair

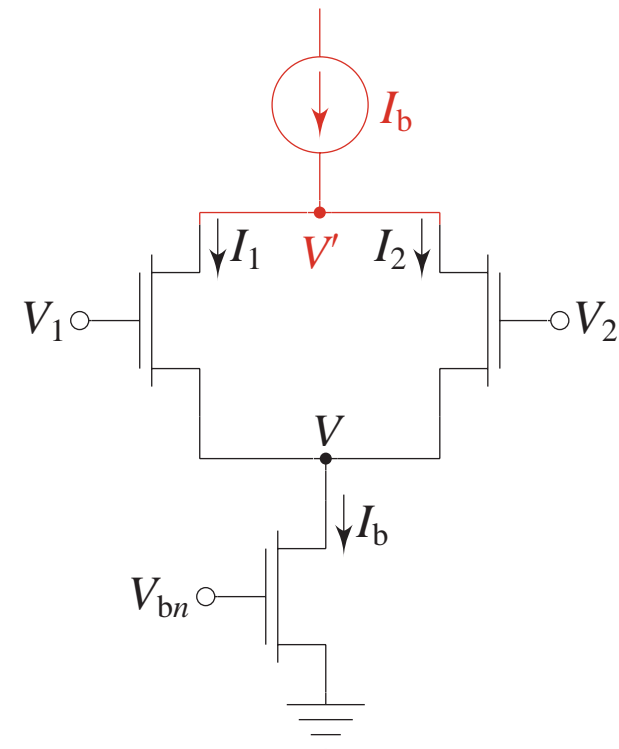- Suppose that we sum I_1 and I_2 and compare the sum to I_b at the drains, as shown.




Extending the Common-Mode Input Range of the Differential Pair

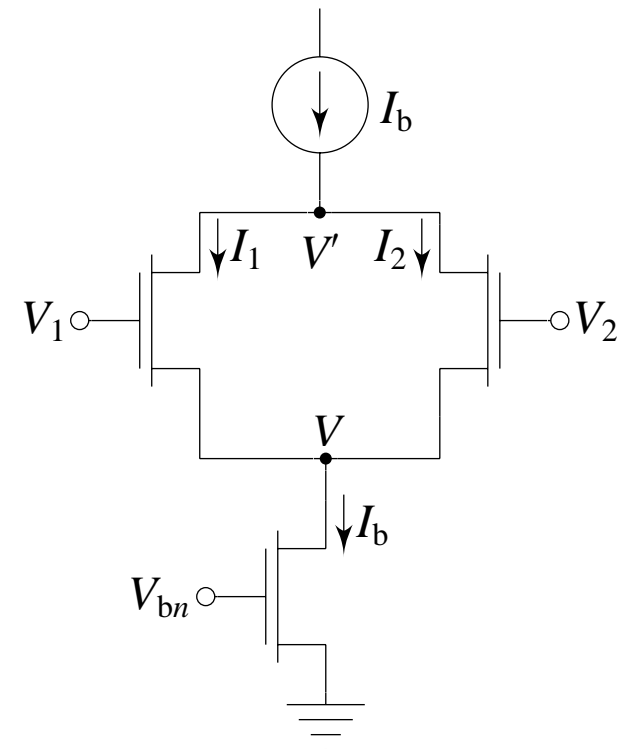- Suppose that we sum I_1 and I_2 and compare the sum to I_b at the drains, as shown.
- Here, the value of V' will encode the result of a comparison between $I_1 + I_2$ and I_b .




Extending the Common-Mode Input Range of the Differential Pair

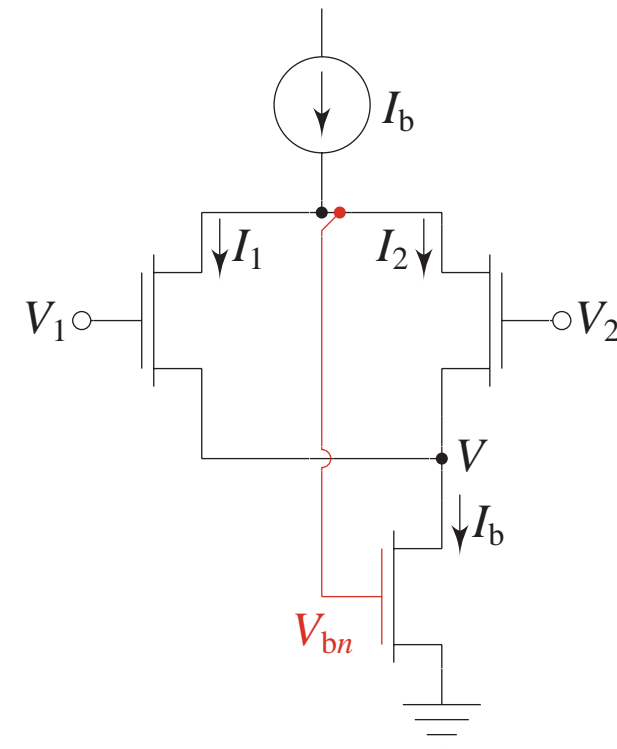- Suppose that we sum I_1 and I_2 and compare the sum to I_b at the drains, as shown.
- Here, the value of V' will encode the result of a comparison between $I_1 + I_2$ and I_b .
- Next, suppose that we connect V' to V_{bn} , as shown, thereby creating a negative feedback loop that adjusts V_{bn} so that $I_1 + I_2 = I_b$, even if $V \leq V_{DSsat}$.




Extending the Common-Mode Input Range of the Differential Pair

- Suppose that we sum I_1 and I_2 and compare the sum to I_b at the drains, as shown.
- Here, the value of V' will encode the result of a comparison between $I_1 + I_2$ and I_b .
- Next, suppose that we connect V' to V_{bn} , as shown, thereby creating a negative feedback loop that adjusts V_{bn} so that $I_1 + I_2 = I_b$, even if $V \leq V_{DSsat}$.
- We call this circuit the *flipped differential pair* after Ramírez-Angulo *et al.*

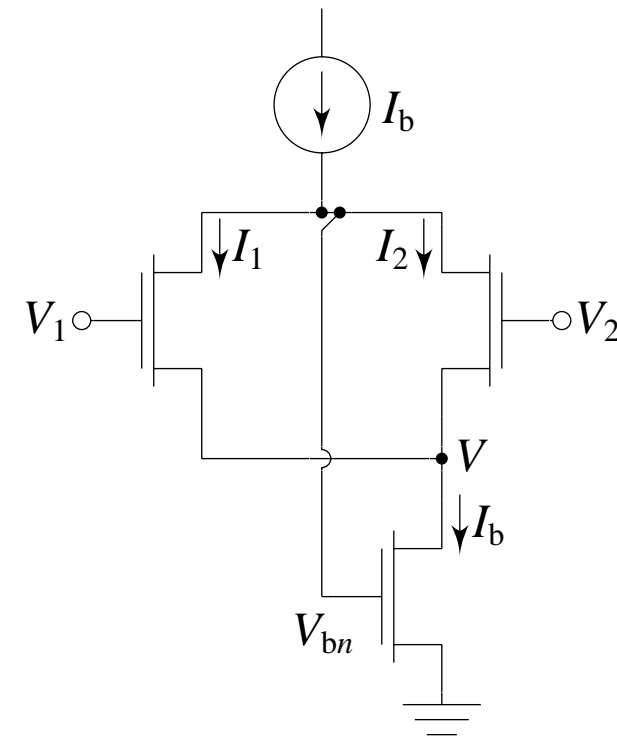


Extending the Common-Mode Input Range of the Differential Pair

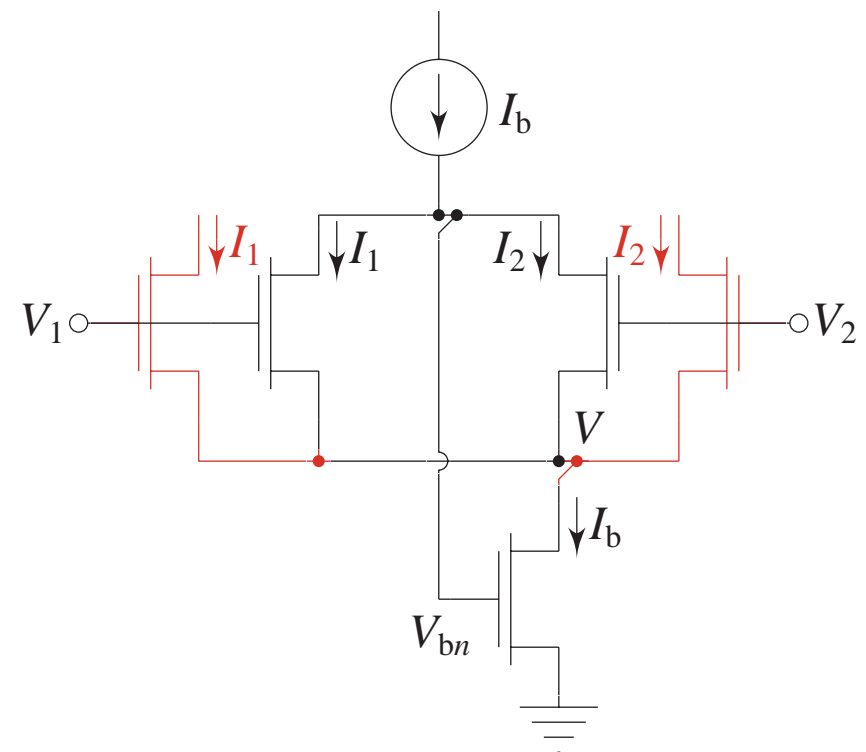- We can generate output currents by adding another pair of transistors to the circuit, as shown.




Extending the Common-Mode Input Range of the Differential Pair

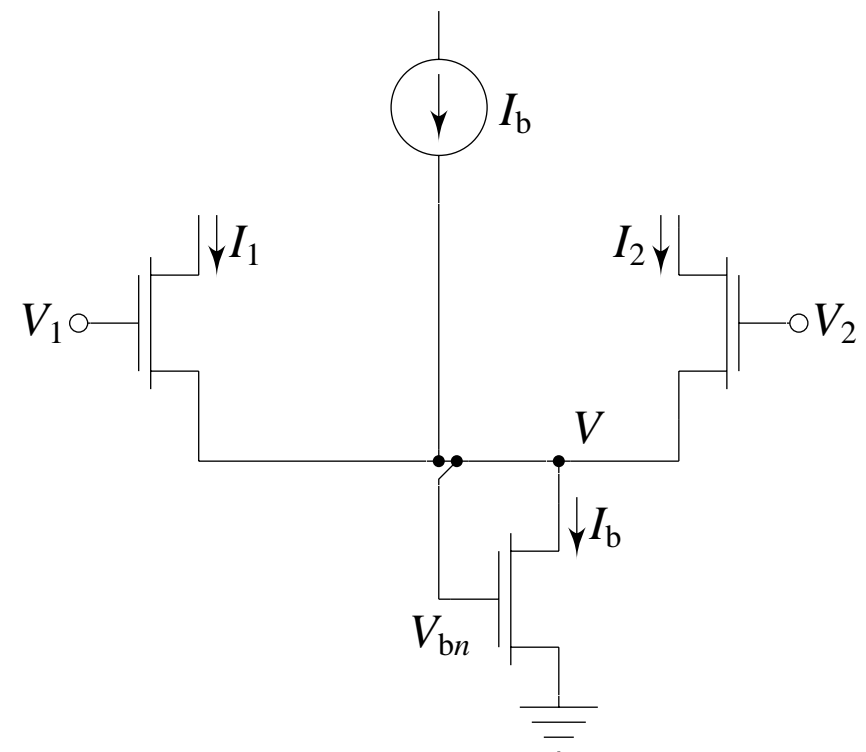- We can generate output currents by adding another pair of transistors to the circuit, as shown.
- If the central pair of transistors remains saturated, this circuit functions as does the conventional diff pair, even if $V \leq V_{DSsat}$.
- As V_{cm} increases, V hits V_{bn} , driving the central pair out of saturation. Beyond this point, the circuit behaves as that shown.




Extending the Common-Mode Input Range of the Differential Pair

- We can generate output currents by adding another pair of transistors to the circuit, as shown.
- If the central pair of transistors remains saturated, this circuit functions as does the conventional diff pair, even if $V \leq V_{DSsat}$.
- As V_{cm} increases, V hits V_{bn} , driving the central pair out of saturation. Beyond this point, the circuit behaves as that shown.
- Nonetheless, this diff pair is useful when V_{DD} is less than about two diode drops.

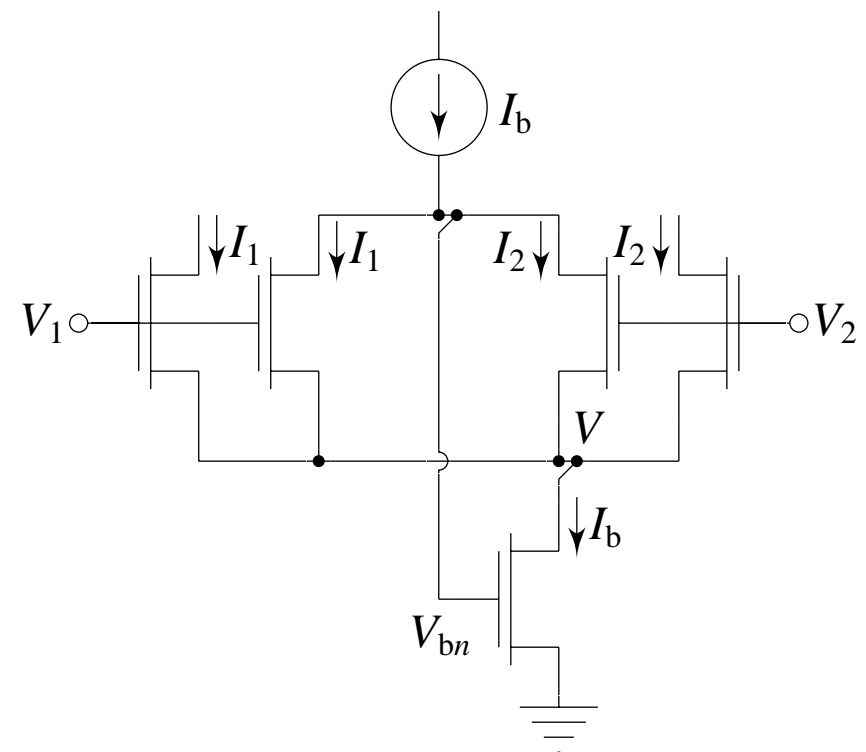


Extending the Common-Mode Input Range of the Differential Pair

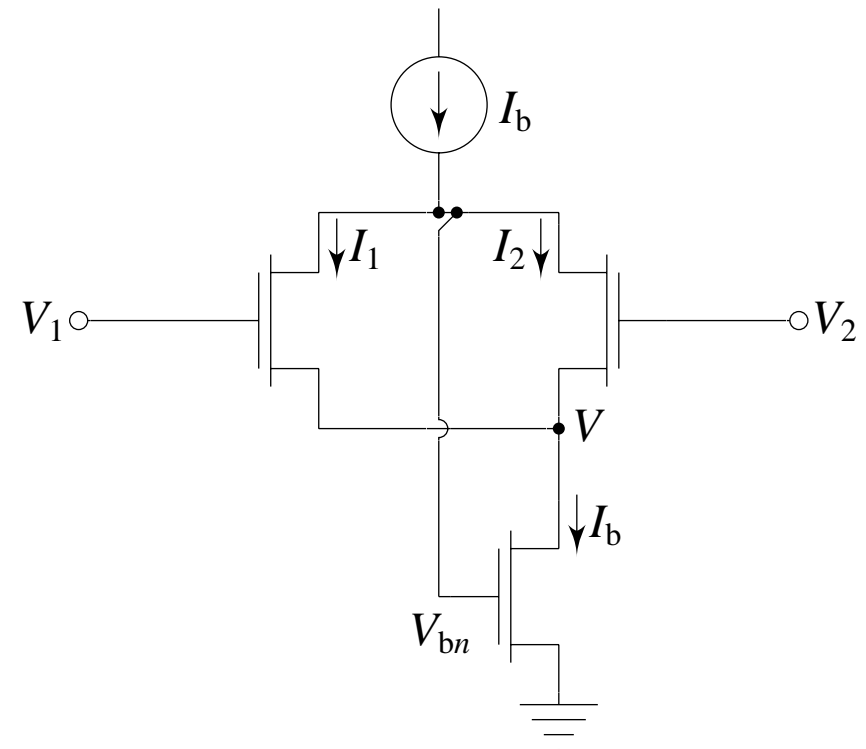- If this upper limit on V_{cm} is undesirable, we can use the flipped diff pair core to bias a normal diff pair adaptively, as shown.




Extending the Common-Mode Input Range of the Differential Pair

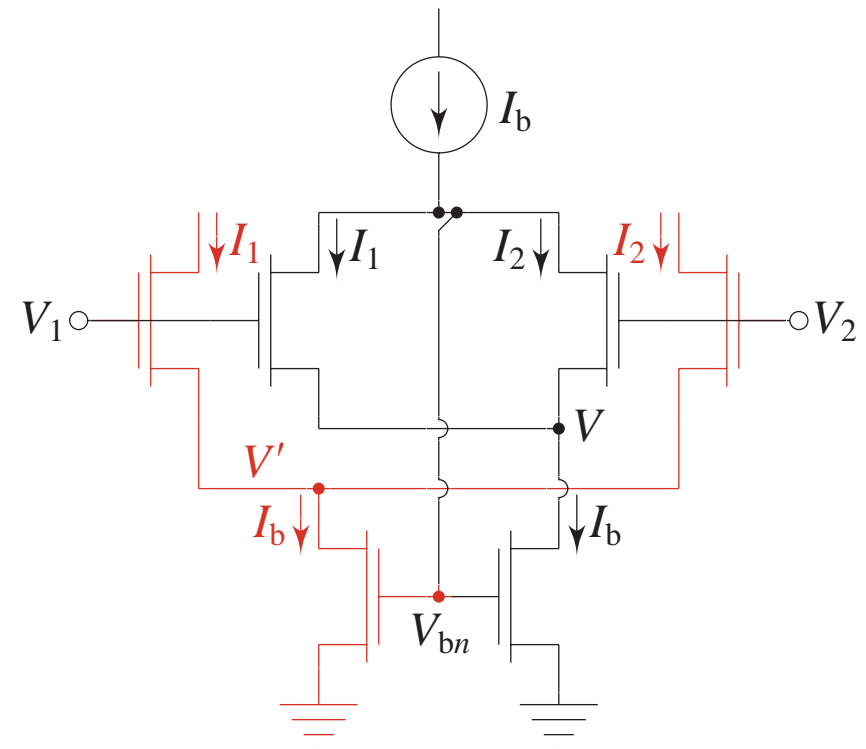- If this upper limit on V_{cm} is undesirable, we can use the flipped diff pair core to bias a normal diff pair adaptively, as shown.




Extending the Common-Mode Input Range of the Differential Pair

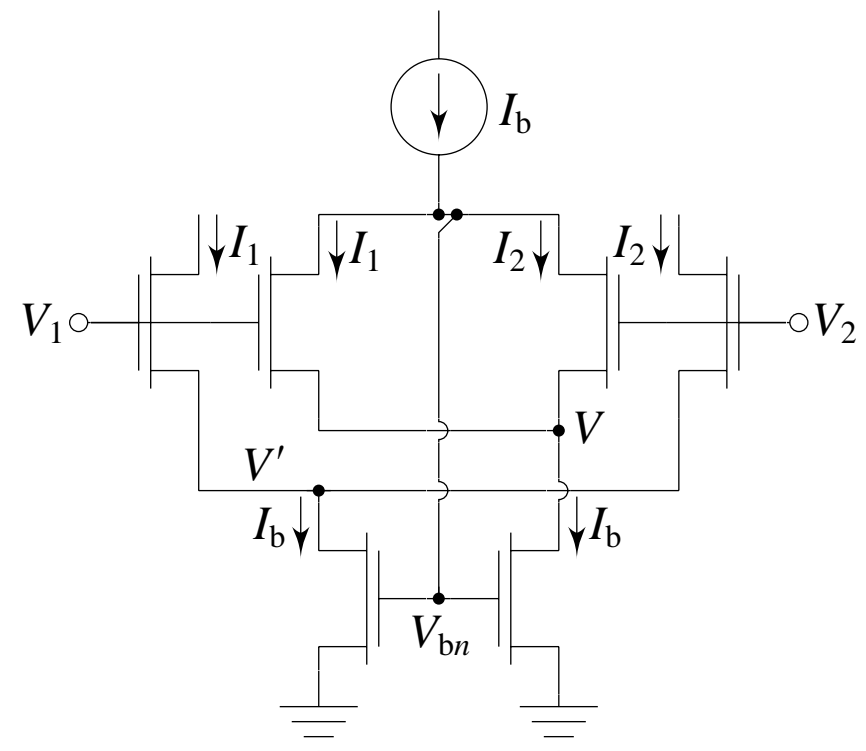- If this upper limit on V_{cm} is undesirable, we can use the flipped diff pair core to bias a normal diff pair adaptively, as shown.
- For high V_{cm} , the flipped diff pair behaves effectively as a diode connected transistor, and the normal diff pair behaves as usual.





Extending the Common-Mode Input Range of the Differential Pair



- If this upper limit on V_{cm} is undesirable, we can use the flipped diff pair core to bias a normal diff pair adaptively, as shown.
- For high V_{cm} , the flipped diff pair behaves effectively as a diode connected transistor, and the normal diff pair behaves as usual.
- For low V_{cm} , the central pair is saturated, $V = V'$, and V_{bn} adjusts itself to keep $I_1 + I_2 = I_b$, even if $V = V' \leq V_{DSsat}$.

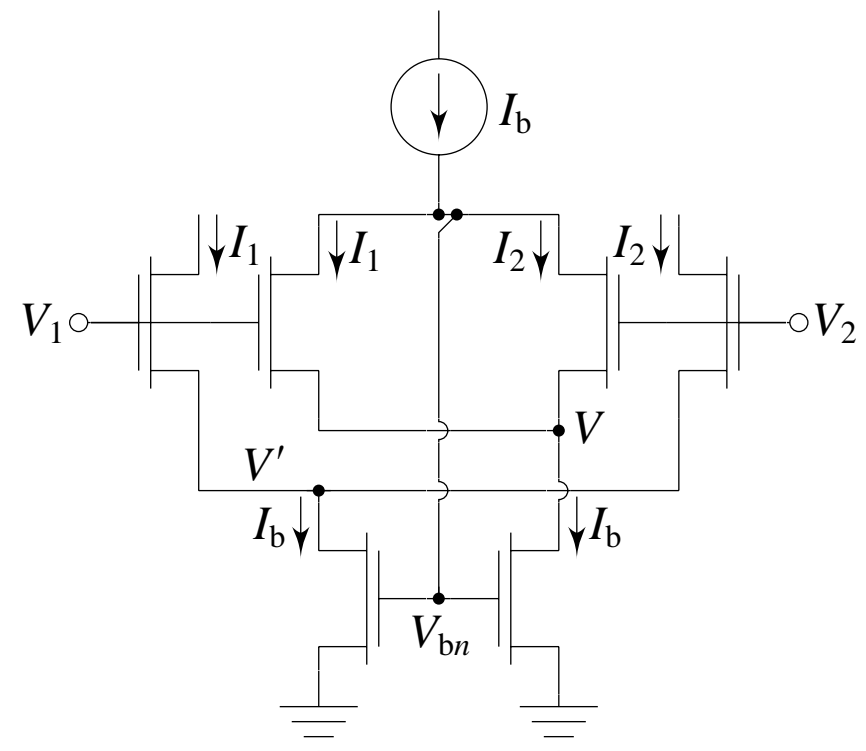



Experimental Common-Mode Characteristics

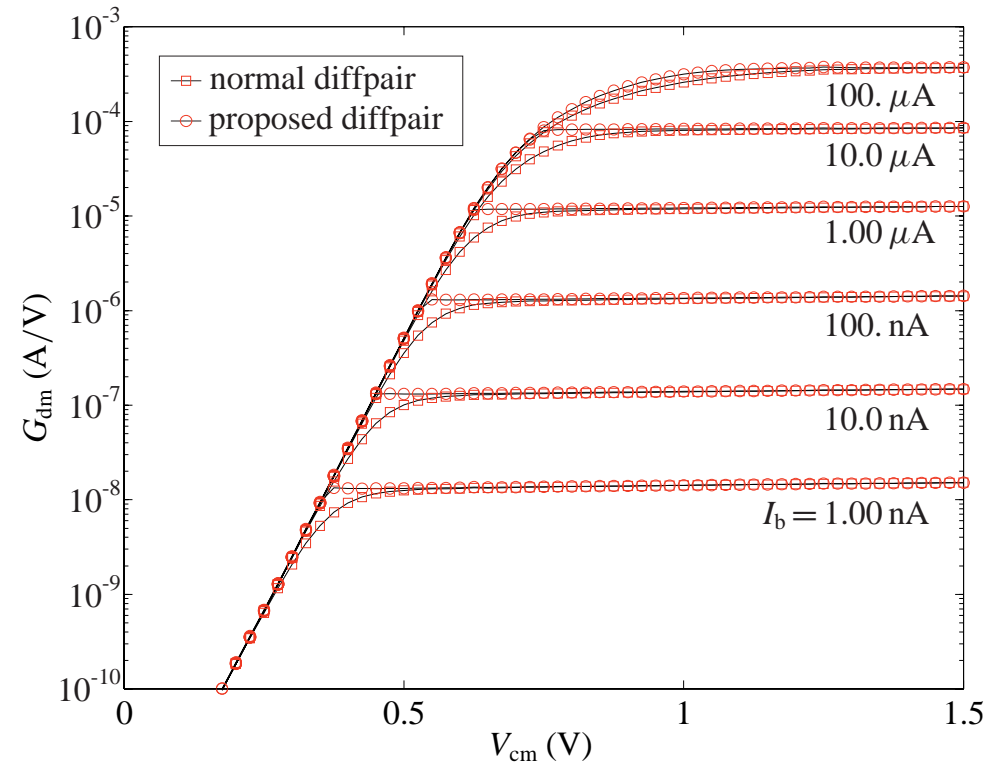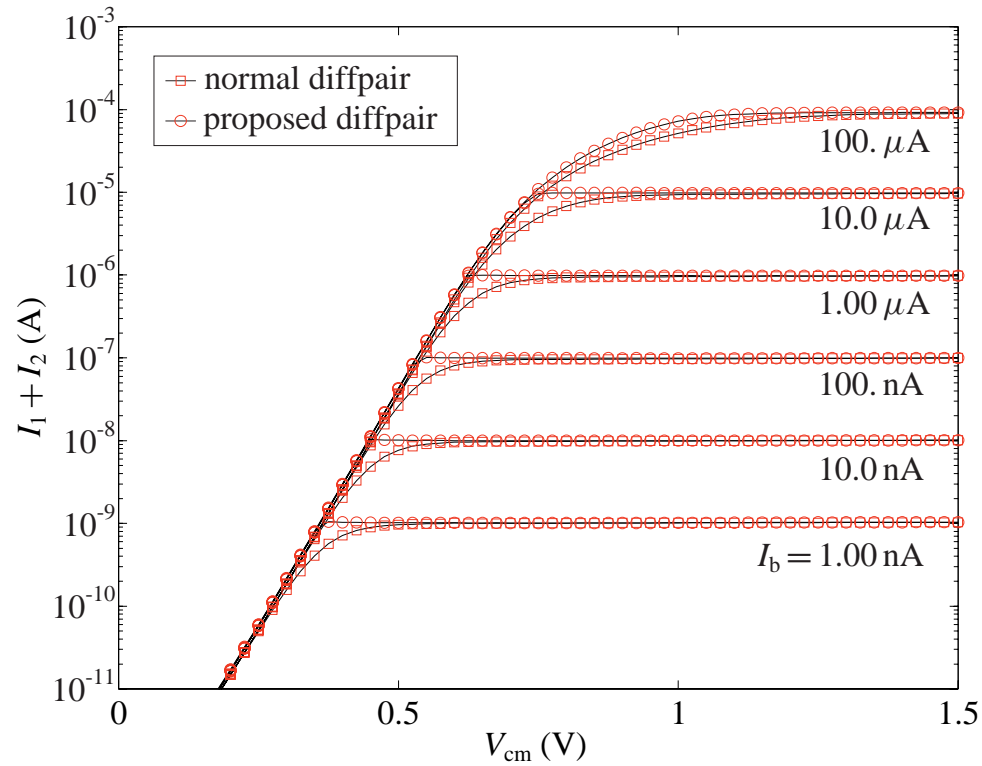

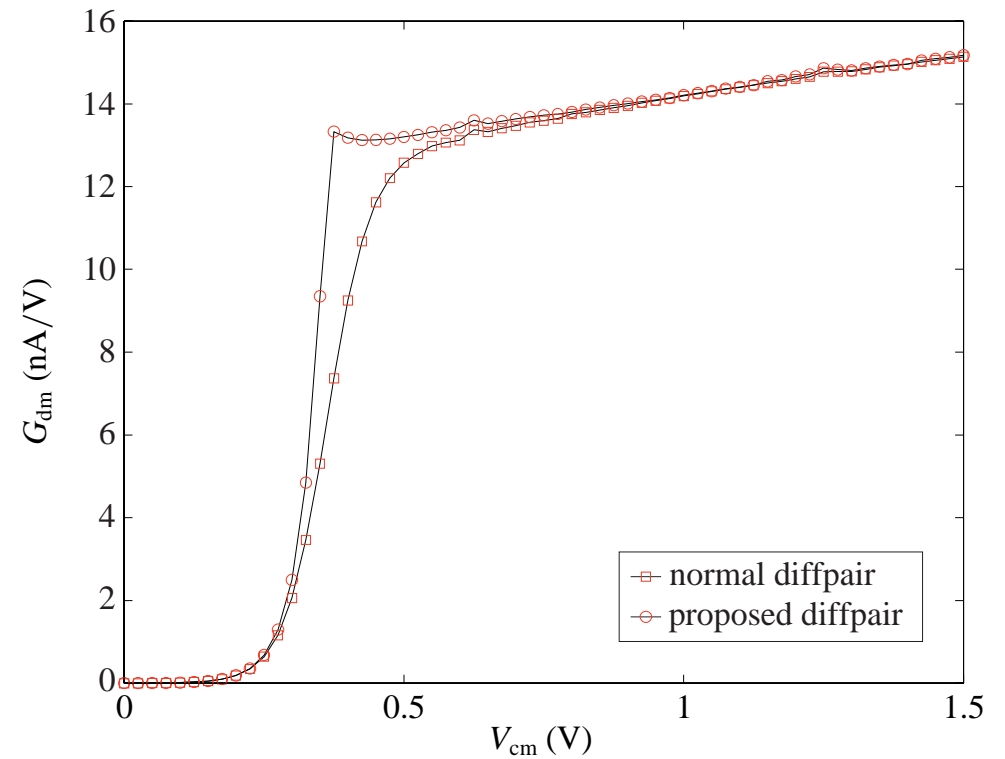
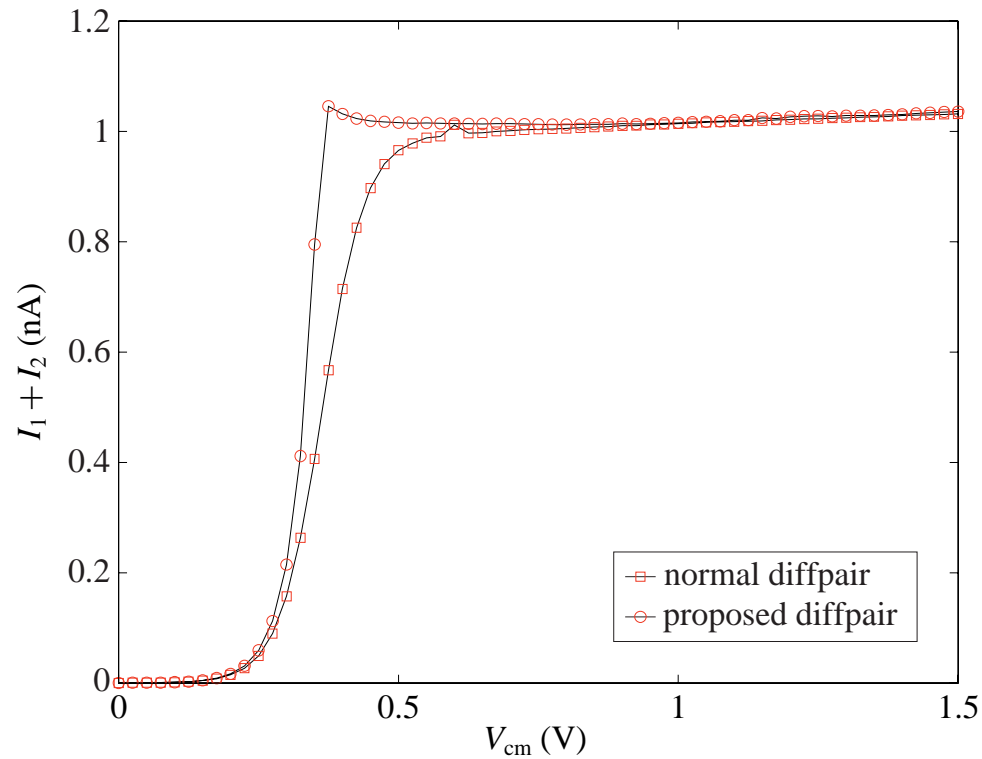
Experimental Common-Mode Characteristics: $I_b = 1.00 \text{ nA}$



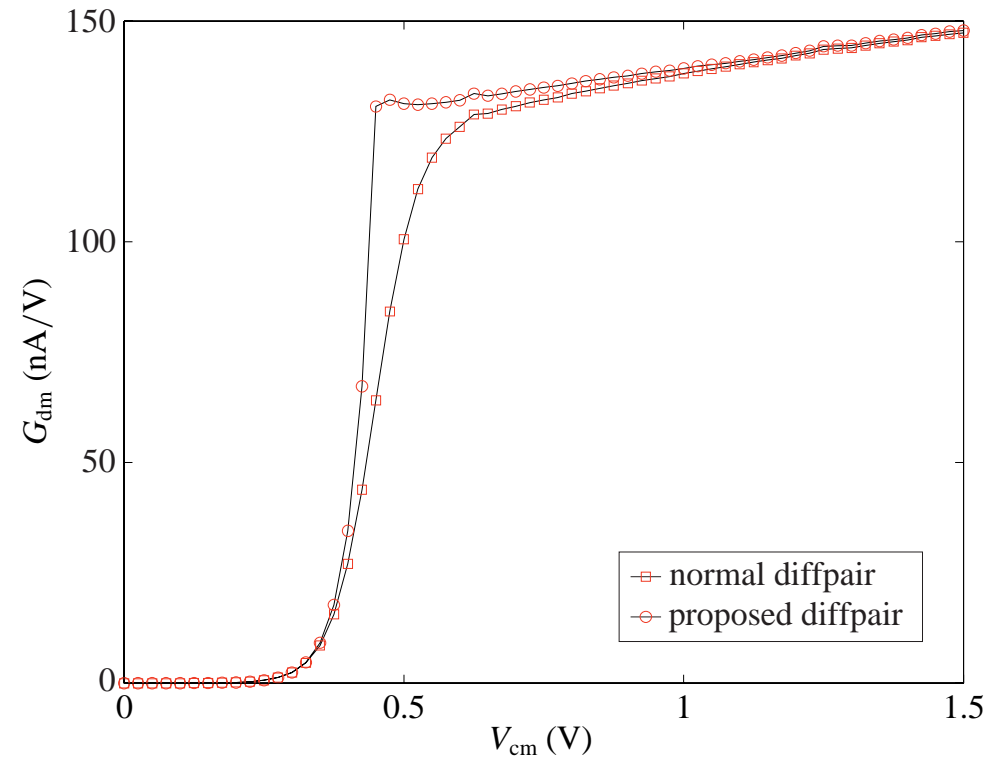
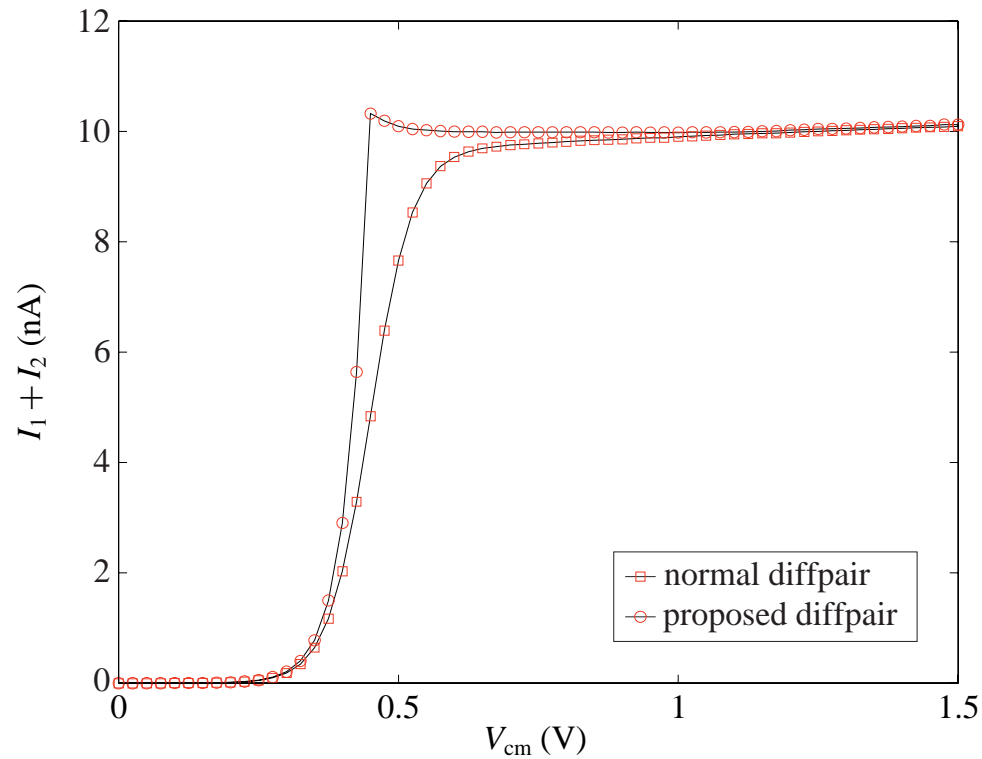
Experimental Common-Mode Characteristics: $I_b = 10.0 \text{ nA}$



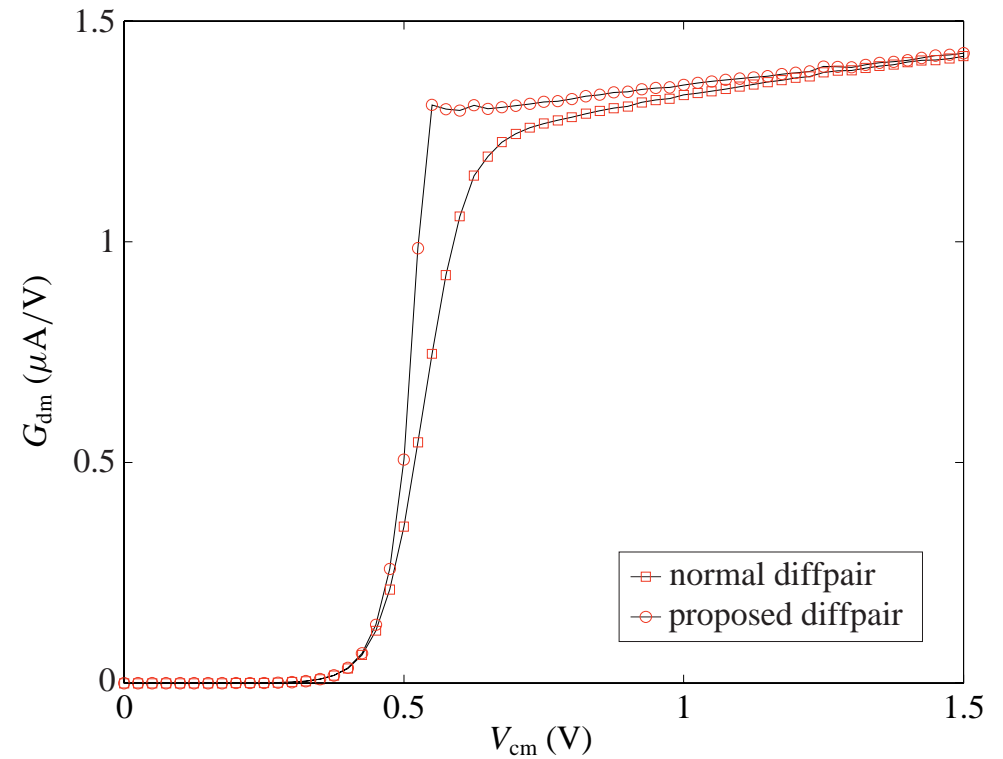
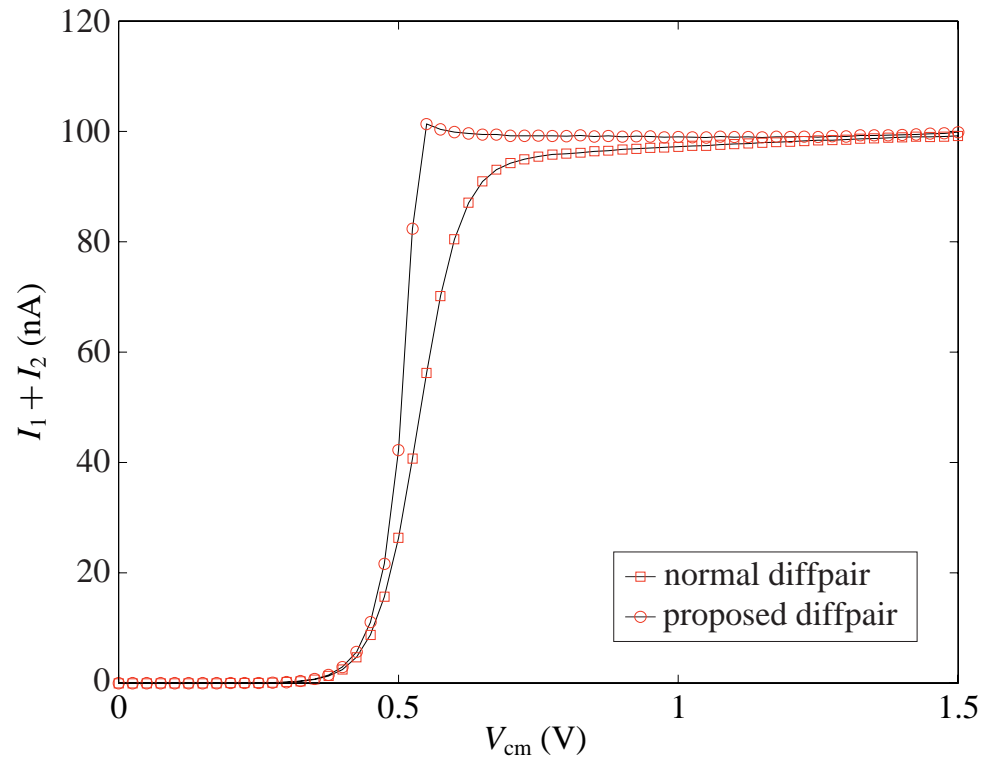
Experimental Common-Mode Characteristics: $I_b = 100. \text{nA}$



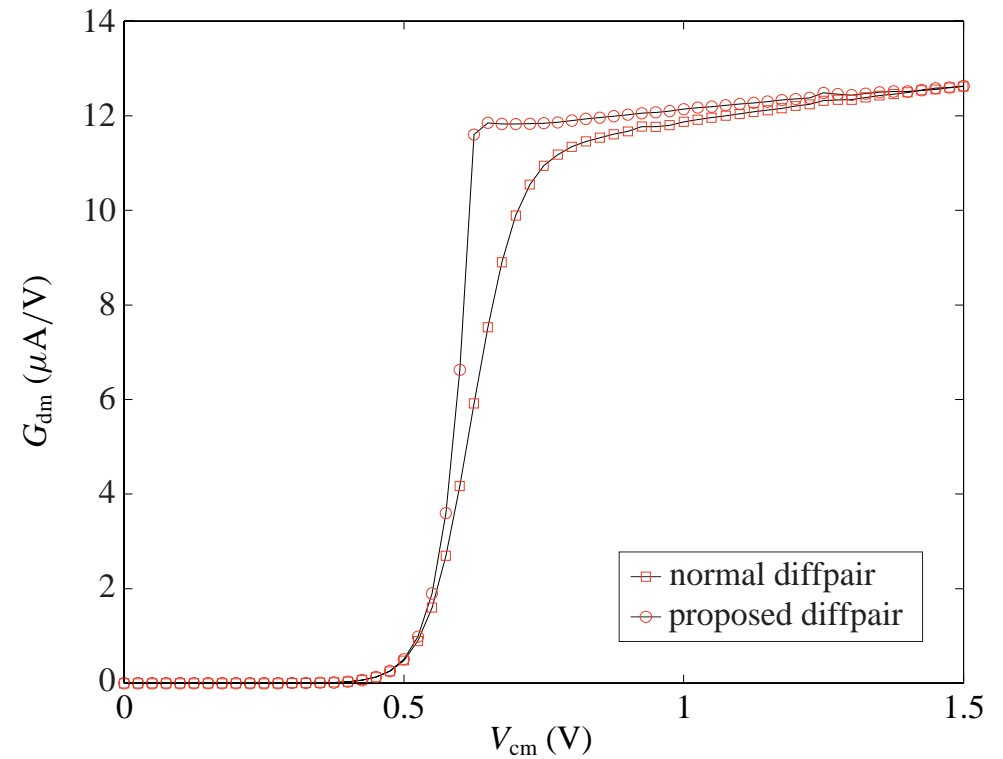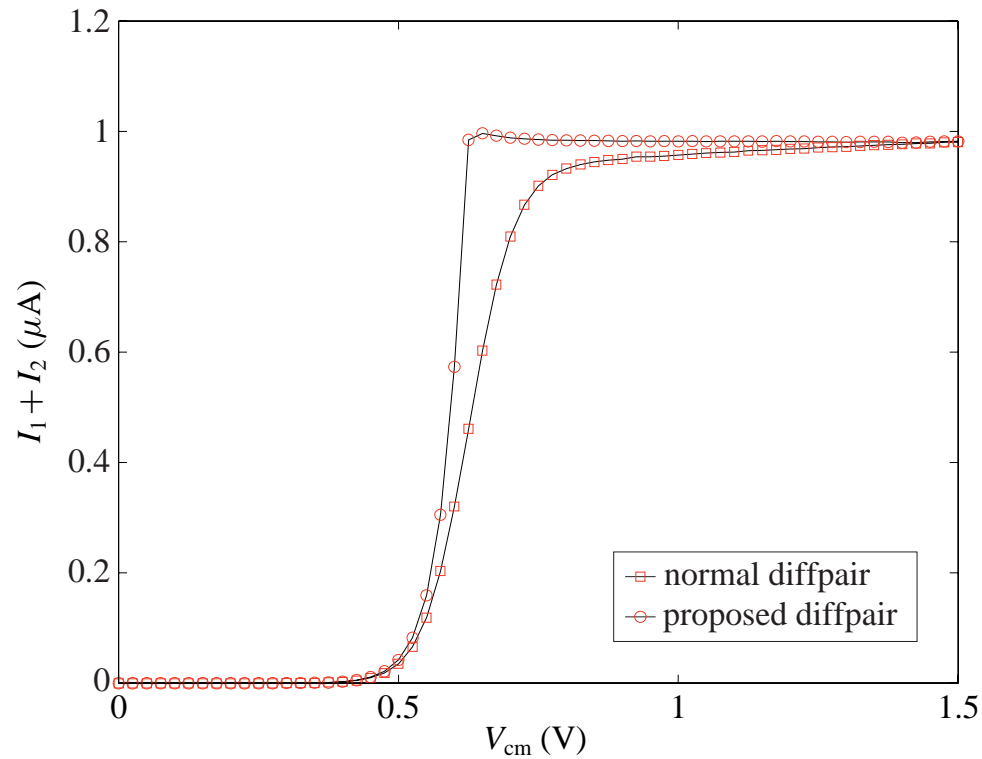Experimental Common-Mode Characteristics: $I_b = 1.00 \mu\text{A}$



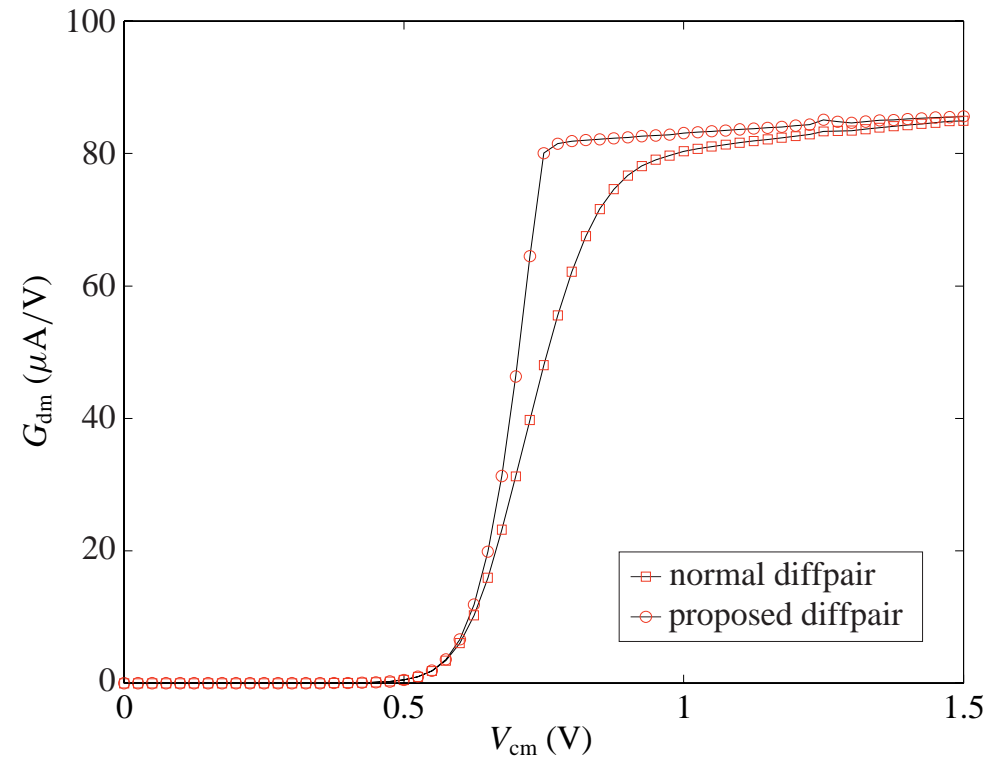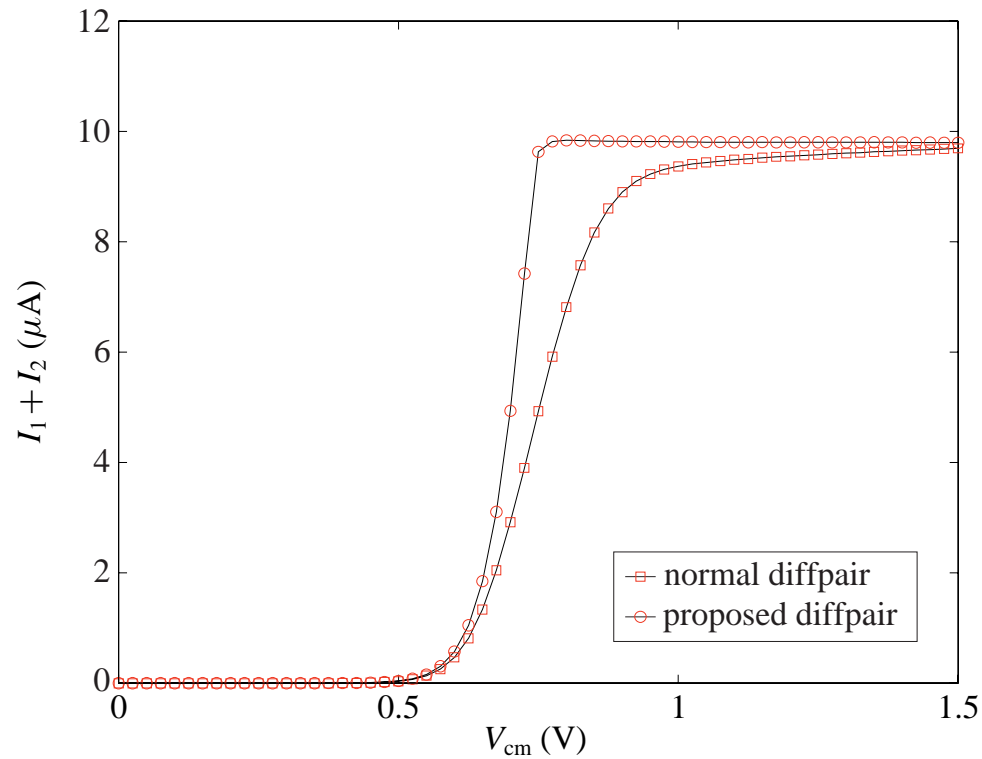Experimental Common-Mode Characteristics: $I_b = 10.0 \mu\text{A}$



Experimental Common-Mode Characteristics: $I_b = 100. \mu\text{A}$

