


A Folded Floating-Gate Differential Pair for Low-Voltage Applications

Bradley A. Minch

School of Electrical and Computer Engineering
Cornell University
Ithaca, NY 14853-5401


minch@ee.cornell.edu
<http://www.ee.cornell.edu/~minch>

Conventional Differential Pairs

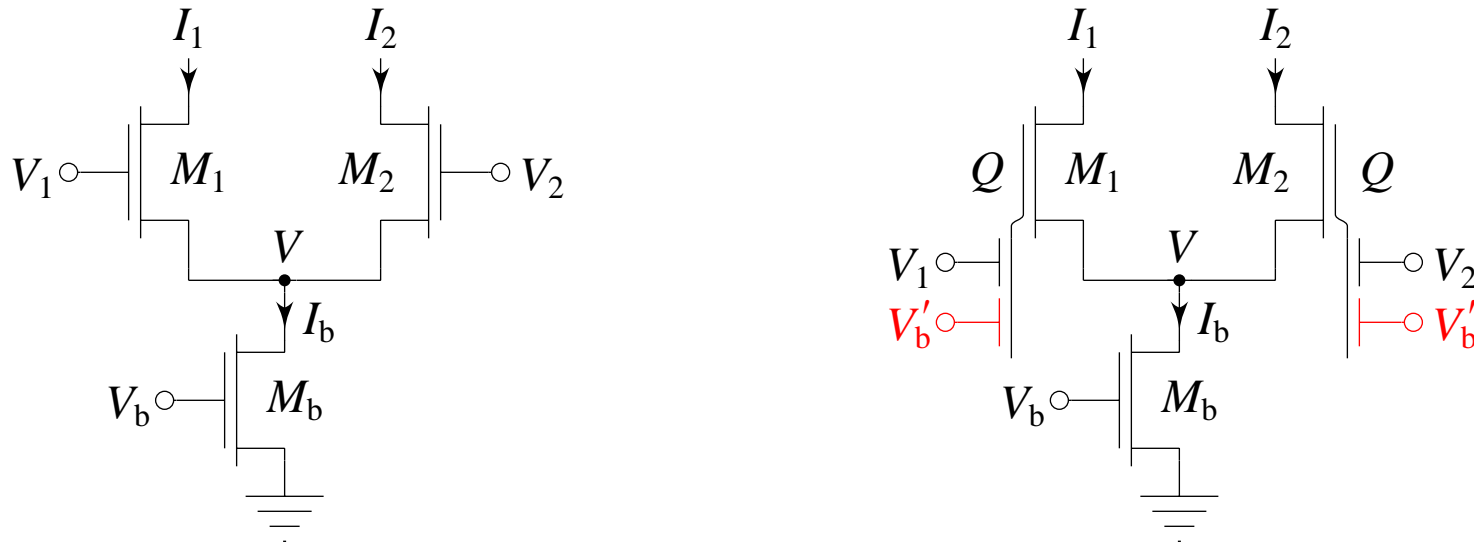


- ▶ We let V adjust itself so that $I_1 + I_2 \rightarrow I_b$.
- ▶ We must ensure that M_1 and M_2 have sufficient V_{gs} to pass I_b and that $V \geq V_{sat}$ to keep M_b saturated.
- ▶ We must ensure that M_1 and M_2 have sufficient V_{ds} to keep them saturated.

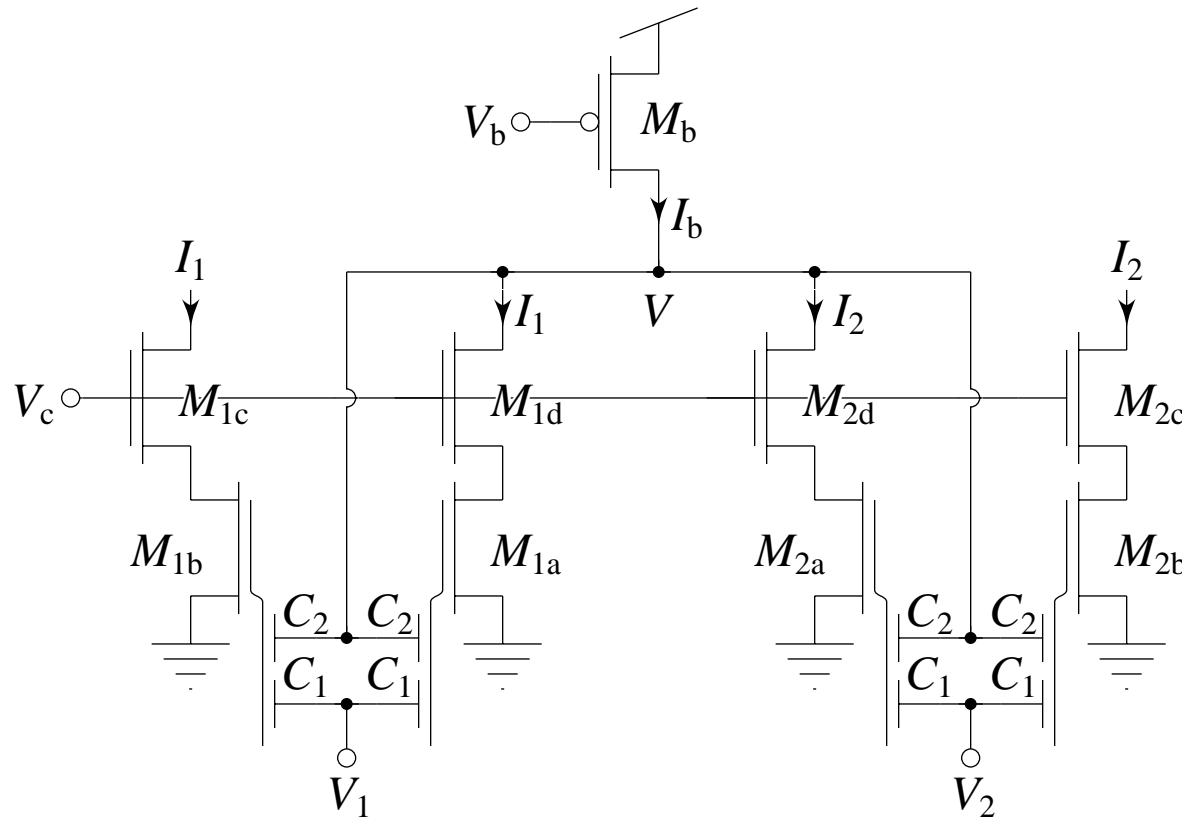A **Folded** Floating-Gate Differential Pair




- ▶ M_{1a} and M_{1b} both pass I_1 and M_{2a} and M_{2b} both pass I_2 .
- ▶ We let V adjust itself so that $I_1 + I_2 \rightarrow I_b$.
- ▶ Bias transistor and the excursion of V are both *folded* relative to a conventional differential pair.
- ▶ Input and output voltage ranges from rail-to-rail.
- ▶ Constant differential-mode transconductance.

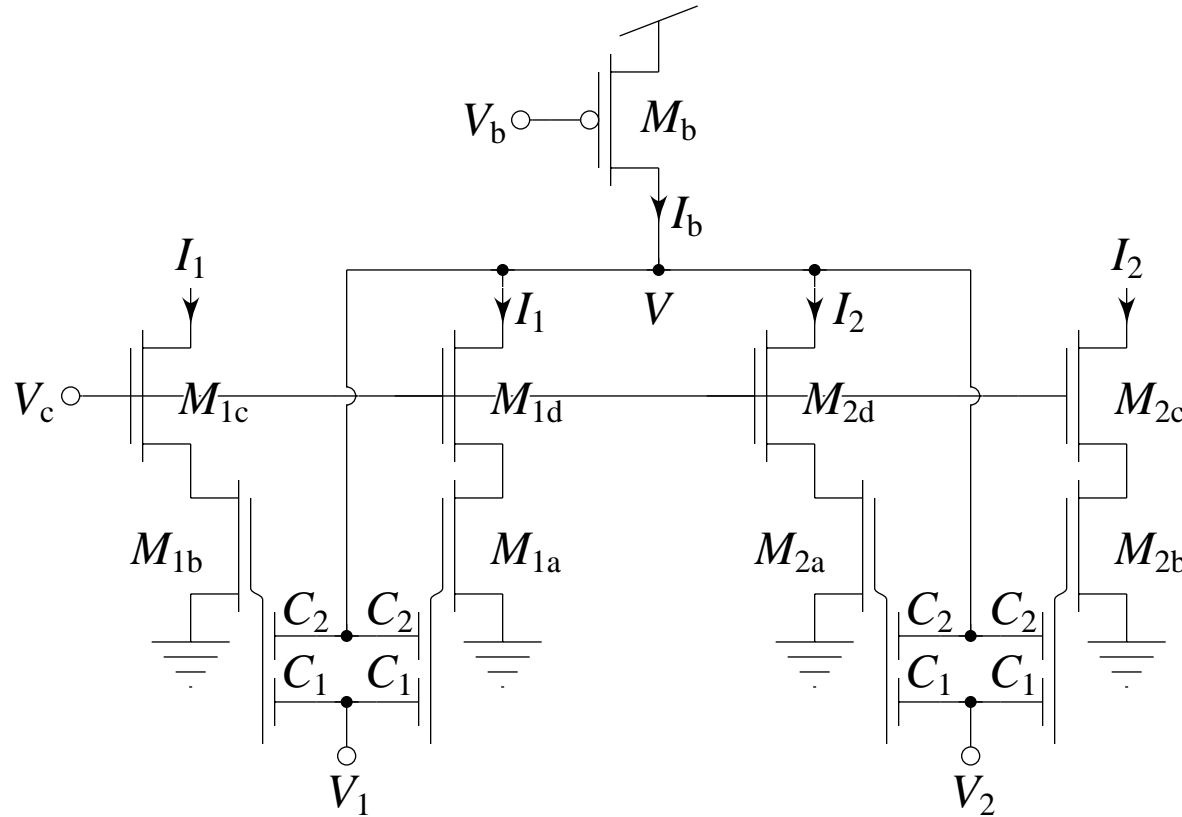A **Folded** Floating-Gate Differential Pair





- ▶ M_{1a} and M_{1b} both pass I_1 and M_{2a} and M_{2b} both pass I_2 .
- ▶ We let V adjust itself so that $I_1 + I_2 \rightarrow I_b$.
- ▶ Bias transistor and the excursion of V are both *folded* relative to a conventional differential pair.

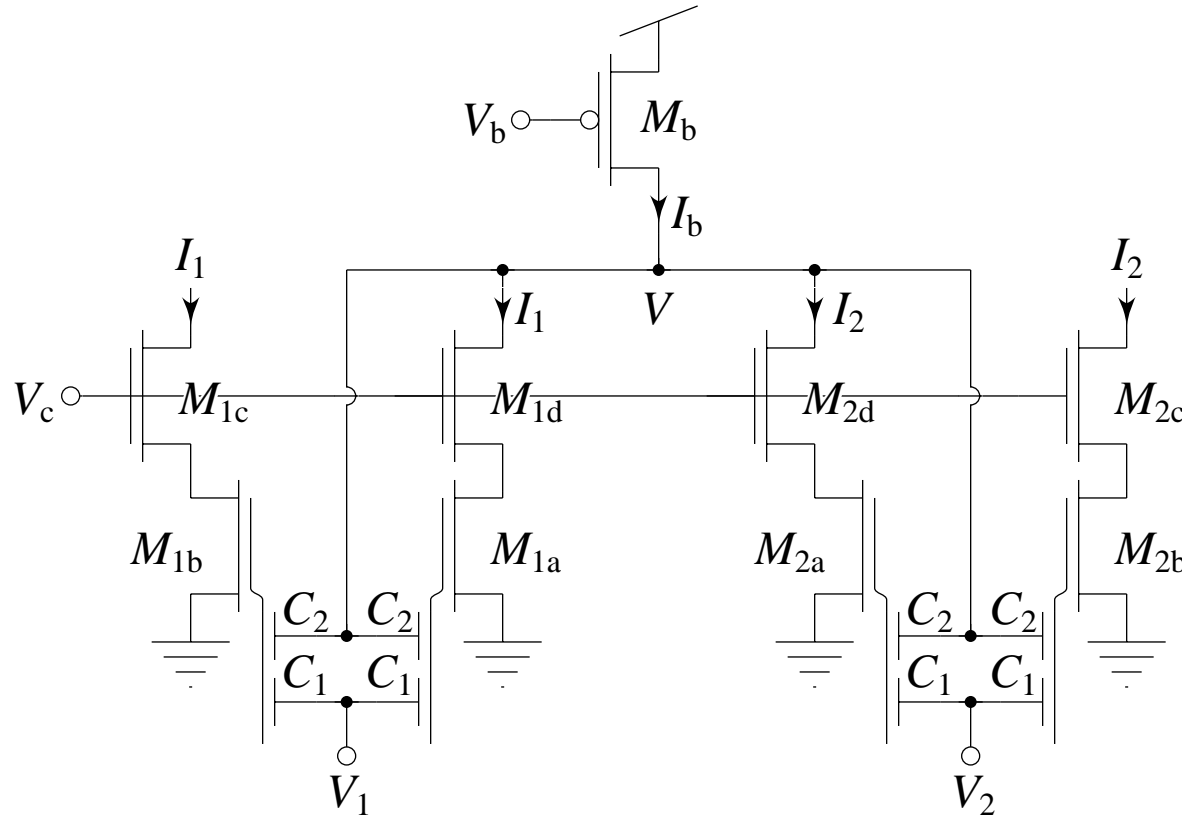A **Folded** Floating-Gate Differential Pair





- ▶ C_1 sets the linear range and transconductance gain.
- ▶ C_2 controls by how much V changes in response to changes in either V_{cm} or I_b .
- ▶ Input and output voltage ranges are from rail-to-rail.
- ▶ Transconductance constant with V_{cm} .

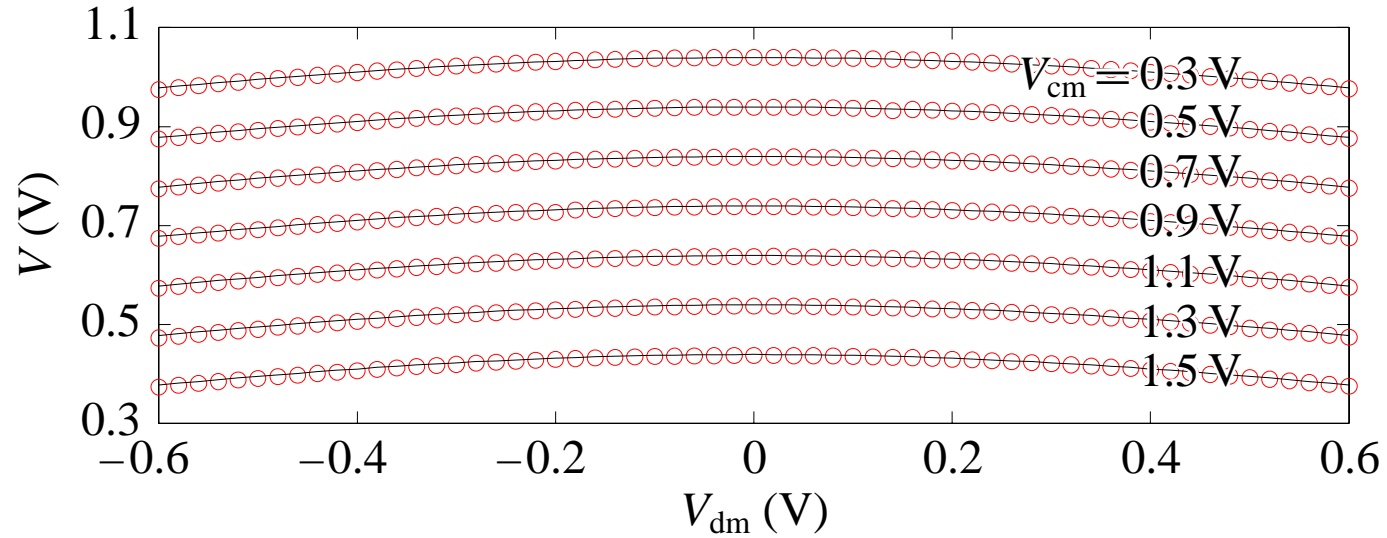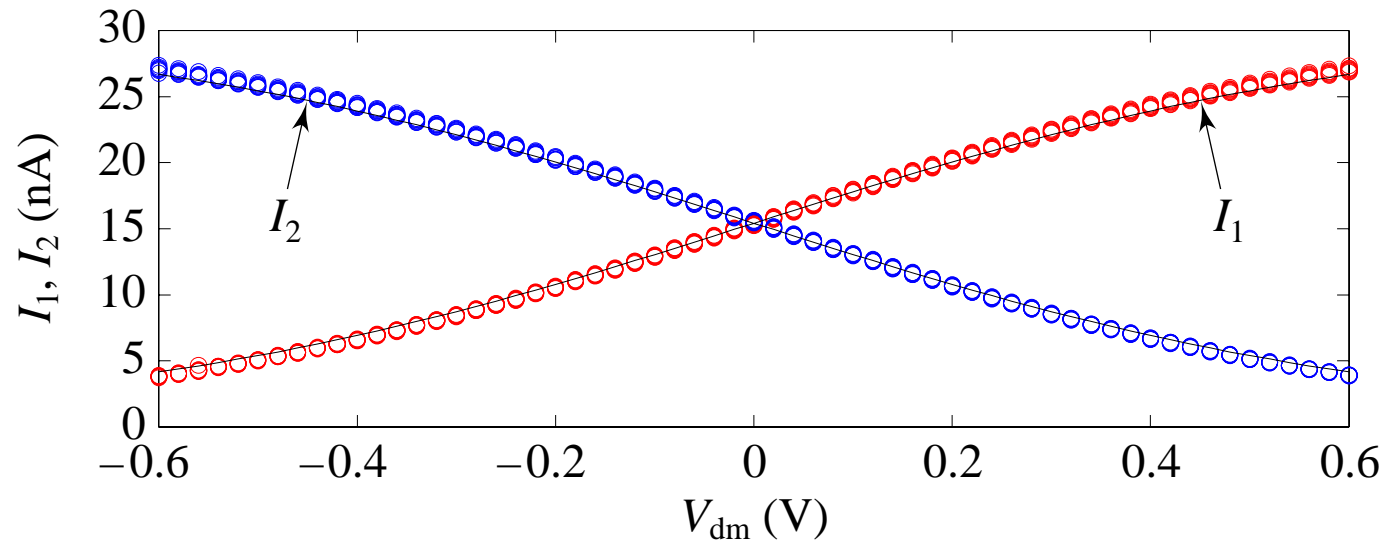
Output Currents vs V_{dm} for $I_b = 31.6$ nA



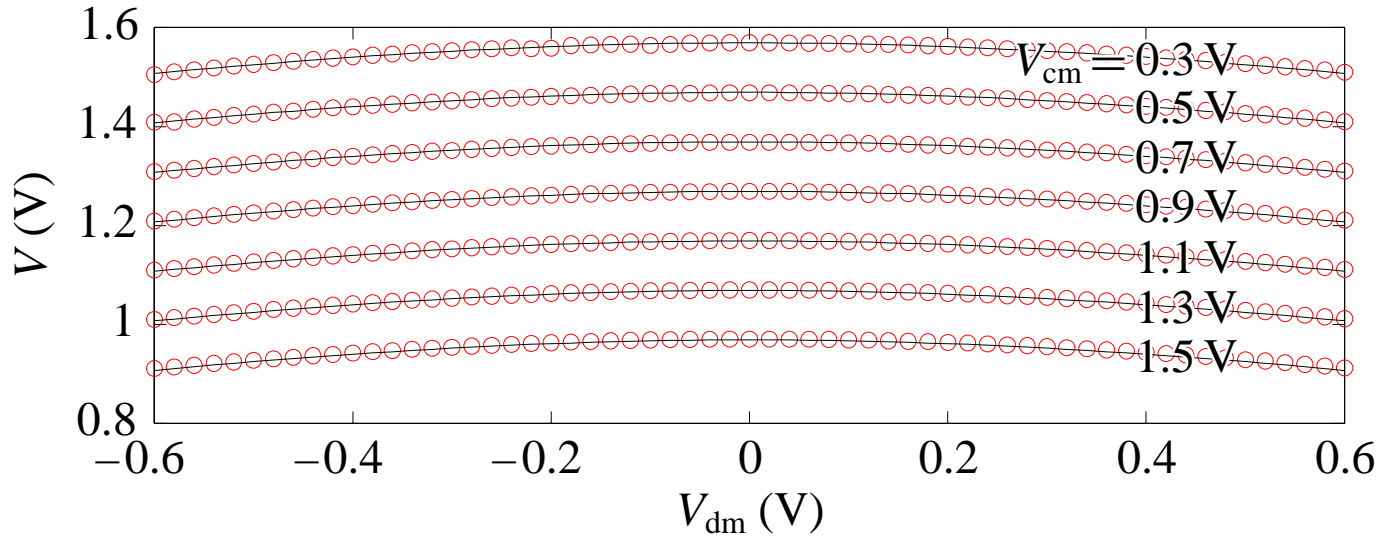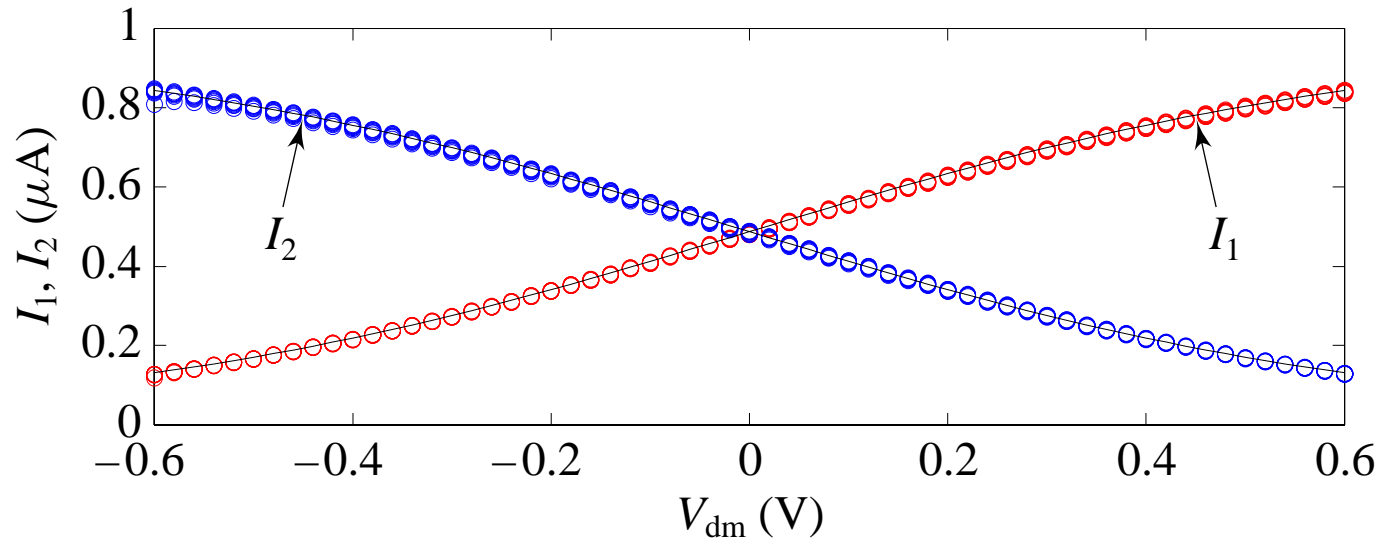Output Currents vs V_{dm} for $I_b = 1.00 \mu A$



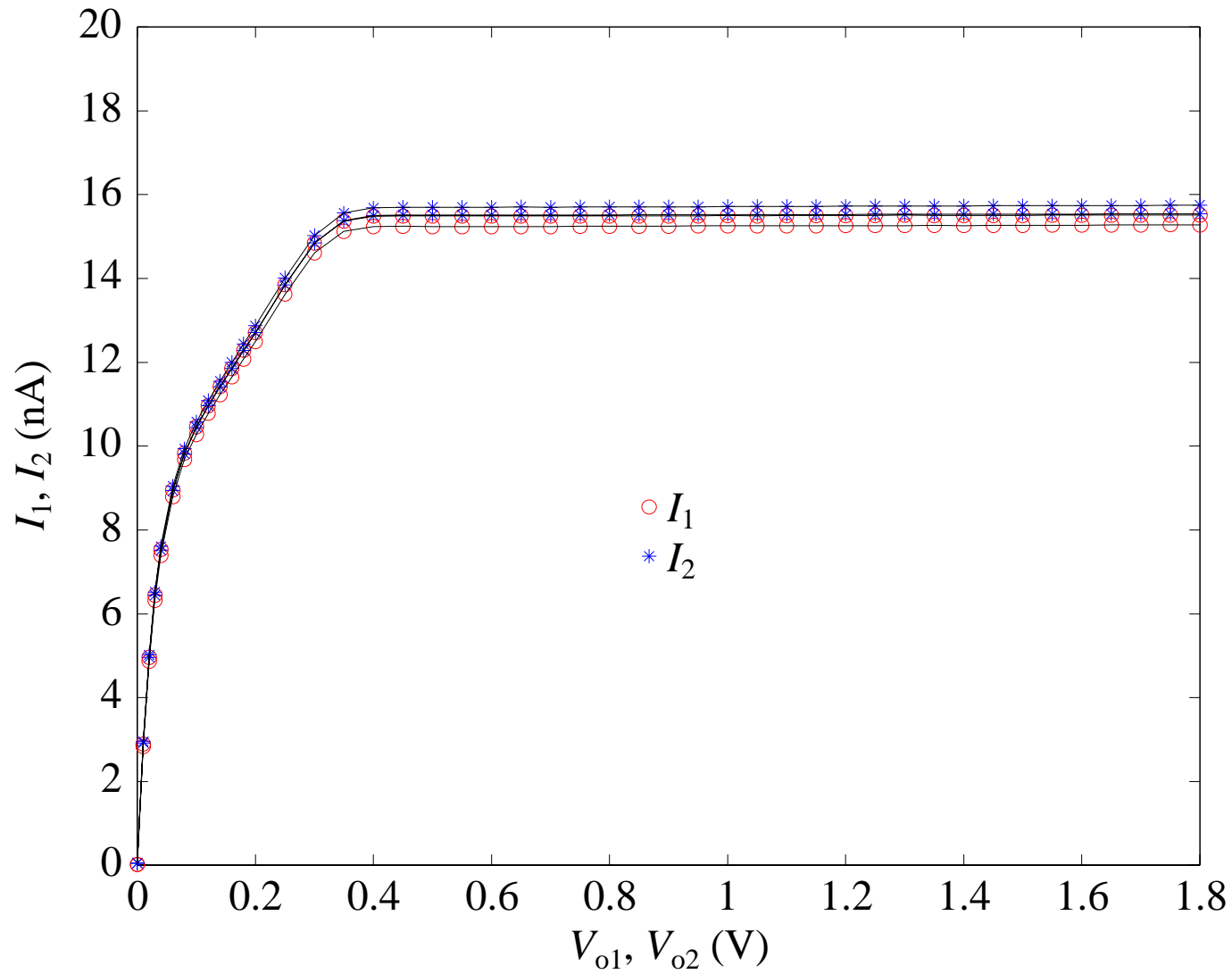Output Characteristics for $I_b = 31.6 \text{ nA}$



Output Characteristics for $I_b = 1.00 \mu\text{A}$

