



Folding the Differential Pair for Low-Voltage Applications

Bradley A. Minch

Mixed Analog-Digital VLSI Circuits and Systems Laboratory
School of Electrical and Computer Engineering
Cornell University
Ithaca, NY 14853–5401



minch@ece.cornell.edu
<http://people.ece.cornell.edu/minch>

Conventional MOS Differential Pairs

  

- ▶ The differential pair is widely used as an input stage for operational amplifiers, comparators, mixers, and many other circuits.
- ▶ This circuit does not function well with a low power-supply voltage, because transistor M_b shuts off if V_1 and V_2 get too close to the appropriate rail.


Conventional MOS Differential Pairs

  

Differential-pair intuition:

- ▶ $I_1 = f(V_1, -V)$ and $I_2 = f(V_2, -V)$, where f is expansive.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.

Capacitive Voltage Dividers

 


$$-C_1(V_1 - V) - C_2(V_2 - V) = Q$$

$$\Rightarrow (C_1 + C_2)V = C_1V_1 + C_2V_2 + Q$$

$$\Rightarrow V = \frac{C_1}{C_1 + C_2} V_1 + \frac{C_2}{C_1 + C_2} V_2 + \frac{Q}{C_1 + C_2}$$


- ▶ The voltage on the middle node is a weighted sum of the two input voltages.
- ▶ If node V is really floating, then the inputs couple into the floating node all the way down to DC!
- ▶ The charge Q linearly offsets the V . The charge can be adjusted either optically or electronically.

Floating-Gate MOS Transistors

 

- ▶ The capacitors C_1 and C_2 are called *control gates*.
- ▶ If floating-gate voltage, V , is a weighted sum of the control-gate voltages.
- ▶ The floating-gate charge, Q , can be thought of as giving us a programmable threshold voltage.

 
A **Folded** Floating-Gate Differential Pair



Differential-pair intuition:

- ▶ $I_1 = f(V_1, V)$ and $I_2 = f(V_2, V)$, where f is expansive.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.

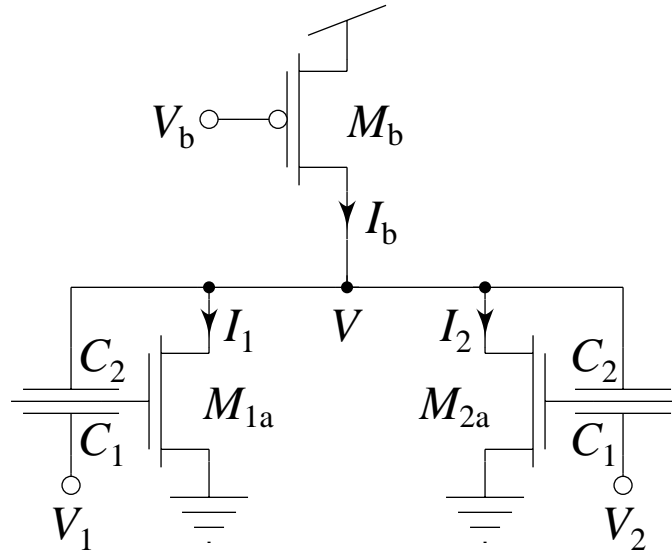A **Folded** Floating-Gate Differential Pair




Differential-pair intuition:

- ▶ $I_1 = f(V_1, V)$ and $I_2 = f(V_2, V)$, where f is expansive.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.

Sign difference permits us to *fold* M_b relative to M_1 and M_2 .

 A **Folded** Floating-Gate Differential Pair




Differential-pair intuition:

- ▶ $I_1 = f(V_1, V)$ and $I_2 = f(V_2, V)$, where f is expansive.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.

M_{1b} and M_{2b} provide mirror copies of I_1 and I_2 .

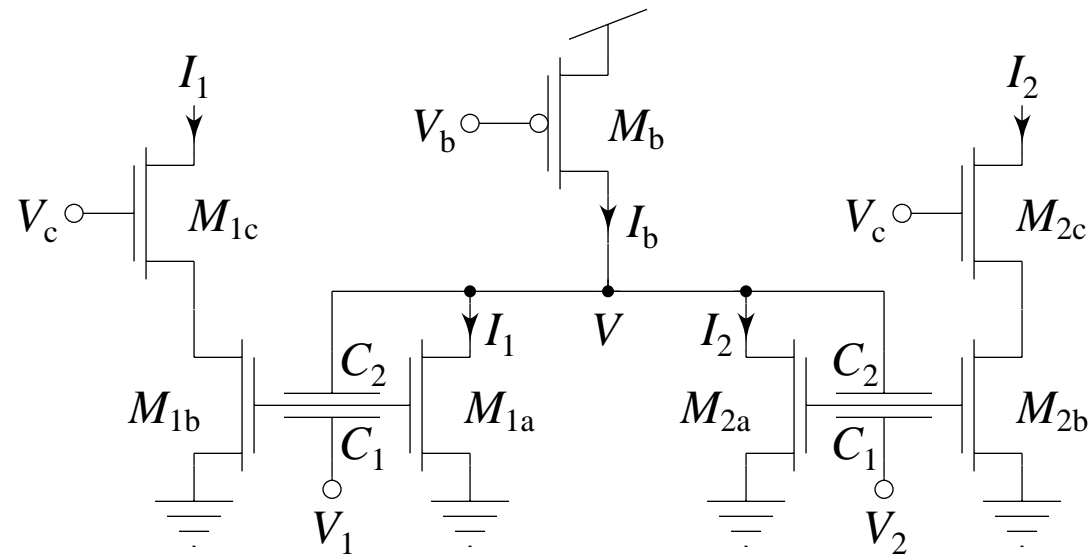A **folded** Floating-Gate Differential Pair




Differential-pair intuition:

- ▶ $I_1 = f(V_1, V)$ and $I_2 = f(V_2, V)$, where f is expansive.
- ▶ V adjusts itself so that $I_1 + I_2 \rightarrow I_b$.


M_{1c} and M_{2c} mitigate the C_{gd} 's of transistors M_{1b} and M_{2b} .

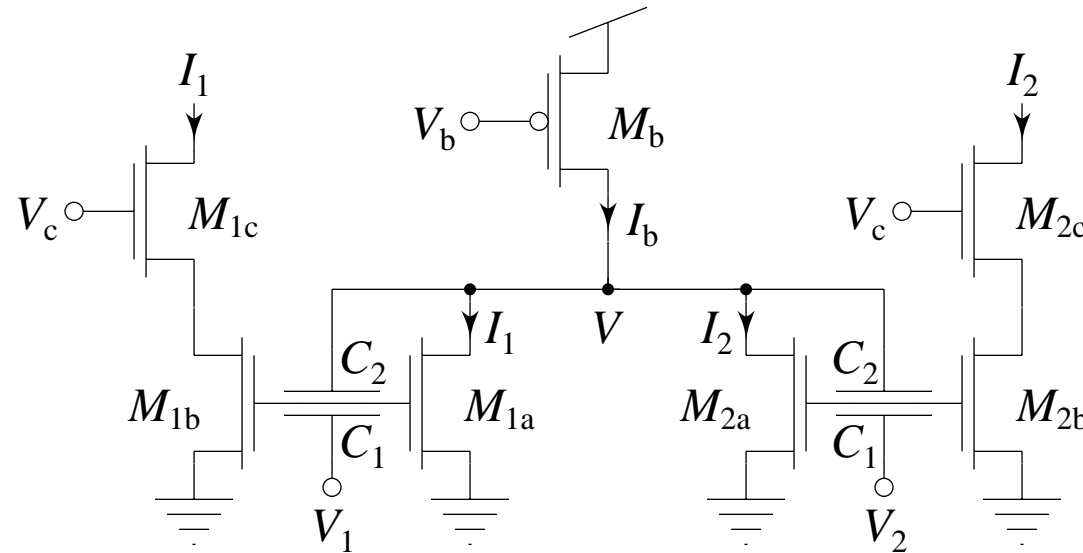A **Folded** Floating-Gate Differential Pair




- ▶ C_1 sets the linear range and transconductance gain.
- ▶ C_2 controls by how much V changes in response to changes in either V_{cm} or I_b .
- ▶ Input and output voltage ranges are from rail-to-rail.
- ▶ Transconductance gain nearly constant with V_{cm} .

 
Output Currents vs. V_{dm} ($I_b = 316 \text{ pA}$)



 
Output Currents vs. V_{dm} ($I_b = 31.6 \mu A$)




Transconductance Gain vs. V_{cm}

 

 
Output Currents vs. V_{out} ($I_b = 300 \text{ pA}$)



 
Output Currents vs. V_{out} ($I_b = 31.6 \mu A$)



Common-Mode Output Current vs. V_{out}

 


Variations on a Theme...

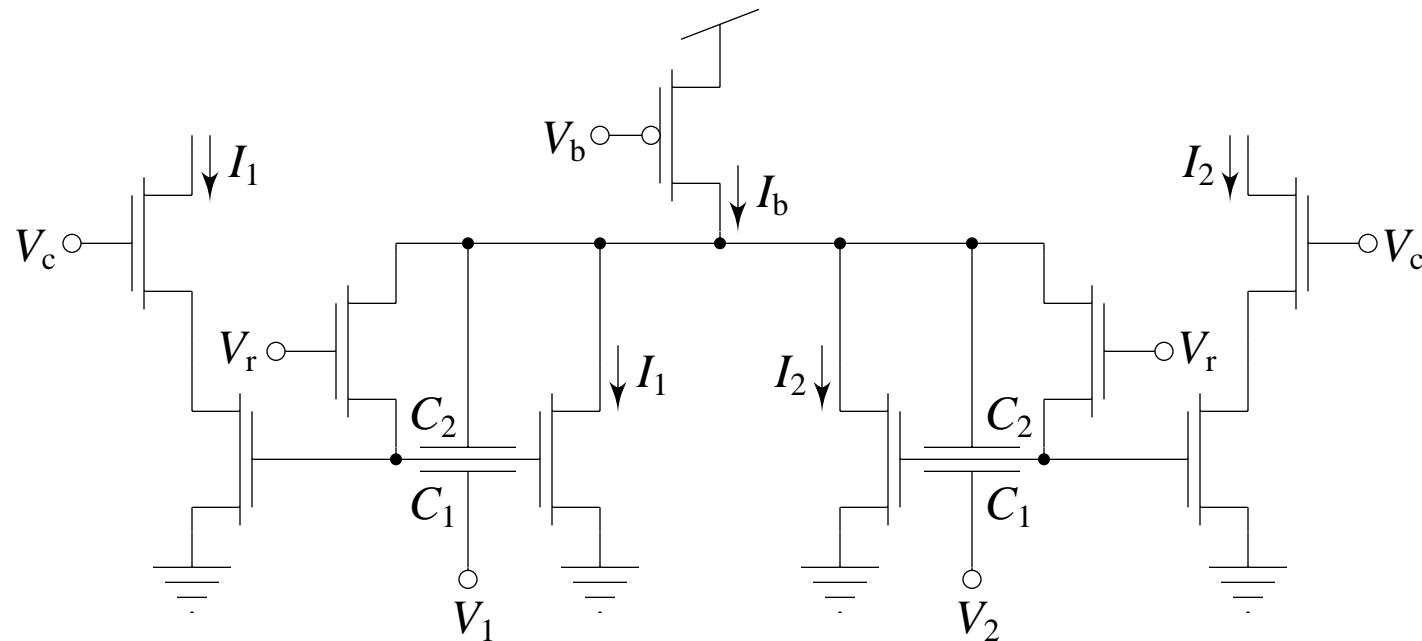


- ▶ Add resistive feedback to the floating gates in parallel with C_2 controlled by V_r .
- ▶ Resistive path introduces a first-order low-frequency roll-off whose corner frequency is set by C_T and V_r .
- ▶ At DC, the circuit is a pair of current mirrors sharing I_b equally. Above the corner, it acts as the FG circuit.

Variations on a Theme...

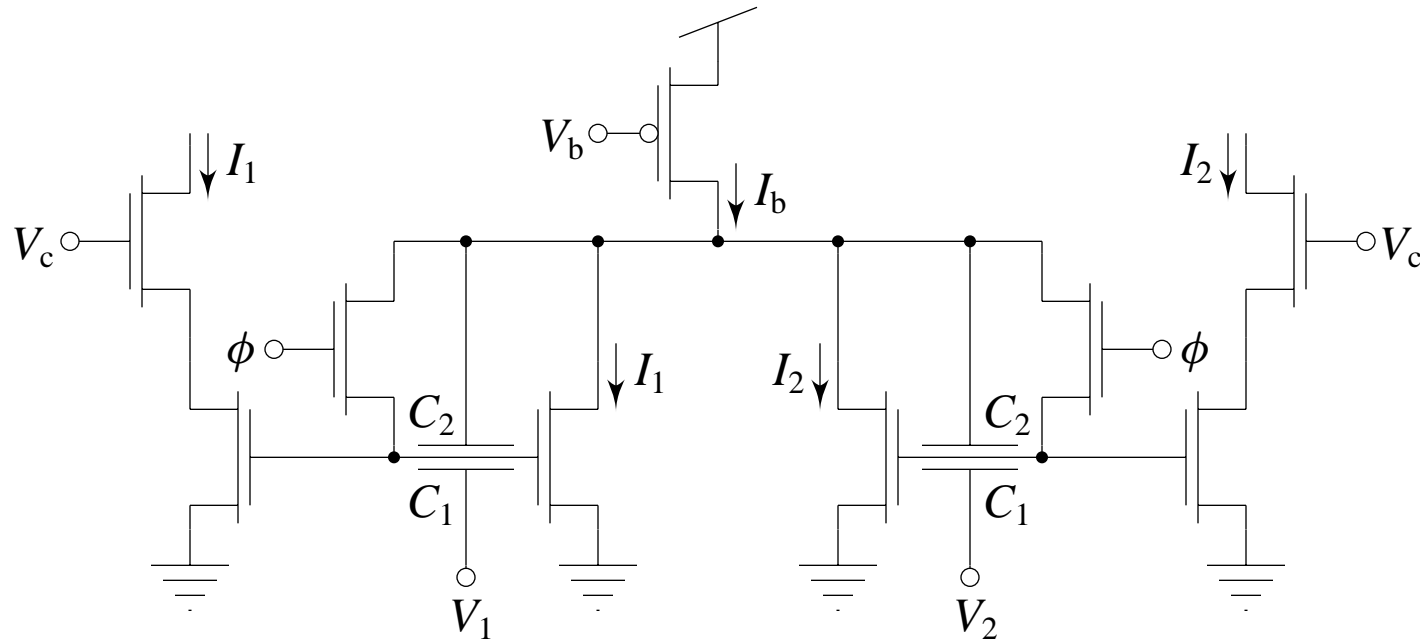


- ▶ Use feedback transistors as switches gated by a clock signal, ϕ .
- ▶ When ϕ is high, the circuit rebalances itself. When ϕ is low, the circuit acts just like the FG circuit.
- ▶ Injected charge is rejected as a common-mode signal if it matches on both sides.

Variations on a Theme...

 

- ▶ Rail-to-rail input common-mode range, wide output voltage swing.
- ▶ Acts very much like an emitter-degenerated bipolar differential pair.
- ▶ Input resistance primarily determined by R because base nodes are basically clamped by shunt feedback.

Incremental High-Frequency Analysis

 


► Given that $g_m(r_{on} \parallel 2r_{op}) \gg 1$ and $C_3 \ll C_2$, we can show that

$$i_{dm} \equiv i_1 - i_2 = g_m \frac{C_1}{C_T} \frac{1 - sC_3/g_m}{1 + s(C_3 + C_4)/g_s} v_{dm}$$

where $C_T \equiv C_1 + C_2 + C_3 + C_b$.

Incremental High-Frequency Analysis

 


...and that

$$i_{cm} \equiv \frac{i_1 + i_2}{2}$$

$$= \frac{C_1/C_2}{r_{on} \parallel 2r_{op}} \frac{(1 - sC_3/g_m)(1 + s(r_{on} \parallel 2r_{op})(C_2 + C/2))}{(1 + s(C_3 + C_4)/g_s)(1 + s(C_2 \parallel (C_1 + C_3 + C_b))/(g_m C_2 / C_T))} v_{cm}$$


Incremental High-Frequency Analysis

 

...and so

$$\text{CMRR} \equiv \frac{i_{\text{dm}}/v_{\text{dm}}}{i_{\text{cm}}/v_{\text{cm}}} = g_m (r_{\text{on}} \parallel 2r_{\text{op}}) \frac{C_2 (1 + s(C_2 \parallel (C_1 + C_3 + C_b)) / (g_m C_2 / C_T))}{C_T (1 + s(r_{\text{on}} \parallel 2r_{\text{op}})(C_2 + C/2))}$$

Folded FGMOS Differential Pair Layout

 

Chip Photomicrograph

