

## 6 Incremental Driving-Point Transfer Function Calculation of CMOS Circuits by Source Splitting

In this section, we shall illustrate the use of (voltage) source splitting to aid in the calculation of the incremental driving-point transfer functions of circuits made from MOS transistors, illustrating the technique by applying it to calculating the incremental input and output resistances of several simple circuits.

### 6.1 Incremental Transconductance Gain of a Source-Degenerated MOS Transistor


In this section, we shall derive a useful result, which gives the change in the channel current of a saturated MOS transistor in response to a small change in the gate voltage with *source degeneration*. If the source voltage were fixed, the change in the saturation current due to a small change in the gate voltage would be given by  $\delta I_{\text{sat}} = g_m \delta V_G$ . However, if the source voltage were connected to another device or circuit with a finite incremental terminal resistance,  $R_X$ , as shown on the left in Fig. 1, then the change in the saturation current also must flow into the terminal of X, causing  $V_S$  to increase. This increase in  $V_S$ , in turn, reduces the original increase in  $I_{\text{sat}}$  caused by the change in  $V_G$ . In such cases, the effective transconductance of the MOS transistor is reduced or *degenerated* from its value with  $V_S$  held constant, whence the name *source degeneration*.

We can write the change in the channel current of the MOS transistor due to the change in both the gate voltage and the source voltage as


$$\delta I_{\text{sat}} = g_m \delta V_G - g_s \delta V_S.$$

This same current increase also must flow into the other part of the circuit, so we can also write that

$$\delta I_{\text{sat}} = \frac{\delta V_S}{R_X}.$$

 

**Figure 1:** Incremental transconductance gain of an MOS transistor with source degeneration.

 

**Figure 2:** Stacked current mirror.

By equating these, we can solve for the change in the source voltage, which is given by

$$\delta V_S = \frac{g_m R_X}{1 + g_s R_X} \cdot \delta V_G.$$

We can substitute this result into the second equation for  $\delta I_{\text{sat}}$  to find that

$$\delta I_{\text{sat}} = \frac{g_m}{1 + g_s R_X} \cdot \delta V_G,$$

from which it follows that the incremental transconductance of the MOS transistor with source degeneration is given by

$$G_m = \frac{\delta I_{\text{sat}}}{\delta V_G} = \frac{g_m}{1 + g_s R_X}.$$

We shall make use of this result again and again in performing incremental circuit analyses.

## 6.2 Source Splitting and Incremental DP Transfer Functions

In this section, we shall illustrate the process of calculating incremental driving-point resistances/conductances using source splitting and superposition via several worked examples. For our first pair of examples, we shall determine the incremental input and output resistances of the stacked cascode current mirror, shown in Fig. 2, using source splitting and superposition. We shall assume that all four  $n$ MOS transistors are identical and that the output voltage,  $V_{\text{out}}$ , is sufficiently far above ground to keep both output transistors saturated.

### Example 6.1

To compute the incremental output resistance of the stacked mirror, we simply change the output voltage by a small amount,  $\delta V_{\text{out}}$ , and see how much additional current,  $\delta I_{\text{out}}$ , goes into the circuit. The ratio  $\delta V_{\text{out}}/\delta I_{\text{out}}$  gives us the incremental output resistance. To facilitate the calculation, we can apply voltage source splitting to  $V_{\text{out}}$  and superposition, as shown in Fig. 3.

The only nonzero components of  $\delta I_{\text{out}}$  occur when we change the first replica test voltage source, because the second one is connected to the drain of the (saturated) cascode transistor. We can write  $\delta I_{\text{out}}$  as

$$\begin{aligned}\delta I_{\text{out}} &= \frac{\delta V_{\text{out}}}{r_o + (r_o \parallel 1/g_s)} \left( 1 - \frac{g_s}{g_s + (1/r_o)} \right) \\ &= \frac{\delta V_{\text{out}}}{r_o + (r_o \parallel 1/g_s)} \cdot \frac{1/r_o}{g_s + (1/r_o)} \\ &= \frac{\delta V_{\text{out}}}{r_o + (r_o \parallel 1/g_s)} \cdot \frac{1}{g_s r_o + 1},\end{aligned}$$


which implies that the incremental output resistance is given by

$$R_{\text{out}} = \frac{\delta V_{\text{out}}}{\delta I_{\text{out}}} = (g_s r_o + 1) (r_o + (r_o \parallel 1/g_s)) \approx (g_s r_o) r_o,$$

because  $g_s r_o \gg 1$ . ■

### Example 6.2

To calculate the incremental input resistance of the stacked mirror, it is convenient to apply a voltage source, whose value is equal to the quiescent value of  $V_{\text{in}}$ , to the input node and change  $V_{\text{in}}$  by  $\delta V_{\text{in}}$  and calculate how much additional current goes into the circuit, as shown in Fig. 4. As we did in computing the incremental output resistance, we shall apply voltage-source splitting and superposition to facilitate the calculation. For each of the two simple current mirrors in the stack, we have a choice about whether or not to account for the Early effect on the input side of the circuit. The Early-effect resistors each effectively appear in parallel with a driving-point resistance that is on the order of  $1/g_s$ . Because  $1/g_s \ll r_o$ , it follows that  $1/g_s \parallel r_o \approx 1/g_s$ , which implies that these Early-effect resistors will have a negligible effect on the calculation. Neglecting the Early effect when possible greatly simplifies the analysis process. While accounting for the Early effect here is not

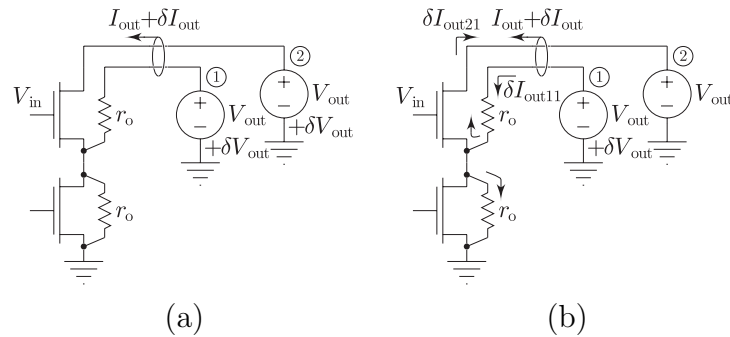

**Figure 3:** Calculation of the incremental output resistance of the stacked current mirror.

“wrong,” it can certainly be counter productive. Unnecessarily accounting for the Early effect complicates greatly the expressions that we get out of the analysis process, which makes them harder to interpret. It also increases our chances of making an error along the way. Learning to recognize where the Early effect is negligible and where it is not is an important bit of circuit intuition to develop.

If we neglect the Early effect on the input side of the circuit, after we apply the test voltage source to the input and split it, we have the circuit shown in Fig. 5a. The only nonzero components of  $\delta I_{\text{in}}$  occur when we change the input voltage source on the second branch, as shown in Fig. 4b. Of these, the only nonzero component occurs in the third branch. So, we can write  $\delta I_{\text{in}}$  as


$$\delta I_{\text{in}} = \frac{g_m \delta V_{\text{in}}}{\underbrace{1 + g_s (1/g_m)}_{\delta I_{\text{in}32}}} = \frac{g_m \delta V_{\text{in}}}{1 + (1/\kappa)} = \frac{\kappa}{\kappa + 1} \cdot g_m \delta V_{\text{in}},$$

which implies that the incremental input resistance is given by


$$R_{\text{in}} = \frac{\delta V_{\text{in}}}{\delta I_{\text{in}}} = \frac{\kappa + 1}{\kappa} \cdot \frac{1}{g_m}.$$

If we had not neglected the Early effect on the input side of the circuit, we would have the situation depicted in Fig. 6 after applying the test input voltage source and splitting it. Of the sixteen components of  $\delta I_{\text{in}}$ , the only nonzero ones occur when we change the input voltage sources on the second and fourth branches. Each of these two cases is illustrated in Fig. 7. By inspection of these circuits, we can write the incremental input current as

$$\begin{aligned} \delta I_{\text{in}} = & \frac{g_m \delta V_{\text{in}}}{\underbrace{1 + g_s (r_o \parallel r_o \parallel 1/g_m)}_{\delta I_{\text{in}32}}} \left( 1 - \frac{1/r_o}{\underbrace{(2/r_o) + g_m}_{\delta I_{\text{out}42}/\delta I_{\text{out}32}}} \right) \\ & + \frac{\delta V_{\text{in}}}{\underbrace{r_o + (1/g_s \parallel 1/g_m \parallel r_o)}_{\delta I_{\text{in}44}}} \left( 1 - \frac{g_s}{\underbrace{g_s + g_m + (1/r_o)}_{\delta I_{\text{out}34}/\delta I_{\text{out}44}}} \right) \end{aligned}$$

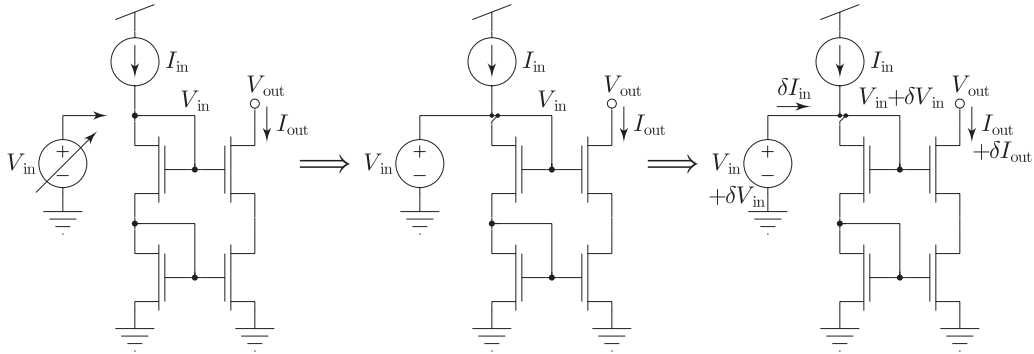

**Figure 4:** Set-up to determine the incremental input resistance of the stacked current mirror using the voltage-source method.

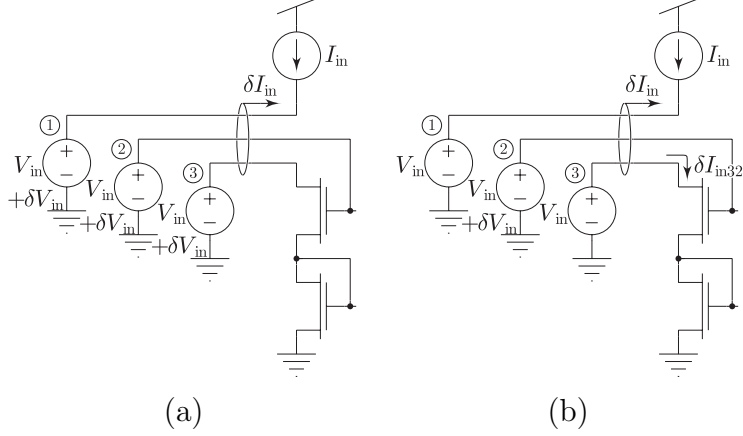


**Figure 5:** Calculation of the incremental input resistance of the stacked current mirror using voltage-source splitting and superposition under the assumption that the Early effect is negligible.


$$= \frac{g_m \delta V_{in}}{1 + g_s (r_o/2 \parallel 1/g_m)} \cdot \frac{g_m r_o + 1}{g_m r_o + 2} + \frac{\delta V_{in}}{r_o + ((1/g_s \parallel 1/g_m) \parallel r_o)} \cdot \frac{g_m r_o + 1}{(g_s + g_m) r_o + 1},$$

which implies that the incremental input resistance is given by


$$\begin{aligned} R_{in} &= \frac{\delta V_{in}}{\delta I_{in}} \\ &= \left( \left( \frac{1}{g_m} + \frac{1}{\kappa} \left( \frac{r_o}{2} \parallel \frac{1}{g_m} \right) \right) \frac{g_m r_o + 2}{g_m r_o + 1} \right) \\ &\quad \parallel \left( \left( r_o + \left( \left( \frac{1}{g_s} \parallel \frac{1}{g_m} \right) \parallel r_o \right) \right) \frac{(g_s + g_m) r_o + 1}{g_m r_o + 1} \right) \end{aligned}$$

 

**Figure 6:** Calculation of the incremental input resistance of the stacked current mirror using voltage-source splitting and superposition with the Early effect.

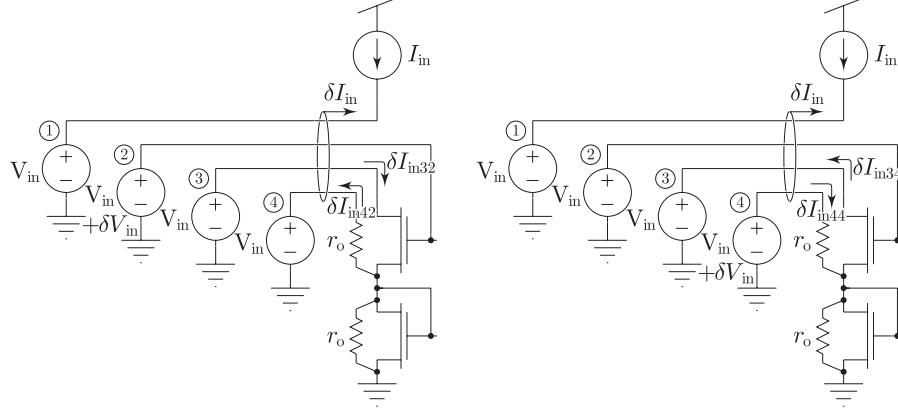

**Figure 7:** Continuation of the calculation of the incremental input resistance of the stacked current mirror using voltage source splitting and superposition with the Early effect.

 

**Figure 8:** Wilson current mirror.

$$\begin{aligned}
&\approx \left( \frac{1}{g_m} + \frac{1}{\kappa} \cdot \frac{1}{g_m} \right) \parallel \left( \left( r_o + \left( \frac{1}{g_s} \parallel \frac{1}{g_m} \right) \right) \frac{g_s + g_m}{g_m} \right) \\
&\approx \left( \frac{\kappa + 1}{\kappa} \cdot \frac{1}{g_m} \right) \parallel \left( \frac{\kappa + 1}{\kappa} \cdot r_o \right) \\
&= \frac{\kappa + 1}{\kappa} \left( \frac{1}{g_m} \parallel r_o \right) \\
&\approx \frac{\kappa + 1}{\kappa} \cdot \frac{1}{g_m},
\end{aligned}$$

where all of the approximations that we just made follow from the fact that  $g_s r_o \gg 1$ . This result is precisely what we found before with a whole lot less difficulty by neglecting the Early effect. ■

Next, we shall determine the incremental input and output resistances of the Wilson current mirror, shown in Fig. 8, using source splitting and superposition. We shall assume that all three  $n$ MOS transistors are identical and that the output voltage,  $V_{\text{out}}$ , is held sufficiently far above ground to keep the output transistor,  $M_3$ , saturated.

### Example 6.3

To calculate the incremental input resistance of the Wilson mirror, it is convenient again to apply a voltage source, whose value is equal to the quiescent value of  $V_{in}$ , to the input node and change  $V_{in}$  by  $\delta V_{in}$  and calculate how much additional current goes into the circuit, as shown in Fig. 9. As we did in computing the incremental input and output resistances of the stacked mirror, we shall apply voltage-source splitting and superposition to facilitate the calculation. Also, we shall neglect the Early effect for each of the three transistors in the circuit, because transistor  $M_1$  is effectively diode connected through  $M_3$  and  $M_2$ , because  $M_2$  is actually diode connected, and because the drain of  $M_3$  is held fixed for this calculation.

After we apply the test voltage source to the input and split it, we have the circuit shown in Fig. 10a. The only nonzero components of  $\delta I_{in}$  occur when we change the input voltage source on the second branch, as shown in Fig. 10b. Of these, the only nonzero component occurs in the third branch. So, we can write  $\delta I_{in}$  as

$$\delta I_{in} = \frac{g_m \delta V_{in}}{\underbrace{1 + g_s(1/g_m)}_{\delta I_{in32}}} = \frac{g_m \delta V_{in}}{1 + (1/\kappa)} = \frac{\kappa}{\kappa + 1} \cdot g_m \delta V_{in},$$


which implies that the incremental input resistance is given by

$$R_{in} = \frac{\delta V_{in}}{\delta I_{in}} = \frac{\kappa + 1}{\kappa} \cdot \frac{1}{g_m}.$$


Thus, the incremental input resistance of the Wilson mirror is the same as that of the stacked mirror. ■

### Example 6.4

To compute the incremental output resistance of the Wilson mirror, we simply change the output voltage by a small amount,  $\delta V_{out}$ , and see how much additional current,  $\delta I_{out}$ , goes into the circuit. The ratio  $\delta V_{out}/\delta I_{out}$  gives us the incremental output resistance. To facilitate the calculation, we can apply voltage source splitting to  $V_{out}$  and superposition, as shown in Fig. 11. As with the stacked mirror, the only nonzero components of  $\delta I_{out}$  occur when we

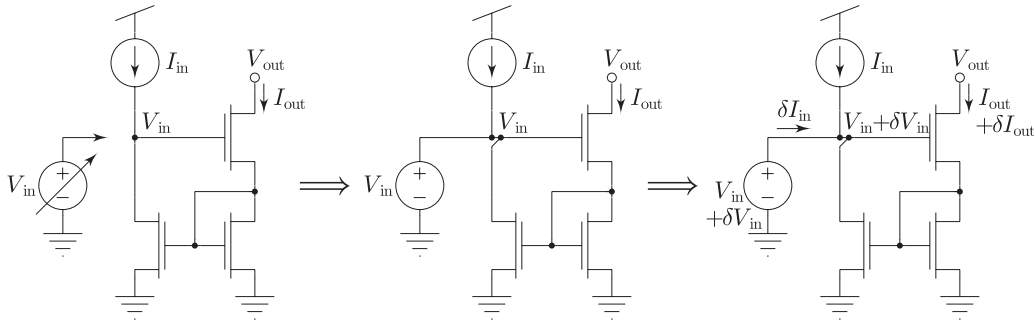

**Figure 9:** Set-up to determine the incremental input resistance of the Wilson current mirror using the voltage-source method.

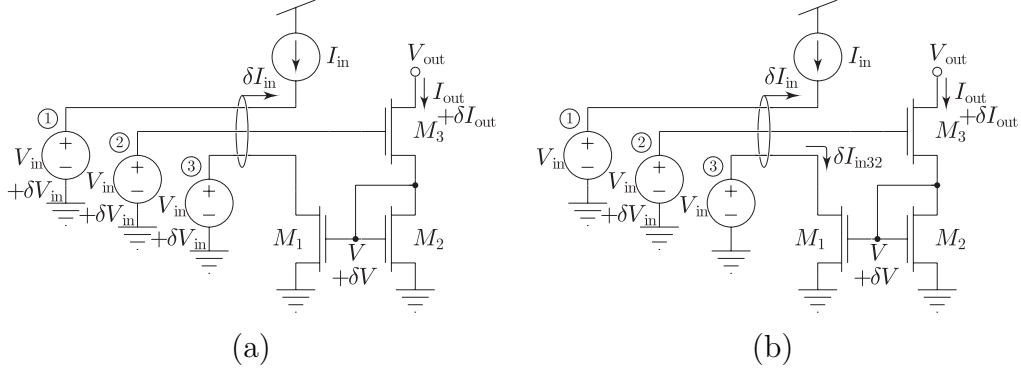


**Figure 10:** Calculation of the incremental input resistance of the Wilson current mirror using voltage-source splitting and superposition.

change the first replica test voltage source, as shown in Fig. 11b, because the second one is connected to the drain of  $M_3$ , which we have assumed to be saturated. We can write  $\delta I_{out}$  as


$$\begin{aligned} \delta I_{out} &= \frac{\delta V_{out}}{r_o + (1/G_S \parallel 1/g_m)} \left( 1 - \frac{G_S}{g_m + G_S} \right) \\ &\approx \frac{\delta V_{out}}{r_o} \left( 1 - \frac{G_S}{g_m + G_S} \right) \\ &= \frac{\delta V_{out}}{r_o} \cdot \frac{g_m}{g_m + G_S}, \end{aligned}$$

where  $G_S$  denotes the effective incremental conductance looking into the source of  $M_3$ ,  $g_m$  is the incremental conductance looking into the gate/drain of  $M_2$ , and the approximation follows from the fact that  $1/g_m \ll r_o$ , regardless of the precise value of  $G_S$ . Recall that  $g_s$  denotes the incremental conductance of the source of a saturated MOS transistor with the

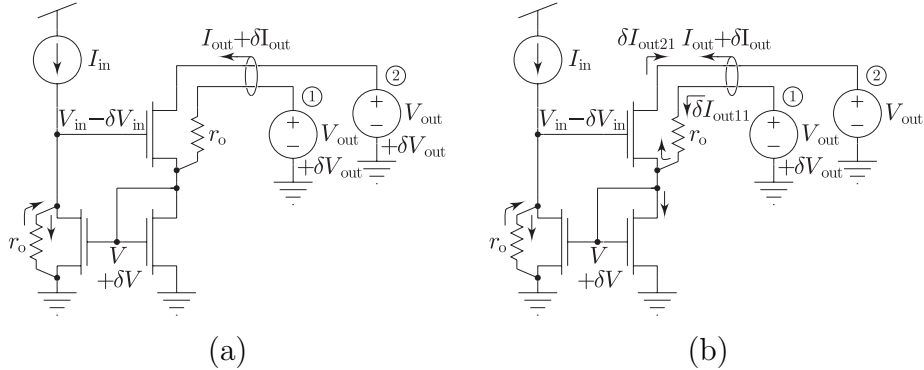

**Figure 11:** Calculation of the incremental output resistance of the Wilson current mirror.



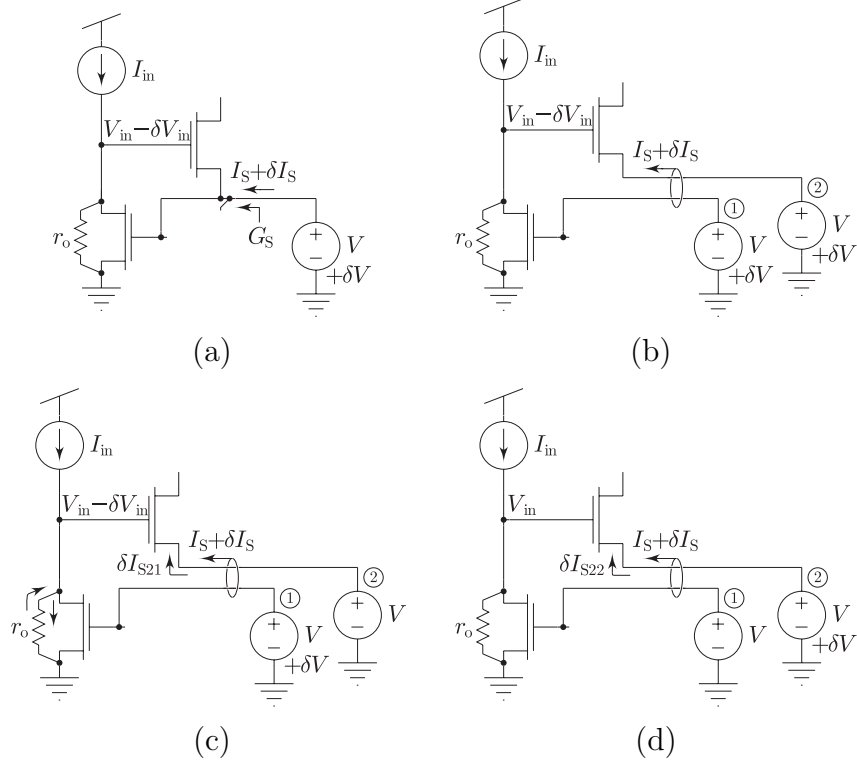

**Figure 12:** Auxiliary calculation of the incremental source conductance of  $M_3$  including the effect of the changing input voltage.

gate voltage fixed, which is not the case in the Wilson mirror. The incremental current that flows through  $M_2$  is mirrored by  $M_1$  to the input of the circuit. Because  $I_{in}$  has not changed,  $V_{in}$ , which is the gate voltage of  $M_3$  will decrease in response.


To compute  $G_S$ , we can recursively apply voltage-source splitting and superposition on the relevant part of the circuit, as shown in Fig. 12a and Fig. 12b. Each of the two replica test voltage sources elicits a single nonzero component of the current flowing into the source of  $M_3$ ,  $I_S$ , as shown in Fig. 12c and Fig. 12d. By inspection of these circuits, we can write  $\delta I_S$  as

$$\begin{aligned} \delta I_S &= \underbrace{-g_m (-g_m r_o \delta V)}_{\delta V_{in}} + \underbrace{g_s \delta V}_{\delta I_{S22}} \\ &= g_s (\kappa g_m r_o + 1) \delta V, \end{aligned}$$

whence it follows that

$$G_S = \frac{\delta I_S}{\delta V} = g_s (\kappa g_m r_o + 1) \approx (g_m r_o) g_m,$$

where the approximation follows from  $g_m r_o \gg 1$ . Thus, we have that the incremental output

 

**Figure 13:** A simple current mirror with a regulated cascode.

resistance of the Wilson mirror is given approximately by

$$R_{\text{out}} = \frac{\delta V_{\text{out}}}{\delta I_{\text{out}}} \approx \left( \frac{G_S}{g_m} + 1 \right) r_o \approx \left( \frac{g_m r_o \cdot g_m}{g_m} + 1 \right) r_o = (g_m r_o + 1) r_o \approx (g_m r_o) r_o,$$


where all of these approximations again follow from the fact that  $g_m r_o \gg 1$ . Thus, the incremental output resistance of the Wilson mirror is on the same order as that of the stacked mirror. ■

Finally, we shall calculate the incremental output resistance of the circuit shown in Fig. 13. This circuit is a simple current mirror with a *regulated cascode* on the output branch. In a regulated cascode, the cascode bias voltage,  $V_c$ , is not fixed, but rather is set by a simple amplifier, comprising the bias current source,  $I_b$ , and transistor  $M_4$ , connected in a negative feedback loop, whose goal is to regulate the voltage,  $V$ , which is the voltage across the output transistor of the simple mirror,  $M_2$ . We shall assume that all of the transistors are matched. Also, we shall assume that  $V_{\text{out}}$  is high enough to keep  $M_3$  in saturation and that transistors  $M_2$  and  $M_4$  are also operating in saturation. Note that transistors  $M_2$  and  $M_3$  are connected in series and must pass the same saturation current. Thus, they will both have the same value of  $g_m$  and  $r_o$ . However, transistor  $M_4$  will be passing  $I_b$ , which is, in general, different from  $I_{\text{out}}$ , so it will have a different set of incremental parameters, which we shall denote by  $g_{m4}$  and  $r_{o4}$ .

### Example 6.5

To compute the incremental output resistance of the circuit of Fig. 13, we simply change the output voltage by a small amount,  $\delta V_{\text{out}}$ , and see how much additional current,  $\delta I_{\text{out}}$ , goes into the circuit, as shown in Fig. 14a and Fig. 14b. The ratio  $\delta V_{\text{out}}/\delta I_{\text{out}}$  gives us the incremental output resistance. To facilitate the calculation, we can apply voltage source splitting to  $V_{\text{out}}$  and superposition, as shown in Fig. 14c. As with the stacked mirror and the Wilson mirror, the only nonzero components of  $\delta I_{\text{out}}$  occur when we change the first replica test voltage source, as shown in Fig. 11b, because the second one is connected to the drain of  $M_3$ , which we have assumed to be saturated. We can write  $\delta I_{\text{out}}$  as

$$\delta I_{\text{out}} = \underbrace{\frac{\delta V_{\text{out}}}{r_o + (1/G_S || r_o)}}_{\delta I_{\text{out}11}} \left( 1 - \underbrace{\frac{G_S}{G_S + (1/r_o)}}_{\delta I_{\text{out}21}/\delta I_{\text{out}11}} \right)$$

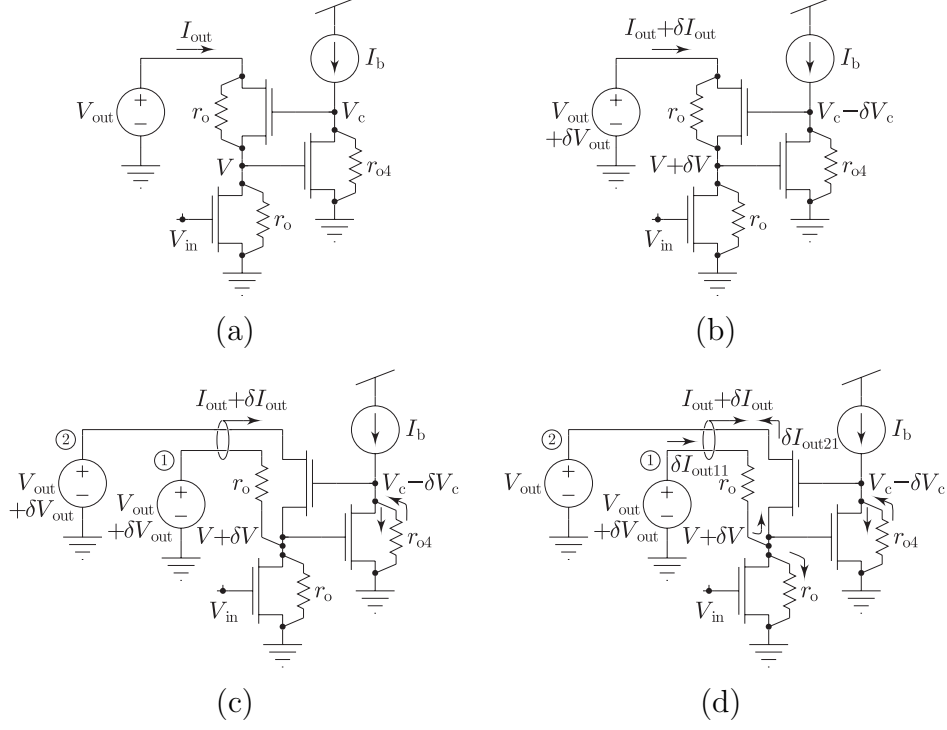

**Figure 14:** Calculation of the incremental output resistance of a regulated cascode.

$$\begin{aligned}
&= \frac{\delta V_{\text{out}}}{r_o + (1/G_S \parallel r_o)} \cdot \frac{1/r_o}{G_S + (1/r_o)} \\
&= \frac{\delta V_{\text{out}}}{r_o + (1/G_S \parallel r_o)} \cdot \frac{1}{G_S r_o + 1},
\end{aligned}$$


where  $G_S$  again denotes the effective incremental conductance looking into the source of  $M_3$ . As with the Wilson mirror, the incremental conductance looking into the source of  $M_3$  is not simply  $g_s$ , because its gate voltage,  $V_c$ , also changes as  $V$  changes by  $\delta V$ .

As we did with the Wilson mirror, to compute  $G_S$ , we can recursively apply voltage-source splitting and superposition on the relevant part of the circuit, as shown in Fig. 15a and Fig. 15b. Each of the two replica test voltage sources elicits a single nonzero component of the current flowing into the source of  $M_3$ ,  $I_S$ , as shown in Fig. 15c and Fig. 15d. By inspection of these circuits, we can write  $\delta I_S$  as

$$\begin{aligned}
\delta I_S &= \underbrace{-g_m (-g_{m4} r_{o4} \delta V)}_{\delta I_{S21}} + \underbrace{g_s \delta V}_{\delta I_{S22}} \\
&= g_s (\kappa g_{m4} r_{o4} + 1) \delta V,
\end{aligned}$$

whence it follows that

$$G_S = \frac{\delta I_S}{\delta V} = g_s (\kappa g_{m4} r_{o4} + 1) \approx (g_{m4} r_{o4}) g_m,$$

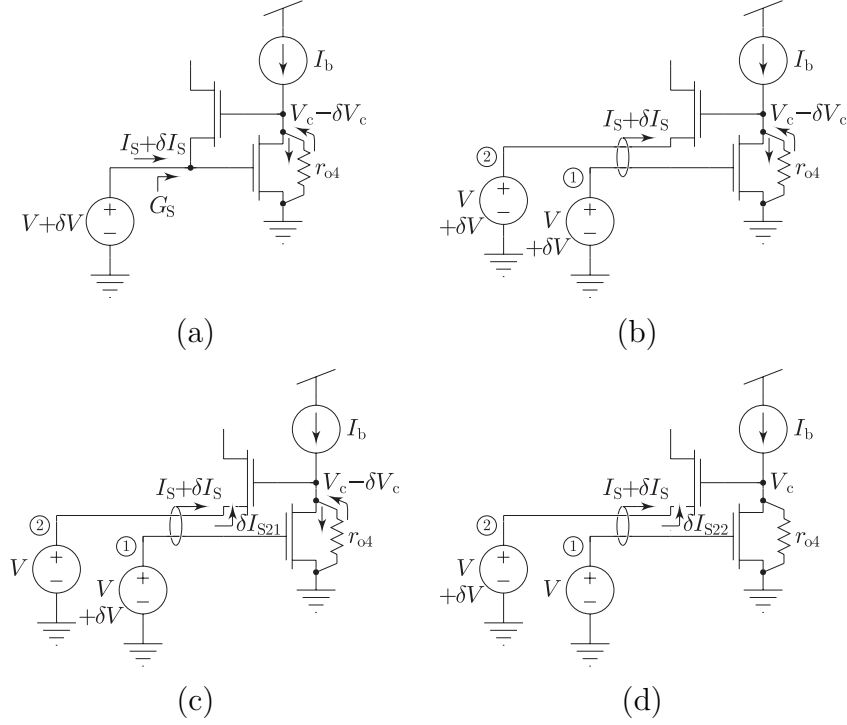

**Figure 15:** Auxiliary calculation of the incremental source conductance of  $M_3$  including the effect of the changing cascode bias voltage.


where the approximation follows from  $g_{m4}r_{o4} \gg 1$ . Using this result, we can write the output resistance of the circuit of Fig. 13 as

$$\begin{aligned}
 R_{\text{out}} &= \frac{\delta V_{\text{out}}}{\delta I_{\text{out}}} \\
 &= \left( r_o + \left( \frac{1}{G_S} \parallel r_o \right) \right) (G_S r_o + 1) \\
 &\approx \left( r_o + \left( \frac{1}{g_m} \cdot \frac{1}{g_{m4}r_{o4}} \parallel r_o \right) \right) (g_m r_o \cdot g_{m4}r_{o4} + 1) \\
 &\approx r_o \cdot g_m r_o \cdot g_{m4}r_{o4},
 \end{aligned}$$

which is larger than the output resistance of a single transistor by a factor of the product of the intrinsic gain factors of transistors  $M_3$  and  $M_4$ . ■

## 7 Incremental Voltage Gain Calculation of CMOS Circuits by Node Fixing

In this section, we shall illustrate the node fixing technique, which we developed earlier in the semester, for calculating the incremental voltage gain of CMOS circuits with several worked examples.

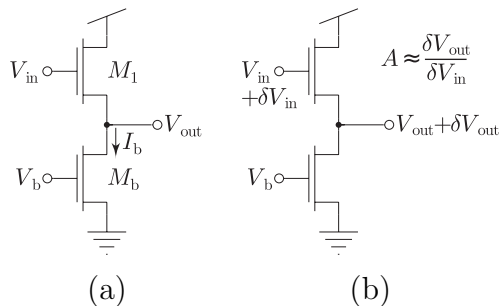

**Figure 16:** Source follower circuit.

For our first example of incremental gain calculation by node fixing, we shall compute the incremental voltage gain of an  $n$ MOS source follower, shown in Fig. 16. For this calculation, we shall assume that both transistors are matched. Further, we shall assume that  $V_{in}$  is far enough above ground that transistor  $M_b$  is saturated and that  $V_{in}$  cannot exceed  $V_{DD}$ . Under these assumptions,  $M_1$  (i.e., the source-follower transistor) will always be saturated in this circuit. To see why, we note that the drain of the source-follower transistor is connected to  $V_{DD}$ . The smallest value that the  $V_{DS}$  of  $M_1$  reaches for any value of  $I_b$  is achieved when  $V_{in}$  is equal to  $V_{DD}$ . Thus, if  $M_1$  is saturated for this value of  $V_{DS}$ , it must be saturated for all other values of  $V_{in}$ , too. However, when  $V_{in}$  is equal to  $V_{DD}$ , both the gate and drain are at the same potential, which is equivalent to  $M_1$  being diode connected. Because the diode-connected transistor operates in saturation for all appreciable current levels, then so will transistor  $M_1$ . Both transistors pass the same current, so both transistors will have the same small-signal parameter values. The output voltage will be just far enough below  $V_{in}$  that the saturation current of  $M_1$  is equal to  $I_b$ .


### Example 7.1

We begin by connecting a test voltage source to the output of the circuit whose value we have adjusted to match the quiescent output voltage, as shown in Fig. 17a. At this point, the circuit exchanges no current with the test source, as shown in Fig. 17b. We can compute the incremental output resistance of this circuit, as shown in Fig. 17c, by increasing  $V_{out}$  by  $\delta V_{out}$  and determining how much current flows into the circuit. Assuming that  $g_s r_o \gg 1$ , neither Early-effect resistor will have an impact on the value of  $V_{out}$ , because they both appear in parallel with the incremental source conductance of  $M_1$ . In this case, the incremental output resistance is simple enough that we should not need to use voltage source splitting and superposition—its value is simply given by

$$R_{out} = \frac{1}{g_s}.$$

To compute the incremental transconductance gain of the circuit, we restore the test source back to its original value and increase  $V_{in}$  by  $\delta V_{in}$ . Under these circumstances, the current in  $M_1$  will increase by

$$\delta I_1 = g_m \delta V_{in},$$

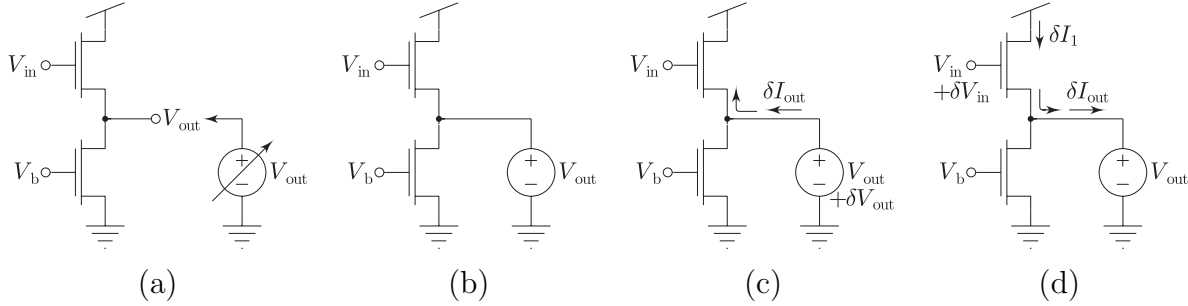

**Figure 17:** Calculation of the incremental voltage gain of the source follower by node fixing.

which all flows into the output test source, so

$$\delta I_{\text{out}} = \delta I_1 = g_m \delta V_{\text{in}},$$

which implies that

$$G_m = \frac{\delta I_{\text{out}}}{\delta V_{\text{in}}} = g_m.$$


Thus, the incremental gain of the source follower is given by

$$A = \frac{\delta V_{\text{out}}}{\delta V_{\text{in}}} = G_m R_{\text{out}} = g_m \cdot \frac{1}{g_s} = \kappa,$$

which is what we found earlier in the course by finding  $V_{\text{out}}$  as a function of  $V_{\text{in}}$  and differentiating the resulting expression. ■

For our next example, we shall calculate the incremental voltage gain of an improved version of the source follower, called the *super source follower*, which is shown in Fig. 18. To the simple source follower of Fig. 16, we add two  $p$ MOS transistors, which provide negative feedback that serves to reduce the incremental output resistance of the circuit over that of the simple source follower. For this calculation, we shall assume that all three  $n$ MOS transistors are matched and that both  $p$ MOS transistors are matched. We shall also assume that  $V_{\text{in}}$  is sufficiently far above ground that  $M_{2a}$  and  $M_{2b}$  are both saturated and that  $V_{\text{in}}$  cannot exceed  $V_{\text{DD}}$ . We shall also assume that  $V_{b_n}$  has been set so that the saturation currents of  $M_{2a}$  and  $M_{2b}$  are  $I_b$  and that  $V_{b_p}$  has been set so that the saturation current of  $M_3$  is also  $I_b$ .

Let us start by assuming all of the transistors in the circuit are saturated. In the steady state, KCL implies that the current flowing through  $M_1$  must equal that flowing through  $M_3$ . If  $M_3$  operates in saturation, then this current would be  $I_b$ . Moreover, if the current flowing through  $M_1$  is  $I_b$ , then KCL implies that the current flowing through  $M_4$  must also equal  $I_b$ , because a total of  $2I_b$  is sunk by the  $n$ MOS bias transistors. If  $M_4$  is saturated and if its Early effect were not too severe, then its gate voltage,  $V$ , would have to be nearly equal to  $V_{b_p}$  in order for it to pass a current of  $I_b$ . From this, we can conclude that  $M_3$  must be saturated, because its gate and drain voltages are nearly equal, making it effectively diode connected. Moreover, in order for transistor  $M_1$  to pass  $I_b$ , it must have a finite positive  $V_{\text{DS}}$ , which implies that  $V$  must be greater than  $V_{\text{out}}$ . This fact, in turn, implies that  $M_4$  has

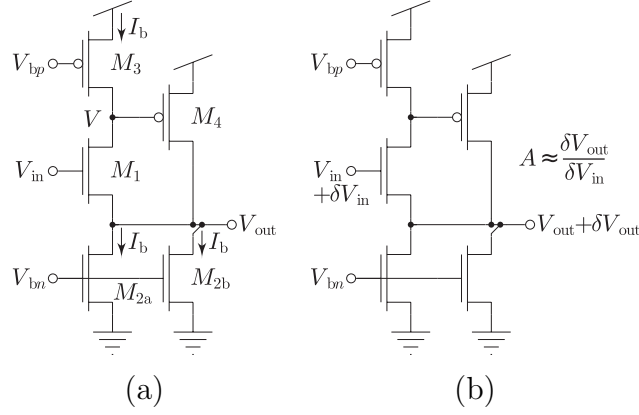

**Figure 18:** Super source follower circuit.


a larger  $V_{SD}$  than does  $M_3$ . Therefore, if  $M_3$  is guaranteed to be saturated, then so is  $M_4$ . Transistors  $M_{2a}$  and  $M_{2b}$  are saturated by hypothesis, leaving us to consider whether or not transistor  $M_1$  will be saturated.

If  $M_1$  were saturated, then using the EKV model and equating the saturation currents of  $M_1$  and  $M_{2a}$ , we can show that


$$V_{out} = \kappa_n (V_{in} - V_{bn}),$$

regardless of whether  $V_{bn} < V_{T0}$ ,  $V_{bn} \approx V_{T0}$ , or  $V_{bn} > V_{T0}$ , just like for the simple source follower. Of course, from this result, we can compute the incremental gain of the super source follower directly by differentiating  $V_{out}$  with respect to  $V_{in}$ . Nevertheless, we shall proceed to calculate the incremental gain of this circuit by node fixing in order to illustrate the technique. Now, in order for  $M_1$  to be saturated, we must have that

$$V_{DS} = V - V_{out} = V_{bp} - \kappa_n (V_{in} - V_{bn}) \geq V_{DSsat},$$

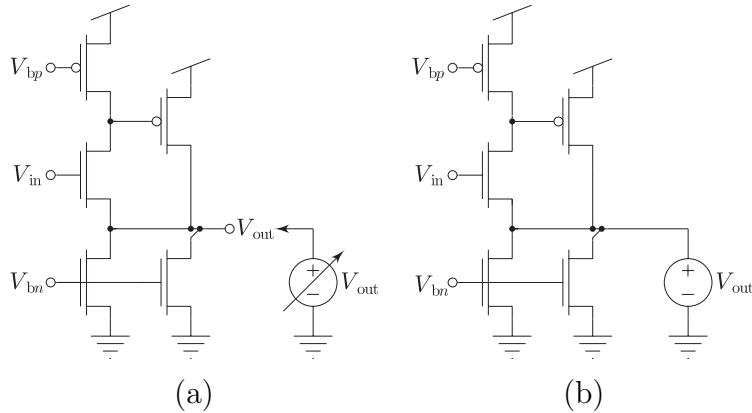

**Figure 19:** Fixing the output voltage of the super source follower.

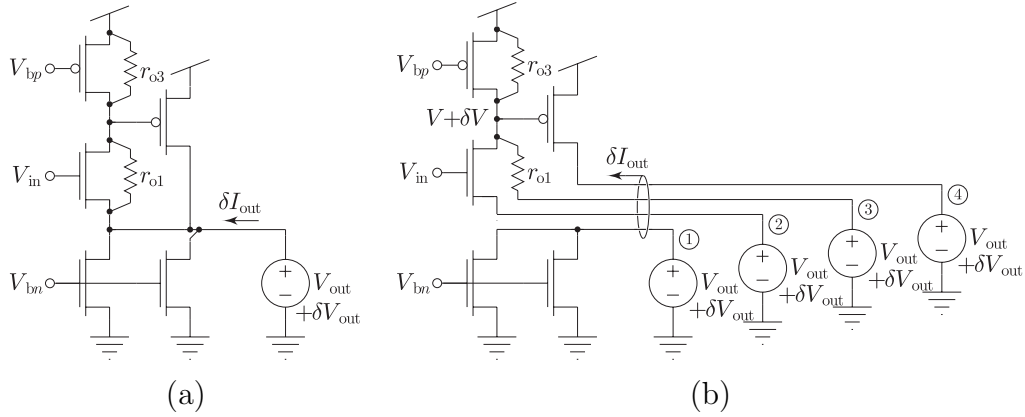

**Figure 20:** Calculation of the incremental output resistance of the super source follower with no applied input signal by voltage source splitting.

which translates into an upper limit on  $V_{in}$  given by

$$V_{in} \leq V_{bn} + \frac{V_{bp} - V_{DSsat}}{\kappa_n}.$$


For typical values of  $V_{bn}$ ,  $V_{bp}$ , and  $\kappa_n$ , this upper limit exceeds  $V_{DD}$ , which we supposed to be the upper limit on  $V_{in}$ . Thus, under most circumstances,  $M_1$  will operate in saturation and the quiescent output voltage will be given by the expression that we just obtained for  $V_{out}$ .

### Example 7.2

We begin by connecting a test voltage source to the output of the circuit whose value we have adjusted to match the quiescent output voltage, as shown in Fig. 19a. At this point, the circuit exchanges no current with the test source, as shown in Fig. 18b. We can compute the incremental output resistance of this circuit, as shown in Fig. 20a, by increasing  $V_{out}$  by  $\delta V_{out}$  and determining how much current flows into the circuit. As with the simple source follower, assuming that  $g_s r_o \gg 1$ , we should expect that the Early-effect resistors of  $M_{2a}$ ,  $M_{2b}$ , and  $M_4$ , will not have a large impact on the value of  $R_{out}$ , because they both appear in parallel with the incremental source conductance of  $M_1$ , which is saturated under most conditions, so we shall not include these in the calculation. We shall, however, include the Early-effect resistors of transistors  $M_1$  and  $M_3$ , as shown in Fig. 20a, because if we were not to include these, there would be no place for a change in the current in  $M_1$  to go when it gets to node  $V$ . Otherwise a change in this current, no matter how small, would drive either  $M_1$  or  $M_3$  into the ohmic region, depending on whether the current in  $M_1$  increased or decreased.

Next, we split  $V_{out}$  into four replica sources, as shown in Fig. 20b. For convenience, we have left the drains of  $M_{2a}$  and  $M_{2b}$  tied together. Because their gate voltages are tied to a constant potential and they are saturated, they will not impact the calculation of  $R_{out}$ . We shall compute each of the components of  $\delta I_{out}$  due to each of the replica test sources individually and assemble them into the total  $\delta I_{out}$  using superposition. The only nonzero



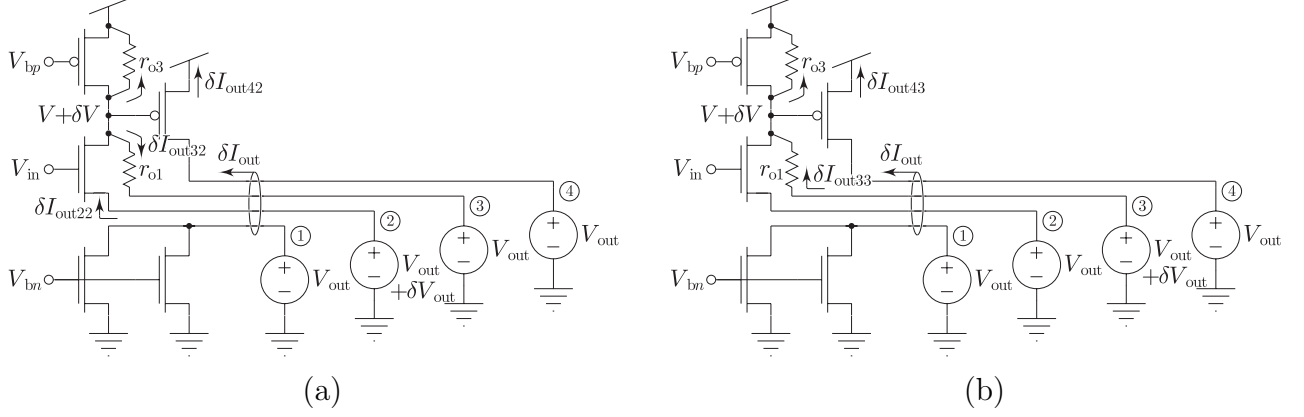


**Figure 21:** The only nonzero components of  $\delta I_{\text{out}}$  occur when we apply  $\delta V_{\text{out}}$  to the replica sources on (a) branch 2 and (b) branch 3.

components of  $\delta I_{\text{out}}$  occur when we change the value of the replica sources on branches 2 and 3, as shown in Fig. 21a and Fig. 21b. By inspection of these circuits, we can write the total output current as

$$\begin{aligned}
\delta I_{\text{out}} &= \underbrace{g_{s1} \delta V_{\text{out}}}_{\delta I_{\text{out}22}} \left( 1 - \frac{r_{o3}}{r_{o1} + r_{o3}} \right) + g_{m4} \underbrace{\left( \frac{g_{s1} \delta V_{\text{out}}}{\delta I_{\text{out}22}} (r_{o1} \parallel r_{o3}) \right)}_{\delta V} \\
&\quad + \underbrace{\frac{\delta V_{\text{out}}}{r_{o1} + r_{o3}}}_{\delta I_{\text{out}33}} + \underbrace{g_{m4} \cdot \frac{r_{o3}}{r_{o1} + r_{o3}} \cdot \delta V_{\text{out}}}_{\delta I_{\text{out}43}} \\
&= g_{s1} \delta V_{\text{out}} \left( \frac{r_{o1}}{r_{o1} + r_{o3}} + g_{m4} (r_{o1} \parallel r_{o3}) \right) + \frac{r_{o3}}{r_{o1} + r_{o3}} \cdot \delta V_{\text{out}} \left( \frac{1}{r_{o3}} + g_{m4} \right) \\
&= g_{s1} (r_{o1} \parallel r_{o3}) \delta V_{\text{out}} \left( \frac{1}{r_{o3}} + g_{m4} \right) + \frac{r_{o1} \parallel r_{o3}}{r_{o1}} \cdot \delta V_{\text{out}} \left( \frac{1}{r_{o3}} + g_{m4} \right) \\
&= (r_{o1} \parallel r_{o3}) \left( \frac{1}{r_{o3}} + g_{m4} \right) \left( g_{s1} + \frac{1}{r_{o1}} \right) \delta V_{\text{out}} \\
&\approx g_{s1} g_{m4} (r_{o1} \parallel r_{o3}) \delta V_{\text{out}},
\end{aligned}$$

where the approximation follows from the fact that  $g_{s1} r_{o1} \gg 1$  and that  $g_{m3} r_{o4} \gg 1$ . Transistors  $M_3$  and  $M_4$  are matched and carrying the same quiescent current, so their  $g_m$  and  $r_o$  values will be equal, so if  $g_{m3} r_{o3} \gg 1$  and  $g_{m4} r_{o4} \gg 1$  then it also follows that  $g_{m3} r_{o4} \gg 1$ . Thus, the incremental output resistance of the circuit is given by

$$R_{\text{out}} = \frac{\delta V_{\text{out}}}{\delta I_{\text{out}}} = \frac{1}{g_{s1}} \cdot \frac{1}{g_{m4} (r_{o1} \parallel r_{o3})} \ll \frac{1}{g_{s1}},$$

 

**Figure 22:** Calculation of the incremental transconductance gain of the super source follower with the output voltage fixed.

which was the incremental output resistance of the simple source follower. Note that this result also validates our assumption that the Early-effect resistors of  $M_{2a}$ ,  $M_{2b}$ , and  $M_4$  would have a negligible impact on the calculation, because they would have appeared in parallel with this very small output resistance.

Next, we must determine the incremental transconductance gain of the circuit from input to output with the output voltage fixed, as shown in Fig. 22.

$$\begin{aligned}
\delta I_{\text{out}} &= \underbrace{g_{m1} \delta V_{\text{in}}}_{\delta I_1} \left( 1 - \underbrace{\frac{r_{o3}}{r_{o1} + r_{o3}}}_{\delta I / \delta I_1} \right) + g_{m4} \underbrace{\left( \underbrace{g_{m1} \delta V_{\text{in}} (r_{o1} \parallel r_{o3})}_{\delta I_1} \right)}_{\delta V} \\
&= g_{m1} \delta V_{\text{in}} \left( \frac{r_{o1}}{r_{o1} + r_{o3}} + g_{m4} (r_{o1} \parallel r_{o3}) \right) \\
&= g_{m1} (r_{o1} \parallel r_{o3}) \delta V_{\text{in}} \left( \frac{1}{r_{o3}} + g_{m4} \right) \\
&\approx g_{m1} g_{m4} (r_{o1} \parallel r_{o3}) \delta V_{\text{in}},
\end{aligned}$$


where the approximation follows from the fact that  $g_{m4} r_{o3} \gg 1$ , as we just argued was the case. Thus, we have that the incremental transconductance gain of the circuit is given by

$$G_m = \frac{\delta I_{\text{out}}}{\delta V_{\text{in}}} \approx g_{m1} g_{m4} (r_{o1} \parallel r_{o3}),$$

so the incremental voltage gain of the circuit is given by

$$A = \frac{\delta V_{\text{out}}}{\delta V_{\text{in}}} = G_m R_{\text{out}} = \frac{g_{m1} g_{m4} (r_{o1} \parallel r_{o3})}{g_{s1} g_{m4} (r_{o1} \parallel r_{o3})} = \frac{g_{m1}}{g_{s1}} = \kappa_n,$$

which is what we would have found originally by differentiating  $V_{\text{out}}$  with respect to  $V_{\text{in}}$ . ■

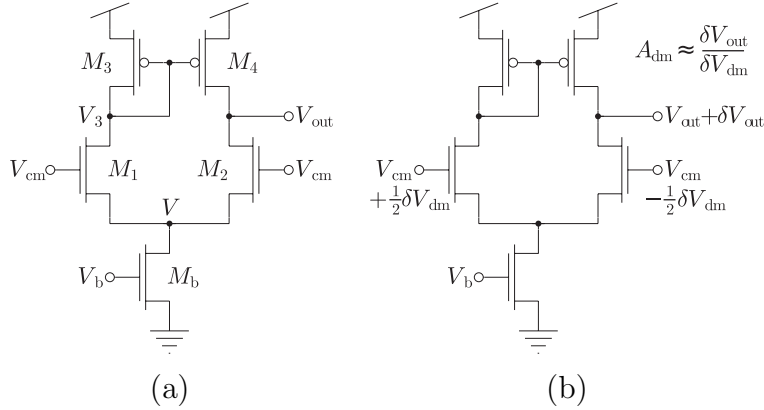


**Figure 23:** Simple differential amplifier circuit.

For our next example, we shall calculate the incremental differential-mode voltage gain of the simple five-transistor differential amplifier, shown in Fig. 23. For this calculation, we shall assume that all three  $n$ MOS transistors are matched, that the  $p$ MOS transistors are matched, and that  $V_{cm}$  is high enough to ensure that the bias transistor operates in saturation. Also, we shall assume that  $M_1$  always operates in saturation, which will usually be the case. Because  $M_3$  is diode connected, the question of whether or not  $M_1$  is saturated is very similar to the one we addressed for  $M_1$  in the super source follower example. We would like to determine what the quiescent output voltage of the circuit shall be under these conditions in order to decide whether or not  $M_2$  and  $M_4$  will operate in saturation. If there were no Early effect, the output voltage would be indeterminate for this circuit, because any value of  $V_{out}$  for which both  $M_2$  and  $M_4$  are saturated will satisfy KCL. To determine the actual quiescent output voltage, we must consider the Early effect in our reasoning process.

We know that the sources of  $M_1$  and  $M_2$  are tied together and that their gates are at the same potential; thus, they operate on the same drain characteristic. If one of these transistors has a larger voltage across it, it will be biased further into saturation and, because of the Early effect, will have a larger channel current. The only point at which both transistors will pass the same current is the one at which they have the same drain-to-source voltage. Likewise, the gates of  $M_3$  and  $M_4$  are tied together as are their sources, which means that they too operate on the same drain characteristic. Consequently, the one with the larger voltage across it must also pass a larger channel current and the only point at which their channel currents are equal is that at which they have equal source-to-drain voltages.

Because  $M_3$  is diode connected, we know that  $V_3$  will adjust itself so that the current flowing through  $M_1$  is equal to that flowing through  $M_3$  in the steady state. Now, if  $V_{out}$  were larger than  $V_3$ , then  $M_2$  would have more voltage across it than would  $M_1$ , and we know that the current flowing through  $M_2$  would exceed that flowing through  $M_1$ . Under these circumstances, we also know that  $M_4$  would have less voltage across it than would  $M_3$ , which means that the current flowing through  $M_4$  would be less than that flowing through  $M_3$ . Therefore, if  $V_{out}$  were higher than  $V_3$ ,  $M_2$  would be sinking more current from the output node than  $M_4$  would be supplying and  $V_{out}$  would have to decrease as the output node is discharged, reducing the difference between  $V_{out}$  and  $V_3$ . On the other hand, if  $V_{out}$

 


**Figure 24:** Fixing the output voltage of the simple differential amplifier.


were lower than  $V_3$ ,  $M_2$  would have less voltage across it than would  $M_1$  and, thus,  $M_2$  would be passing less current than  $M_1$ . Also,  $M_4$  would have more voltage across it than would  $M_3$ , so  $M_4$  would be passing a larger current than  $M_3$ . Consequently,  $M_4$  would be passing a larger current than  $M_2$ . Thus, if  $V_{\text{out}}$  were lower than  $V_3$ ,  $M_4$  would be sourcing more current onto the output node than  $M_2$  would be sinking, and  $V_{\text{out}}$  would increase, again reducing the difference between  $V_{\text{out}}$  and  $V_3$ . So, we have that if  $V_{\text{out}}$  were different from  $V_3$ , that situation would not persist, and  $V_{\text{out}}$  would eventually become equal to  $V_3$ . Now, if  $M_1$  is saturated, then so is  $M_2$ , because they each have the same drain-to-source voltage. Likewise, if  $M_3$  is saturated, then so is  $M_4$ . So,  $M_2$  and  $M_4$  both operate in saturation under these circumstances.

### Example 7.3


We begin the node-fixing process by connecting a test voltage source to the output of

 

**Figure 25:** Calculation of the incremental output resistance of the differential amplifier with no applied input signal by voltage source splitting.

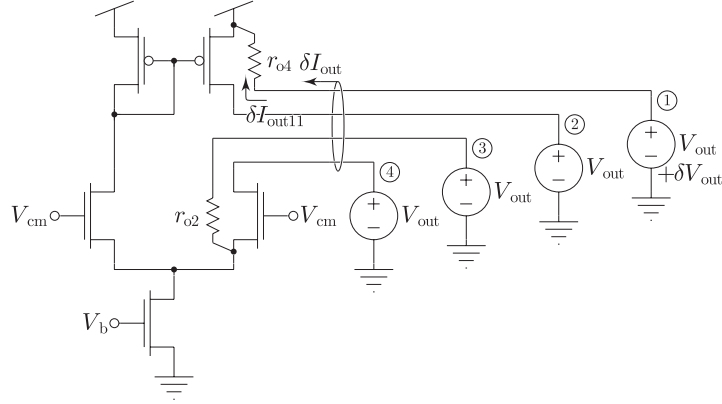

(a)

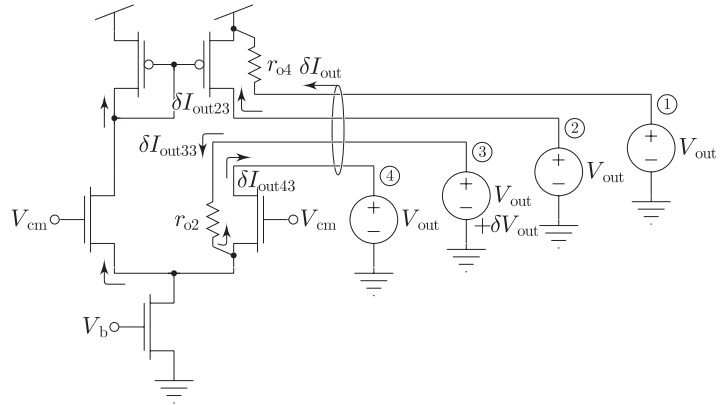


(b)

**Figure 26:** The only nonzero components of  $\delta I_{\text{out}}$  occur when we apply  $\delta V_{\text{out}}$  to the replica sources on (a) branch 1 and (b) branch 3.

the circuit whose value we have adjusted to match the quiescent output voltage, which we have just established is equal to the value of  $V_3$ , as shown in Fig. 24a. At this point, the circuit exchanges no current with the test source, as shown in Fig. 24b. We can compute the incremental output resistance of this circuit, as shown in Fig. 25a, by increasing  $V_{\text{out}}$  by  $\delta V_{\text{out}}$  and determining how much current flows into the circuit. Because  $M_2$  and  $M_4$  are both saturated and their drains are the only things connected to the output node, we must include Early-effect resistors for these transistors, as shown in Fig. 25a, in our calculation of the amplifier's output resistance, otherwise we should conclude that the output resistance, and, therefore, the circuit's differential-mode gain is infinite. All of the other Early-effect resistors would appear in parallel with device terminals which have a comparably high incremental conductance, which means that the Early-effect resistors would shunt away a negligible amount of current from these other terminals, and, therefore, we should expect that they will have a negligible effect on the calculation.

Next, we split  $V_{\text{out}}$  into four replica sources, as shown in Fig. 25b. We shall compute each of the components of  $\delta I_{\text{out}}$  due to each of the replica test sources individually and assemble

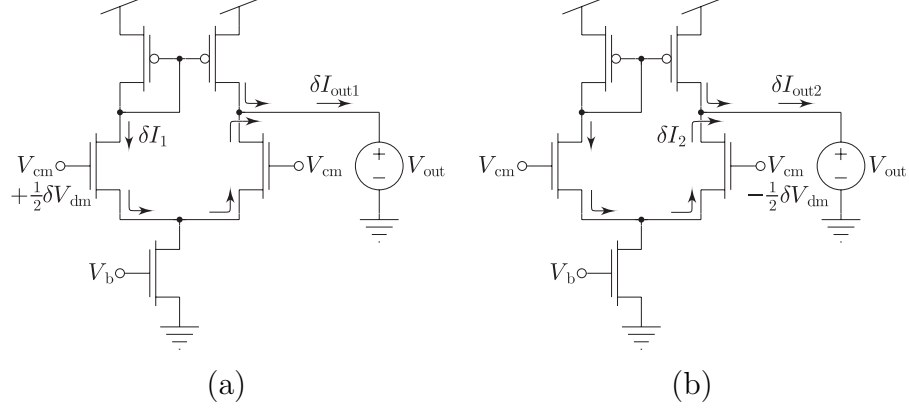

**Figure 27:** Calculation of the incremental transconductance gain of the simple differential amplifier with the output voltage fixed by superposition.

them into the total  $\delta I_{\text{out}}$  using superposition. The only nonzero components of  $\delta I_{\text{out}}$  occur when we change the value of the replica sources on branches 1 and 3, as shown in Fig. 26a and Fig. 26b. By inspection of these circuits, we can write the total output current as

$$\begin{aligned}
 \delta I_{\text{out}} &= \underbrace{\frac{\delta V_{\text{out}}}{r_{o4}}}_{\delta I_{\text{out}11}} + \underbrace{\frac{\delta V_{\text{out}}}{r_{o2} + (1/g_{s1} \parallel 1/g_{s2})}}_{\delta I_{\text{out}33}} \left( 1 - \underbrace{\frac{g_{s2}}{g_{s1} + g_{s2}}}_{\delta I_{\text{out}43}/\delta I_{\text{out}33}} + \underbrace{\frac{g_{s1}}{g_{s1} + g_{s2}}}_{\delta I_{\text{out}23}/\delta I_{\text{out}33}} \right) \\
 &= \frac{\delta V_{\text{out}}}{r_{o4}} + \frac{\delta V_{\text{out}}}{r_{o2} + (1/2g_{sn})} \left( 1 - \frac{g_{sn}}{2g_{sn}} + \frac{g_{sn}}{2g_{sn}} \right) \\
 &\approx \frac{\delta V_{\text{out}}}{r_{o4}} + \frac{\delta V_{\text{out}}}{r_{o2}},
 \end{aligned}$$

where we have made use of the fact that, at the quiescent operating point,  $g_{s1} = g_{s2} = g_{sn}$ , because  $M_1$  and  $M_2$  are matched and both have a quiescent channel current of  $I_b/2$ , and the approximation follows from the fact that  $g_{s2}r_{o2} \gg 1$ . Thus, the incremental output resistance of the circuit is given approximately by

$$R_{\text{out}} = \frac{\delta V_{\text{out}}}{\delta I_{\text{out}}} \approx r_{o2} \parallel r_{o4}.$$

Next, we must determine the incremental transconductance gain of the circuit from input to output with the output voltage fixed, as shown in Fig. 27. Because the output voltage source maintains the voltage across  $r_{o4}$  constant, the current flowing through it will not change for this calculation, so it will have no impact on the calculation whatsoever. Because the source conductances of  $M_1$  and  $M_2$  are much larger than  $1/r_{o2}$ , any current diverted by  $r_{o2}$  from the sources of  $M_1$  and  $M_2$  would represent a negligible loss from that which flows into the sources of  $M_1$  and/or  $M_2$ , so we would expect it too to have a negligible impact on this calculation. Consequently, we shall omit both in calculating the circuit's incremental transconductance gain, as shown in Fig. 27. Also, as indicated in Fig. 23b, we

shall apply a pure differential-mode input to the circuit for this calculation, which means that we apply half of  $\delta V_{\text{dm}}$  to the noninverting input and half of  $\delta V_{\text{dm}}$  to the inverting input so that the common-mode input voltage remains unchanged. To compute  $\delta I_{\text{out}}$ , we shall apply superposition, considering the effect of each half of  $\delta V_{\text{dm}}$  separately and superposing the resulting components of  $\delta I_{\text{out}}$ , as shown in Fig. 27.

First, we consider increasing the gate of  $M_1$  by  $\delta V_{\text{dm}}/2$ , as shown in Fig. 27a. This increase in the gate voltage of  $M_1$  results in an increase in its channel current,  $\delta I_1$ , given by

$$\delta I_1 = \frac{g_{m1} \delta V_{\text{dm}}/2}{1 + g_{s1} (1/g_{s2})} = \frac{g_{mn}}{4} \cdot \delta V_{\text{dm}},$$

where we have again made use of the fact that the incremental source conductances and transconductance gains of  $M_1$  and  $M_2$  are equal to one another under quiescent conditions. Now, this incremental current flowing into the drain of  $M_1$  also flows out of the gate/drain of  $M_3$  and is reflected to the output by the  $p$ MOS current mirror, as shown in Fig. 27a. It also flows out of the source of  $M_1$  and into the the source of  $M_2$  and out of the circuit, as shown. Note that the total current in  $M_2$  still flows from drain to source. By indicating that the incremental current flows up into the source of  $M_2$  is that the total current in  $M_2$  is decreasing relative to its quiescent value. Recall that KCL implies that, in the steady state, the sum of the currents flowing through  $M_1$  and  $M_2$  must equal the bias current  $I_b$ . If the current in  $M_1$  has increased by some amount, the current flowing through  $M_2$  by an equal amount so that their sum remains unchanged. Thus, the first component of the incremental output current is given by

$$\delta I_{\text{out1}} = 2\delta I_1 = \frac{g_{mn}}{2} \cdot \delta V_{\text{dm}}.$$

Next, we consider decreasing the gate of  $M_2$  by  $\delta V_{\text{dm}}/2$ , as shown in Fig. 27b. This decrease in the gate of  $M_2$  results in a decrease in its channel current,  $\delta I_2$ , whose magnitude is given by

$$\delta I_2 = \frac{g_{m2} \delta V_{\text{dm}}/2}{1 + g_{s2} (1/g_{s1})} = \frac{g_{mn}}{4} \cdot \delta V_{\text{dm}},$$

where we have once again made use of the fact that the incremental source conductances and transconductance gains of  $M_1$  and  $M_2$  are equal to one another under quiescent conditions. This decrease in the current flowing through  $M_2$  again can be thought of as a positive incremental current flowing from source of  $M_2$  to its drain and out of the circuit, as shown in Fig. 27b. This incremental current must come from the source of  $M_1$ . It also flows through the channel of  $M_1$  and from the input of the  $p$ MOS current mirror, which reflects the current increase to the output through  $M_4$ , as shown in Fig. 27b. Thus, the second component of  $\delta I_{\text{out}}$  is given by


$$\delta I_{\text{out2}} = 2\delta I_2 = \frac{g_{mn}}{2} \cdot \delta V_{\text{dm}}.$$

Superposing these two components of the output currents, we obtain the total incremental output current as

$$\delta I_{\text{out}} = \delta I_{\text{out1}} + \delta I_{\text{out2}} = g_{mn} \delta V_{\text{dm}},$$

which implies that the incremental transconductance gain of the circuit with the output voltage held fixed is given by

$$G_m = \frac{\delta I_{\text{out}}}{\delta V_{\text{dm}}} = g_{mn}.$$

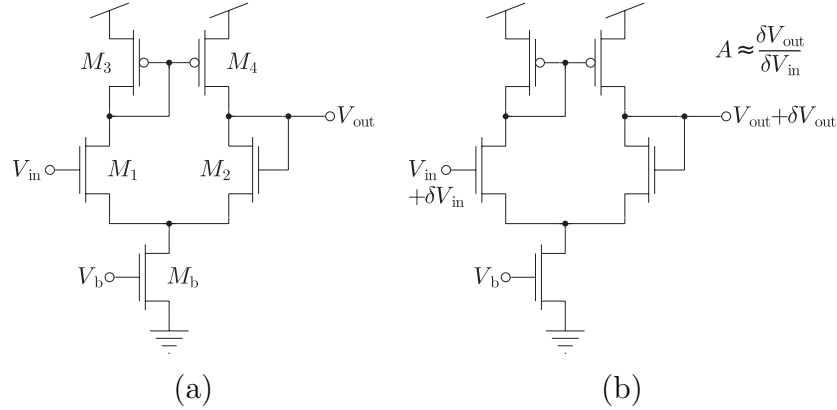

**Figure 28:** Simple differential amplifier connected as a unity-gain follower.

Therefore, the incremental differential-mode gain of the circuit is given approximately by

$$A_{dm} = \frac{\delta V_{out}}{\delta V_{dm}} = G_m R_{out} \approx g_{mn} (r_{o2} || r_{o4}).$$


■

For our next example, we shall use node fixing to calculate the incremental voltage gain of the simple five-transistor differential amplifier configured as a unity-gain follower with its output connected to its inverting input, as shown in Fig. 28. As with the last example, we shall assume that all three  $n$ MOS transistors are matched, that the  $p$ MOS transistors are matched, and that  $V_{in}$  is high enough to ensure that the bias transistor operates in saturation. Also, we shall assume that  $M_1$  and  $M_3$  operate in saturation for all possible values of  $V_{in}$ . In this circuit,  $M_2$  is diode connected and so operates in saturation. Moreover, the output voltage (i.e., the drain/gate of transistor  $M_2$ ), adjusts itself relative to the common-source node voltage so that  $M_2$  passes the current being supplied by  $M_4$ . If  $M_4$  operates in saturation, then this current is a mirror copy of the channel current of  $M_1$ . If the Early effect is small, then these currents will be equal. Because  $M_1$  and  $M_2$  are matched and are both operating in saturation, they must have nearly equal gate-to-source voltages if they pass the same channel current. Because their sources are shorted together, nearly equal gate-to-source voltages also translates into nearly equal gate voltages. So,  $V_{out}$  will be very nearly equal to  $V_{in}$ . The story will be somewhat different if  $V_{in}$  is within a saturation voltage of  $V_{DD}$ . In this case,  $M_4$  will not be saturated, and so the current flowing  $M_2$  will be smaller than that flowing in  $M_1$ , because the current flowing in  $M_4$  will be smaller than that flowing in  $M_3$ . However, we shall not consider this case any further in this example. Instead, we shall assume that  $M_4$  operates in saturation and that  $M_1$  and  $M_2$  each carry half of the bias current being sunk by  $M_b$ .

### Example 7.4


We begin the node-fixing process by connecting a test voltage source to the output of the circuit whose value we have adjusted to match the quiescent output voltage, which we have just established is equal to the quiescent value of  $V_{in}$ , as shown in Fig. 29a. At this point,



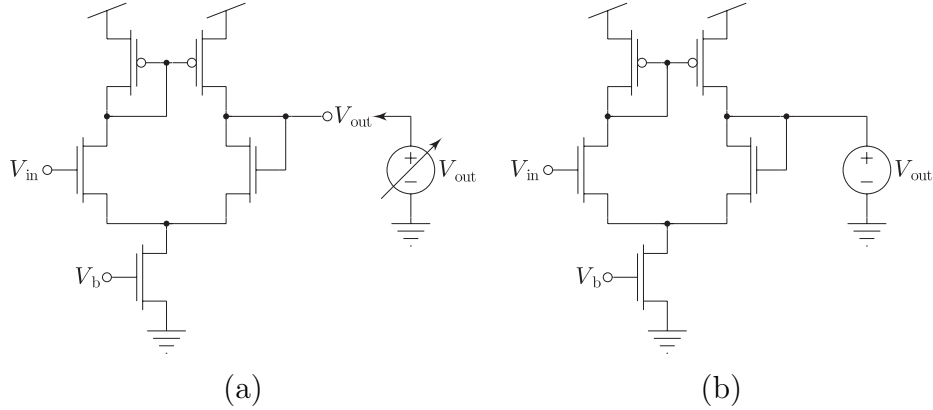


**Figure 29:** Fixing the output voltage of the follower-connected differential amplifier.

the circuit exchanges no current with the test source, as shown in Fig. 29b. We can compute the incremental output resistance of this circuit, as shown in Fig. 30a, by increasing  $V_{out}$  by  $\delta V_{out}$  and determining how much current flows into the circuit. In this case, because we have connected the output back to the inverting input of the amplifier, if we change the output voltage, the amplifier will draw in a relatively large amount of current, which would be on the order of that which flowed out of the differential amplifier when we computed its incremental transconductance gain in the last example. This current would be much larger than that which flowed into the the amplifier due to the Early-effect resistors of  $M_2$  and  $M_4$  when we changed the output voltage in the last example. So, we should expect that the Early-effect resistors of  $M_2$  and  $M_4$  will have a negligible impact on the calculation of the incremental output resistance of the unity-gain follower. To illustrate this point, we shall perform the calculation using source splitting and superposition both without and with these Early-effect resistors.

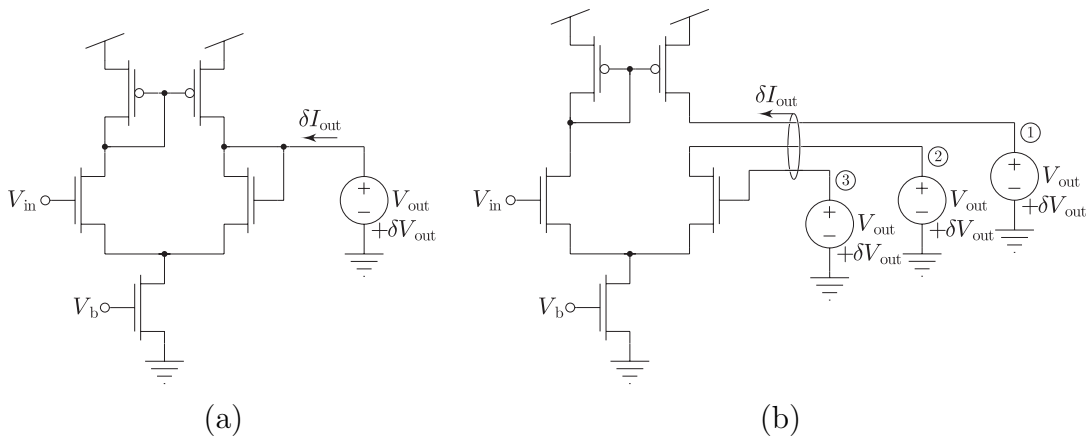

**Figure 30:** Calculation of the incremental output resistance of the follower-connected differential amplifier with no applied input signal by voltage-source splitting and superposition.

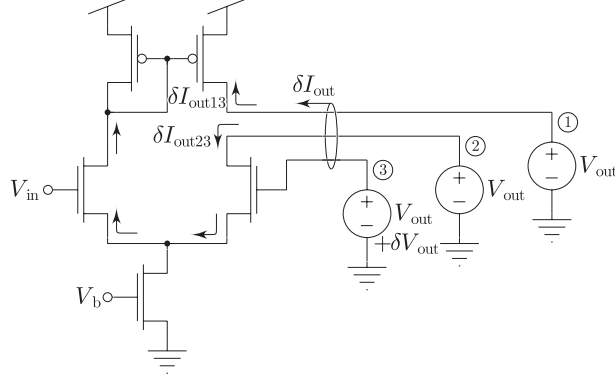

**Figure 31:** The only nonzero components of  $\delta I_{\text{out}}$  occur when we apply  $\delta V_{\text{out}}$  to the replica source on branch 3.

Without the Early-effect resistors of  $M_2$  and  $M_4$ , we have the situation depicted in Fig. 30a. In this case, we split  $V_{\text{out}}$  into three replica sources, as shown in Fig. 30b. We shall compute each of the components of  $\delta I_{\text{out}}$  due to each of the replica test sources individually and assemble them into the total  $\delta I_{\text{out}}$  using superposition. The only nonzero components of  $\delta I_{\text{out}}$  occur when we change the value of the replica source on branch 3, as shown in Fig. 31. By inspection of this circuit, we can write the total output current as


$$\delta I_{\text{out}} = \underbrace{\frac{g_{m2}\delta V_{\text{out}}}{1 + g_{s2}(1/g_{s1})}}_{\delta I_{\text{out}23}} (1 + 1) = g_{mn}\delta V_{\text{out}},$$

where we have once again made use of the fact that the incremental source conductances and transconductance gains of  $M_1$  and  $M_2$  are equal to one another under quiescent conditions. Note that the first 1 in parentheses accounts for  $\delta I_{\text{out}23}$  and the second one accounts for  $\delta I_{\text{out}13}$ . In this case, we have that the incremental output resistance of the circuit is given by

$$R_{\text{out}} = \frac{\delta V_{\text{out}}}{\delta I_{\text{out}}} = \frac{1}{g_{mn}}.$$

With the Early-effect resistors of  $M_2$  and  $M_4$ , we have the situation shown in Fig. 32a. In this case, we split  $V_{\text{out}}$  into five replica sources, as shown in Fig. 32b. We shall again compute each of the components of  $\delta I_{\text{out}}$  due to each of the replica test sources individually and assemble them into the total  $\delta I_{\text{out}}$  using superposition. The only nonzero components of  $\delta I_{\text{out}}$  occur when we change the value of the replica sources on branch 1, branch 3, and branch 5, as shown in Fig. 33a, Fig. 33b, and Fig. 33c, respectively. By inspection of these circuits, we can write the total output current as

$$\delta I_{\text{out}} = \underbrace{\frac{\delta V_{\text{out}}}{r_{o4}}}_{\delta I_{\text{out}11}} + \underbrace{\frac{\delta V_{\text{out}}}{r_{o2} + (1/g_{s1} || 1/g_{s2})}}_{\delta I_{\text{out}33}} \left( 1 - \underbrace{\frac{g_{s2}}{g_{s1} + g_{s2}}}_{\delta I_{\text{out}43}/\delta I_{\text{out}33}} + \underbrace{\frac{g_{s1}}{g_{s1} + g_{s2}}}_{\delta I_{\text{out}23}/\delta I_{\text{out}33}} \right)$$

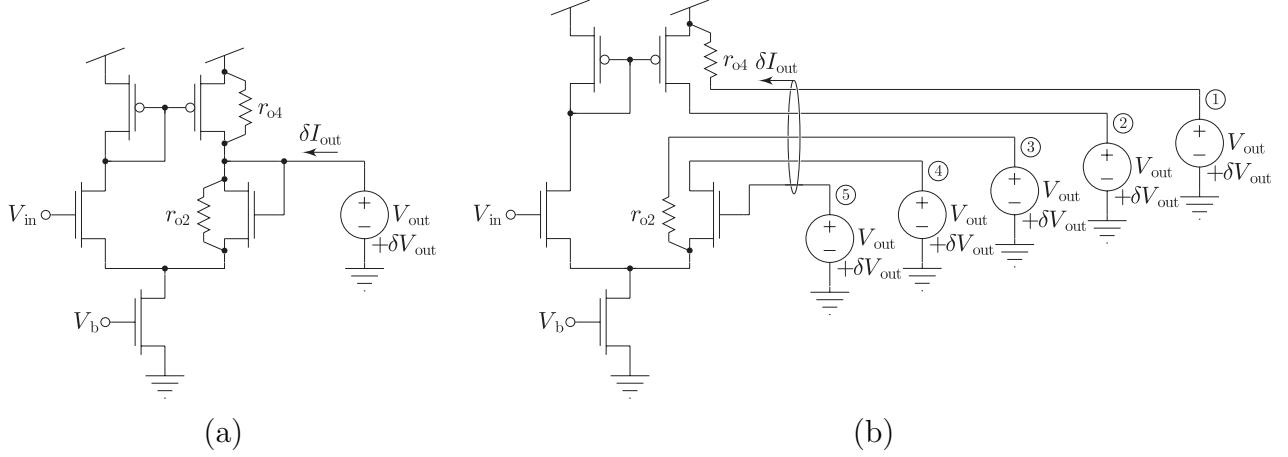

**Figure 32:** Calculation of the incremental output resistance of the follower-connected differential amplifier with no applied input signal by voltage source splitting including the Early-effect resistors of  $M_2$  and  $M_4$ .

$$\begin{aligned}
& + \underbrace{\frac{g_{m2}\delta V_{\text{out}}}{1 + g_{s2}(1/g_{s1}||r_{o2})}}_{\delta I_{\text{out}45}} \left( 1 - \underbrace{\frac{1/r_{o2}}{g_{s1} + 1/r_{o2}}}_{\delta I_{\text{out}35}/\delta I_{\text{out}45}} + \underbrace{\frac{g_{s1}}{g_{s1} + 1/r_{o2}}}_{\delta I_{\text{out}25}/\delta I_{\text{out}45}} \right) \\
= & \frac{\delta V_{\text{out}}}{r_{o4}} + \frac{\delta V_{\text{out}}}{r_{o2} + (1/2g_{sn})} \left( 1 - \frac{g_{sn}}{2g_{sn}} + \frac{g_{sn}}{2g_{sn}} \right) + \frac{g_{mn}\delta V_{\text{out}}}{1 + (g_{sn}/g_{sn})} \cdot \frac{2g_{sn}r_{o2}}{g_{sn}r_{o2} + 1} \\
\approx & \frac{\delta V_{\text{out}}}{r_{o4}} + \frac{\delta V_{\text{out}}}{r_{o2}} + g_{mn}\delta V_{\text{out}} \\
\approx & g_{mn}\delta V_{\text{out}},
\end{aligned}$$

where we again have made use of the fact that incremental source conductances and transconductance gains of  $M_1$  and  $M_2$  are equal to one another under quiescent conditions, and the approximations follow from the fact that  $g_{s2}r_{o2} \gg 1$ . We have also assumed that  $g_{s2}r_{o4} \gg 1$ , which will be the case if the Early voltages of the  $p$ MOS transistors are not too different from those of the  $n$ MOS transistors, because  $M_2$  and  $M_4$  both carry equal quiescent channel currents. Thus, the incremental output resistance of the circuit is given approximately by

$$R_{\text{out}} = \frac{\delta V_{\text{out}}}{\delta I_{\text{out}}} \approx \frac{1}{g_{mn}},$$

which is precisely what we found with substantially less effort when we omitted  $r_{o2}$  and  $r_{o4}$ .

Next, we must determine the incremental transconductance gain of the circuit from input to output with the output voltage fixed, as shown in Fig. 34. As with the incremental output resistance calculation, none of the Early-effect resistors will matter for this one either. We increase the gate of  $M_1$  by  $\delta V_{\text{in}}$ , as shown in Fig. 34. This increase in the gate voltage of  $M_1$  results in an increase in its channel current,  $\delta I_1$ , given by

$$\delta I_1 = \frac{g_{m1}\delta V_{\text{in}}}{1 + g_{s1}(1/g_{s2})} = \frac{g_{mn}}{2} \cdot \delta V_{\text{in}},$$

where we have again made use of the fact that the incremental source conductances and transconductance gains of  $M_1$  and  $M_2$  are equal to one another under quiescent conditions. Now, this incremental current flowing into the drain of  $M_1$  also flows out of the gate/drain of  $M_3$  and is reflected to the output by the  $p$ MOS current mirror, as shown in Fig. 34. It also flows out of the source of  $M_1$  and into the the source of  $M_2$  and out of the circuit, as shown. Thus, the incremental output current is given by

$$\delta I_{\text{out}} = 2\delta I_1 = g_{mn}\delta V_{\text{in}},$$

so the incremental voltage gain of the unity-gain follower is given by

$$A = \frac{\delta V_{\text{out}}}{\delta V_{\text{in}}} = G_m R_{\text{out}} = g_{mn} \cdot \frac{1}{g_{mn}} = 1.$$

■

For our final example, we shall use the node fixing technique to compute the incremental differential-mode gain of the simplified folded-cascode differential amplifier, shown in Fig. 35. For this calculation, we shall assume that all of the  $n$ MOS transistors are matched, that all of the  $p$ MOS transistors are matched, and that  $V_{\text{cm}}$  is sufficiently far above ground that  $M_b$  operates in saturation. Additionally, we shall assume that the cascode bias voltage,  $V_c$ , is set low enough that  $M_3$  and  $M_4$  are saturated, but high enough that  $M_1$  and  $M_2$  are saturated for all allowable values of  $V_{\text{cm}}$ . Transistor  $M_7$  is diode connected, and thus operates in saturation. The question of whether or not  $M_5$  operates in saturation is again very similar to the one that we addressed for  $M_1$  in the super source follower example.

By a similar line of reasoning to that which we followed for the simple five-transistor differential amplifier, the quiescent output voltage of this circuit will be equal to the drain/gate voltage of  $M_7$ . When  $V_{\text{out}} = V_7$ , the currents flowing in  $M_7$  and  $M_8$  will be identical as will be the currents flowing in  $M_5$  and  $M_6$ . Also, at this point, if  $M_5$  and  $M_7$  are both saturated under these conditions, then so are  $M_6$  and  $M_8$ . If  $M_5$  and  $M_6$  are both saturated and both have the same drain and gate voltage, then their source voltages,  $V_5$  and  $V_6$  must also be equal to one another. Under these conditions,  $M_1$  and  $M_2$  have the same gate, source, and drain voltages, and must therefore be passing the same current. Likewise,  $M_3$  and  $M_4$  have the same gate, source, and drain voltages, and so must also pass the same amount of current. With the circuit in such a state, KCL is satisfied everywhere.

### Example 7.5

We begin the node fixing process by connecting a test voltage source to the output of the circuit whose value we have adjusted to match the quiescent output voltage of the amplifier, which we have just established is equal to the value of  $V_7$ , as shown in Fig. 36a. At this point, the amplifier exchanges no current with the test source, as indicated in Fig. 35b. We can compute the incremental output resistance of the amplifier, as shown in Fig. 37a, by increasing  $V_{\text{out}}$  by  $\delta V_{\text{out}}$  and determining how much current flows into the circuit as a result. In doing so, we shall account for the Early effect of transistors  $M_2$ ,  $M_4$ ,  $M_6$ , and  $M_8$ , as shown in Fig. 37a. Given that the name *folded cascode* contains the word *cascode*, we might expect that the incremental resistance seen looking into the drain of  $M_6$  (i.e., the cascode transistor connected to the output) would be much larger than that looking into the drain of

$M_8$ , which is the output of a simple  $n$ MOS mirror, and hence  $r_{o8}$  would dominate the parallel combination of the two. As we shall see, this does turn out to be the case. Nevertheless, we shall proceed with the calculation to illustrate the techniques involved.

To compute  $\delta I_{\text{out}}$ , we split  $V_{\text{out}}$  into four replica sources, as shown in Fig. 37b. We shall compute each of the components of  $\delta I_{\text{out}}$  due to each of the replica test sources individually and assemble them into the total  $\delta I_{\text{out}}$  by superposition. As shown in Fig. 38a and Fig. 38b, the only nonzero components of  $\delta I_{\text{out}}$  occur when we change the value of the replica source on branches 1 and 4. The only component of the output current excited by the voltage change on branch 1 flows into  $r_{o8}$ , as shown in Fig. 38a. The voltage change on branch 4 causes current components to flow in branches 2, 3, and 4, as shown in Fig. 38b.

In order to compute how the current components divide at the source of  $M_6$ , we need to know the incremental resistance seen looking into the drain of  $M_2$  in parallel with its Early-effect resistor, as shown in Fig. 39a. To determine the equivalent incremental resistance,  $R_{\text{eq}}$ , indicated in Fig. 39a, we can recursively apply source splitting and superposition, by excising the differential pair from the circuit. Then, we apply a test voltage source to the drain of  $M_2$  whose value is adjusted to match the quiescent drain voltage of  $M_2$  in the original circuit. Finally, we compute the additional current that flows into the drain of  $M_2$  when we change the test voltage source by a small amount. The only nonzero components of  $\delta I_2$  occur when we change the replica source on branch 2, as shown in Fig. 39b. We can compute the change in  $I_2$  as

$$\begin{aligned}\delta I_2 &= \frac{\delta V}{\underbrace{r_{o2} + (1/g_{s1} || 1/g_{s2})}_{\delta I_{222}}} \left( 1 - \frac{g_{s2}}{\underbrace{g_{s1} + g_{s2}}_{\delta I_{212}/\delta I_{222}}} \right) \\ &= \frac{\delta V}{r_{o2} + (1/g_{s1} || 1/g_{s2})} \cdot \frac{g_{s1}}{g_{s1} + g_{s2}} \\ &= \frac{\delta V}{2r_{o2} + 1/g_{sn}},\end{aligned}$$

if  $g_{s1} = g_{s2} = g_{sn}$ . Thus, we have that the incremental resistance seen looking into the right side of the differential pair is given by

$$R_{\text{eq}} = \frac{\delta V}{\delta I_2} = 2r_{o2} + 1/g_{sn} \approx 2r_{o2}.$$

With this result, we can write the total current flowing into the output of the amplifier in response to a small change in  $V_{\text{out}}$  by inspection of the circuits shown in Fig. 38a and Fig. 38b as

$$\begin{aligned}\delta I_{\text{out}} &= \underbrace{\frac{\delta V_{\text{out}}}{r_{o8}}}_{\delta I_{\text{out}11}} + \frac{\delta V_{\text{out}}}{\underbrace{r_{o6} + (1/g_{s6} || r_{o4} || 2r_{o2})}_{\delta I_{\text{out}44}}} \left( 1 - \frac{g_{s6}}{\underbrace{g_{s6} + 1/r_{o4} + 1/2r_{o2}}_{\delta I_{\text{out}34}/\delta I_{\text{out}44}}} \right. \\ &\quad \left. + \frac{1/2r_{o2}}{\underbrace{g_{s6} + 1/r_{o4} + 1/2r_{o2}}_{\delta I_{\text{out}24}/\delta I_{\text{out}44}}} \right)\end{aligned}$$

$$\begin{aligned}
&= \frac{\delta V_{\text{out}}}{r_{\text{o8}}} + \frac{\delta V_{\text{out}}}{r_{\text{o6}} + (1/g_{\text{s6}}\|r_{\text{o4}}\|2r_{\text{o2}})} \cdot \frac{1/r_{\text{o4}} + 1/r_{\text{o2}}}{g_{\text{s6}} + 1/r_{\text{o4}} + 1/2r_{\text{o2}}} \\
&= \frac{\delta V_{\text{out}}}{r_{\text{o8}}} + \frac{\delta V_{\text{out}}}{r_{\text{o6}} + (1/g_{\text{s6}}\|r_{\text{o4}}\|2r_{\text{o2}})} \cdot \frac{1}{g_{\text{s6}}(r_{\text{o2}}\|r_{\text{o4}})} \cdot \frac{1}{1 + 1/g_{\text{s6}}(r_{\text{o4}}\|2r_{\text{o2}})} \\
&\approx \frac{\delta V_{\text{out}}}{r_{\text{o8}}} + \frac{\delta V_{\text{out}}}{g_{\text{s6}}r_{\text{o6}}(r_{\text{o2}}\|r_{\text{o4}})},
\end{aligned}$$

which means that the incremental output resistance of the folded-cascode amplifier is given approximately by

$$R_{\text{out}} = r_{\text{o8}}\|(g_{\text{s6}}r_{\text{o6}}(r_{\text{o2}}\|r_{\text{o4}})) \approx r_{\text{o8}}.$$

Next, we must determine the incremental transconductance gain of the circuit from input to output with the output voltage fixed, as shown in Fig. 40. Because the output voltage source maintains the voltage across  $r_{\text{o8}}$  constant, the current flowing through it will not change for this calculation, so it will have no impact on the calculation whatsoever. Because the source conductances of  $M_1$  and  $M_2$  are much larger than  $1/r_{\text{o2}}$ , any current diverted by  $r_{\text{o2}}$  from the sources of  $M_1$  and  $M_2$  would represent a negligible loss from that which flows into the sources of  $M_1$  and/or  $M_2$ , so we would expect it too to have a negligible impact on this calculation. The same can be said for  $1/r_{\text{o4}}$  and  $1/r_{\text{o6}}$  in comparison to  $g_{\text{s6}}$ . Consequently, we shall omit all four Early-effect resistors in calculating the circuit's incremental transconductance gain, as shown in Fig. 40. Also, as indicated in Fig. 35b, we shall apply a pure differential-mode input to the circuit for this calculation, which means that we apply half of  $\delta V_{\text{dm}}$  to the noninverting input and half of  $\delta V_{\text{dm}}$  to the inverting input so that the common-mode input voltage remains unchanged. To compute  $\delta I_{\text{out}}$ , we shall apply superposition, considering the effect of each half of  $\delta V_{\text{dm}}$  separately and superposing the resulting components of  $\delta I_{\text{out}}$ , as shown in Fig. 40.

First, we consider increasing the gate of  $M_1$  by  $\delta V_{\text{dm}}/2$ , as shown in Fig. 40a. This increase in the gate voltage of  $M_1$  results in an increase in its channel current,  $\delta I_1$ , given by

$$\delta I_1 = \frac{g_{\text{m1}}\delta V_{\text{dm}}/2}{1 + g_{\text{s1}}(1/g_{\text{s2}})} = \frac{g_{\text{mn}}}{4} \cdot \delta V_{\text{dm}},$$

where we have again made use of the fact that the incremental source conductances and transconductance gains of  $M_1$  and  $M_2$  are equal to one another under quiescent conditions. This increase in the current flowing through  $M_1$  results in an equal decrease in the current flowing through  $M_5$ , which we can think of as an incremental current flowing out of the source of  $M_5$ , as shown in Fig. 40a. In turn, this current flows from the input of the current mirror and is reflected to the output through  $M_8$ , as shown in Fig. 40a. The original increase in  $I_1$  also flows back up through  $M_2$  and into the source of  $M_6$  (i.e., the decrease in  $I_2$  is compensated by an equal increase in the current flowing through  $M_6$ ) and out of the circuit, as shown in Fig. 40a. Thus, the first component of the incremental output current is given by

$$\delta I_{\text{out1}} = 2\delta I_1 = \frac{g_{\text{mn}}}{2} \cdot \delta V_{\text{dm}}.$$

Next, we consider decreasing the gate of  $M_2$  by  $\delta V_{\text{dm}}/2$ , as shown in Fig. 40b. This decrease in the gate of  $M_2$  results in a decrease in its channel current,  $\delta I_2$ , whose magnitude

is given by

$$\delta I_2 = \frac{g_{m2}\delta V_{dm}/2}{1 + g_{s2}(1/g_{s1})} = \frac{g_{mn}}{4} \cdot \delta V_{dm},$$

where we have once again made use of the fact that the incremental source conductances and transconductance gains of  $M_1$  and  $M_2$  are equal to one another under quiescent conditions. This decrease in the current flowing through  $M_2$  again can be thought of as a positive incremental current flowing from source of  $M_2$  to its drain and out of the circuit through  $M_6$ , as shown in Fig. 40b. This incremental current must come from the source of  $M_1$ . It also flows through the channel of  $M_1$  and from the source of  $M_5$ . It also flows through  $M_5$  and from the input of the  $n$ MOS mirror, which reflects it to the output of the circuit, as shown in Fig. 40b. Thus, the second component of  $\delta I_{out}$  is given by

$$\delta I_{out2} = 2\delta I_2 = \frac{g_{mn}}{2} \cdot \delta V_{dm}.$$

Superposing these two components of the output currents, we obtain the total incremental output current as

$$\delta I_{out} = \delta I_{out1} + \delta I_{out2} = g_{mn}\delta V_{dm},$$


which implies that the incremental transconductance gain of the circuit with the output voltage held fixed is given by

$$G_m = \frac{\delta I_{out}}{\delta V_{dm}} = g_{mn}.$$


Therefore, the incremental differential-mode gain of the circuit is given approximately by

$$A_{dm} = \frac{\delta V_{out}}{\delta V_{dm}} = G_m R_{out} \approx g_{mn} r_{o8} = g_{mn} r_{on},$$

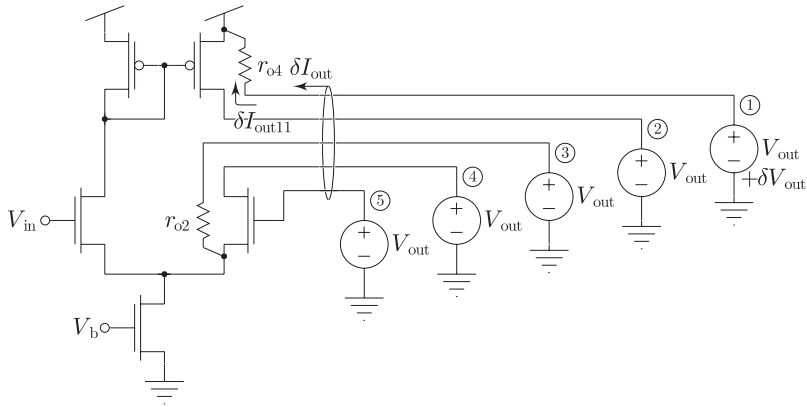
which is the intrinsic gain of each of the  $n$ MOS transistors in the circuit except for  $M_b$ , which carries a different current from the rest. ■



(a)

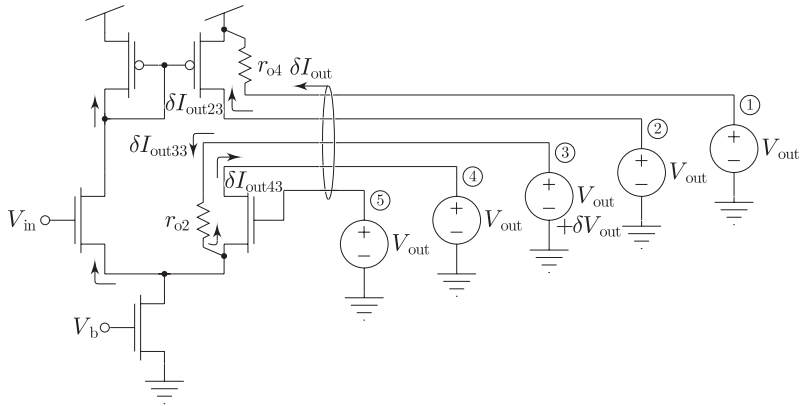


(b)

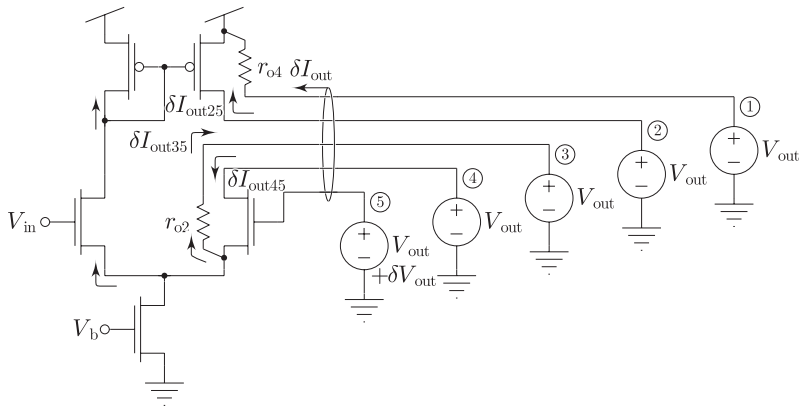


(c)

 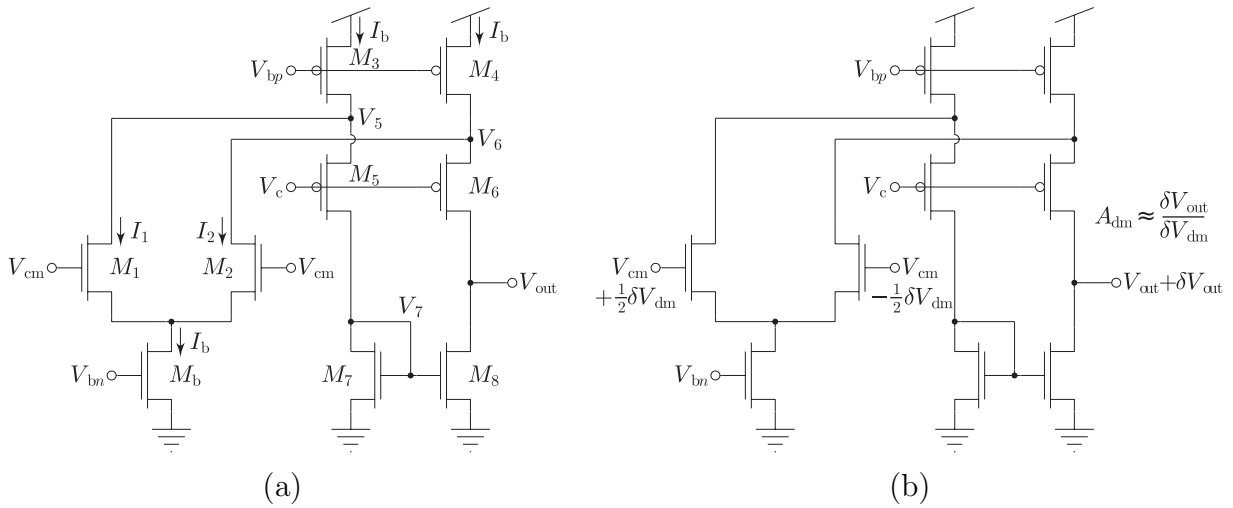**Figure 33:** The only nonzero components of  $\delta I_{out}$  occur when we apply  $\delta V_{out}$  to the replica sources on (a) branch 1, (b) branch 3, and (c) branch 5.

 





**Figure 34:** Calculation of the incremental transconductance gain of the follower-connected differential amplifier with the output voltage fixed.



**Figure 35:** Folded-cascode differential amplifier.




(a)

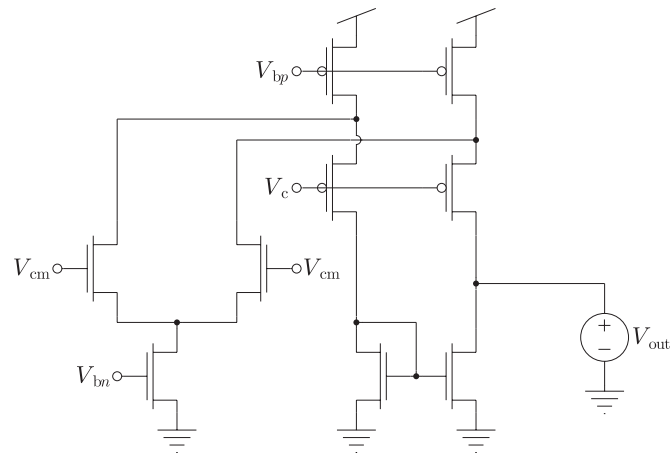


(b)


**Figure 36:** Fixing the output voltage of the folded-cascode differential amplifier.

 


**Figure 37:** Calculation of the incremental output resistance of the folded-cascode differential amplifier with no applied input signal by voltage source splitting.

 


**Figure 38:** The only nonzero components of  $\delta I_{out}$  occur when we apply  $\delta V_{out}$  to the replica sources on (a) branch 1 and (b) branch 4.

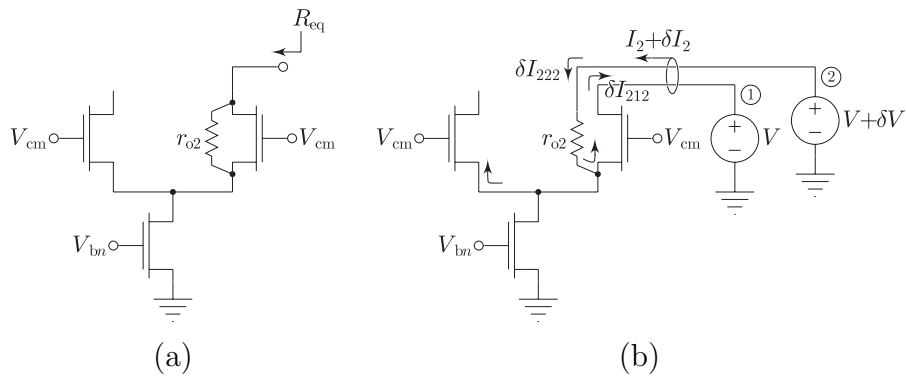

**Figure 39:** Auxiliary calculation of the incremental resistance seen looking into the drain of  $M_2$  by voltage source splitting and superposition.

 

(a)

 

(b)

**Figure 40:** Calculation of the incremental transconductance gain of the folded-cascode differential amplifier with the output voltage fixed by superposition.