







# Layout for Digital Integrated Circuits

- ▶ **Layout** is the process of specifying the physical placement of and interconnections between all of the devices in a circuit.
- ▶ Layout is used to generate all of the mask layers used for chip fabrication.
- ▶ Layout for **digital** circuits:
  - Most transistors are minimum length
  - Transistor widths are sized to minimize delay

## Scaleable **CMOS** Design Rules



- ▶ All device dimensions and placements are specified in terms of a scalable unit of distance called lambda (i.e.,  $\lambda$ ).
- ▶  $\lambda$  is **half** of the **minimum feature size** specify-able in a given process (e.g., min. gate length).
- ▶ We will focus on a 0.5- $\mu\text{m}$  *n*-well CMOS process with three metal layers. ( $\lambda = 0.3 \mu\text{m}$ )

# Common **SCMOS** Design Rules

     
 


# Common **SCMOS** Design Rules



Contacts

  


Contact Spacing

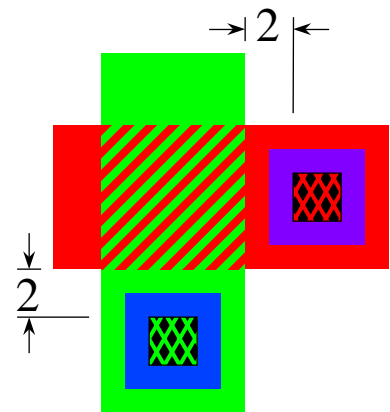 


Vias

  

Via Spacing

 


# Common **SCMOS** Design Rules

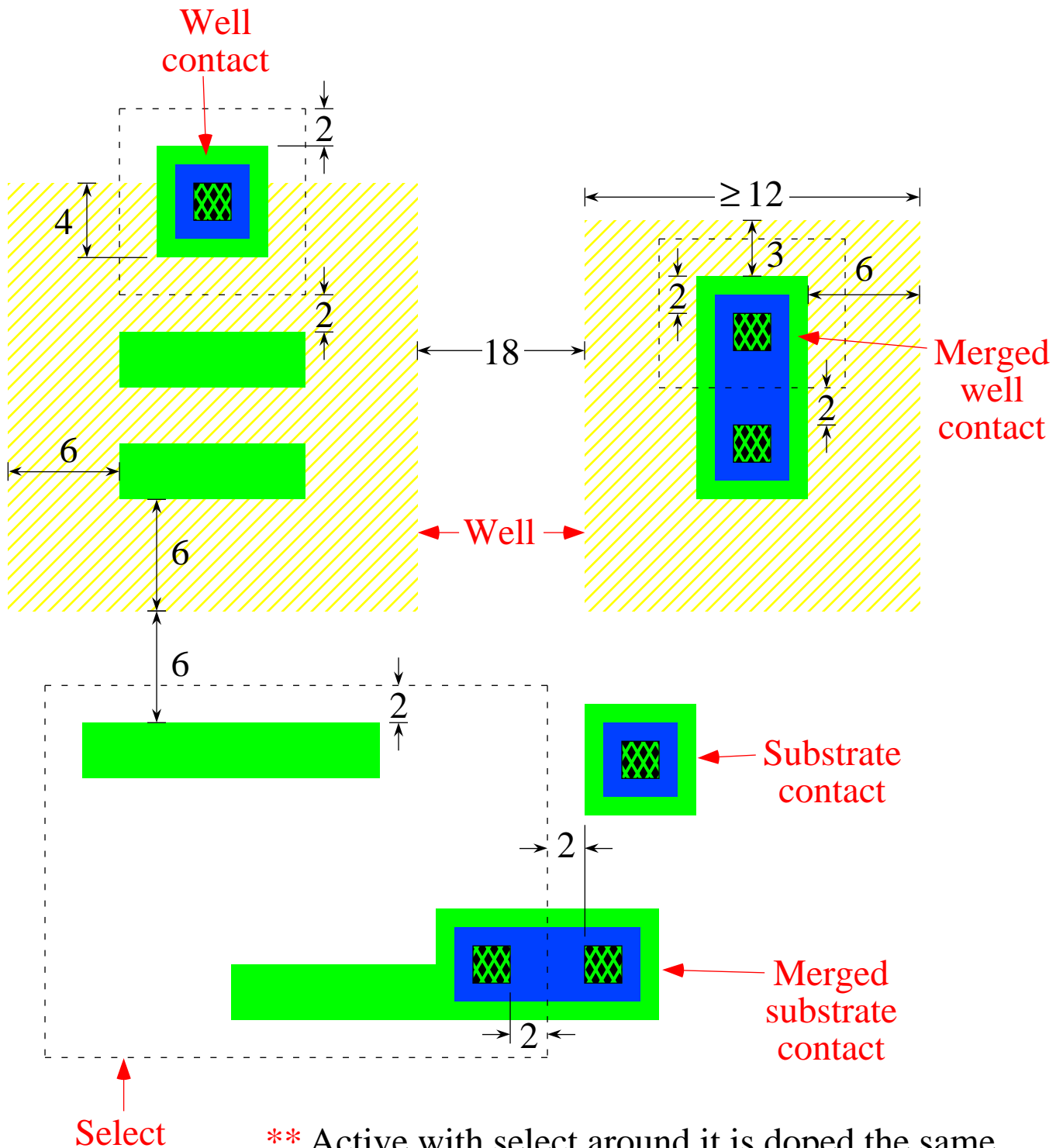


\*\* Active with select around it is doped the same type as the well. Active without select is doped the same type as the substrate.


# MOS Transistor Layout

 

 Minimum size  
 $W_{\min}$  and  $L_{\min}$  set by design rules




Wide  
Strong  
Large  $W/L$

 


Long  
Weak  
Small  $W/L$
 
# Very Wide MOS Transistors: Serpentine Transistors




 $W \gg L$   
Source and drain  
are interdigitated







Minimize source  
and drain series  
resistance by using  
many contacts
 
# Very Wide MOS Transistors: Stacked Transistors




- ▶ Similar to serpentine transistors, but no bends.
- ▶ Source/drain regions shared  $\Rightarrow$  reduced  $C_S$  and  $C_D$ .
   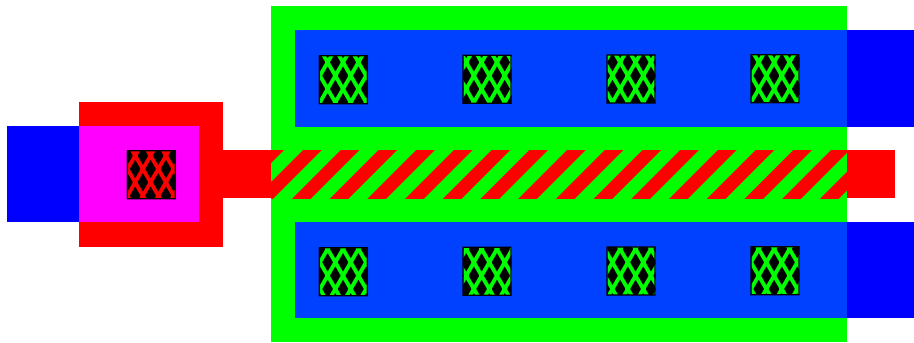
# Stacking Reduces Source/Drain Diffusion Area




 
# Very Long MOS Transistors: **Serpentine** Transistors





$$W \ll L$$

One large gate covers  
the entire serpentine channel





# Layout Guidelines for Complex CMOS Gates

- ▶ Run power rails in metal parallel to strips of active.
- ▶ Run a strip of poly for each input orthogonal to the power rails.
- ▶ Order the input signals in order to maximize the number of shared source/drain diffusion regions and to minimize the number of broken poly lines.
- ▶ Finish connections in metal or poly (only use poly for short runs).
- ▶ Minimize internal node parasitics (both  $C$  and  $R$ ) by
  - Keeping runs of active as short as possible
  - Sharing as many source/drain diffusions as possible
- ▶ Avoid using higher level metal layers for local interconnects.
- ▶ Consistently run horizontal connections in one metal layer (e.g., metal1) and vertical ones in another (e.g., metal2).

# Which NAND Gate Layout is Better?

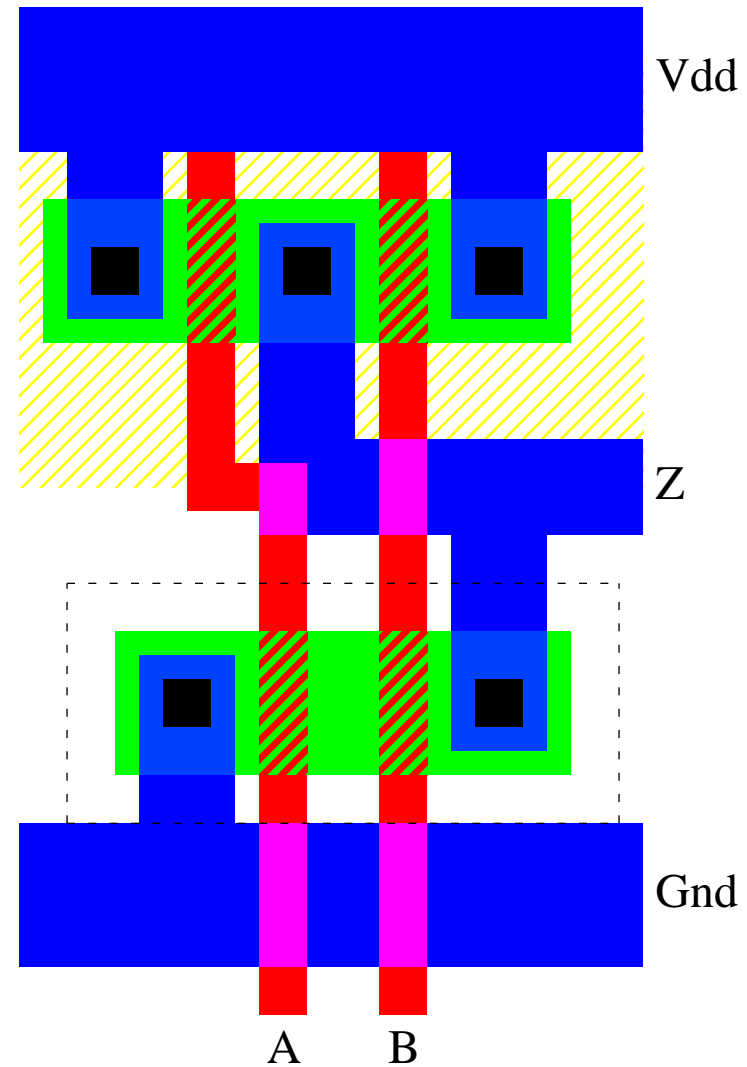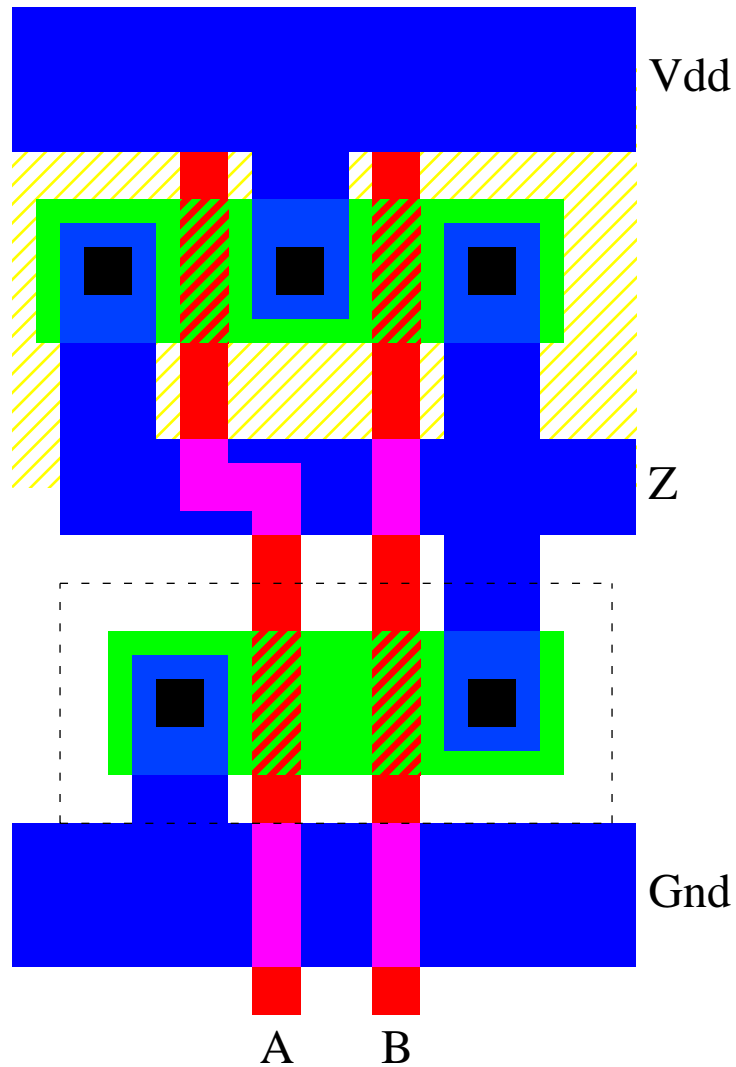



# Logic Graphs for PDNs and PUNs

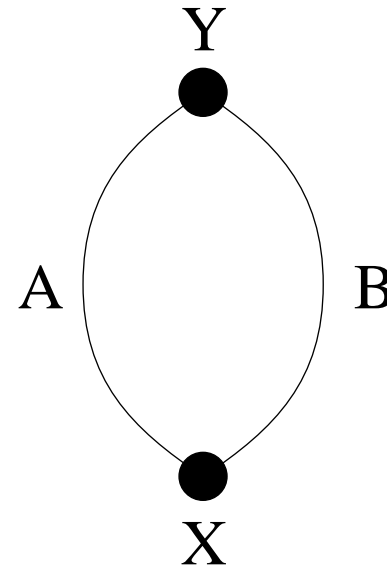   



# Euler Paths Through Logic Graphs

- ▶ **Euler path:** A path through all nodes in a graph such that each edge is traversed exactly once.
- ▶ If we can find *consistent* Euler paths through the PUN logic graph and the PDN logic graph, then we can order the inputs so that the poly strips are continuous and source/drain diffusions are shared maximally.
- ▶ The order of the inputs is the same as the order of the edges in our Euler paths.
- ▶ Some Euler path caveats:
  - Euler paths are not unique
  - Not all Boolean expressions have consistent Euler paths
  - One form of a Boolean expression may have consistent Euler paths while an equivalent form may not.

 
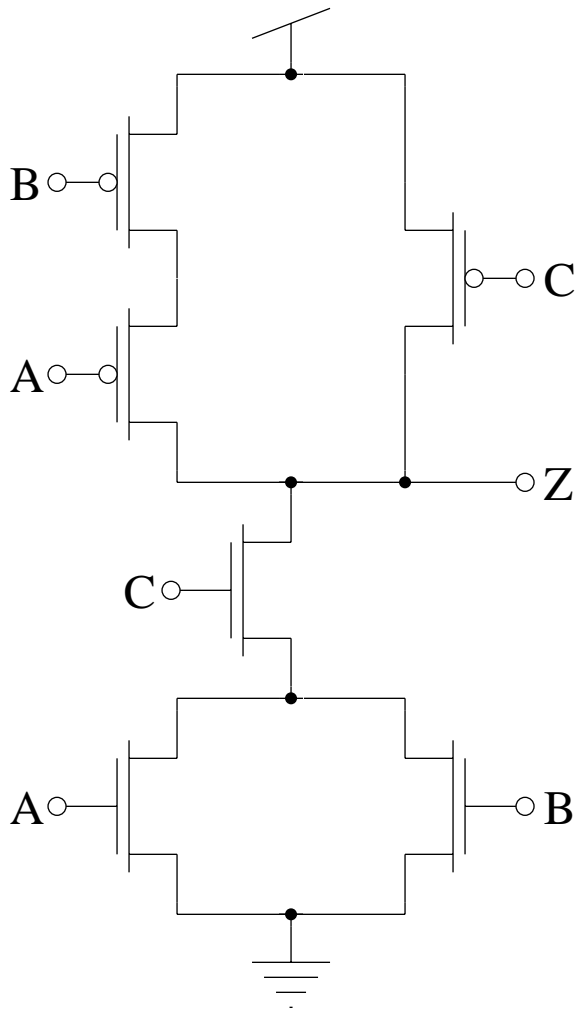
# Euler Path Example: $Z = \bar{A}\bar{B} + \bar{C}$


  
# Euler Path Example: $Z = \bar{A}\bar{B} + \bar{C}$




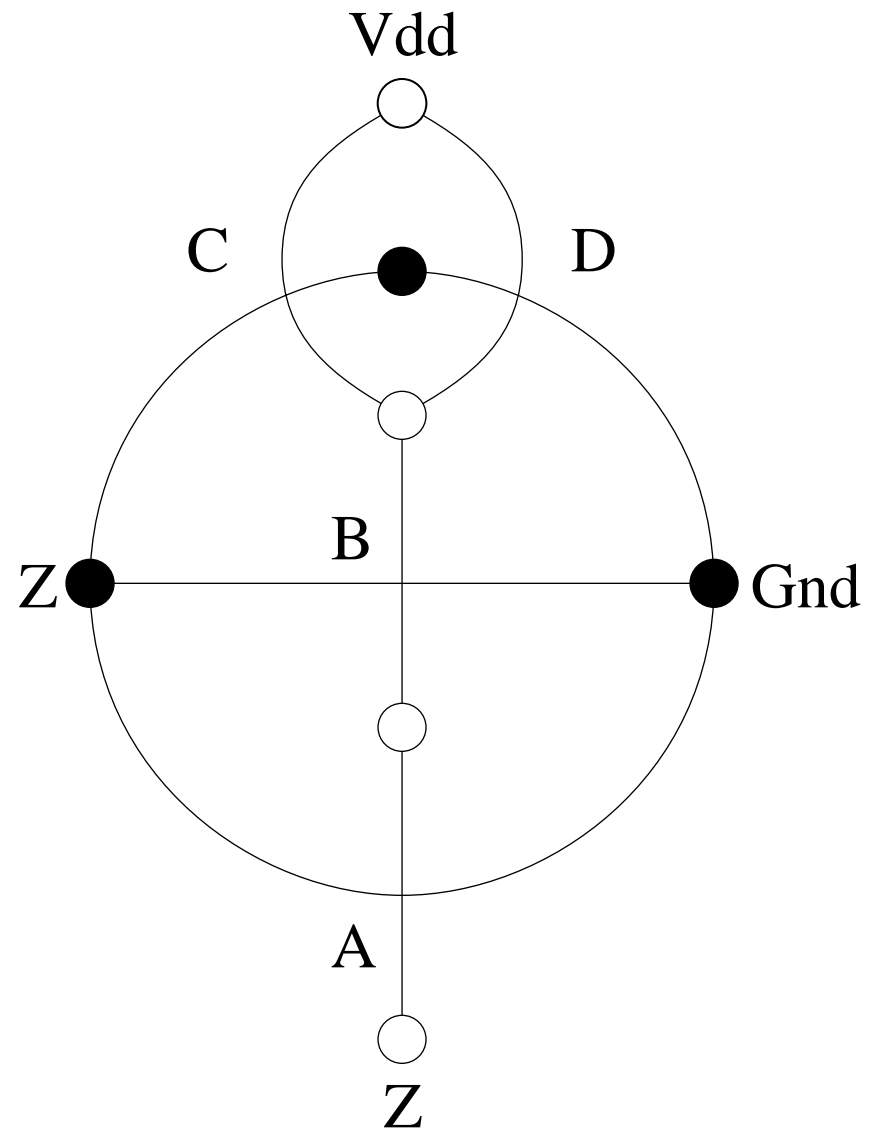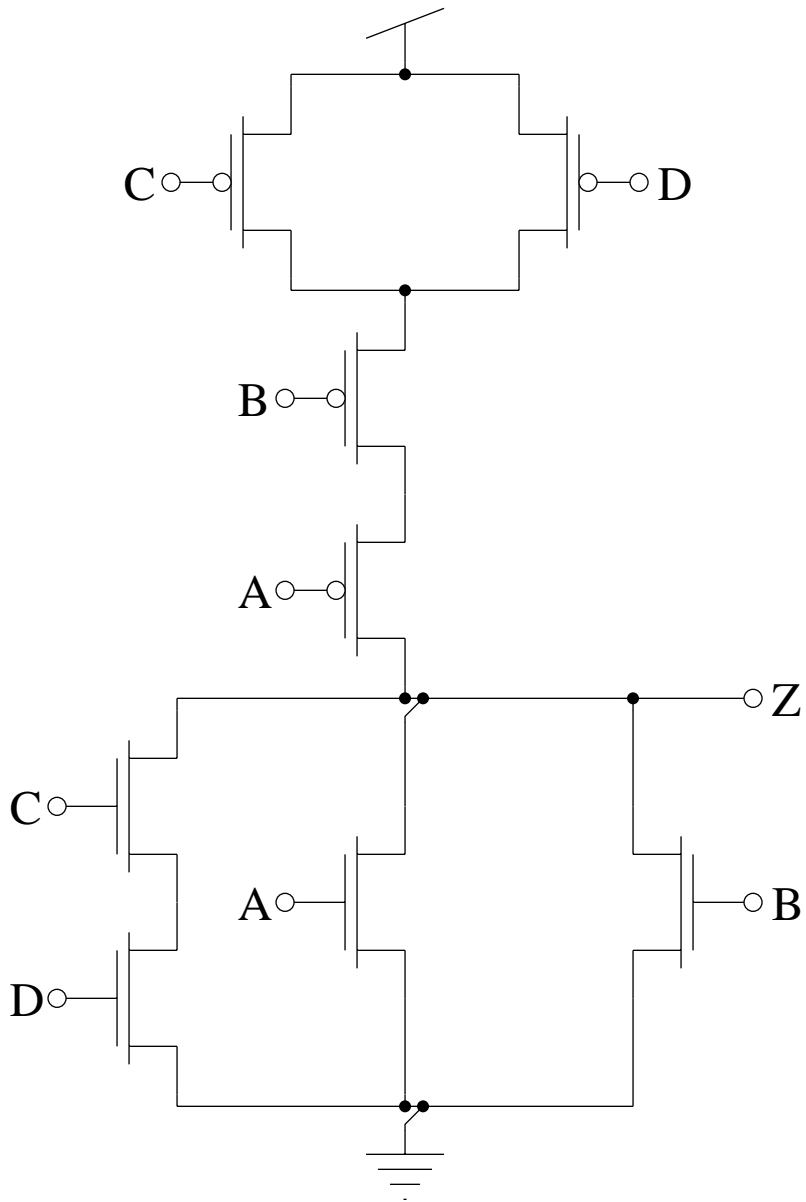
# Euler Path Example: $Z = \bar{A} \bar{B} (\bar{C} + \bar{D})$







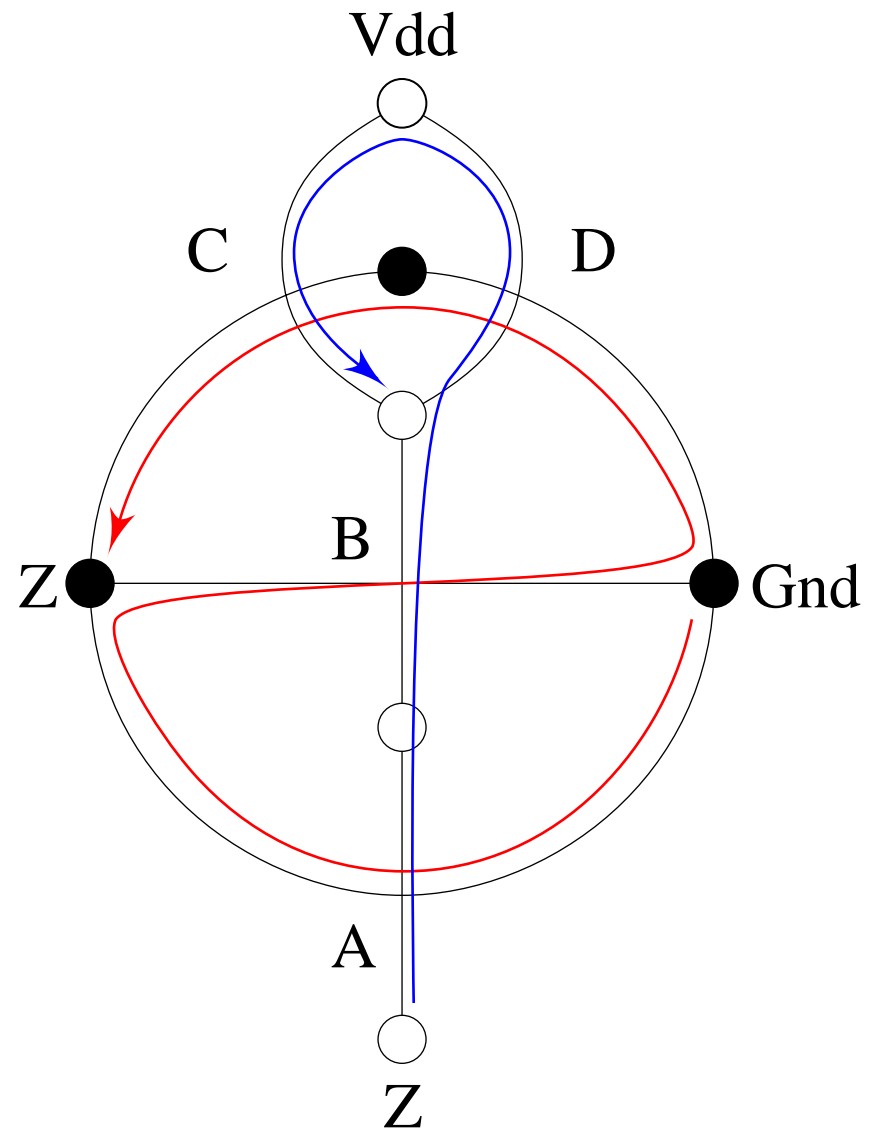
 
# Euler Path Example: $Z = \bar{A} \bar{B} (\bar{C} + \bar{D})$



# Compacting Layout of CMOS Gates

  

# Compacting Layout of CMOS Gates

  

# Compacting Layout of CMOS Gates

